

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2017/2018**

COURSE NAME : ELECTRONIC INSTRUMENTS
AND MEASUREMENTS

COURSE CODE : BEF 24002

PROGRAMME CODE : BEV

EXAMINATION DATE : JUNE/JULY 2018

DURATION : 2 HOURS AND 30 MINUTES

INSTRUCTION : ANSWER ALL QUESTIONS

TERBUKA

THIS QUESTION PAPER CONSISTS OF **FOUR (4)** PAGES

CONFIDENTIAL

- Q1** (a) (i) Draw the block diagram of an electronic instrument. (3 marks)
- (ii) Briefly explain each block drawn at **Q1(a)(i)**. (6 marks)
- (b) (i) Differentiate between static and dynamic characteristics of an instrument. (4 marks)
- (ii) State **four (4)** types of noises. (4 marks)
- (c) Shortly explain the generation and their respective sources of generation of any **two (2)** noises, enumerated at **Q1(b)(ii)**. (8 marks)
- Q2** (a) (i) Sketch the block diagram of an analogue electronic measurement. (5 marks)
- (ii) Highlight the design considerations of an analogue electronic instrument. (5 marks)
- (b) Draw the circuit schematic diagrams of ammeter, voltmeter, ac voltmeter, and ohmmeter by employing basic permanent magnetic moving coil for their operation. (8 marks)
- (c) If the instrument has a $20 \text{ k}\Omega/\text{V}$ sensitivity, an accuracy 1% of full scale deflection and the meter is connected across R_b as shown in **Figure Q2(c)**, analyse the voltage reading and percentage error of each reading obtained with a voltmeter on; 5 V, 10 V, and 30 V ranges. (7 marks)
- Q3** (a) With the help of a circuit diagram, respective equations and frequency response, explain the working principle of low pass filter (LPF). (10 marks)
- (b) A LPF circuit consisting of a resistance, R of $47 \text{ k}\Omega$ in series with a capacitance, C of 47 nF is connected across a 10 V sinusoidal supply.
- (i) Calculate the output voltage V_{out} at a frequency of 100 Hz and 10 kHz. (2 marks)

- (ii) Calculate the cut off frequency. (2 marks)
- (iii) Calculate the phase shift angle. (2 marks)
- (iv) Discuss on the output voltage result in terms of frequency response. (2 marks)
- (c) With the help of a circuit diagram, discuss:
 - (i) Average reading voltmeter. (3 marks)
 - (ii) Peak responding voltmeter. (4 marks)
- Q4** (a) Explain the construction features of high impedance probes. (5 marks)
- (b) With the help of a neat diagram, summarize the working principle of thermocouple. (10 marks)
- (c) (i) Define the noise. (2 marks)
- (ii) Name its **two (2)** sources. (2 marks)
- (iii) Discuss any **two (2)** but different from explained at **Q1(c)**. (6 marks)

- END OF QUESTIONS-

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : II / 2017/2018
COURSE NAME : ELECTRONIC INSTRUMENTS
AND MEASUREMENTS

PROGRAMME CODE : BEV
COURSE CODE : BEF 24002

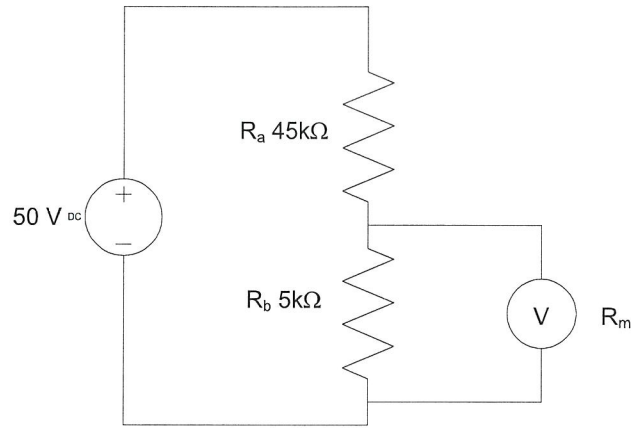


Figure Q2(c)

TERBUKA