

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
(ONLINE)
SEMESTER I
SESSION 2020/2021**

COURSE NAME : PHYSICS III
COURSE CODE : DAS 24603
PROGRAMME CODE : DAU
EXAMINATION DATE : JANUARY / FEBRUARY 2021
DURATION : 3 HOURS
INSTRUCTIONS : ANSWER ALL QUESTIONS

TERBUKA

THIS QUESTION PAPER CONSISTS OF SIX (6) PAGES

CONFIDENTIAL

- Q1** In **Figure Q1**, a 20.0 V battery is connected across capacitors of capacitances $C_1 = C_6 = 3.5 \mu\text{F}$ and $C_3 = C_5 = 5 \mu\text{F}$ and $C_2 = C_4 = 4.7 \mu\text{F}$. Calculate
- (a) the equivalent capacitance C_{eq} of the capacitors
(17 marks)
 - (b) the charge stored in capacitor C_1 .
(5 marks)
 - (c) the voltage drop across capacitor C_1 .
(5 marks)
 - (d) the energy stored in capacitor C_1 .
(3 marks)
- Q2** (a) Resistors $R_1 - R_7$ are connected to the terminals of a battery as in **Figure Q2 (a)**. Given the emf voltage is 15.0 V, internal resistance of the battery is 0.35Ω , and $R_1 = R_2 = 60 \Omega$, $R_3 = R_4 = R_5 = 120 \Omega$, $R_6 = 70 \Omega$, and $R_7 = 90 \Omega$. Calculate:
- (i) the equivalent resistance of the resistors.
(10 marks)
 - (ii) the current flow in the circuit.
(2 marks)
- (b) For the circuit as in **Figure Q2 (b)**, given $R_1 = R_2 = R_3 = 1.2 \text{ k}\Omega$, $V_1 = 5 \text{ V}$, $V_2 = 7.5 \text{ V}$, and $V_3 = 3.5 \text{ V}$. By applying Kirchoff's Current Law and Kirchoff's Voltage Law,
- (i) re-draw the circuit and label the polarity of all electronic components.
(3 marks)
 - (ii) calculate the current I_1 , I_2 , and I_3 that flows in the circuit.
(10 marks)
- Q3** An AC generator with amplitude emf of 220 V and operating at 360 Hz in a series RLC circuit. Given $R = 160 \Omega$, $C = 29.5 \mu\text{F}$, and $L = 199 \text{ mH}$. Determine
- (a) the impedance of the circuit.
(8 marks)
 - (b) the power factor and the phase difference of the circuit.
(5 marks)

TERBUKA

- (c) the average power at which energy is dissipated in the resistance. (6 marks)
- (d) the new capacitance needed to maximize the average power if the other parameters of the circuit remain constant. (4 marks)
- (e) From your answer in **Q3 (b)**, conclude the relationship between the current and voltage in the RLC circuit. (2 marks)

Q4 (a) **Figure Q4 (a)** shows a schematic diagram of a logic circuit.

- (i) Write the logic statement of the logic circuit. (4 marks)
- (ii) From your answer in **Q4(a)(i)**, state the minimum number of NOT gates required to implement in the circuit. (1 mark)
- (b) A logic statement of a logic circuit is given by:
 $Y = 1$ if (A is 1 AND B is NOT 1) AND (A is NOT 1 AND C is NOT 1) OR (B is 1 AND C is 1)
- (i) Write the logic statement in terms of Boolean expression. (2 marks)
- (ii) Draw the logic circuit for the given logic statement. (7 marks)
- (iii) Complete the truth table as in **Figure Q4 (b)** for the given logic statement (4 marks)
- (iv) By using Boolean Algebra Laws, simplified the logic statement. (5 marks)
- (v) Draw the simplified logic circuit as in **Q4 (b) (iv)**. (2 marks)

- END OF QUESTION-

TERBUKA

SEMESTER / SESSION : SEM I / 2020/2021

PROGRAMME CODE : DAU

COURSE NAME : PHYSICS III

COURSE CODE : DAS 24603

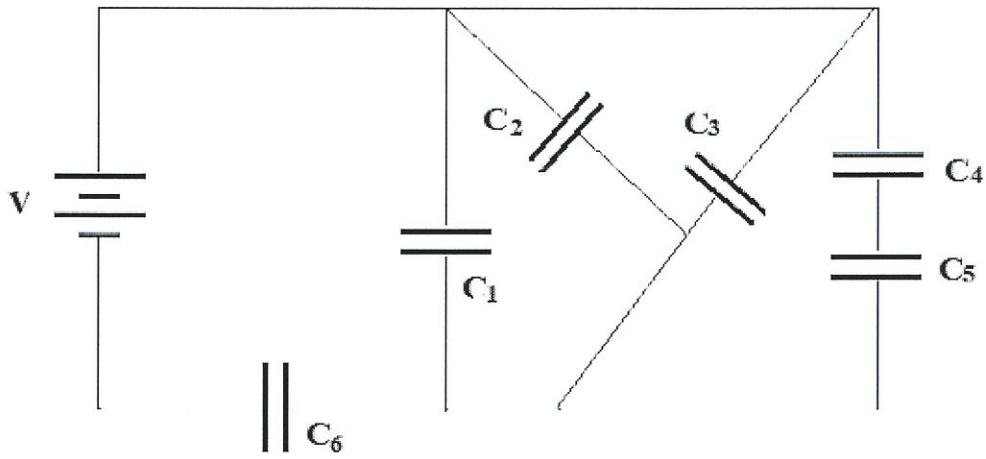


Figure Q1

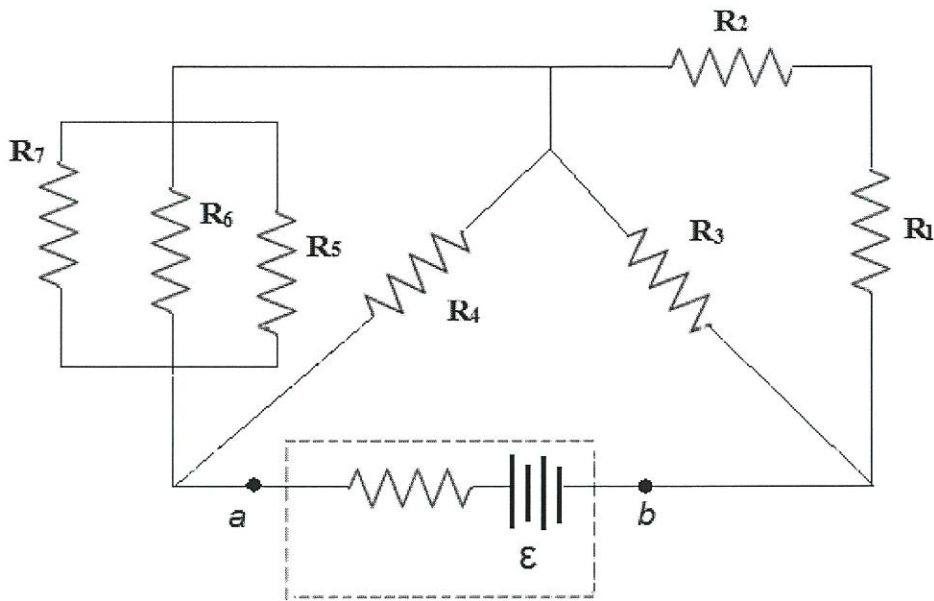


Figure Q2 (a)

TERBUKA

SEMESTER / SESSION : SEM I / 2020/2021

PROGRAMME CODE : DAU

COURSE NAME : PHYSICS III

COURSE CODE : DAS 24603

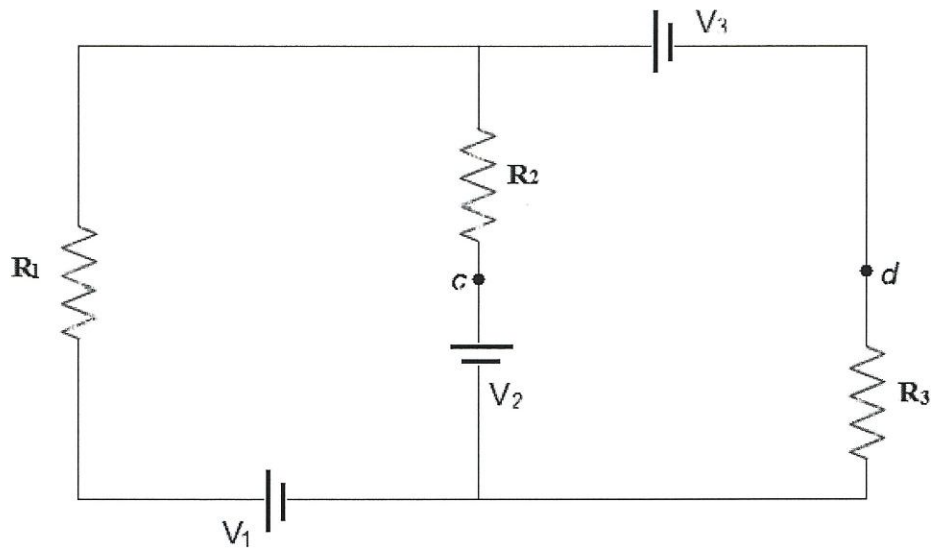


Figure Q2 (b)

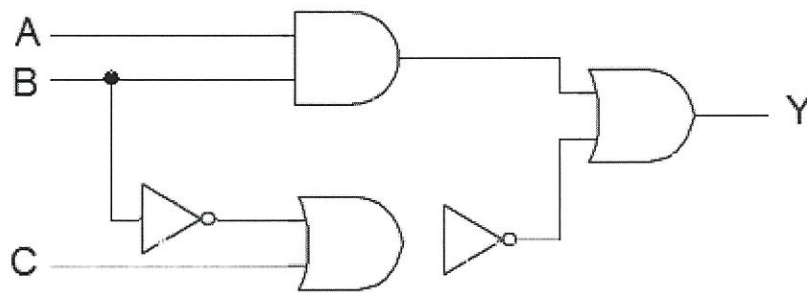


Figure Q4 (a)

TERBUKA

SEMESTER / SESSION : SEM I / 2020/2021

PROGRAMME CODE : DAU

COURSE NAME : PHYSICS III

COURSE CODE : DAS 24603

A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Figure Q4 (b)

TERBUKA