

**CONFIDENTIAL**



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION**

**(ONLINE)**

**SEMESTER II**

**SESSION 2020/2021**

COURSE NAME : INSTRUMENTATION &  
MEASUREMENT

COURSE CODE : BEJ10702

PROGRAMME CODE : BEJ

EXAMINATION DATE : JULY 2021

DURATION : 2 HOURS

INSTRUCTION : ANSWER ALL QUESTIONS  
OPEN BOOK EXAMINATION

**TERBUKA**

THIS PAPER CONSISTS OF SEVEN (7) PAGES

**CONFIDENTIAL**

- Q1** (a) (i) Define transducer in instrumentation and measurement. (2 marks)
- (ii) Show a block diagram of a transducer. (2 marks)
- (b) Using the help of a diagram, explain the working principle of a strain gauge. (4 marks)
- (c) A simple force transducer is illustrated in **Figure Q1(c)**. A round steel bar, 0.02m in diameter and 0.40m in length, is subjected to a tensile force, **F** of 33,000kg, where the steel Young Modulus,  $E = 2 \times 10^{12} \text{ kg/m}^2$ .
- (i) Calculate the elongation of the round steel bar,  $\Delta L$ , in meters. (4 marks)
- (ii) Calculate the strain. (3 marks)
- (iii) Given that the strain gauge with a gauge factor of 2 is fastened to the round steel bar and the original resistance value of the gauge is  $130\Omega$ . Calculate its change in resistance if a strain obtained in **Q1(c)(ii)** is observed. (5 marks)
- (iv) Using the same strain gauge stated in **Q1(c)(iii)**, sketch an electrical circuitry deploying Wheatstone Bridge to measure the force. (Propose the suitable values for all resistors.) (5 marks)
- Q2** (a) A typical Wheatstone bridge is shown in **Figure Q2(a)**.
- (i) Explain the use of Wheatstone bridge in instrumentation and measurement. (2 marks)
- (ii) Illustrate the formulation steps of the equation of the resistors when it is balanced. (5 marks)
- (iii) Given that  $R_1 = 12\text{k}\Omega$ ,  $R_2 = 15\text{k}\Omega$ ,  $R_3 = 32\text{k}\Omega$ ,  $R_4 = \text{unknown}$ . Calculate  $R_4$  when the galvanometer read null. (2 marks)

TERBUKA

- (b) Another Wheatstone circuit is shown in **Figure Q2(b)**. The Wheatstone bridge is slightly unbalanced. The galvanometer resistance,  $R_g = 125\Omega$ , and is a current sensitivity of  $1\text{mm}/\mu\text{A}$ .
- Draw Thevenin's equivalent circuit across terminal 'b' and 'c'.  
(5 marks)
  - Calculate Thevenin's equivalent voltage,  $E_{\text{TH}}$  and Thevenin's equivalent resistance,  $R_{\text{TH}}$ , across terminal 'b' and 'c'.  
(6 marks)
  - Calculate the current through the galvanometer.  
(3 marks)
  - Calculate the deflection in mm of the galvanometer.  
(2 marks)

**Q3** An AC bridge is shown in **Figure Q3**. It has an AC excitation input and four arms of impedances, labelled as  $Z_1$ ,  $Z_2$ ,  $Z_3$  and  $Z_4$  and a null detector.

- Identify the criteria for 'balanced' condition.  
(2 marks)
- Give three examples of null detectors applicable in the circuit.  
(3 marks)
- Select three applications using an AC bridge for instrumentation and measurements.  
(3 marks)
- Illustrate the formulation of balanced condition using the labels,  $Z_1$ ,  $Z_2$ ,  $Z_3$  and  $Z_4$ .  
(6 marks)
- Given that the components of each impedance as:  
 $Z_1$  consists of  $R_1 = 400\Omega$   
 $Z_2$  consists of  $R_2 = 200\Omega$  and  $L_2 = 15.92\text{mH}$   
 $Z_3$  consists of  $R_3 = 300\Omega$  and  $C_3 = 0.4\mu\text{F}$   
 $Z_4$  is unknown.
  - If the input,  $E = 6\text{V}$  and frequency,  $f = 1\text{kHz}$ , calculate the unknown  $Z_4$ .  
(4 marks)
  - If the input,  $E = 6\text{V}$  and frequency,  $f = 100\text{kHz}$ , calculate the unknown  $Z_4$ .  
(4 marks)

TERBUKA (4 marks)

- (iii) Discover the effect of frequency as obtained in **Q3(e)(i)** and **Q3(e)(ii)**.  
(3 marks)

- Q4** (a) Explain the working principle of a rotary encoder for positioning purpose.  
(2 marks)
- (b) Explain the conversion of linear length when a rotary encoder of  $m$  pulses/rev is being attached to a roller of diameter,  $d$ .  
(4 marks)
- (c) A caddy packing machine would apply a rotary encoder to read the length of the package. Mechanically a rotary encoder is attached to the main shaft of the rotary rollers as simplified in **Figure Q4(c)**, in order to convert rotary measurement into linear measurement. The rest of the mechanism for packaging is not shown. The rollers, A and B, clamp firmly the caddy bar and feed it into the rotary cutter. Given that the encoder has 1000 pulses/rev; roller A and B are identical and its diameter is 200mm. (Assuming no slip happens between the rollers and the caddy.)
- (i) Calculate the length of the caddy being fed if a pulse is read.  
(5 marks)
- (ii) If the caddy bar is to be cut into 20mm, calculate the number of pulses signalled by the rotary encoder.  
(4 marks)
- (iii) If the caddy bar is to move at 10000mm/min and the cut size is 20mm, calculate the number of cut per minute.  
(5 marks)
- (iv) Calculate the encoder pulse rate if the caddy bar is to move at 10000mm/min.  
(5 marks)

- END OF QUESTIONS -

TERBUKA



FINAL EXAMINATION

SEMESTER/SESSION : II / 2020/2021

PROGRAMME CODE : BEJ

COURSE NAME : INSTRUMENTATION AND MEASUREMENT

COURSE CODE : BEJ10702

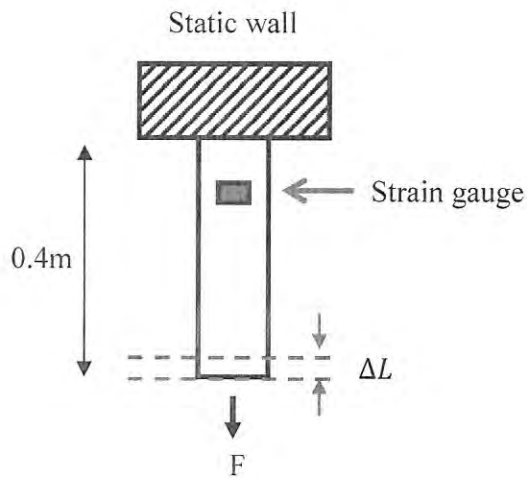


Figure Q1(c)

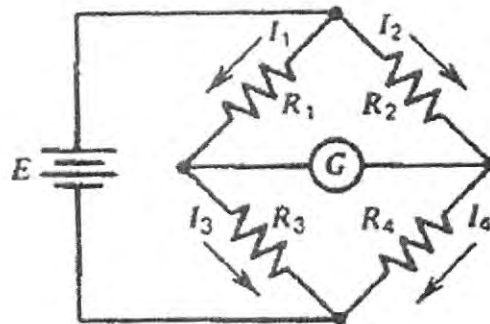


Figure Q2(a)

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION : II / 2020/2021  
 COURSE NAME : INSTRUMENTATION AND MEASUREMENT

PROGRAMME CODE : BEJ  
 COURSE CODE : BEJ10702

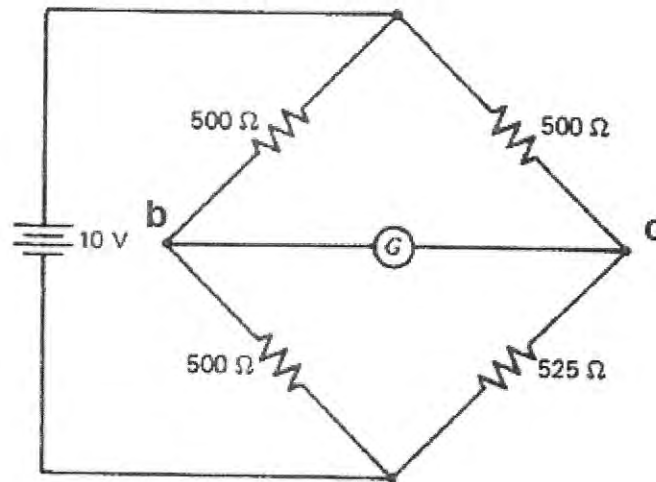


Figure Q2(b)

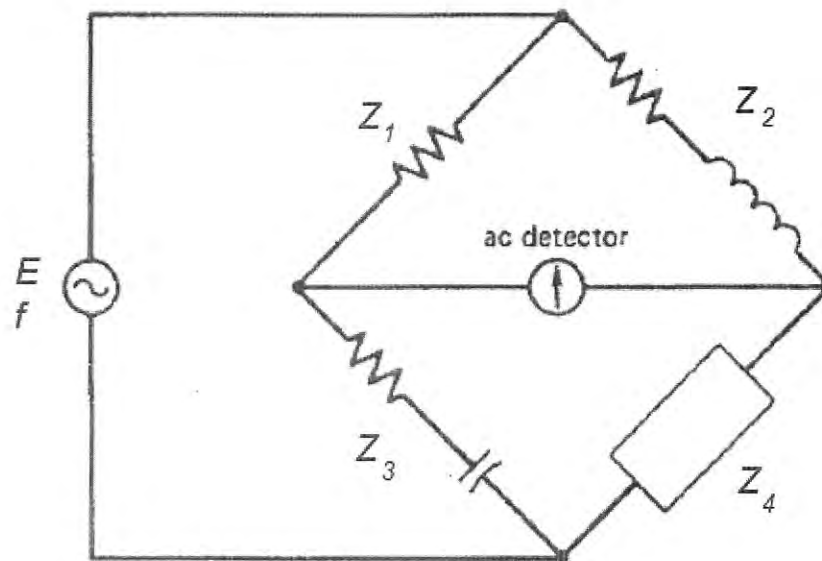


Figure Q3

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION : II / 2020/2021  
COURSE NAME : INSTRUMENTATION AND MEASUREMENT

PROGRAMME CODE : BEJ  
COURSE CODE : BEJ10702

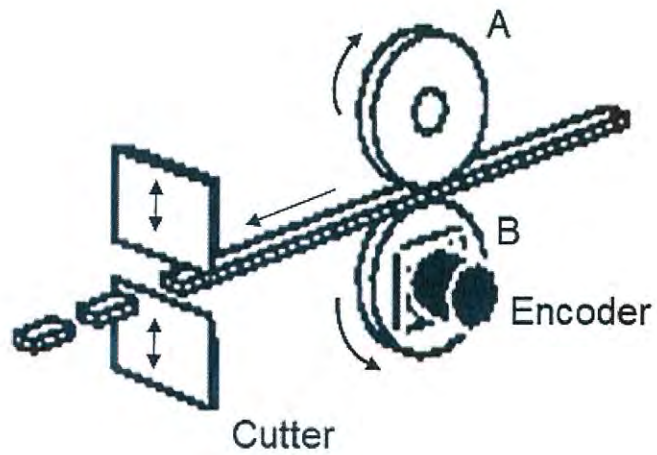


Figure Q4(c)

TERBUKA