

**CONFIDENTIAL**



**UTHM**  
Universiti Tun Hussein Onn Malaysia

**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
(TAKE HOME)  
SEMESTER II  
SESSION 2020/2021**

COURSE NAME : VLSI SYSTEM / VLSI DESIGN  
COURSE CODE : BEJ 43103 / BED 30303  
PROGRAMME CODE : BEJ  
EXAMINATION DATE : JULY 2021  
DURATION : 4 HOURS  
INSTRUCTION : ANSWER **ALL** QUESTIONS.  
PLEASE UPLOAD YOUR  
ANSWER IN PDF FORM TO  
AUTHOR (UTHM LMS) WITHIN  
THE SPECIFIED TIME GIVEN.

**TERBUKA**

THIS QUESTION PAPER CONSISTS OF **SIX (6)** PAGES

**CONFIDENTIAL**

- Q1** (a) Discuss the term ‘Beyond CMOS’ and relate it to the Moore’s Law. (5 marks)
- (b) (i) Analyse a NOR CMOS dynamic logic circuit and demonstrate how a contention problem can occur in the circuit. (6 marks)
- (ii) Propose and explain a solution to eliminate the contention problem in the NOR circuit in **Q1(b)(i)**. (4 marks)
- (c) (i) State the monotonicity requirement in the CMOS dynamic logic circuits. (2 marks)
- (ii) Explain with suitable diagram the violation of monotonicity requirement in the CMOS dynamic logic circuits. (3 marks)

**TERBUKA**

**Q2** Given the following Boolean equation:

$$Y = \overline{A E + B(CG + D + F)}$$

- (a) Draw the fully complementary static CMOS logic circuit that represent the equation using minimum number of transistors.

(8 marks)

- (b) Design a stick diagram for the equation that will produce the most compact layout.

(12 marks)

**TERBUKA**

- Q3** (a) (i) List **TWO (2)** sources of leakage current in CMOS transistor. (2 marks)
- (ii) Describe the reason why leakage current increases with the advancement of technology scaling in CMOS transistor. (4 marks)
- (b) A CMOS circuit is shown in **Figure Q3(b)**. The circuit should have an equivalent driving capability of an inverter. The minimum length for each transistor in the circuit is  $2\lambda$  and the electron mobility is three (3) times faster than the mobility of hole.
- (i) Determine the size of each transistor in the circuit to fulfil the stated requirement. (9 marks)
- (ii) Calculate the parasitic delay for the circuit and justify whether the calculated parasitic delay is the minimum value. (5 marks)


 


Figure Q3(b)

TERBUKA

**Q4** (a) Define a hold time for a falling edge triggered flip-flop. Clearly illustrate the hold time using a timing diagram. (4 marks)

(b) (i) A D-latch is shown in **Figure Q4(b)(i)**. Determine the equation for Q of the D-latch. (2 marks)

 

**Figure Q4(b)(i)**

(ii) Draw the circuit inside the D-latch using multiplexer and inverter. (4 marks)

(c) Construct a negative edge D-flip-flop circuit and draw the circuit fully at transistor level. (10 marks)

**TERBUKA**

Q5 (a) Figure Q5(a) is a block diagram of a 1-to-4 demultiplexer.

 


Figure Q5(a)

- (i) Construct a truth table to show the relationship between the data input (D), enable input (E), the select line ( $S_1$  and  $S_0$ ) and the output ( $Y_0$  to  $Y_3$ ).  
(5 marks)
  - (ii) Determine the equation for the output  $Y_n$ .  
(Note: Each student will be assigned to a different output)  
(4 marks)
  - (iii) Design the demultiplexer at transistor level with minimum number of transistors using pseudo-nMOS method by showing the circuit for  $Y_n$ . Clearly label the designed circuit. Assume all the inverted form of the inputs are available.  
(5 marks)
- (b)
- (i) Discuss about controllability and observability, the key concept in Design for Testability (DFT) for integrated circuit (IC).  
(4 marks)
  - (ii) Explain Built-In Self Test (BIST) in Design for Testability (DFT) for integrated circuit (IC).  
(2 marks)

– END OF QUESTIONS –

**TERBUKA**