



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2021/2022**

COURSE NAME : ELECTRICAL AND ELECTRONICS TECHNOLOGY

COURSE CODE : BNJ10903

PROGRAMME CODE : BNL

EXAMINATION DATE : JULY 2022

DURATION : 3 HOURS

INSTRUCTION :
1. ANSWER **ALL** QUESTIONS.
2. THIS FINAL EXAMINATION IS CONDUCTED VIA **CLOSE BOOK**.
3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES DURING THE EXAMINATION CONDUCTED VIA CLOSED BOOK

THIS QUESTION PAPER CONSISTS OF **SEVEN (7)** PAGES

- Q1**
- (a) Based on the circuit in **Figure Q1(a)**;
(i) determine the type of dependent source. (2 marks)
(ii) calculate the current, i_o . (3 marks)
- (b) Identify the equivalent resistance, R_{ab} for the circuit in **Figure Q1(b)**. (10 marks)
- (c) Based on the circuit in **Figure Q1(c)**;
(i) identify the current i and voltage v of the circuit under steady state dc conditions. (6 marks)
(ii) determine the energy stored in the capacitor and inductor. (4 marks)
- Q2**
- (a) Identify the value of V_o for the circuit in **Figure Q2(a)**, by using nodal analysis. (8 marks)
- (b) Verify the answer of V_o in **Question Q2(a)** by using mesh analysis. (7 marks)
- (c) Calculate the voltage V_o for the circuit in **Figure Q2(c)** by using source transformation. (10 marks)
- Q3**
- (a) State Faraday's Law. (2 marks)
- (b) A ferromagnetic core is shown in **Figure Q3(b)**. The depth of the core (into the page) is 5 cm, and the other dimensions are as shown in **Figure Q3(b)**. There are 500 turns coil wrapped around the left side of the core. Assume that the relative permeability of the core is 1000.
- (i) Determine the value of current that will produce a flux of 0.003 Wb. (6 marks)
- (ii) Determine the flux density at the right side of the core. (2 marks)

- (iv) Demonstrate the flow of the magnetic flux induced in the ferromagnetic core in a magnetic circuit analogy. (2 marks)
- (c) Explain **THREE (3)** advantages of AC system over the DC system. (6 marks)
- (d) A circuit is connected to a sinusoidal voltage source having a frequency of 60 Hz, an amplitude of 100 V_{rms} and combination of series resistance, R₁ and R₂. The following circuit is shown in the **Figure Q3(d)**.
- (i) Illustrate the waveform of the signal and label properly the period of the waveform. (2 marks)
- (ii) Determine the rms current, rms voltage, peak voltage, peak-to-peak voltage and average voltage across R₁. (5 marks)
- Q4** (a) The circuit shown in the **Figure Q4(a)**, has $R = 1/3 \Omega$, $L = 1/4 \text{ H}$ and $C = 3 \text{ H}$. The input voltage of the circuit is $v(t) = \sin 2t$. Analyse the circuit and determine:
- (i) the total impedance, Z (3 marks)
- (ii) the total current $i(t)$ (3 marks)
- (iii) the phase angle and its phasor diagram (2 marks)
- (iv) the voltage across each element (3 marks)
- (b) For each clipper circuit shown in **Figure Q4(b)**, draw the output waveform by showing all the necessary steps. In all cases, assume the diodes is made of Si, the peak input voltage is $V_P = V_{in} = 10 \text{ V}$ and the battery voltage is 2 V. (6 marks)
- (c) Build the truth table for the combinational logic circuit shown in **Figure Q4(c)**. (8 marks)

- END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER / SESSION: SEM II / 2021/2022
 COURSE NAME : ELECTRICAL AND ELECTRONICS TECHNOLOGY

PROGRAMME CODE: BNL
 COURSE CODE : BNJ 10903

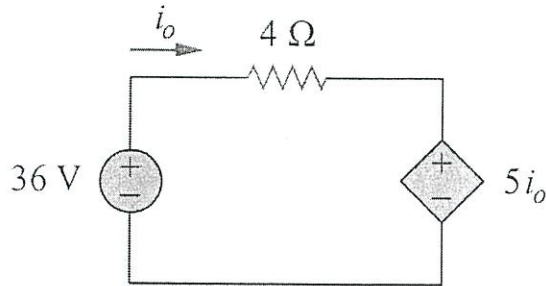


Figure Q1(a)

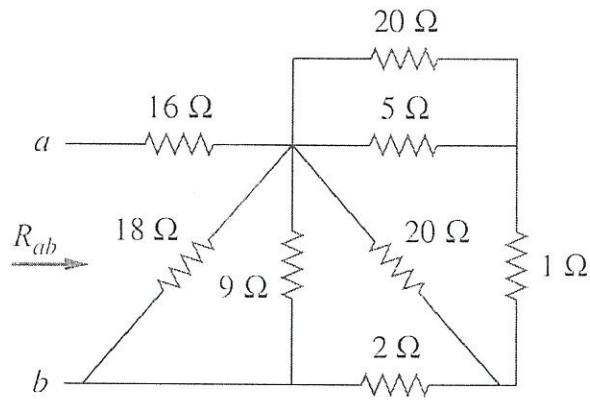


Figure Q1(b)

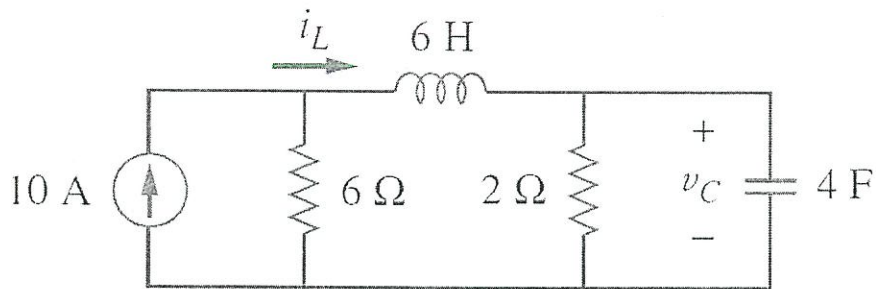


Figure Q1(c)

FINAL EXAMINATION

SEMESTER / SESSION: SEM II / 2021/2022
COURSE NAME : ELECTRICAL AND
ELECTRONICS TECHNOLOGY

PROGRAMME CODE: BNL
COURSE CODE : BNJ 10903

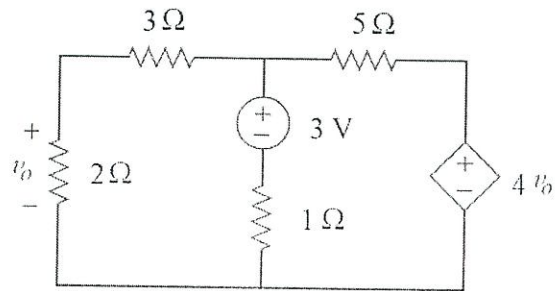


Figure Q2 (a)

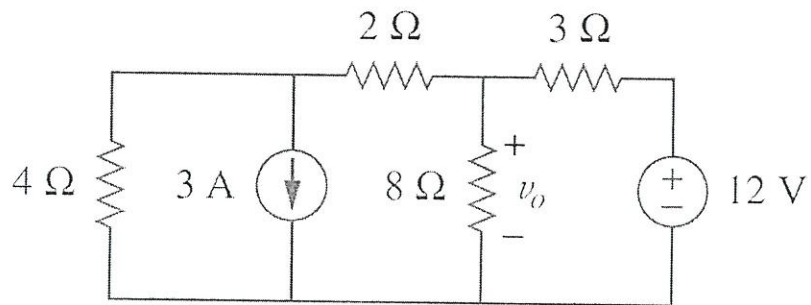


Figure Q2 (c)

FINAL EXAMINATION

SEMESTER / SESSION: SEM II / 2021/2022
COURSE NAME : ELECTRICAL AND
ELECTRONICS TECHNOLOGY

PROGRAMME CODE: BNL
COURSE CODE : BNJ 10903

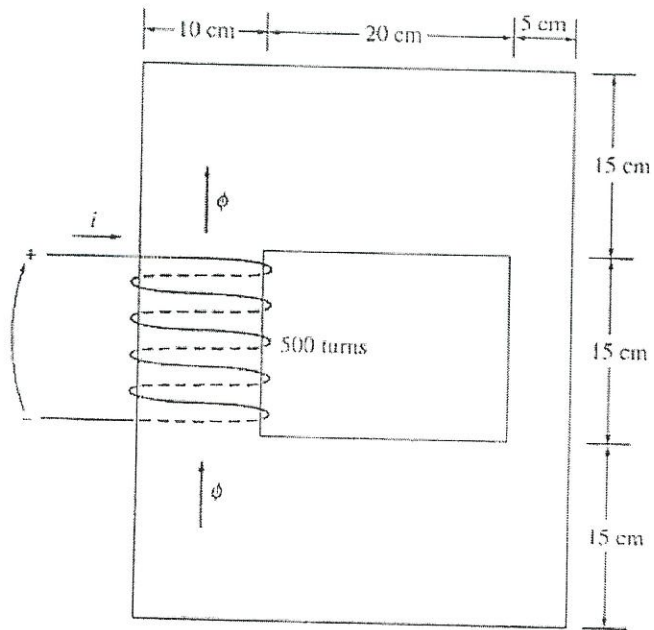


Figure Q3(b)

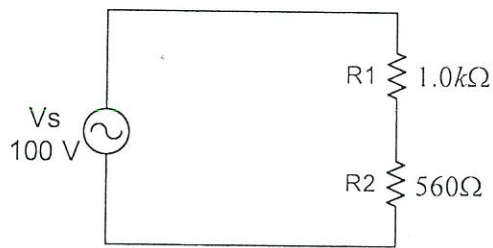


Figure Q3(d)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION: SEM II / 2021/2022
 COURSE NAME : ELECTRICAL AND ELECTRONICS TECHNOLOGY

PROGRAMME CODE: BNL
 COURSE CODE : BNJ 10903

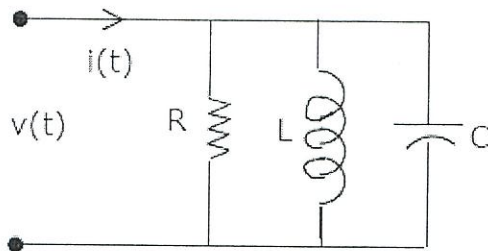


Figure Q4(a)

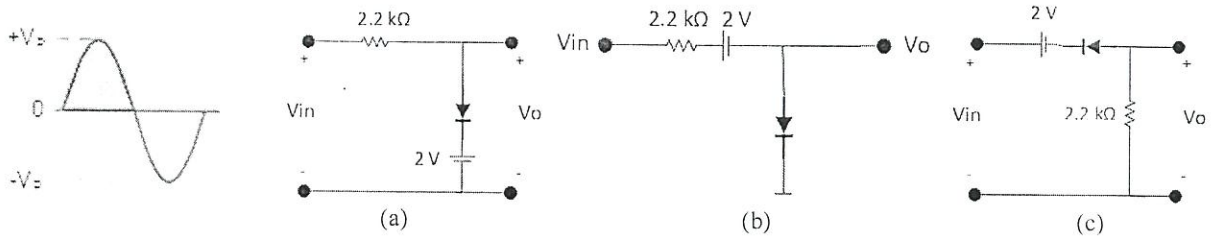


Figure Q4(b)

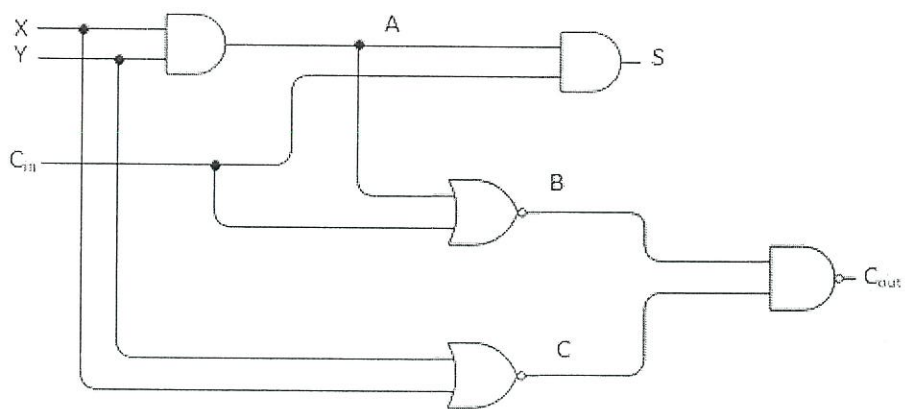


Figure Q4(c)