

**CONFIDENTIAL**



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER 2  
SESSION 2021/2022**

COURSE NAME : ELECTRIC CIRCUITS 1  
COURSE CODE : BEJ 10303  
PROGRAMME CODE : BEJ  
EXAMINATION DATE : JULY 2022  
DURATION : 3 HOURS  
INSTRUCTION : 1. ANSWERS ALL QUESTIONS.  
2. THIS FINAL EXAMINATION IS AN  
**ONLINE ASSESSMENT AND  
CONDUCTED VIA OPEN BOOK.**

THIS QUESTION PAPER CONSISTS OF SEVEN (7) PAGES

**TERBUKA**

**CONFIDENTIAL**

- Q1** (a) An electric element, represented by box A (**Figure Q1(a)**). The direction for the current,  $i$  and the voltage across the element are shown in **Figure Q1(a)**. Calculate the power for the element and state whether the power is being absorbed or supplied for each of the following sets of numerical values:-
- (i)  $i = 1.5 \text{ A}$ ,  $v = 4 \text{ V}$
  - (ii)  $i = -5 \text{ A}$ ,  $v = 25 \text{ V}$
  - (iii)  $i = 10 \text{ A}$ ,  $v = -30 \text{ V}$
  - (iv)  $i = -1 \text{ A}$ ,  $v = -30 \text{ V}$
- (8 marks)
- (b) Describe the voltage divider and current divider rule concept with the aid of a diagram. (6 marks)
- (c) Determine voltage,  $V_o$  in the circuit shown in **Figure Q1(c)**. (6 marks)
- (d) A wiring circuit for a special lamp in a home is shown in **Figure Q1(d)**. The lamp has a resistance of  $2\Omega$  and the lamp will light up when  $I > 50\text{mA}$  but will burn out when  $I > 75\text{mA}$ . Determine the current in the lamp and identify if either it will light up when  $R = 100\Omega$ . (5 marks)
- Q2** (a) Explain the concept of supermesh and supernode in an electric circuit. (4 marks)
- (b) Nodal and mesh analysis provide a systematic way of analysing a complex network. Referring to the circuit in **Figure Q2(b)**, find the value of voltage,  $v_o$  and current,  $i_o$  by using either nodal or mesh analysis. Justify the chosen method. (15 marks)
- (c) By implementing the source transformation theorem, find the value of voltage,  $v_x$  for **Figure Q2(c)** (6 marks)
- Q3** (a) In the network shown in **Figure Q3(a)**, two independent voltage sources act on the elements in the circuit. By using the superposition theorem, calculate the current,  $I_z$ . (15 marks)
- (b) In the circuit shown in **Figure Q3(b)**,
- (i) Find the value of open circuit voltage,  $V_{TH}$  and equivalent resistance,  $R_{TH}$  at terminal a-b. (8 marks)
  - (ii) Draw the Thevenin equivalent circuit at terminal a-b. (2 marks)

- Q4** (a) The circuit shown in **Figure Q4(a)** is used to represent one part of the overall automatic watering system for a plantation in Batu Pahat with the input voltage,  $v_s(t)$ .
- (i) Compute the instantaneous current flows through  $1k\Omega$  resistor over a period and sketch the waveform. (10 marks)
- (ii) Calculate the average and the effective current flows through  $1k\Omega$  resistor. (4 marks)
- (b) Given a voltage and current waveforms  $v(t) = 160 \cos 50t$  V and  $i(t) = -20 \sin (50t - 30^\circ)$  A, being applied to a passive linear network. Find the instantaneous power and average power absorbed by the passive linear network. (5 marks)
- (c) By using an example of a sine wave, describes the difference between the instantaneous value, the average value, and the effective value of this voltage signal. (6 marks)

-END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER / SESSION : SEM 2 2021/2022  
 COURSE NAME : ELECTRIC CIRCUITS 1

PROGRAMME CODE : BEJ  
 COURSE CODE : BEJ 10303

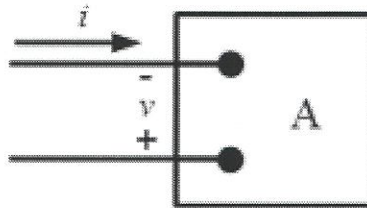


Figure Q1(a)

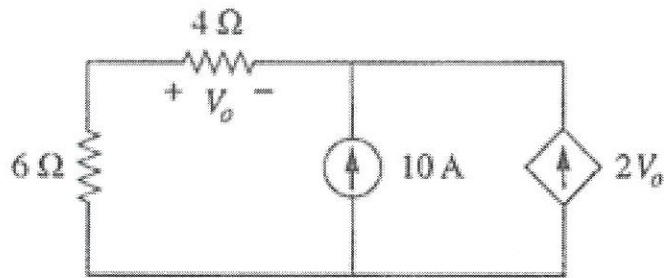


Figure Q1(c)

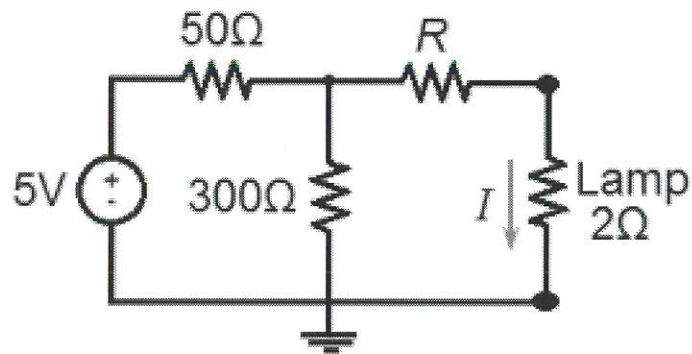


Figure Q1(d)

FINAL EXAMINATION

SEMESTER / SESSION : SEM 2 2021/2022  
COURSE NAME : ELECTRIC CIRCUITS 1

PROGRAMME CODE : BEJ  
COURSE CODE : BEJ 10303

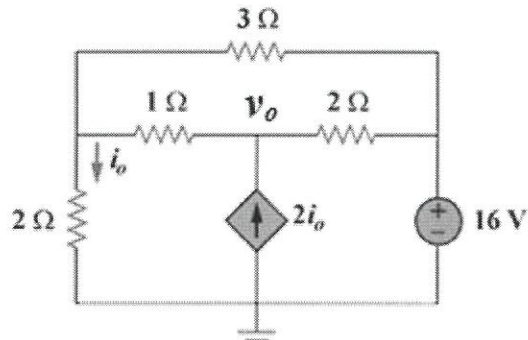


Figure Q2(b)

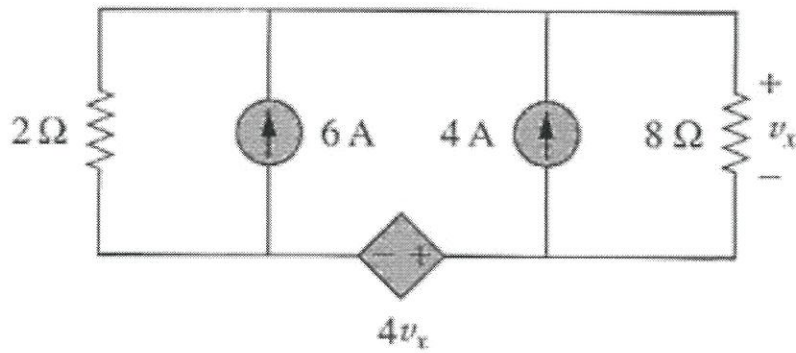


Figure Q2(c)



FINAL EXAMINATION

SEMESTER / SESSION : SEM 2 2021/2022  
 COURSE NAME : ELECTRIC CIRCUITS 1

PROGRAMME CODE : BEJ  
 COURSE CODE : BEJ 10303

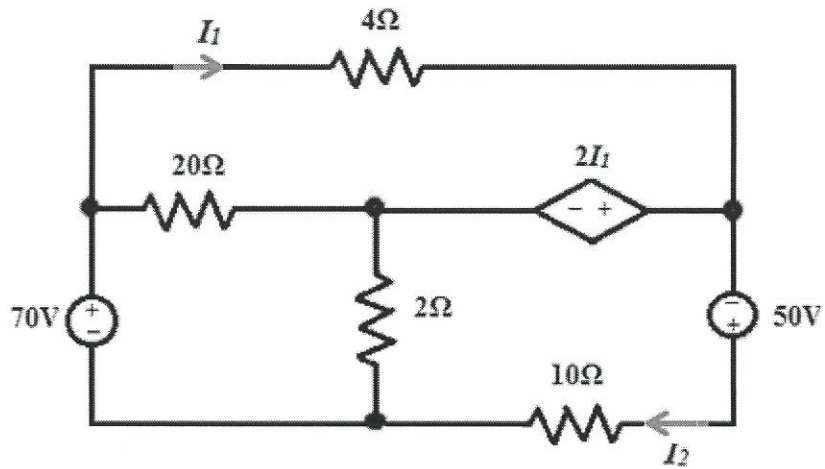


Figure Q3(a)

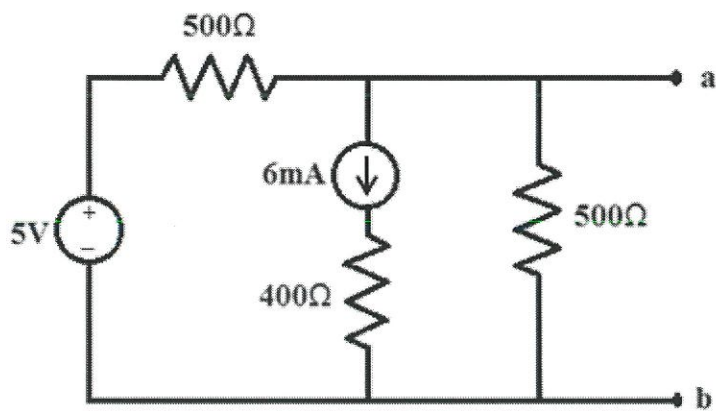


Figure Q3(b)

FINAL EXAMINATION

SEMESTER / SESSION : SEM 2 2021/2022  
COURSE NAME : ELECTRIC CIRCUITS 1

PROGRAMME CODE : BEJ  
COURSE CODE : BEJ 10303

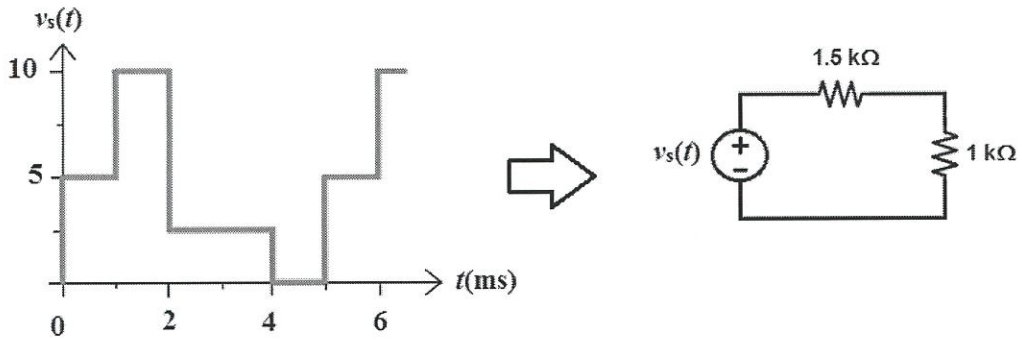


Figure Q4(a)