

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2021/2022**

COURSE NAME : POWER SYSTEMS

COURSE CODE : BEJ 20603

PROGRAMME CODE : BEJ

EXAMINATION DATE : JULY 2022

DURATION : 3 HOURS

INSTRUCTION

1. ANSWER ALL QUESTIONS
2. THIS FINAL EXAMINATION IS AN **ONLINE ASSESSMENT AND CONDUCTED VIA OPEN BOOK**

THIS QUESTION PAPER CONSISTS OF FIVE (5) PAGES

CONFIDENTIAL

TERBUKA

- Q1** (a) (i) Describe the generation of a single phase AC voltage. (2 marks)
- (ii) Sketch the waveform of instantaneous single phase voltage and its direction varying according to the position of the coil within the magnetic field. (4 marks)
- (b) An equivalent circuit of a power system consists of voltage supply, $V_s = 400 V_{\text{rms}}$ and frequency of 50 Hz, respectively is supplying various loads as illustrated in **Figure Q1(b)**. Given $R_1 = 0.5 \Omega$, $R_2 = 2 \Omega$, $L_1 = 4 \text{ mH}$, $L_2 = 2 \text{ mH}$, $C_1 = 1600 \mu\text{F}$, $C_2 = 1000 \mu\text{F}$.
- (i) Find the impedance at each load. (3 marks)
- (ii) Find the current at each load and the total current (4 marks)
- (iii) Compute the complex power at each load. (3 marks)
- (iv) Determine the total real power and reactive power of the system. (2 marks)
- (v) Prove the total complex power in **Q1(b)(iv)** based on the voltage supply and the total current. (2 marks)
- (vi) Draw the phasor diagram and the power triangle of the system and calculate the power factor. (5 marks)
- Q2** (a) A three-phase star-connected source is connected to a three-phase transmission line. The transmission per-phase is $1+j2 \Omega$. The line feeds a balanced delta-connected load, with inductor impedance per-phase is 15 ohm. If the line voltage across the load terminal has a magnitude of 400 V.
- (i) Draw the three-phase circuit of the system. (3 marks)
- (ii) Draw the three-phase Y-Y connected equivalent circuit and find impedance in Y connected per-phase. (2 marks)
- (iii) Draw the equivalent circuit per-phase. (1 mark)

- (iv) Calculate the magnitude of the phase-voltage and the line voltage at the source end. (5 marks)
- (b) A balanced abc sequence source $V_{ab} = 400\angle 30^\circ$ volt is connected to a star-connected (four wires) unbalanced load $Z_{AN} = 8 \Omega$; $Z_{CN} = j8 \Omega$. If the total load is $10000 \text{ W} + j6699 \text{ VAR}$.
- (i) Draw the three-phase circuit and find load voltage per-phase. (5 marks)
- (ii) Calculate the phase current of each load. (7 marks)
- (iii) Determine the load Z_{BN} . (2 marks)
- Q3** (a) A balanced three-phase delta-connected source supplies line current of 8 A to a balanced three-phase load. The source has acb sequence and I_a as reference.
- (i) Draw the three-phase electric source circuit and determine the source line current. (5 marks)
- (ii) Draw phasor diagram of the source line current. (3 marks)
- (b) A balanced abc sequence source $V_{AB} = 400\angle -30^\circ$ volt is connected to a delta-connected unbalanced load $Z_{AB} = 2 \Omega$; $Z_{BC} = 4 + j3 \Omega$ and $Z_{CA} = j5 \Omega$. Assume that the impedance of each transmission line between source and load is ignored.
- (i) Draw the circuit and find load voltage per-phase. (5 marks)
- (ii) Calculate the current of each line source. (6 marks)
- (iii) Determine total real and reactive power of the loads. (4 marks)
- (c) Brief explain reliability of the delta-connected three-phase voltage sources in term of winding failure. (2 marks)

- Q4** (a) A single phase power supply, 230 V_{rms} and 50 Hz is connected to three loads in parallel as follows:
- Load 1 – 10 kW with 0.80 lagging power factor
 - Load 2 – 7 kVA with 0.75 lagging power factor
 - Load 3 – 5 kW with power factor of 0.85 (Inductive load)
- (i) Determine the total complex power and power factor of the power supply. (10 marks)
- (ii) Calculate the total current drawn from the supply. (2 marks)
- (iii) Find the kVAr rating and capacitance required to improve the power factor to 0.95 lagging. (5 marks)
- (iv) Determine the new supply current and reduction of supply current when the capacitor in **Q4(a)(iii)** connected to the system. (4 marks)
- (b) Describe the **TWO (2)** advantages of the high power factor. (4 marks)

-END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER / SESSION : SEM II 2021/2022
COURSE NAME : POWER SYSTEMS

PROGRAMME CODE : BEJ
COURSE CODE : BEJ 20603

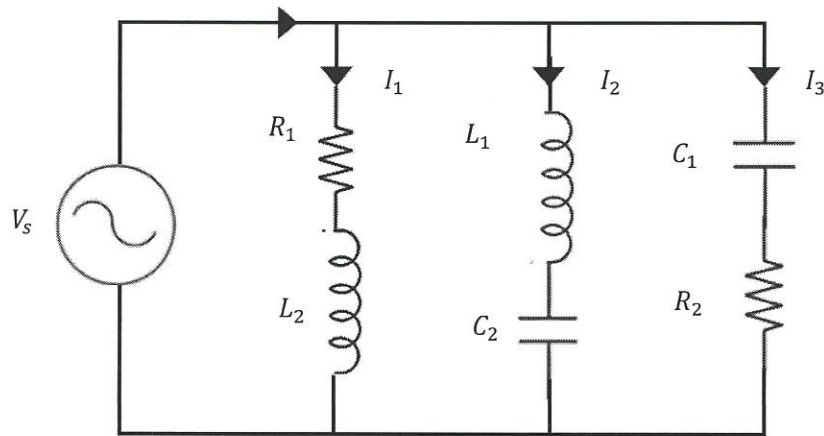


Figure Q1(b)