

**CONFIDENTIAL**



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER I  
SESSION 2021/2022**

COURSE NAME : DIGITAL ELECTRONICS  
COURSE CODE : DAE 21203  
PROGRAMME CODE : DAE  
EXAMINATION DATE : JANUARY / FEBRUARY 2022  
DURATION : 2 HOURS 30 MINUTES  
INSTRUCTION : 1. ANSWER **ALL** QUESTIONS.  
2. THIS FINAL EXAMINATION IS A  
**ONLINE** ASSESSMENT AND  
CONDUCTED VIA **OPEN BOOK**.

THIS QUESTION PAPER CONSISTS OF **SIXTEEN (16)** PAGES


**TERBUKA**

**CONFIDENTIAL**

**PART A: ANSWER ALL QUESTIONS IN THE ANSWER SHEET**

(1 mark each)

- Q1** A quantity that has continuous values is  
 A. a digital quantity  
 B. a binary quantity  
 C. an analog quantity  
 D. a natural quantity
- Q2** Which of the following is not an advantage of digital system?  
 A. Less affected by noise  
 B. Operation can be programmed  
 C. Energy usage is minimal  
 D. Information storage is easy
- Q3** The term *bit* means  
 A. a small amount of data  
 B. binary digit  
 C. a "1" or "0"  
 D. both answers B and C
- Q4** How much time is required for a parallel transfer of 16 bits data if the clock frequency is 100 MHz?  
 A. 10 ms  
 B. 16  $\mu$ s  
 C. 1  $\mu$ s  
 D. 10 ns
- Q5** Which quantity below representing an analog quantity?  
 A. the hourly changes of air temperature  
 B. vehicle speed over an hour  
 C. original sound wave  
 D. recorded data on CD tracks
- Q6** Convert binary 111011110010<sub>2</sub> to hexadecimal.  
 A. EF<sub>16</sub>  
 B. FF<sub>16</sub>  
 C. FE<sub>16</sub>  
 D. FD<sub>16</sub>
- Q7** Convert binary 010111100<sub>2</sub> numbers to octal.  
 A. 172<sub>8</sub>  
 B. 272<sub>8</sub>  
 C. 174<sub>8</sub>  
 D. 274<sub>8</sub>
- Q8** Identify gate X based on the waveform in the **Figure Q8**.

 

**Figure Q8**

- A. AND  
 B. XNOR  
 C. NAND  
 D. XOR

**TERBUKA**

Q9 Find the Boolean expression for the combinational logic circuit in the Figure Q9.

 


Figure Q9

- |    |  |    |  |
|----|--|----|--|
| A. | $Z = (\overline{AB}) \cdot (\overline{ABC}) \cdot (\overline{BC})$ | C. | $Z = (\overline{AB}) + (\overline{ABC}) + (\overline{BC})$         |
| B. | $Z = (\overline{AB}) \cdot (\overline{ABC}) \cdot (\overline{BC})$ | D. | $Z = (\overline{AB}) \cdot (\overline{ABC}) \cdot (\overline{BC})$ |

Q10 A 5 variable Karnaugh map contains

- |    |          |    |          |
|----|----------|----|----------|
| A. | 16 cells | C. | 64 cells |
| B. | 32 cells | D. | 25 cells |

Q11 On a Karnaugh map, grouping the 0s produces

- |    |                          |    |                  |
|----|--------------------------|----|------------------|
| A. | a POS expression         | C. | a SOP expression |
| B. | a "don't care" condition | D. | AND-OR logic     |

Q12 Which one is NOT a valid rule for Boolean algebra?

- |    |                 |    |                 |
|----|-----------------|----|-----------------|
| A. | $A + I = I$     | C. | $A \cdot I = A$ |
| B. | $A \cdot A = A$ | D. | $A + I = A$     |

Q13  $A(A + B) = ?$

- |    |      |    |            |
|----|------|----|------------|
| A. | $AB$ | C. | $(I + AB)$ |
| B. | $I$  | D. | $A$        |

Q14 The AND operation can be produced with

- |    |                |    |                  |
|----|----------------|----|------------------|
| A. | two NAND gates | C. | three NAND gates |
| B. | one NOR gate   | D. | three OR gates   |

Q15 The expression  $\overline{A}BCD + ABC\overline{D} + \overline{A}\overline{B}\overline{C}D$

- |    |  |    |   |
|----|--|----|---|
| A. | cannot be simplified   | C. | is simplified to $ABC\overline{D} + \overline{A}\overline{B}\overline{C}$ |
| B. | is simplified to $\overline{A}BC + \overline{A}\overline{B}$ | D. | None of the answers is correct  |

TERBUKA

Q16 Which of the following input and output value are **incorrect** for the 4-bit parallel binary adder/subtractor circuit in the **Figure Q16**?

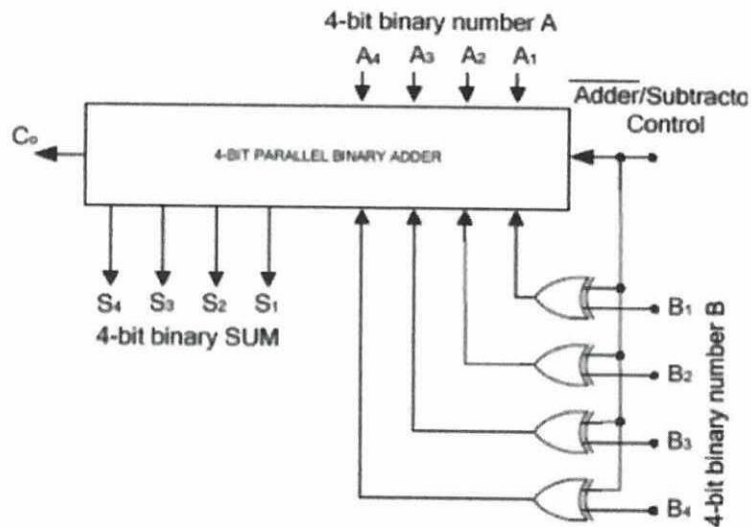


Figure Q16

	[A]	[B]	Adder/Subtractor	Cout	[Σ]
A.	1101	0110	0	1	0011
B.	1001	1000	0	1	0001
C.	1111	1011	1	0	0100
D.	0101	1000	1	0	1011

Q17 Data selectors are basically the same as

- A. decoders
- B. demultiplexers
- C. multiplexers
- D. encoders

Q18 Determine the summation of this binary: 101101+01011

- A. 011010
- B. 1010100
- C. 101110
- D. 1001000

Q19 An example of a SOP expression is

- A.  $A+B(C+D)$
- B.  $(A+B+C)(\bar{A}+B+C)$
- C.  $\bar{A}B+AC+\bar{A}BC$
- D. Both answers A and B

Q20 Add the two BCD numbers: 1001 + 0100

- A. 1101
- B. 00001101
- C. 00010011
- D. 00110001

TERBUKA

Q21 The device shown in the **Figure Q21** is most likely a \_\_\_\_\_

 


Figure Q21

- A. Comparator
- B. Multiplexer
- C. Inverter
- D. Demultiplexer

Q22 To expand a 4 bit parallel adder to an 8 bit parallel adder you must

- A. use 4 bit adders with no connections.
- B. use eight 4 bit adders with no interconnections.
- C. use two 4 bit adders and connect to the sum outputs of one to the bit output of the other.
- D. use two 4 bit adders with the carry output of one connected to the carry input of the other.

Q23 In 1-to-8 demultiplexer, how many select lines are required?

- A. 2
- B. 3
- C. 4
- D. 5

Q24 If a 74LS85 magnitude comparator has  $A = 1011$  and  $B = 1001$  on the inputs, the outputs are:

- A.  $A > B = 0, A < B = 1, A = B = 0$
- B.  $A > B = 1, A < B = 1, A = B = 0$
- C.  $A > B = 1, A < B = 0, A = B = 0$
- D.  $A > B = 0, A < B = 0, A = B = 1$

Q25 The full-adder shown by the **Figure Q25** is tested under all input conditions with the input waveforms shown. From your observation of the SUM and COUT waveforms, is it operating properly, and if not, what is the most likely fault?

 


Figure Q25

- A. Yes, the output SUM and COUT are correct.
- B. No, the input B is accidentally connected to VCC.
- C. No, the input CIN is accidentally connected to VCC.
- D. No, the input A is accidentally connected to VCC.



**Q26** Table shown is a truth table for a 4-to-2 line priority encoder. Determine the correct combination of inputs and outputs.

	Inputs				Outputs		
	En	D0	D1	D2	D3	A1	A0
A.	0	0	0	0	1	x	x
B.	1	1	0	0	1	0	0
C.	1	0	1	0	1	0	1
D.	1	0	0	1	1	1	1

**Q27** The following data input has been applied to the multiplexer shown in **Figure Q27(a)**:  $D_0=0$ ,  $D_1=1$ ,  $D_2=1$ , and  $D_3=0$ . The data-select inputs to the multiplexer are sequenced as shown by the waveforms in **Figure Q27(b)**, determine the output waveform.


 


Figure Q27

 

TERBUKA

Q28 What is the combinational logic circuit in the Figure Q28 represent?


 


Figure Q28

 - A. 3-to-8 decoder
  - B. BCD-to-7 segment decoder
  - C. 3-to-8 encoder
  - D. 8-to-3 encoder
- Q29 2's complement of 1011101 is
- A. 0101110
  - B. 1001101
  - C. 0100010
  - D. 0100011
- Q30 Serial data transmission is employed to send data from a computer to a modem. The least significant bit is sent first. What is the data received at the modem if the data is 01001110?
- A. 01001110
  - B. 01100010
  - C. 01110010
  - D. 01011110
- Q31 A \_\_\_\_\_ is a combinational circuit element that selects data from one of many inputs and directs it to a single output.
- A. encoder
  - B. decoder
  - C. multiplexer
  - D. demultiplexer
- Q32 Convert the following binary number into gray code: 100101<sub>2</sub>
- A. 101101<sub>GRAY</sub>
  - B. 001110<sub>GRAY</sub>
  - C. 110111<sub>GRAY</sub>
  - D. 111001<sub>GRAY</sub>
- Q33 In a 4 variable Karnaugh map , a 2- variable a product term is produced by grouping
- A. two adjacent cells of bit 1s
  - B. two adjacent cells of bit 0s
  - C. four adjacent cells of bit 1s
  - D. eight adjacent cells of bit 1s
- Q34 In 1-to-4 demultiplexer, if S1 = 1 & S2 = 1, then the output will be
- A. Z0
  - B. Z1
  - C. Z2
  - D. Z3



- Q35** How many inputs will a decimal-to-BCD encoder have?  
A. 4  
B. 8  
C. 10  
D. 16
- Q36** How many outputs will a decimal-to-BCD encoder have?  
A. 4  
B. 8  
C. 10  
D. 16
- Q37** How many VALID entries for an R-S flip-flop?  
A. 1  
B. 2  
C. 3  
D. 4
- Q38** Which of the following is correct for a gated D-type flip-flop?  
A. The Q output is either SET or RESET as soon as the D input goes HIGH or LOW  
B. The output complement follows the input when enabled  
C. Only one of the inputs can be HIGH at a time  
D. The output toggles if one of the inputs is held HIGH
- Q39** A counter circuit is usually constructed of \_\_\_\_\_  
A. A number of latches connected in cascade form  
B. A number of NAND gates connected in cascade form  
C. A number of flip-flops connected in cascade  
D. A number of NOR gates connected in cascade form
- Q40** BCD counter is also known as \_\_\_\_\_  
A. Parallel counter  
B. Decade counter  
C. Synchronous counter  
D. Asynchronous counter

**TERBUKA**



**PART A: ANSWER SHEET**

Q1	
Q2	
Q3	
Q4	
Q5	
Q6	
Q7	
Q8	
Q9	
Q10	
Q11	
Q12	
Q13	
Q14	
Q15	
Q16	
Q17	
Q18	
Q19	
Q20	

Q21	
Q22	
Q23	
Q24	
Q25	
Q26	
Q27	
Q28	
Q29	
Q30	
Q31	
Q32	
Q33	
Q34	
Q35	
Q36	
Q37	
Q38	
Q39	
Q40	

**TERBUKA**

**PART B: ANSWER ALL QUESTIONS**

**Q1** Given Boolean expression of:

$$Z = \bar{C} \cdot \bar{D} + A \cdot \bar{B} \cdot \bar{D} + \bar{A} \cdot B + A \cdot B \cdot D + B \cdot C$$

(a) Change the Boolean expression to its standard SOP form.

(4 marks)

ANSWER:

(b) Obtain the truth table for the logic circuit showing all inputs, A, B, C and D and output, Z.

(4 marks)

ANSWER:

**TERBUKA**

- (c) By using the Karnaugh map method shown in **Figure Q1(c)**, show that the Boolean expression can further be simplified.

(6 marks)

ANSWER:

Z	$\bar{C}$ $\bar{D}$	$\bar{C}$ D	C D	C $\bar{D}$
$\bar{A}$ $\bar{B}$				
$\bar{A}$ B				
A B				
A $\bar{B}$				

**Figure Q1(c)**

- (d) Construct the circuit of simplified expression in **Q1(c)** with NAND gates only.

(6 marks)

ANSWER:

(This area is left blank for the student to provide the circuit diagram for part (d).)

**TERBUKA**

**Q2** (a) Design a system with four inputs, P, Q, R and S, and one output, Z such that  $Z = 1$  if three or more of the inputs are 0.

(i) Build the truth table for the system.

(4 marks)

ANSWER:

(ii) Construct the circuit of the system using 16-to-1 multiplexer

(6 marks)

ANSWER:

**TERBUKA**

- (b) Circuit in **Figure Q2(b)(i)** has three inputs (A, B and C) and one output (Z), connected to a decoder IC 74LS138 and NAND gate IC SN7420N. Construct and fill in the truth table shown in **Table Q2(b)** for the output, Z. Refer to **Figure Q2(b)(ii)** for datasheet pin assignment.

(10 marks)

 


Figure Q2(b)(i)

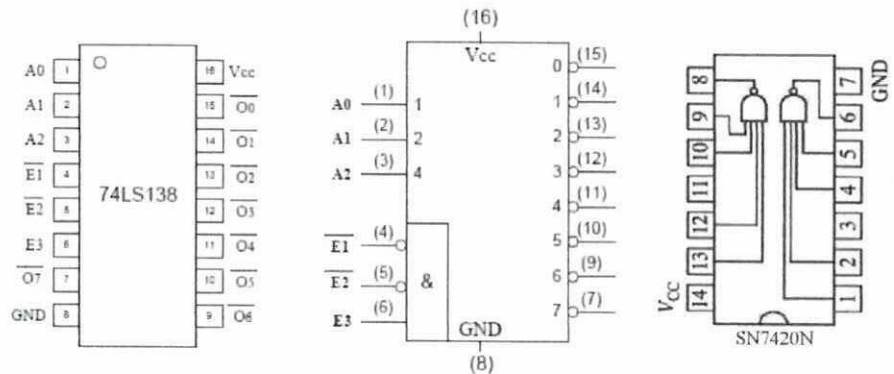


Figure Q2(b)(ii)

ANSWER:

Table Q2(b)

C	B	A	Z

TERBUKA

**Q3** (a) The waveforms for signals A and B shown in **Figure Q3(a)(i)** are applied to the circuit shown in **Figure Q3(b)(ii)**. Evaluate the waveforms for P, Q, R and S in the **Figure Q3(a)(iii)**. Assumes that initially R=0 and S=1.

(6 marks)

 


Figure Q3(a)(i)

 


Figure Q3(a)(ii)

ANSWER:

 


Figure Q3(a)(iii)

TERBUKA

- (b) Design a synchronous counter using JK flip-flop to count 4 digits number. The count sequence is 2,0,1,3 and repeat. The JK excitation table is shown in **Table Q3(b)**. Show all steps and the design should include the following :

**Table Q3(b): JK FF's Excitation Table**

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

- (i) State diagram.

(2marks)

ANSWER:

- (ii) Excitation table.

(4 marks)

ANSWER:

**TERBUKA**

(iii) K-maps to generate minimal expression.

(4 marks)

ANSWER:

(iv) Circuit implementation.

(4 marks)

ANSWER:

- END OF QUESTIONS -

**TERBUKA**