

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2014/2015**

COURSE NAME : LOGIC SYSTEMS
COURSE CODE : DAE 21603
PROGRAMME : 2 DAE
EXAMINATION DATE : DECEMBER 2014/ JANUARY 2015
DURATION : 2 HOURS 30 MINUTES
INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF NINE (9) PAGES

CONFIDENTIAL

- Q1** (a) With the aid of truth tables, describe the differences between the following flip flops:
- (i) RS flip flop
 - (ii) JK flip flop
 - (iii) D flip flop
- (8 marks)
- (b) Given J, K, Preset, Clear and Clock input for a JK flip-flop in **Figure Q1(b)**.
- (i) Draw the Q output waveform.
 - (ii) Explain the operation of this JK flip-flop.
- (10 marks)
- (c) For the circuit in **Figure Q1(c)**:
- (i) State the function of this circuit
 - (ii) Determine the external resistors R1 and R2 to give an output frequency of 10 kHz and duty cycle of 60% if the external capacitor C is 3 nF.
- (7 marks)
- Q2** (a) State the key difference between flip-flops and latches.
- (3 marks)
- (b) Connect 3 negative edge triggered JK Flip flops as an asynchronous count up counter. This flip-flop has an active low asynchronous clear input.
- (i) Draw the circuit diagram
 - (ii) Draw the timing diagram (Use **Figure Q2(b)**) and show the count sequence.
 - (iii) Modify the circuit to operate as a MOD 6 counter.
 - (iv) If the input clock frequency is 2 kHz, determine the output frequency of the MOD 6 counter.
- (11 marks)
- (c) Design a synchronous counter using JK flip-flops to count 4 digits. The count sequence is 2,0,3,1 and repeat. The JK excitation table is shown in **Table Q2**. Show all steps and the design should include the following:
- (i) State diagram
 - (ii) Circuit excitation table used to determine JK flip-flop inputs.
 - (iii) K-maps used to generate minimal expressions for JK inputs.
 - (iv) Logic circuit.
- (11 marks)

- Q3** (a) Show the following connections:
- (i) Use JK flip-flops to divide a digital signal frequency by 8.
 - (ii) Use D-type flip-flops to divide a digital signal frequency by 4. (6 marks)
- (b) The logic diagram and Dual-In-Line Package for IC 7493 is given in **Figure Q3(b)**. Draw the connections diagrams for the following 7493-based counters and determine the output frequency if the input clock frequency is 100 kHz. Show all steps and label the input clock as well as the outputs.
- (i) MOD 8 counter
 - (ii) MOD 16 counter
 - (iii) MOD 11 counter. (11 marks)
- (c) Determine the maximum input clock frequency (f_{\max}) for the counter shown in **Figure Q3(c)** if the propagation delay, t_{pd} for each flip-flop is 50 ns and t_{pd} for AND gate is 20 ns. Compare this with a MOD-16 ripple counter. (8 marks)
- Q4** (a) Determine the number of flip-flops needed to construct a shift register capable of storing:
- (i) a 5-bit binary number
 - (ii) decimal numbers up to 32
 - (iii) hexadecimal numbers up to E. (5 marks)
- (b) With the aid of logic circuits and tables showing the sequence of states, describe the differences between a Ring counter and a Johnson counter. (12 marks)
- (c) **Figure Q4(c)** shows a bidirectional shift register. The serial input (IN) is LOW. Assume that initially outputs $Q_0Q_1Q_2Q_3 = 1010$. Do the following if $\overline{RIGHT/LEFT}$ input is held HIGH.
- (i) Analyze **two (2)** of the combinational logic circuit outputs to determine how the output of each flip-flop is connected. Show all steps.
 - (ii) Redraw the 4 flip-flops (without showing the combinational circuits) indicating the correct shift. (8 marks)

- Q5** (a) Describe **five (5)** basic steps taken to create and load a digital circuit into a PLD?
(5 marks)
- (b) Name **three (3)** advantages of constructing a digital circuit prototype using a PLD instead of standard logic devices.
(3 marks)
- (c) Several types of architecture are used in PLDs. Draw the block diagram of three common types and describe their differences.
(6 marks)
- (d) Use the PLA in **Figure Q5(d)** to implement the following functions. Label all inputs and outputs.
- (i) $F1(W, X, Y) = \sum(1,2,3,5,7)$
(ii) $F2(W, X, Y) = \sum(0,4,6,7)$
(11 marks)
- Q6** (a) **Figure Q6(a)** shows a simplified view of a typical computer system.
- (i) Describe the semiconductor memory devices used.
(ii) Explain the differences between the **three (3)** storage devices based on the technology each uses.
(iii) Describe the functions of the **three (3)** buses shown.
(13 marks)
- (b) A certain memory has a capacity of 4K x 8, determine
- (i) the number of data inputs and data outputs .
(ii) the number of address lines.
(iii) its capacity in bytes.
(6 marks)
- (c) List and describe the **three (3)** major operations in a flash memory.
(6 marks)

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015
 COURSE NAME : LOGIC SYSTEMS

PROGRAMME : 2 DAE
 COURSE CODE: DAE 21603

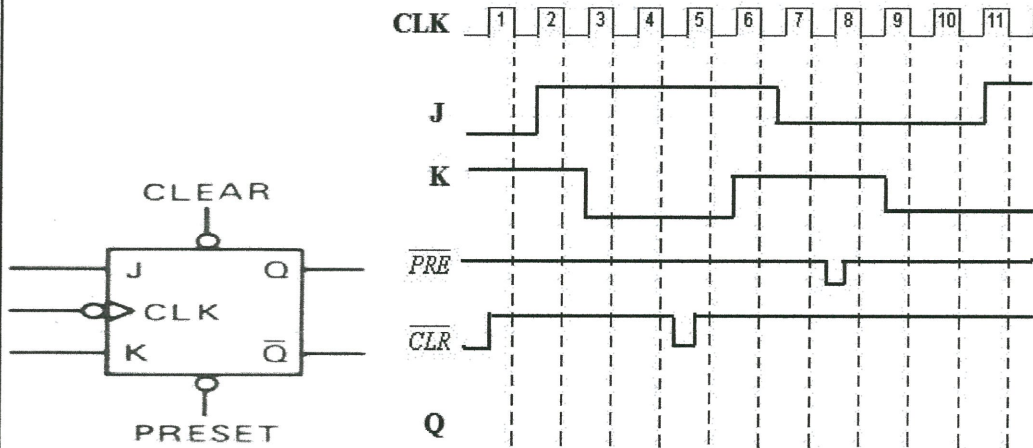


FIGURE Q1(b)

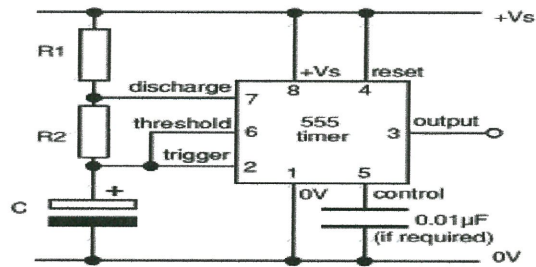


FIGURE Q1(c)

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015
 COURSE NAME : LOGIC SYSTEMS

PROGRAMME : 2 DAE
 COURSE CODE: DAE 21603

 


FIGURE Q2(b)

TABLE Q2: JK Excitation Table

| Q(t) | Q(t+1) | J | K |
|------|--------|---|---|
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | X |
| 1 | 0 | X | 1 |
| 1 | 1 | X | 0 |

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015
 COURSE NAME : LOGIC SYSTEMS

PROGRAMME : 2 DAE
 COURSE CODE: DAE 21603

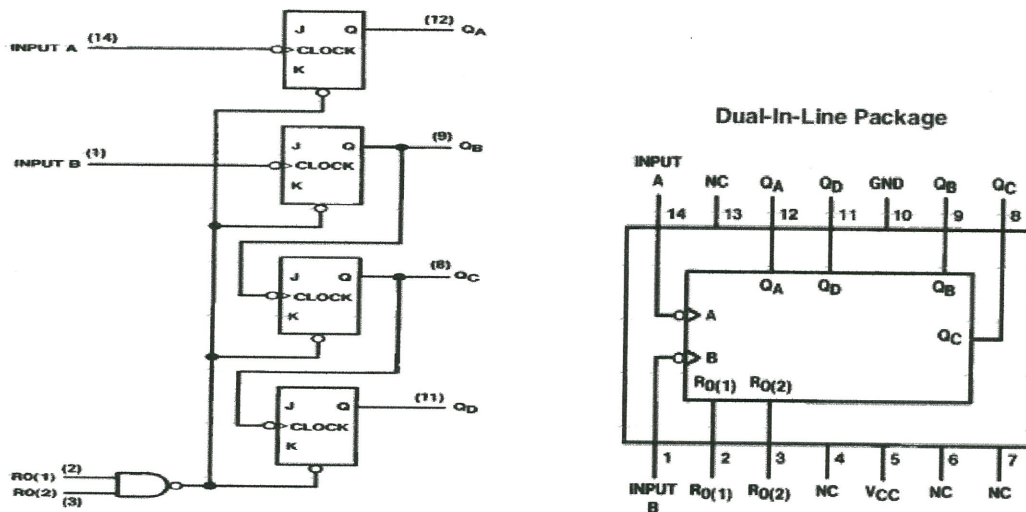


FIGURE Q3(b)

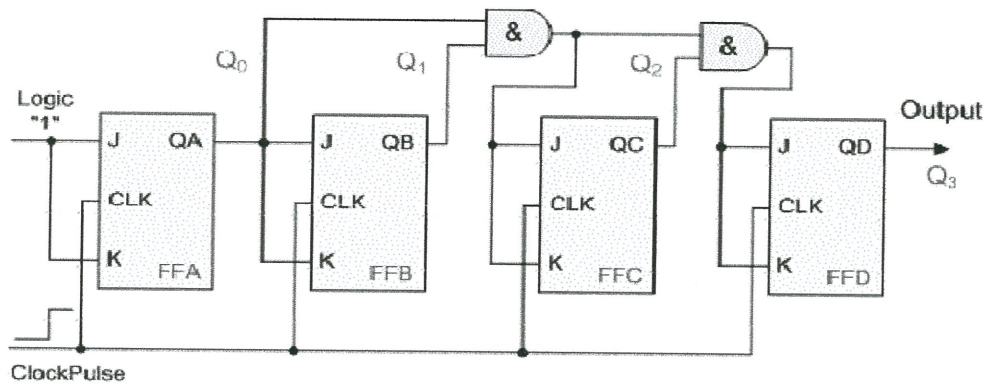


FIGURE Q3(c)

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015
 COURSE NAME : LOGIC SYSTEMS

PROGRAMME : 2 DAE
 COURSE CODE: DAE 21603

 


FIGURE Q4(c)

 


FIGURE Q5(d)

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015
COURSE NAME : LOGIC SYSTEMS

PROGRAMME : 2 DAE
COURSE CODE: DAE 21603

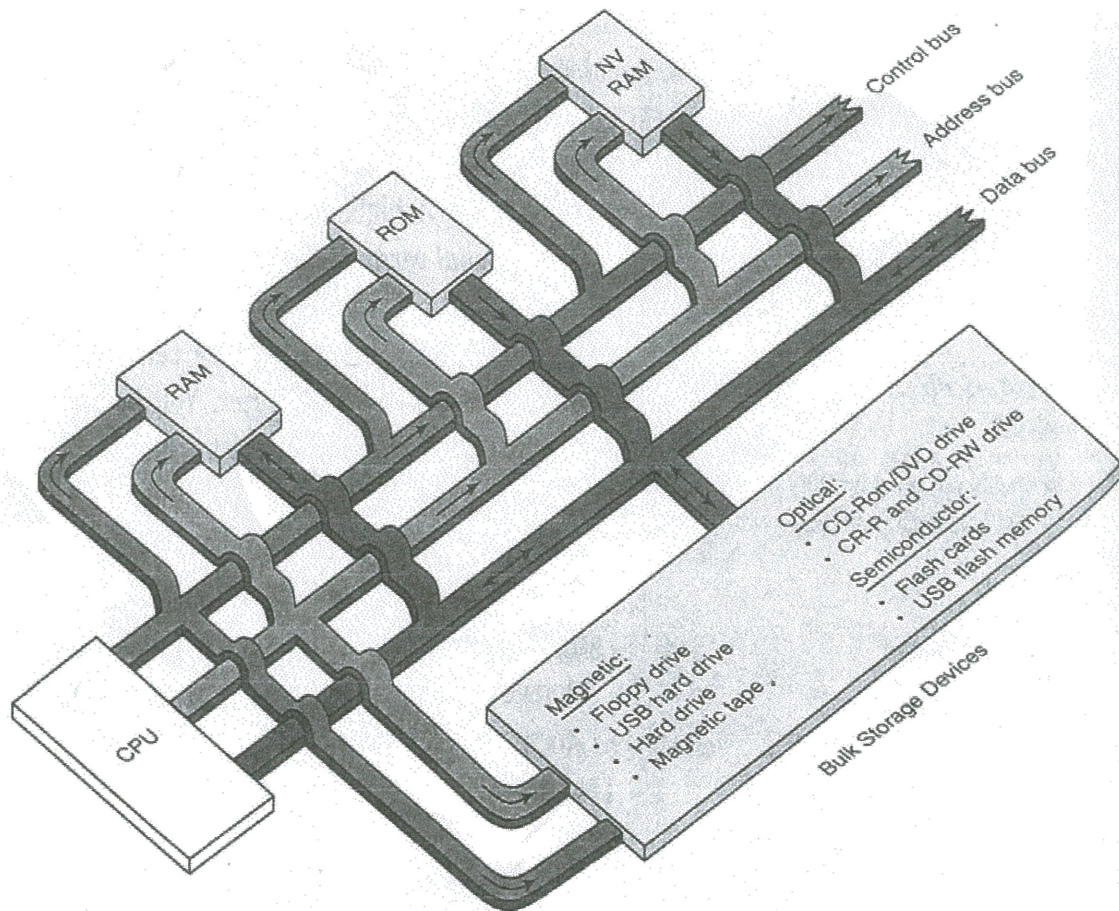


FIGURE Q6(a)