



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESI 2022/2023**

COURSE NAME : FUNDAMENTAL OF ELECTRICAL TECHNOLOGY

COURSE CODE : BBP 10703

PROGRAMME CODE : BBG

EXAMINATION DATE : JULY / AUGUST 2023

DURATION : 3 HOURS

INSTRUCTION

1. ANSWER **ALL** QUESTIONS
2. THIS FINAL EXAMINATION IS CONDUCTED VIA **CLOSED BOOK**
3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES DURING THE EXAMINATION CONDUCTED VIA CLOSED BOOK

THIS QUESTION PAPER CONSISTS OF **SIX** (6) PAGES

- Q1**
- (a) Explain how an electricity is produced from light. (5 marks)
  - (b) Explain how an electricity is produced in chemical action. (6 marks)
  - (c) Explain how an electricity is produced in wet cells and give **TWO** (2) examples of its uses. (6 marks)
  - (d) Discuss the principal of operation of the thermocouple and use a sketch to support your answer. (8 marks)

- Q2**
- (a) Define a resistor in detail. (4 marks)
  - (b) List **FIVE** (5) uses of resistor. (5 marks)
  - (c) In some motor vehicles, the length of the motor copper cable (motor stator) is 1.3m. Cable resistance is  $0.007\Omega$ . Calculate the value of the diameter of the cable if the copper resistance is  $1.92 \times 10^{-8}\Omega\text{m}$ . (8 marks)
  - (d) Interpret the value of the resistance according to the colors below. Obtain your answer using the resistor color code in **Figure Q2(d)**; indicate the maximum and the minimum values of the resistor.
    - 1) Violet.
    - 2) Yellow.
    - 3) Black.
    - 4) Green.
    - 5) Gold.
 (8 marks)

- Q3**
- (a) Sketch the following Figures as instructed below:
    - a) T-Connection and Star Equivalent Network.
    - b) Pi -Connection and Delta equivalent network.
 (6 marks)
  - (b) Calculate the power consumed in the circuit in **Figure Q3(b)**. (6 marks)
  - (c) Discuss the procedure steps to measure a resistance using a multimeter. (7 marks)
  - (d) Calculate the total current ( $I_T$ ) of the series-parallel circuit as shown in **Figure Q3(d)**, if the source voltage (V) applied to the circuit is 25volts. (6 marks)

- Q4**
- (a) State the Ohm's Law. (4 marks)
  - (b) Calculate the total inductance ( $L_{AB}$ ) for the circuits in **Figure Q4(b)**. (5 marks)
  - (c) Identify the different types of capacitor symbols in **Figure Q4(c)**. (3 marks)
  - (d) Calculate the total Capacitance ( $C_{AB}$ ) for the circuits in **Figure Q4(d)**. (5 marks)
  - (e) Analyze the graph in **Figure Q4(e)** and write down the different information in the provided squares. (8 marks)


- END OF QUESTIONS -

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION: SEM II 2022/2023  
 COURSE NAME : FUNDAMENTAL OF ELECTRICAL TECHNOLOGY

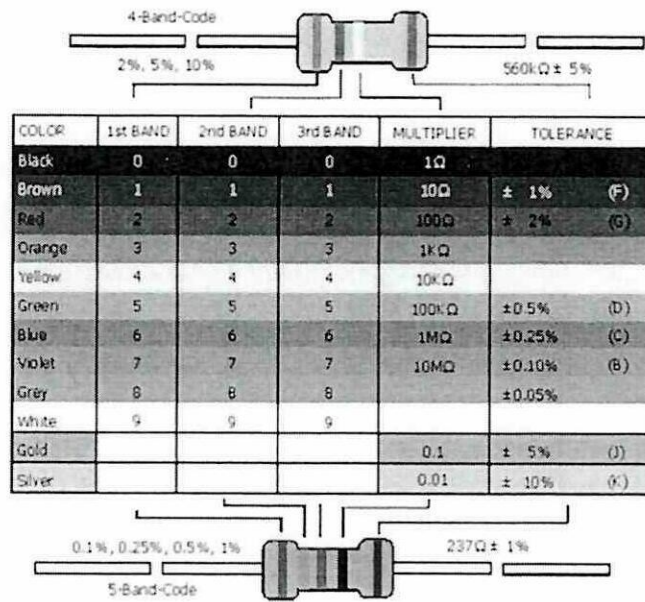PROGRAMME CODE: BBJ  
 COURSE CODE : BBP10703



Electronic Express / RSR  
<http://www.elexp.com>

1-800-972-2225  
 In NJ 732-381-8020

Figure Q2(d)

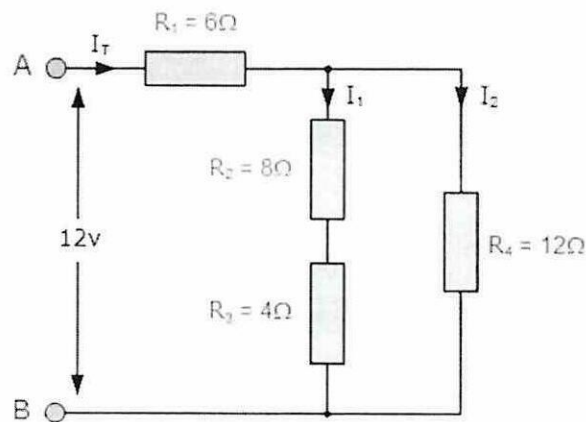


Figure Q3(b)

**TERBUKA**

FINAL EXAMINATION

SEMESTER / SESSION: SEM II 2022/2023  
 COURSE NAME : FUNDAMENTAL OF ELECTRICAL TECHNOLOGY

PROGRAMME CODE: BBJ  
 COURSE CODE : BBP10703

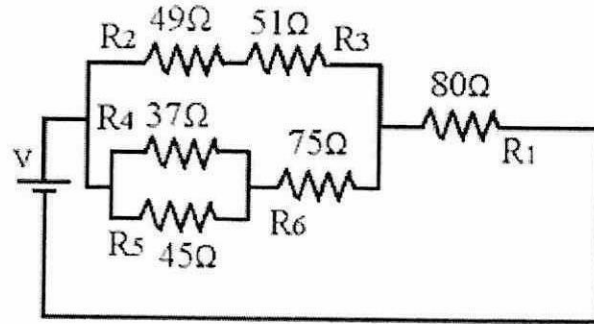


Figure Q3(d)

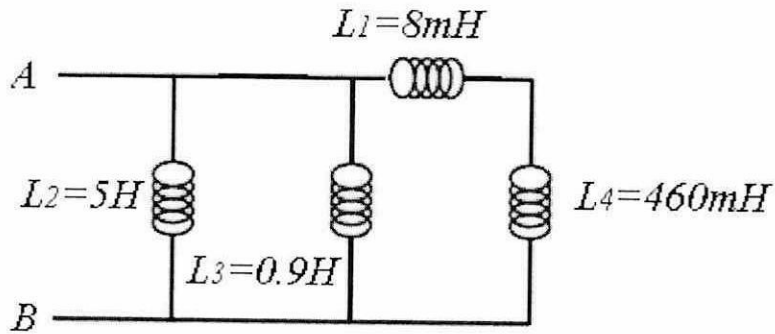


Figure Q4(b)

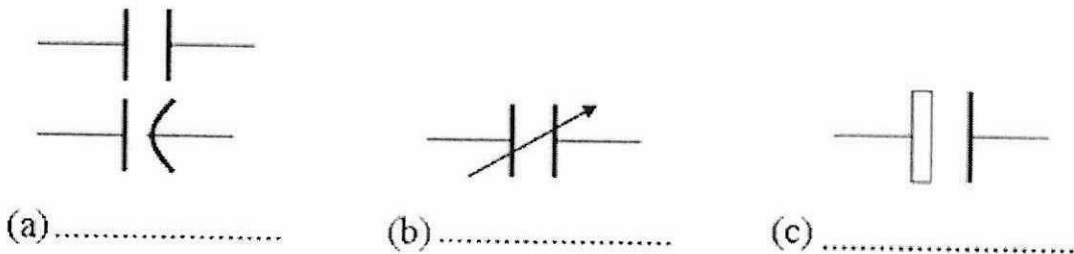


Figure Q4(c)

**TERBUKA**

FINAL EXAMINATION

SEMESTER / SESSION: SEM II 2022/2023  
 COURSE NAME : FUNDAMENTAL OF ELECTRICAL  
 TECHNOLOGY

PROGRAMME CODE: BBJ  
 COURSE CODE : BBP10703

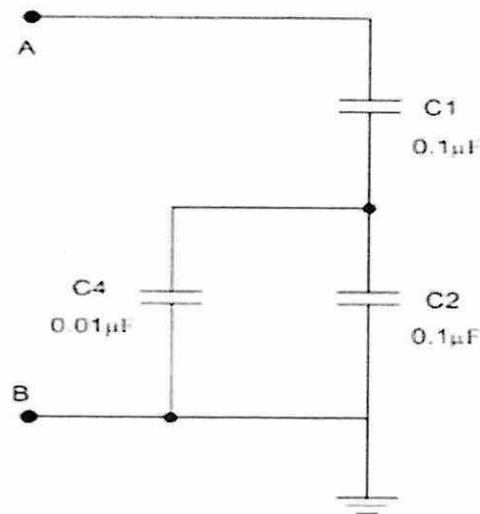


Figure Q4(d)

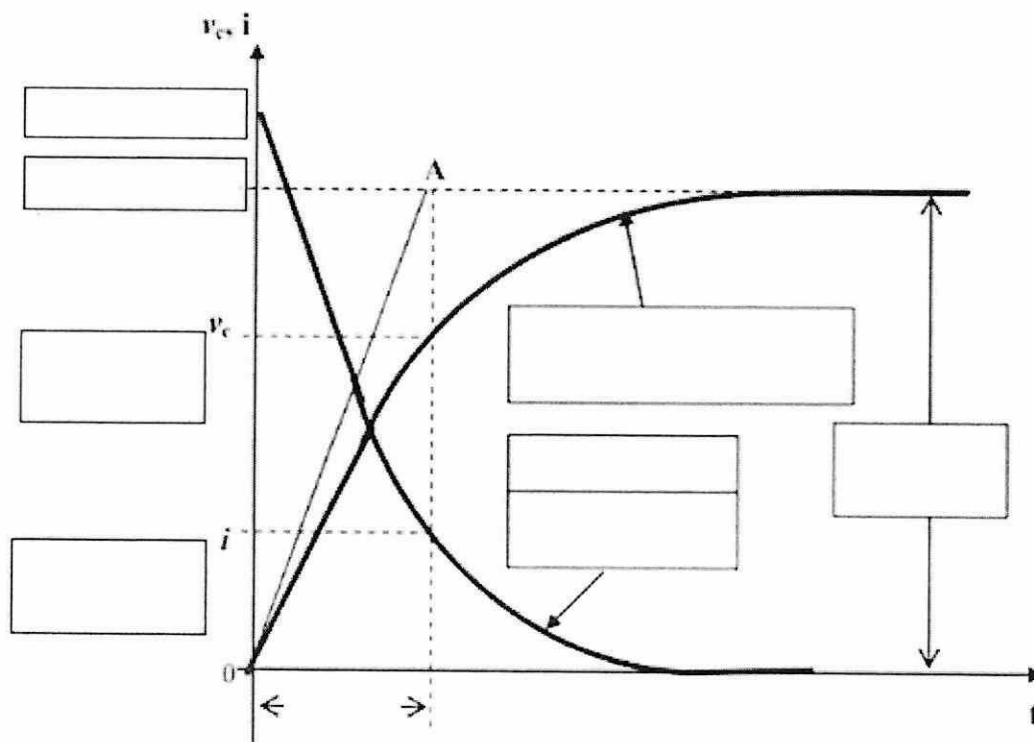


Figure Q4(e)