

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2022/2023**

COURSE NAME : DIGITAL DESIGN

COURSE CODE : BEJ 30503

PROGRAMME CODE : BEJ

EXAMINATION DATE : JULY / AUGUST 2023

DURATION : 3 HOURS

INSTRUCTION : 1. ANSWER **ALL** QUESTIONS
2. THIS FINAL EXAMINATION IS
CONDUCTED VIA **CLOSED BOOK**.
3. STUDENTS ARE **PROHIBITED** TO
CONSULT THEIR OWN MATERIAL OR
ANY EXTERNAL RESOURCES
DURING THE EXAMINATION
CONDUCTED VIA CLOSED BOOK

THIS QUESTION PAPER CONSISTS OF **SIX (6)** PAGES.

CONFIDENTIAL

TERBUKA

CONFIDENTIAL

BEJ 30503

- Q1** (a) Verilog is a popular Hardware Description Language (HDL) used when working with programmable devices.
- Explain the purpose of the language and how it interacts to an actual programmable chip.
(4 marks)
 - Specify **TWO (2)** synthesizable constructs and **TWO (2)** non-synthesizable constructs for Verilog language.
(4 marks)
- (b) **Figure Q1(b)i** and **Figure Q1(b)ii** illustrate schematic circuits of 2-to-1 multiplexer and 4-to-1 multiplexer, respectively.
- Explain the relation between **Figure Q1(b)i** and **Figure Q1(b)ii**.
(4 marks)
 - Specify the methodology being applied to design the circuit of **Figure Q1(b)ii**.
(1 mark)
 - Develop a flow chart to specifically illustrate the process to test the functionality of Verilog code in **Figure Q1(b)ii** using Computer Aided Design (CAD) tool.
(7 marks)
- Q2** (a) Convert the decimal number -120 into signed 8-bit numbers in the following representations:
- Sign and magnitude
(2 marks)
 - 1's complement
(1 mark)
 - 2's complement
(1 marks)
- (b) **Figure Q2(b)** illustrates Functional Block Diagram (FBD) of a four-bit adder-subtractor that is designed using full adder modules. Verilog code of the full adder module is given in **Listing Q2(b)**. Input M controls the operation mode of the FBD.
- Determine the operation mode of the FBD when $M = 0$ and $M = 1$. Justify your answer.
(3 marks)
 - Determine S and c values, if $M = 0$, $A = 1010_2$, $B = 1100_2$.
(3 marks)
 - Write the Verilog gate-level hierarchical description for the FBD of **Figure Q2(b)**.
(10 marks)

CONFIDENTIAL

BEJ 30503

- Q3** (a) Explain the difference between latch and flip-flop. (2 marks)
- (b) **Figure Q3(b)i** shows a simple sequential circuit, while **Figure Q3(b)ii** is input waveform signals to drive the sequential circuit. Sketch output signals for Q_a , Q_b , and Q_c . (6 marks)
- (c) **Figure Q3(c)** gives sample of input and output relation for a sequence detector to detect a pattern of "101". Finite-State Machine (FSM) uses state diagram for representing every possible state behavior for the detector.
- Discuss the concept of Finite-State Machine, FSM state diagram. (4 marks)
 - Derive state diagram for the FSM to capture all possible state behavior given in **Figure Q3(c)**. (8 marks)
- Q4** A digital system is modelled by register transfer level (RTL) code given in **Listing Q4**. The system loads data when $f=0$, while adding A and B values when $f=1$.
- Derive datapath unit for the digital system given in **Listing Q4**. (7 marks)
 - Design FBD control unit (CU) for the digital system. (6 marks)
 - Derive RTL control sequence (RTL-CS) table, for the control vector format $sel1$, LdA , LdB , f , and $done$. (7 marks)
- Q5** Given x and y expressions as follows:
- $$x = e \times (a + b + c) \quad (1)$$
- $$y = (a + c) \times (c + d) \quad (2)$$
- Restructure the expressions by using coarse-level restructuring technique. (2 marks)
 - Create data flow graph (DFG) based on restructured expressions in **Q5(a)**. The DFG must comply the following constraints:
 - One multiplier and one adder resource allocation.
 - Apply 'as late as possible' (ALAP) register allocation.
 - As minimum as possible of total number execution cycles.(8 marks)
 - Derive the datapath unit (DU) based on the DFG in **Q5(b)**. (10 marks)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II 2022/2023
COURSE NAME : DIGITAL DESIGN

PROGRAMME CODE : BEJ
COURSE CODE : BEJ30503

 


Figure Q1(b)i

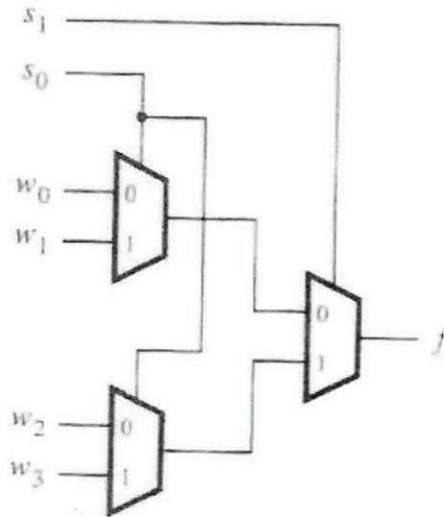


Figure Q1(b)ii

FINAL EXAMINATION

SEMESTER / SESSION : SEM II 2022/2023
 COURSE NAME : DIGITAL DESIGN

PROGRAMME CODE : BEJ
 COURSE CODE : BEJ30503

 


Figure Q2(b)

```

module fulladd (ci, a, b, s, co);
    input ci, a, b;
    output s, co;

    assign s = a^b^ci;
    assign co = (a&b) | (a&ci) | (b&ci);
endmodule
    
```

Listing Q2(b)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM II 2022/2023
COURSE NAME : DIGITAL DESIGN

PROGRAMME CODE : BEJ
COURSE CODE : BEJ30503

 


Figure Q3(b)i

 


Figure Q3(b)ii

Input, w = 100101000010101010001101....

Output, Z = 000001000000101010000001....

Figure Q3(c)

```
S0: Reg1 ← A;  
S1: Reg2 ← Reg1;  
S2: Reg1 ← B;  
S3: Reg1 ← Reg1 + Reg2;  
done
```

Listing Q4