



UTHM

Universiti Tun Hussein Onn Malaysia

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

FINAL EXAMINATION SEMESTER II SESSION 2022/2023

COURSE NAME : ELECTRICAL AND ELECTRONICS TECHNOLOGY

COURSE CODE : BDU 10803

PROGRAMME CODE : BDM

EXAMINATION DATE : JULY/AUGUST 2023

DURATION : 3 HOURS

INSTRUCTION :

1. ANSWER **ALL** QUESTIONS
2. THIS FINAL EXAMINATION IS CONDUCTED VIA **CLOSED BOOK**.
3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES DURING THE FINAL EXAMINATION CONDUCTED VIA CLOSED BOOK.

THIS QUESTION PAPER CONSISTS OF **EIGHT (8)** PAGES

TERBUKA

CONFIDENTIAL

PART A: Answer **all** questions.

- Q1**
- (a) State **three (3)** examples of passive components. (3 marks)
- (b) Define the term “supernode”. (2 marks)
- (c) A circuit in **Figure Q1(c)** is supplied with 40 V voltage source. By transforming the arrangement of the resistors, find:
- (i) the equivalent resistance. (5 marks)
- (ii) the current delivered by the voltage source. (2 marks)
- (iii) the power drain on the voltage source. (2 marks)
- (d) Consider the circuit shown in **Figure Q1(d)**. By using mesh-current method, determine:
- (i) the mesh currents. (6 marks)
- (ii) the power associated with each voltage source. (3 marks)
- (iii) the voltage v_o across the 8Ω resistor. (2 marks)
- Q2**
- (a) State **four (4)** factors that can affect the value of inductance in a solenoid. (4 marks)
- (b) A circuit shown in **Figure Q2(b)** is connected to a 75 mA current source. Examine the circuit and determine:
- (i) the Thevenin’s voltage with respect to the terminals a,b. (7 marks)
- (ii) the Norton’s equivalent circuit with respect to the terminals a,b. (5 marks)
- (c) A sinusoidal voltage is given by the expression $v = 300 \cos(120\pi t + 30^\circ)$. Calculate:
- (i) The period of the voltage in milliseconds. (2 marks)
- (ii) The frequency in hertz (2 marks)
- (iii) The magnitude of v at $t = 2.778$ ms (3 marks)
- (iv) The rms value of v (2 marks)

- Q3**
- (a) Analyze the logic circuit in **Figure Q3(a)** and derive the Boolean expression for the intermediate and the final outputs. (7 marks)
 - (b) Construct a truth table for the Boolean expression in **Q3(a)**. (5 marks)
 - (c) Distinguish a single logic gate that can be applied to replace the entire circuit in **Figure Q3(a)**. (2 marks)
 - (d) Reconstruct the combinational logic circuit in **Figure Q3(a)** using only NAND gate. (5 marks)
 - (e) Draw a logic gate circuit for this function:
$$A\bar{B} + \bar{C}(A + B)$$
 (6 marks)

PART B: Answer **one (1)** question only.

- Q4** (a) A bar magnet has two poles. Sketch the magnetic field pattern around the bar magnet and explain what the flux lines represent. (6 marks)
- (b) Discuss the difference between permanent magnet and electromagnet in terms of the following:
- (i) production of magnetic field
 - (ii) strength of the magnetic field
 - (iii) control of the magnetic field
- (6 marks)
- (c) Describe **two (2)** ways to increase the strength of a magnetic field. (4 marks)
- (d) Draw the structure of a basic transformer and its symbol. Label the core, primary winding and secondary winding. (5 marks)
- (e) Differentiate the primary winding and the secondary winding of a transformer. (4 marks)
- Q5** (a) Differentiate generators and motors in terms of their energy conversion characteristics. (2 marks)
- (b) The basic parts of any DC machine are a stator and a rotor. Describe the behavior of each of them and what they are comprised of. (6 marks)
- (c) Explain **three (3)** advantages and disadvantages of a brushed DC motor. (6 marks)
- (d) Sketch the basic diode structure and symbol. Provide a proper labelling and explanation. (5 marks)
- (e) Describe **three (3)** types of diodes and their functions. (6 marks)

– END OF QUESTIONS –

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2022/2023
 COURSE NAME : ELECTRICAL AND ELECTRONIC TECHNOLOGY

PROGRAMME CODE: BDM
 COURSE CODE: BDU10803

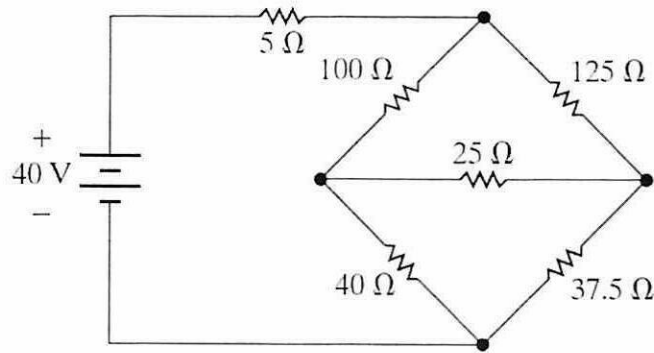


Figure Q1(c)

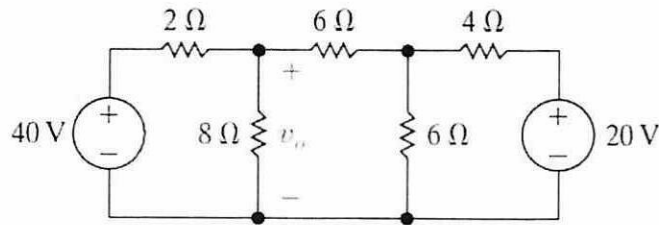


Figure Q1(d)

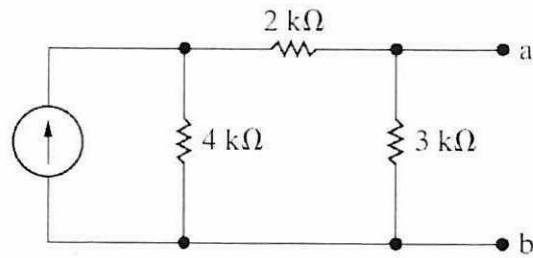


Figure Q2(b)

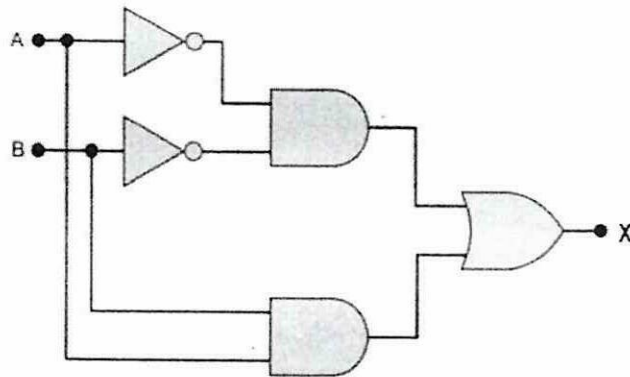


Figure Q3(b)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2022/2023
 COURSE NAME : ELECTRICAL AND ELECTRONIC TECHNOLOGY

PROGRAMME CODE: BDM
 COURSE CODE: BDU10803

LIST OF FORMULA

OHMS LAW

$$V = IR$$

JOULE'S LAW


$$P = IV$$

KIRCHHOFF LAW

$$\sum_{k=1}^n i_k = 0$$

$$\sum_{v=1}^n v_k = 0$$

WYE-DELTA TRANSFORMATION

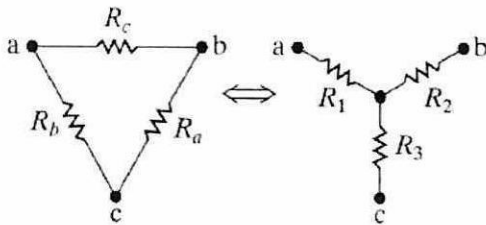

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$


$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

SOURCE TRANSFORMATION

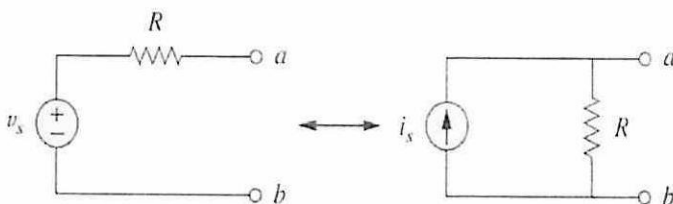

$$V_s = I_s R$$

THEVENIN AND NORTON EQUIVALENT CIRCUIT

$$R_{TH} = R_N$$

$$I_N = \frac{V_{TH}}{R_{TH}}$$

$$P = i^2 R_L = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

When $R_L \neq R_{TH}$

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}}$$

When $R_L = R_{TH}$

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2022/2023
 COURSE NAME : ELECTRICAL AND ELECTRONIC TECHNOLOGY

PROGRAMME CODE: BDM
 COURSE CODE: BDU10803

THEVENIN AND NORTON EQUIVALENT CIRCUIT

$$R_{TH} = R_N$$

$$I_N = \frac{V_{TH}}{R_{TH}}$$


$$P = i^2 R_L = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

When $R_L \neq R_{TH}$

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}}$$

When $R_L = R_{TH}$

MAXIMUM POWER TRANSFER

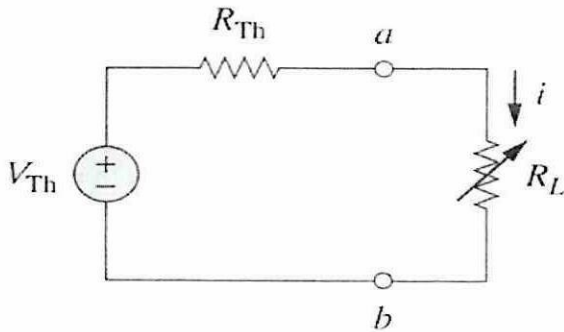

$$P = i^2 R_L = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

CAPACITOR AND INDUCTOR

$$C = \frac{\epsilon A}{d}$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt + v(t_0)$$

$$i = C \frac{dv}{dt}$$

$$w = \frac{1}{2} C v^2$$

$$L = \frac{N^2 \mu A}{l}$$

$$v = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

$$w = \frac{1}{2} L i^2$$

$$\tau = RC$$

$$\tau = \frac{L}{R}$$

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2022/2023
 COURSE NAME : ELECTRICAL AND ELECTRONIC TECHNOLOGY

PROGRAMME CODE: BDM
 COURSE CODE: BDU10803

PHASOR RELATIONSHIP

$$v(t + T) = v(t)$$

$$f = \frac{1}{T}$$

$$z = x + jy = r \angle \phi = r(\cos \phi + j \sin \phi)$$

ALTERNATING CURRENT POWER CALCULATION

$$P(t) = v(t)i(t) \quad \text{Instantaneous power}$$

$$P = \frac{1}{2} \text{Re}[VI^*] = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad \text{Average power}$$

$$i_{RMS} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

$$P_{RMS} = I_{RMS}^2 R = \frac{V_{RMS}^2}{R}$$

TRANSFORMERS

$$\frac{V_P}{V_S} = \frac{N_P}{N_S}$$

LOGIC GATES

Name	NOT	AND	NAND	OR	NOR	XOR	XNOR																																																																																																
Alg. Expr.	\bar{A}	AB	\overline{AB}	$A+B$	$\overline{A+B}$	$A \oplus B$	$\overline{A \oplus B}$																																																																																																
Symbol																																																																																																							
Truth Table	<table border="1"> <tr><th>A</th><th>X</th></tr> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </table>	A	X	0	1	1	0	<table border="1"> <tr><th>B</th><th>A</th><th>X</th></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	B	A	X	0	0	0	0	1	0	1	0	0	1	1	1	<table border="1"> <tr><th>B</th><th>A</th><th>X</th></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	B	A	X	0	0	1	0	1	1	1	0	1	1	1	0	<table border="1"> <tr><th>B</th><th>A</th><th>X</th></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	B	A	X	0	0	0	0	1	1	1	0	1	1	1	1	<table border="1"> <tr><th>B</th><th>A</th><th>X</th></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	B	A	X	0	0	1	0	1	0	1	0	0	1	1	0	<table border="1"> <tr><th>B</th><th>A</th><th>X</th></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	B	A	X	0	0	0	0	1	1	1	0	1	1	1	0	<table border="1"> <tr><th>B</th><th>A</th><th>X</th></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	B	A	X	0	0	1	0	1	0	1	0	0	1	1	1
A	X																																																																																																						
0	1																																																																																																						
1	0																																																																																																						
B	A	X																																																																																																					
0	0	0																																																																																																					
0	1	0																																																																																																					
1	0	0																																																																																																					
1	1	1																																																																																																					
B	A	X																																																																																																					
0	0	1																																																																																																					
0	1	1																																																																																																					
1	0	1																																																																																																					
1	1	0																																																																																																					
B	A	X																																																																																																					
0	0	0																																																																																																					
0	1	1																																																																																																					
1	0	1																																																																																																					
1	1	1																																																																																																					
B	A	X																																																																																																					
0	0	1																																																																																																					
0	1	0																																																																																																					
1	0	0																																																																																																					
1	1	0																																																																																																					
B	A	X																																																																																																					
0	0	0																																																																																																					
0	1	1																																																																																																					
1	0	1																																																																																																					
1	1	0																																																																																																					
B	A	X																																																																																																					
0	0	1																																																																																																					
0	1	0																																																																																																					
1	0	0																																																																																																					
1	1	1																																																																																																					