



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2023/2024**

- COURSE NAME : ELECTRICAL TECHNOLOGY
- COURSE CODE : DAE 11003
- PROGRAMME CODE : DAE
- EXAMINATION DATE : JANUARY / FEBRUARY 2024
- DURATION : 3 HOURS
- INSTRUCTIONS :
1. ANSWER **FOUR (4)** QUESTIONS **ONLY** FROM **FIVE (5)** QUESTIONS PROVIDED.
 2. THIS FINAL EXAMINATION IS CONDUCTED VIA
 - Open book
 - Closed book
 3. STUDENTS ARE **PROHIBITED** TO CONSULT THEIR OWN MATERIAL OR ANY EXTERNAL RESOURCES

THIS QUESTION PAPER CONSISTS OF **SEVEN (7)** PAGES

TERBUKA

CONFIDENTIAL

- Q1**
- (a) Give the difference between conductor, insulator and semiconductor in term of electrical properties and valence electrons. (6 marks)
 - (b) Determine the resistance and tolerance value for the following 4-band resistors.
 - (i) Red, Violet, Orange, Silver (2 marks)
 - (ii) Green, Blue, Green, Gold (2 marks)
 - (c) An energy source forces a constant current of 2 A for 10 s to flow through a light bulb. If 2.3 kJ is given off in the form of light and heat energy, calculate the voltage drop across the bulb. (5 marks)
 - (d) Determine whether the resistor in each circuit of **Figure Q1 (d)** has possibly been damaged by overheating.

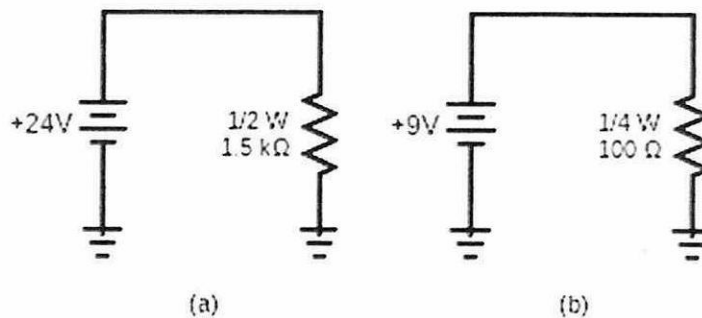


Figure Q1 (d)

(6 marks)

- (e) A power supply has efficiency of 75%. If P_{IN} is 50 W, calculate:
 - (i) P_{OUT} (2 marks)
 - (ii) P_{LOSS} (2 marks)

TERBUKA

- Q2** (a) State the definition of Kirchhoff's Current Law and Kirchhoff's Voltage Law by giving an appropriate circuit diagram. (5 marks)
- (b) A series circuit consists of $\frac{1}{2}$ W, $\frac{1}{4}$ W and $\frac{1}{8}$ W resistors. The total resistance, R_T is 2400Ω . If each of the resistors is operating in the circuit at its maximum power dissipation, calculate the current, I_T of the circuit. (8 marks)
- (c) Find R_1 , R_2 and R_3 in **Figure Q2 (c)**.

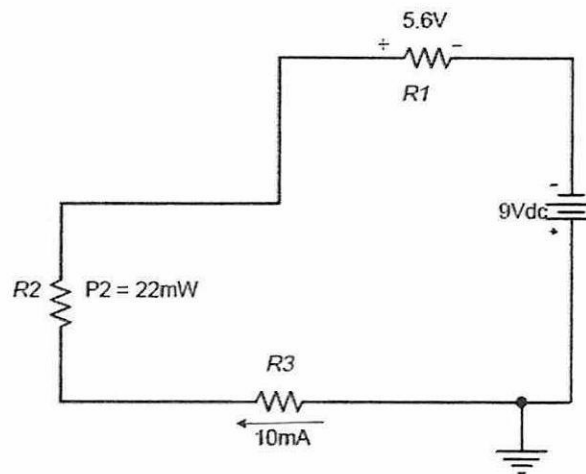


Figure Q2 (c)

(6 marks)

- (d) A circuit with resistors and potential voltage of 15 V is connected to a fuse with 0.5 A as shown in **Figure Q2 (d)**. Justify the minimum value of the 100Ω rheostat in the circuit could be adjusted before the 0.5 A fuse blows?

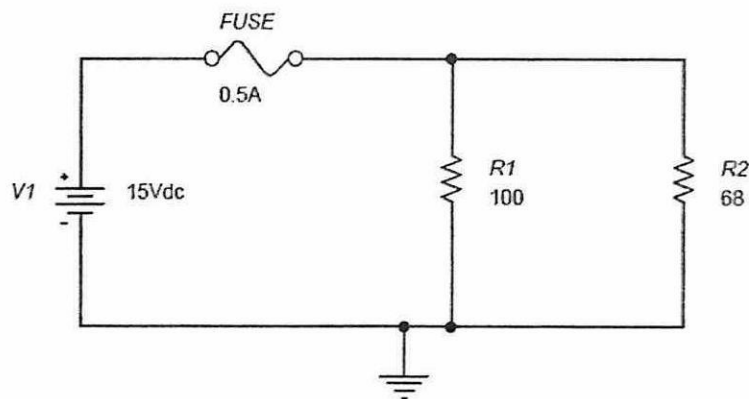


Figure Q2 (d)

(6 marks)

TERBUKA

Q3 (a) Referring to **Figure Q3 (a)**;

- (i) Calculate the total resistance (R_T) when S_1 and S_2 are closed. (3 marks)
- (ii) Which switch should be closed to obtain the total resistance of the circuit equal 2Ω ? (1 mark)
- (iii) When $V_{AB} = 210 \text{ V}$, calculate the value of voltage across one of the 4Ω resistors if only the S_2 switch is closed. (5 marks)
- (iv) If the current 4 A flows through the 5Ω resistor in with all switches open, calculate the voltage between point A and B .

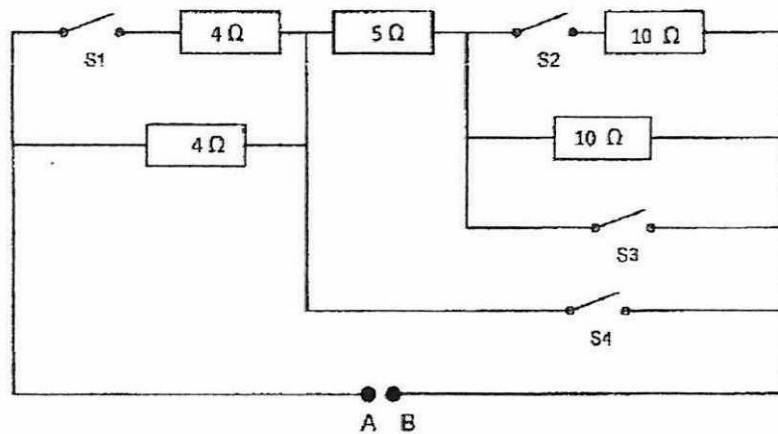


Figure Q3 (a)

(2 marks)

(b) A Wheatstone bridge circuit consists of four (4) resistors and a dc voltage source which look alike a ‘diamond’ configuration.

- (i) Draw the Wheatstone bridge (complete with R_1, R_2, R_3, R_4 , dc source and V_{out} terminals). (3 marks)
- (ii) Derive $R_1 = R_3 \left[\frac{R_2}{R_4} \right]$ under balance condition. (3 marks)
- (iii) Give **two (2)** conditions of the balanced Wheatstone bridge. (2 marks)

TERBUKA

- (c) Referring to circuit in **Figure Q3 (c)**, calculate the total resistance (R_T) between terminals A and B .

(6 marks)

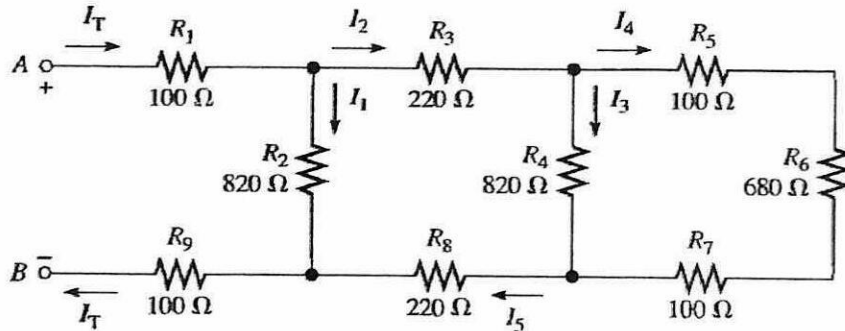


Figure Q3 (c)

- Q4** (a) Define 'flux density', state the formula and its unit.

(3 marks)

- (b) Referring to **Figure Q4 (b)(i)** and **Figure Q4 (b)(ii)**, redraw each of the figure and show the magnetic field lines.

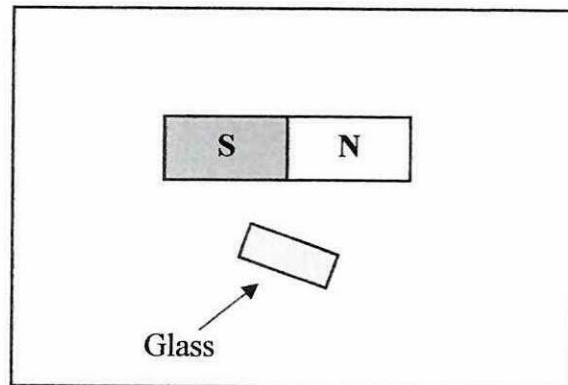


Figure Q4 (b)(i)

(2 marks)

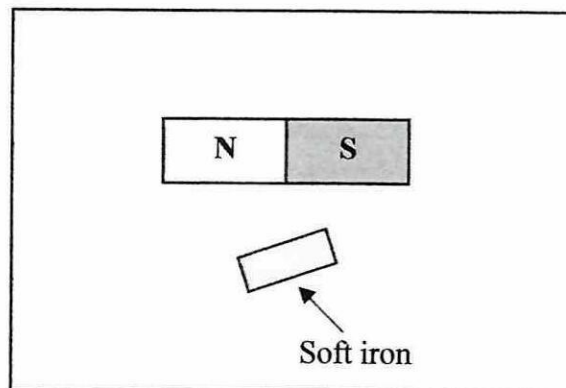


Figure Q4 (b)(ii)

(2 marks)

- (c) There are 8 A current through a wire with 11 turns.
- (i) Obtain the Magnetomotive Force (mmf) (2 marks)
- (ii) Obtain the reluctance of the circuit if the magnetic flux is $350 \mu\text{Wb}$. (2 marks)
- (d) Define 'RMS value' of a sine wave. (2 marks)
- (e) With the aid of diagram, illustrate a frequency sine wave of 6 Hz. (2 marks)
- (f) Determine the value of sine wave A in **Figure Q4 (f)** at each of the following times, measured from the positive-going zero crossing. Assume the frequency is 5 kHz.
- i. $30 \mu\text{s}$ (5 Marks)
- ii. $75 \mu\text{s}$ (5 Marks)

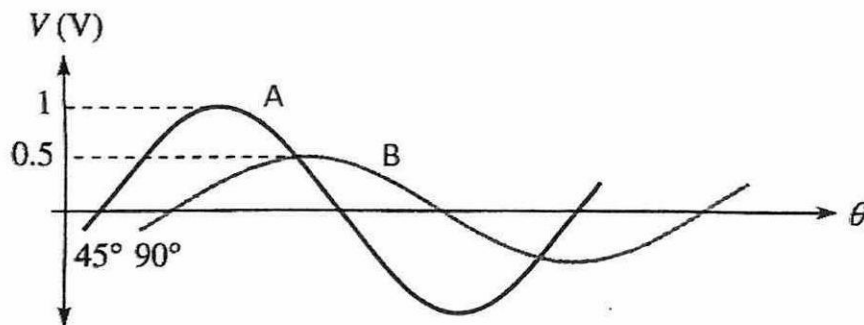


Figure Q4 (f)

- Q5** (a) Draw a phasor diagram that represent the sine wave illustrated in **Figure Q5(a)**.

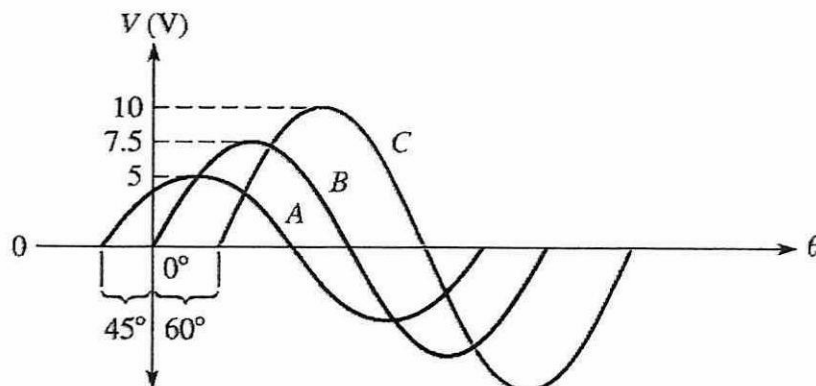


Figure Q5 (a).

(3 marks)

TERBUKA

- (b) Perform the following operations. Write your solution in rectangular form with three decimal places.

$$(i) \frac{(25\angle 30^\circ + 75\angle 45^\circ)(50 - j10)}{(12 + j19)(35\angle 50^\circ)}$$

(2 marks)

$$(ii) \frac{20\angle 65^\circ - (18 - j30)}{15\angle 25^\circ}$$

(2 marks)

$$(iii) \frac{100\angle 15^\circ}{20 + j40} - j\left(\frac{1}{2} - j\frac{2}{3}\right)$$

(2 marks)

- (c) Explain **two (2)** significant difference between rectangular and polar form of a complex numbers.

(4 marks)

- (d) Define transformer efficiency and the relevance formula involve.

(4 marks)

- (e) A transformer is designed to have the following specification. The magnetic flux produced by a primary coil linking to secondary coil of the transformer is 375 μWb and total magnetic flux generated by primary coil is 500 μWb . The inductance of primary coil is 1 mH and secondary coil is 600 μH . The turn ratio of the transformer is 3:4. Calculate:

- (i) Coefficient of coupling, k .

(2 marks)

- (ii) Mutual Inductance, L_M .

(2 marks)

- (iii) Secondary voltage of the transformer (V_{SEC}), when 120 VAC is applied to the primary winding.

(2 marks)

- (iv) Secondary load current (I_{SEC}), when primary current of 90 mA is applied.

(2 marks)

- END OF QUESTIONS -

TERBUKA