

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER III
SESSION 2014/2015**

COURSE NAME : ELECTRONICS
COURSE CODE : DAR 21203
PROGRAMME : 2 DAR
EXAMINATION DATE : AUGUST 2015
DURATION : 3 HOURS
INSTRUCTION : ANSWER FIVE (5) QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF TWELVE (12) PAGES

CONFIDENTIAL

CONFIDENTIAL

- Q1** (a) Briefly describe the following:
- (i) Valence electrons (2 marks)
 - (ii) Covalent bonding (2 marks)
 - (iii) Extrinsic semiconductor (2 marks)
- (b) Draw and completely label the output waveform, V_O for the circuit shown in **Figure Q1(b)**. Assume all the diodes are silicon. Show all your steps in obtaining the waveforms. (6 marks)
- (c) The following **Figure Q1(c)** shows the Zener diode circuit. Given, P_{ZM} (maximum power) = 40 mW. Assume the Zener diode is ideal.
- (i) Calculate the output voltage, V_o (2 marks)
 - (ii) Identify the voltage drop across load, V_{RL} (2 marks)
 - (iii) Indicate the zener current, I_z (2 marks)
 - (iv) Solve the power dissipated by the zener diode, P_z (2 marks)
- Q2** (a) Draw the P-N junction analogy and the symbol of bipolar junction transistor. (4 marks)
- (b) Based on the circuit in **Figure Q2(b)**,
- (i) Determine the collector current, I_C (2 marks)
 - (ii) Compute the value of V_{CC} (2 marks)
 - (iii) Calculate the value of gain, β (2 marks)
 - (iv) Evaluate the value of resistor, R_B for the circuit given. (2 marks)

CONFIDENTIAL

CONFIDENTIAL

- (c) Based on the voltage feedback biasing circuit given in **Figure Q2(c)**.
- (i) Identify the value of quiescent level of collector current, I_{CQ}
(4 marks)
 - (ii) Determine the value of quiescent level of collector-emitter voltage, V_{CEQ}
(2 marks)
 - (iii) Calculate the collector current, V_C
(2 marks)

- Q3** (a) With the aid of an appropriate circuit, illustrate how the transistor can be used as a switch.
(8 marks)
- (b) By analysing the circuit given in **Figure Q3(b)**, based on the voltage-divider configuration,
- (i) Estimate the value of Thevenin equivalent resistor, R_{TH}
(2 marks)
 - (ii) Compute the Thevenin equivalent voltage, V_{TH}
(2 marks)
 - (iii) Determine the collector current, I_C
(4 marks)
 - (iv) Draw the Thevenin equivalent circuit with labelling
(2 marks)
 - (v) Identify the collector-emitter voltage, V_{CE}
(2 marks)

CONFIDENTIAL

CONFIDENTIAL

Q4 The common-emitter amplifier circuit configuration is shown in **Figure Q4**. By referring to the figure;

- (a) Draw the AC equivalent circuit by using the PIE (π) model with complete labelling. (3 marks)
- (b) By using the same model given in **Figure Q4**;
- (i) Calculate the AC emitter resistance, r_e (5 marks)
 - (ii) Determine the input impedance of the base, Z_{in} (base) (2 marks)
 - (iii) Find the input impedance of the stage, Z_{in} (stage) (2 marks)
 - (iv) Identify the AC collector resistance, r_c (2 marks)
 - (v) Compute the input voltage, V_{in} (2 marks)
 - (vi) Solve the voltage gain, A_v (2 marks)
 - (vii) Estimate the output voltage across resistor R_L , V_{out} (2 marks)

Q5 (a) List **two (2)** characteristics for each of the following classes of amplifiers.

- (i) Class A (2 marks)
- (ii) Class B (2 marks)
- (iii) Class C (2 marks)

CONFIDENTIAL

CONFIDENTIAL

- (b) For a power amplifier configuration of **Figure Q5(b)** with $I_{CQ} = 13.24 \text{ mA}$, solve the following requirements;
- (i) Calculate the transistor power dissipation, P_{DQ} (4 marks)
 - (ii) Determine the voltage gain, A_v (3 marks)
 - (iii) Find the Peak-peak output voltage, V_{out} (2 marks)
 - (iv) Evaluate the AC load power, P_{out} (2 marks)
 - (v) Identify DC input power, P_{dc} (2 marks)
 - (vi) Compute the Stage efficiency, η (1 mark)

Q6 Given the JFET CS amplifier self-bias circuit configuration shown in **Figure Q6**.

- (a) Draw the AC equivalent circuit for the given circuit configuration with complete labelling (4 marks)
- (b) By applying $I_{DSS} = 9\text{mA}$ and $V_{GS(off)} = -4.5\text{V}$,
 - (i) Calculate the input impedance, Z_i (3marks)
 - (ii) Determine the output impedance, Z_o (3marks)
 - (iii) Compute the output voltage, V_o (5marks)
 - (iv) Identify the voltage gain, A_v (5marks)

CONFIDENTIAL

CONFIDENTIAL

- Q7** (a) For the Colpitts CB oscillator circuit as shown in **Figure Q7(a)**,
- (i) Calculate the frequency of the oscillator (4marks)
 - (ii) Determine the value of feedback fraction, Beta (4marks)
 - (iii) Estimate the minimum value of voltage gain, A_v , for the oscillator to start (2marks)
- (b) By referring to **Figure Q7(b)**:
- (i) Sketch the circuit of a 555 timer connected as an astable multivibrator for operation at 350 kHz. (3marks)
 - (ii) Determine the value of capacitor C needed using $R_A = R_B = 7.5 \text{ k}\Omega$ (4marks)
 - (iii) Sketch the output waveform resulting from that astable circuit. (3marks)

- END OF QUESTIONS -

CONFIDENTIAL

CONFIDENTIAL

FINAL EXAMINATION

SEMESTER/SESSION: SEM III/2014/2015
 COURSE NAME : ELECTRONICS

PROGRAMME : 2 DAR
 COURSE CODE : DAR 21203

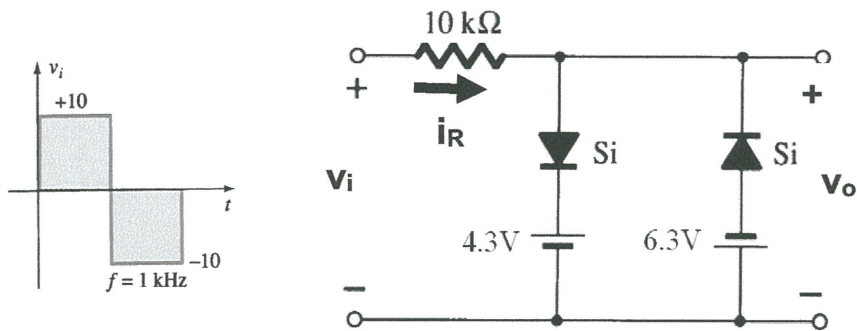


FIGURE Q1(b)

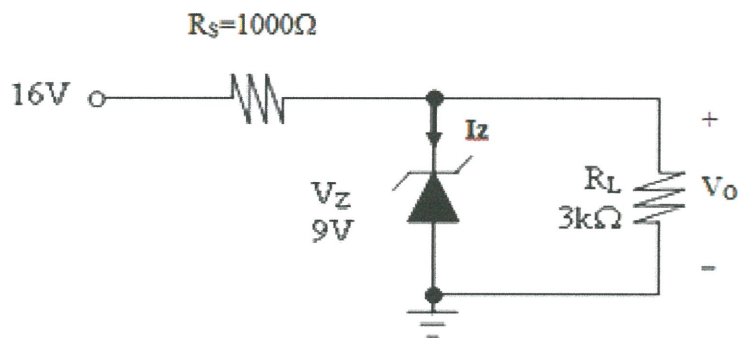


FIGURE Q1(c)

CONFIDENTIAL

FINAL EXAMINATION

SEMESTER/SESSION: SEM III/2014/2015
COURSE NAME : ELECTRONICS

PROGRAMME : 2 DAR
COURSE CODE : DAR 21203

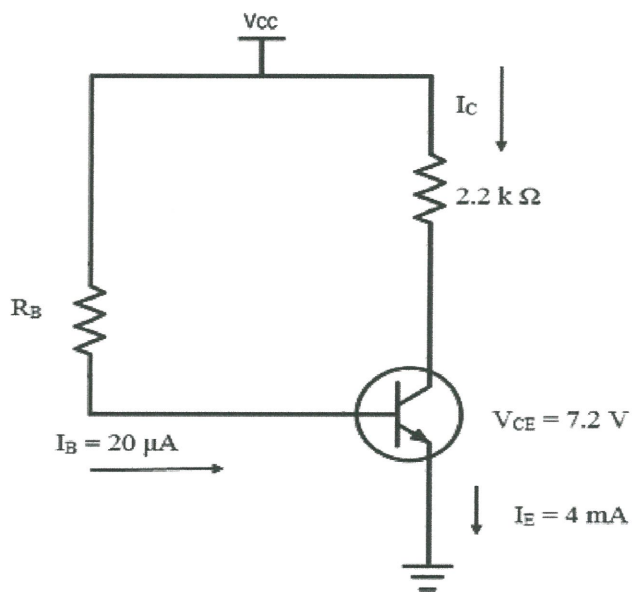


FIGURE Q2(b)

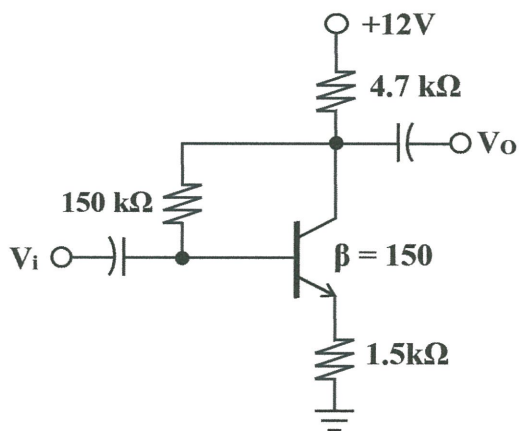


FIGURE Q2(c)

FINAL EXAMINATION

SEMESTER/SESSION: SEM III/2014/2015
COURSE NAME : ELECTRONICS

PROGRAMME : 2 DAR
COURSE CODE : DAR 21203

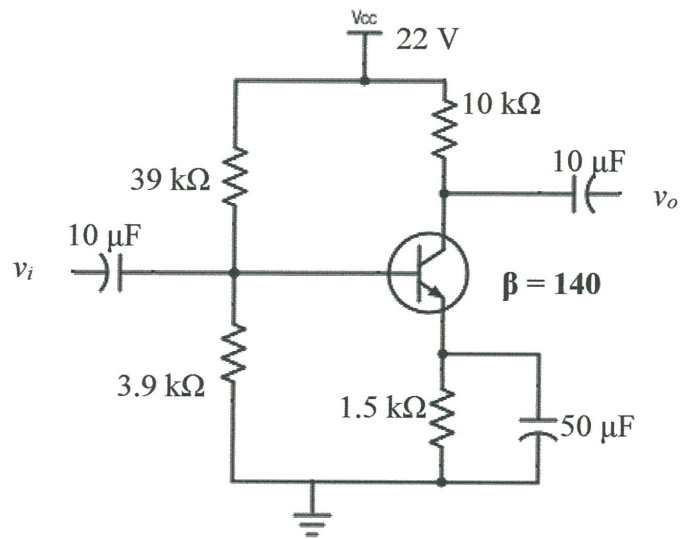


FIGURE Q3(b)

FINAL EXAMINATION

SEMESTER/SESSION: SEM III/2014/2015
COURSE NAME : ELECTRONICS

PROGRAMME : 2 DAR
COURSE CODE : DAR 21203

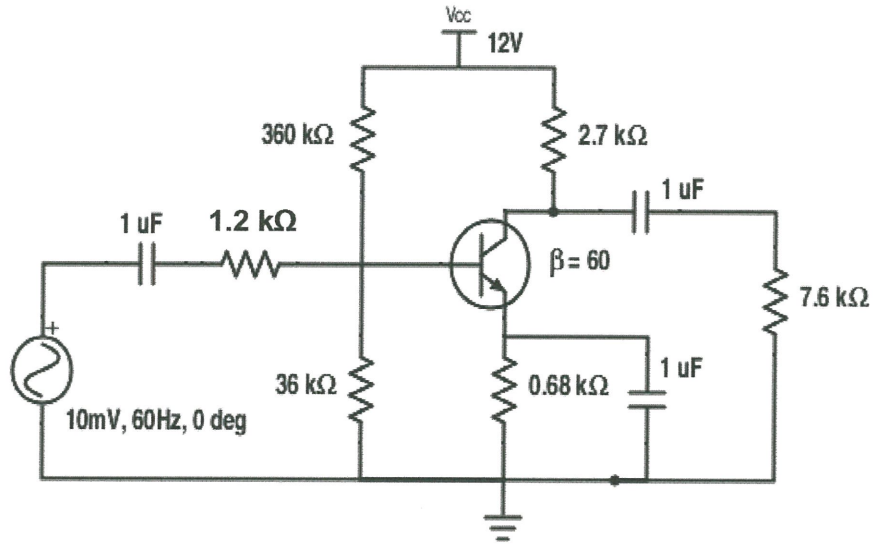


FIGURE Q4

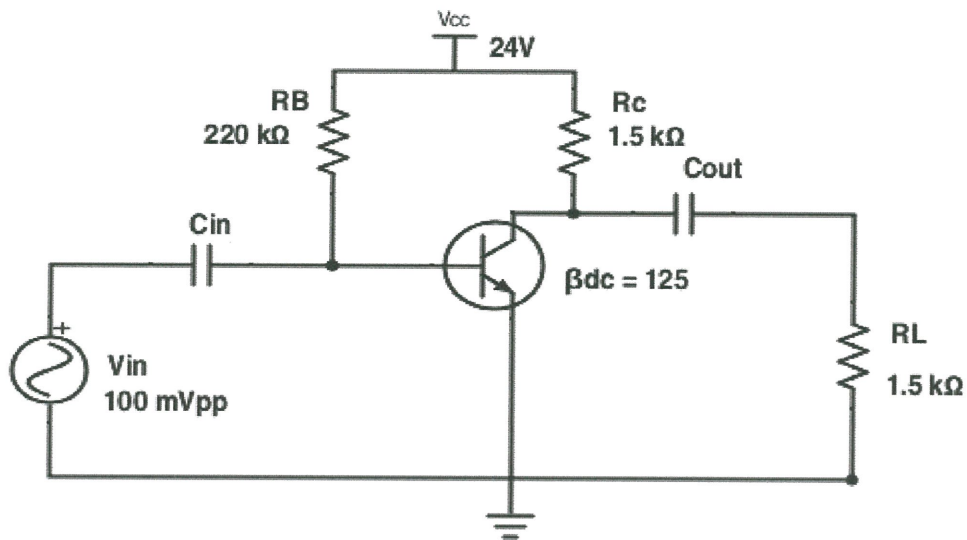


FIGURE Q5(b)

CONFIDENTIAL

FINAL EXAMINATION

SEMESTER/SESSION: SEM III/2014/2015
 COURSE NAME : ELECTRONICS

PROGRAMME : 2 DAR
 COURSE CODE : DAR 21203

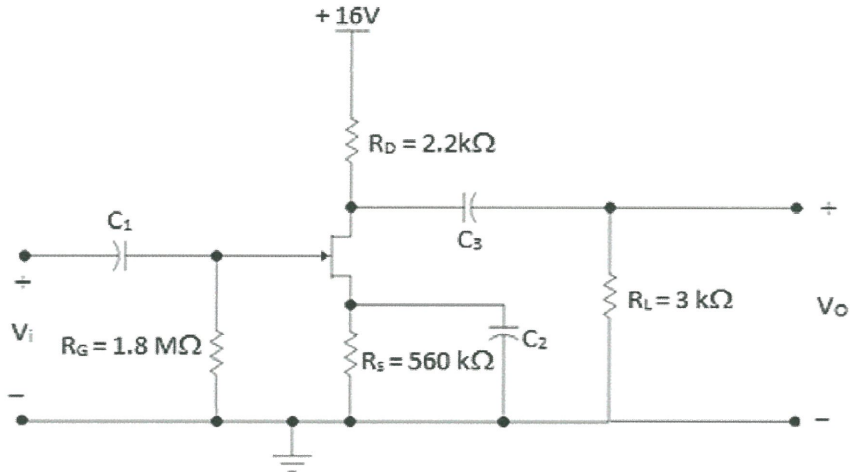


FIGURE Q6

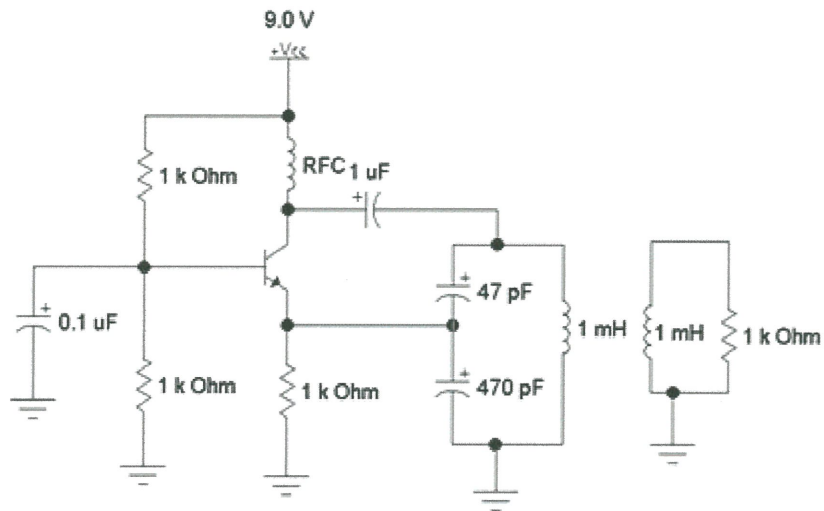


FIGURE Q7(a)

CONFIDENTIAL

CONFIDENTIAL

FINAL EXAMINATION

SEMESTER/SESSION: SEM III/2014/2015
COURSE NAME : ELECTRONICS

PROGRAMME : 2 DAR
COURSE CODE : DAR 21203

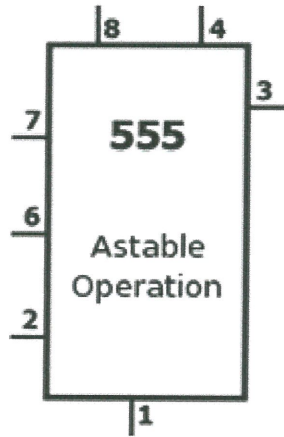


FIGURE Q7(b)

CONFIDENTIAL