

**CONFIDENTIAL**



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER I  
SESSION 2017/2018**

COURSE NAME : LOGIC SYSTEMS  
COURSE CODE : DAE 21603  
PROGRAMME : 2 DAE  
EXAMINATION DATE : DECEMBER 2017/ JANUARY 2018  
DURATION : 2 HOURS AND 30 MINUTES  
INSTRUCTION : SECTION A  
ANSWER ALL QUESTIONS  
  
SECTION B  
ANSWER **TWO (2)** QUESTIONS  
ONLY

THIS QUESTION PAPER CONSISTS OF **TEN (10)** PAGES

**CONFIDENTIAL**

**SECTION A**

- Q1** (a) Explain **two (2)** primary type of a logic circuit. (3 marks)
- (b) With the aid of diagrams, show the difference between latches and flip-flops. (3 marks)
- (c) With the aid of truth tables, describe the differences between the following flip-flops (12 marks)
- (i) RS flip flop.
  - (ii) JK flip-flop.
  - (iii) D flip-flop.
- (d) Given J, K, and Clock input for a JK flip-flop in **Figure Q1(d)**.
- (i) Draw the Q1 output waveform (4 marks)
  - (ii) Draw the  $\overline{Q2}$  output waveform (3 marks)
- Q2** (a) Design a synchronous counter using JK flip-flop to count 4 digits. The count sequence is 2,0,3,1 and repeat. The JK excitation table is shown in **Table 1**. Show all steps and the design should include the following :
- (i) State diagram (2 marks)
  - (ii) Circuit excitation table used to determine JK flip-flop inputs. (5 marks)
  - (iii) K-maps used to generate minimal expressions for JK inputs. (5 marks)
  - (iv) Logic circuit. (3 marks)
- (b) Explain **four (4)** mode of data movement in shift register. (4 marks)
- (c) (i) Determine the number of flip-flops needed to construct a shift register capable of storing a 5-bit binary number. (1 marks)
- (ii) Draw the logic diagram as a serial input/output shift register. (5 marks)

**SECTION B**

**Q3** (a) List **four(4)** applications of flip-flops/latches. (4 marks)

(b) For the circuit in **Figure Q3(b)**:  
(i) State the function of this circuit. (2 marks)

(ii) Determine the external resistors R1 and R2 to give output frequency of 10kHz with duty cycle of 50% if the external capacitor C is 3nF. (6 marks)

(c) **Figure Q3(c)** show JK flip-flop configured as a ripple carry up counter.  
(i) Draw the timing diagram in **Figure Q3(c)**. (9 marks)

(ii) Modify the circuit to operate as MOD 6 counter. (4 marks)

**Q4** (a) **Figure Q4(a)** shows the block diagram of a 4-bit counter. Show how it can be configured as the following counter. Shows all steps and if the input frequency is 200kHz determine each of the counter output frequency.

- (i) MOD 10 counter
  - (ii) MOD 11 counter
  - (iii) MOD 14 counter
- (15 marks)

(b) For the **Figure Q4(b)**, the propagation delay,  $t_{pd}$  for each flip-flop is 40ns and  $t_{pd}$  for AND gate is 10ns.

- (i) Determine the maximum input clock frequency ( $f_{max}$ ) for the counter. (4 marks)
- (ii) Determine the maximum input clock frequency ( $f_{max}$ ) with a MOD-16 ripple counter. (6 marks)

# CONFIDENTIAL

DAE 21603

**Q5** (a) A shift register in **Figure 5(a)** has *SHIFT/LOAD* and *CLK* inputs. The serial data input (*SER*) is a 0. The parallel data inputs are  $D0 = 1$ ,  $D1 = 0$ ,  $D2 = 1$  and  $D3 = 0$  as shown. Develop the data-output waveform in relation to the inputs for  $Q_0$ ,  $Q_1$ ,  $Q_2$  and  $Q_3$ . (4 marks)

(b) Several types of architecture are used in PLDs. Draw the block diagram of **three (3)** common types and describe their differences. (6 marks)

(c) List **five (5)** limitations of PLAs. (5 marks)

(d) Show how the PLA shown in **Figure Q5(d)** can be configured to implement the following functions. Label all inputs and outputs.

(i)  $F1(W, X, Y) = \sum(1, 2, 3, 5, 7)$

(ii)  $F2(W, X, Y) = \sum(0, 4, 6, 7)$

(10 marks)

**Q6** (a) Define each basic memory operations terms below.

- (i) Write
- (ii) Read.
- (iii) Address.

(6 marks)

(b) A certain memory has a capacity of  $4K \times 8$ , determine

- (i) The number of data inputs and data outputs .
- (ii) The number of address lines.
- (iii) Its capacity in bytes.

(9 marks)

(c) Define each of the following terms.

(i) RAM

(2 marks)

(iii) ROM

(2 marks)

(iv) EPROM

(3 marks)

(iv) Internal Memory


(3 marks)

- END OF QUESTION -

**FINAL EXAMINATION**

SEMESTER/SESSION: SEM I/2017/2018  
 COURSE NAME : LOGIC SYSTEMS

PROGRAMME : 2 DAE  
 COURSE CODE: DAE 21603

 

**FIGURE Q1(d)**


**TABLE 1: JK Excitation Table**

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0



**FINAL EXAMINATION**

SEMESTER/SESSION: SEM I/2017/2018  
 COURSE NAME : LOGIC SYSTEMS

PROGRAMME : 2 DAE  
 COURSE CODE: DAE 21603

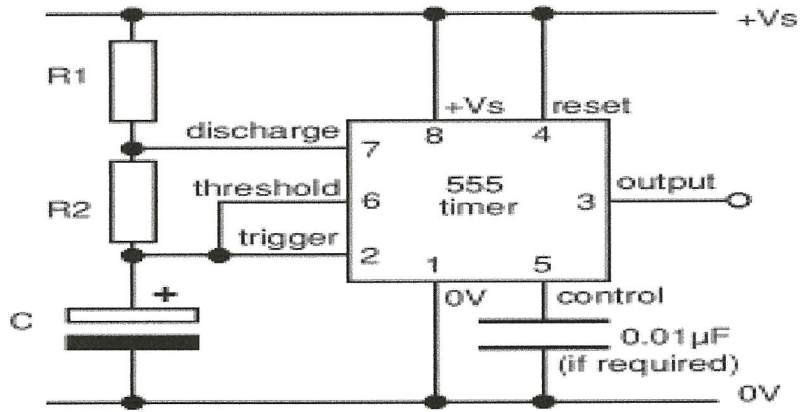

 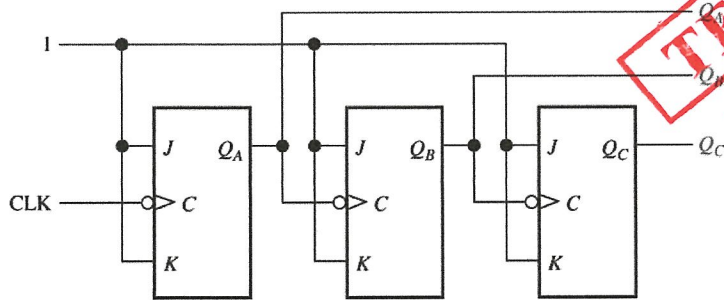**FIGURE Q3(b)**

 


**FIGURE Q3(c)**


**FINAL EXAMINATION**

SEMESTER/SESSION: SEM I/2017/2018  
 COURSE NAME : LOGIC SYSTEMS

PROGRAMME : 2 DAE  
 COURSE CODE: DAE 21603



**TERBUKA**

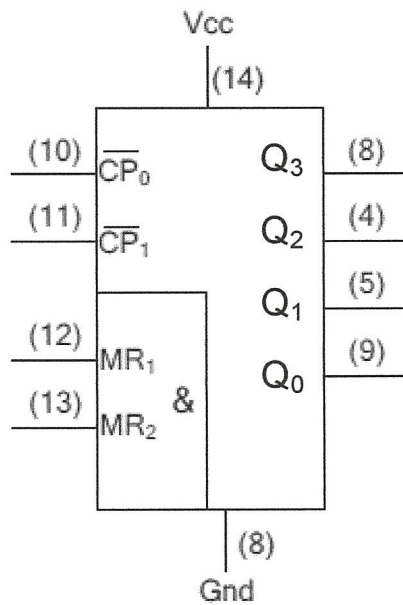

**FIGURE Q4(a)**

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2017/2018  
COURSE NAME : LOGIC SYSTEMS

PROGRAMME : 2 DAE  
COURSE CODE: DAE 21603

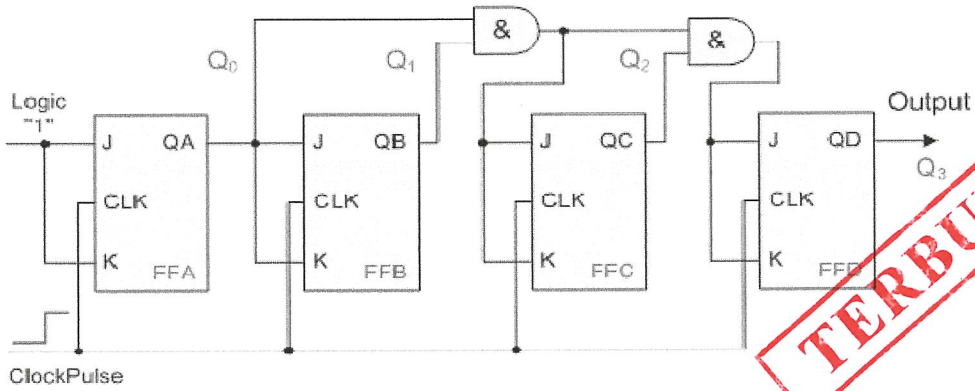



FIGURE Q4(b)



FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2017/2018  
COURSE NAME : LOGIC SYSTEMS

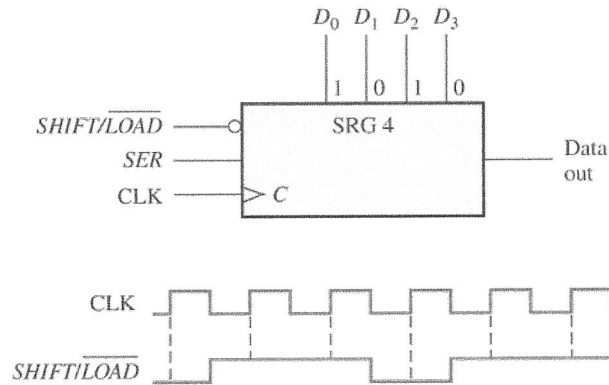PROGRAMME : 2 DAE  
COURSE CODE: DAE 21603



TERBUKA


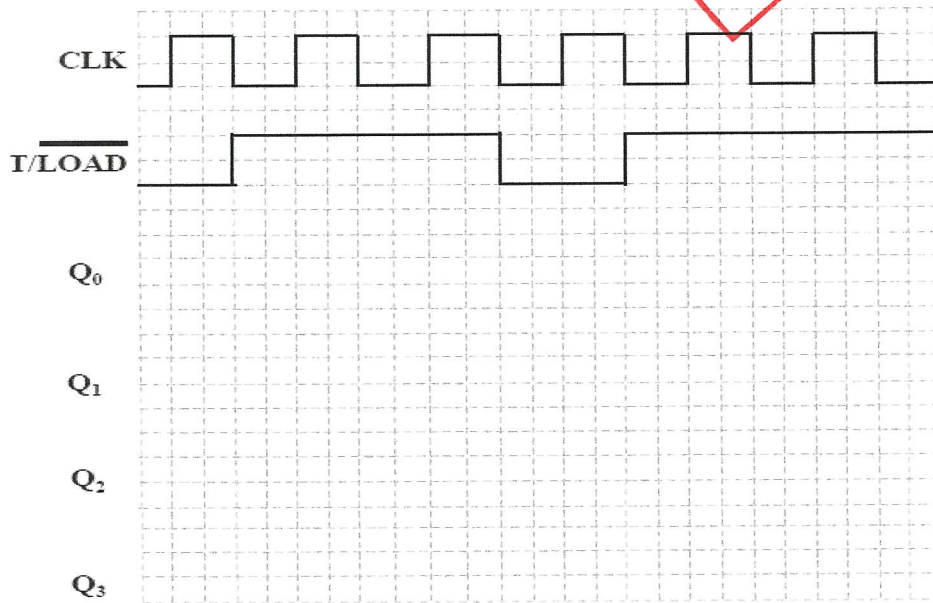


FIGURE Q5(a)

**FINAL EXAMINATION**

SEMESTER/SESSION: SEM I/2017/2018  
COURSE NAME : LOGIC SYSTEMS

PROGRAMME : 2 DAE  
COURSE CODE: DAE 21603

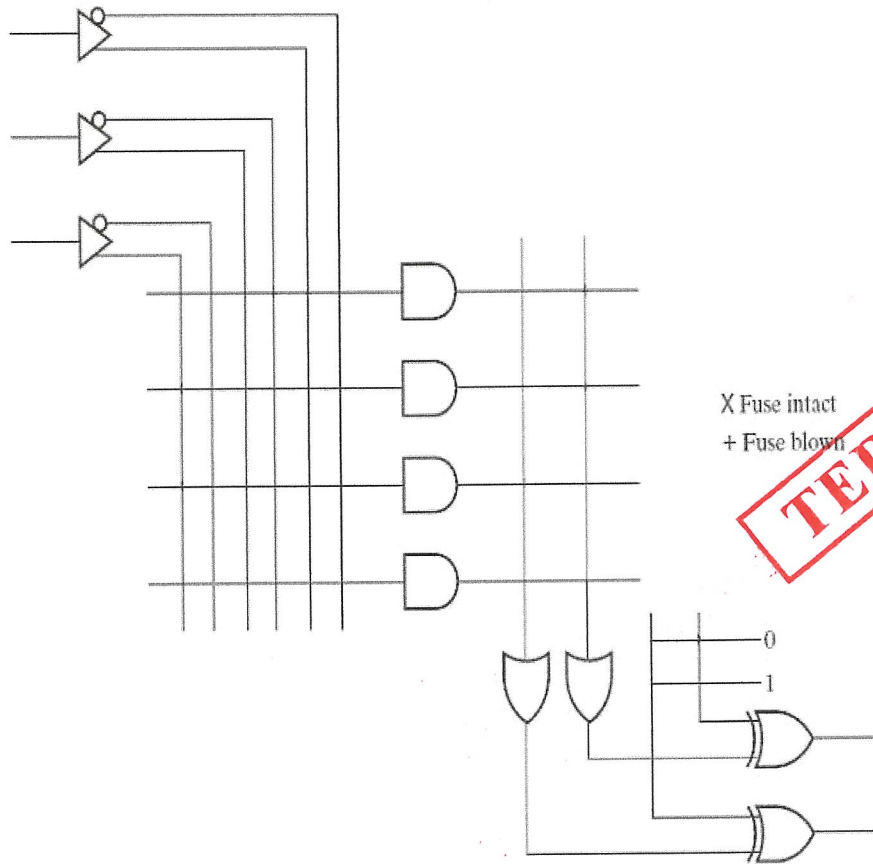

**FIGURE Q5(d)**