

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2017/2018**

COURSE NAME : CIRCUIT THEORY
COURSE CODE : DAE 11103
PROGRAMME CODE : DAE
EXAMINATION DATE : JUNE / JULY 2018
DURATION : 3 HOURS
INSTRUCTION : PART A
ANSWER ALL QUESTIONS

TERBUKA

PART B
ANSWER TWO (2) QUESTIONS
ONLY

THIS QUESTION PAPER CONSISTS OF NINE (9) PAGES

CONFIDENTIAL

PART A

- Q1** (a) Define briefly Kirchhoff's Voltage Law. (2 marks)
- (b) The current of a device is $i(t) = 5e^{-4t}$ A and the voltage is $v(t) = 10 di/dt$ V. Determine the energy absorbed in 3 s. (6 marks)
- (c) Compute the power absorbed or supplied by each component of the circuit in **Figure Q1(c)**. (6 marks)
- (d) Use Ohm's law and Kirchhoff's laws to find the value of R in the circuit shown in **Figure Q1(d)**. (6 marks)
- Q2** (a) Given the following circuit configuration of **Figure Q2(a)**. Calculate the voltage v_o using nodal analysis. (10 marks)
- (b) In the circuit of **Figure Q2 (b)**, find the voltage V_x using mesh analysis. (10 marks)
- Q3** (a) Use the superposition theorem to find i_2 in the circuit shown in **Figure Q3(a)**. (7 marks)
- (b) Find the Thévenin equivalent circuit for the network external to the resistor R in **Figure Q3(b)**. (7 marks)
- (c) Find the Norton equivalent circuit for the network external to the resistor R in **Figure Q3(c)**. (6 marks)

TERBUKA

PART B

- Q4** (a) Three capacitors, $C_1 = 5\mu\text{F}$, $C_2 = 10\mu\text{F}$ and $C_3 = 20\mu\text{F}$, are connected in parallel across a 150V d.c. source. Determine:
- (i) the total capacitance. (3 marks)
 - (ii) the charge on each capacitor. (3 marks)
 - (iii) the total energy stored in the parallel combination of the capacitors. (3 marks)
- (b) Switch S_1 in **Figure Q4(b)** has been closed for a long time. At $t = 0$ s, S_1 is opened at the same instant that S_2 is closed to avoid an interruption in current through the coil.
- (i) Find the initial current through the coil, $i_{L(0)}$. (3 marks)
 - (ii) Find the mathematical expression for the current i_L following the closing of switch S_2 . (8 marks)

TERBUKA

- Q5** (a) In a linear circuit, the voltage source is $v_s = 12 \sin(10^3 t + 24^\circ)$ V.
- (i) What is the angular frequency of the voltage? (1 mark)
 - (ii) What is the frequency of the source? (2 marks)
 - (iii) Find the period of the voltage. (2 marks)
 - (iv) Express v_s in cosine form. (2 marks)
 - (v) Determine v_s at $t = 2.5$ ms. (3 marks)
- (b) For the circuit shown in **Figure Q5(b)** :
- (i) Find the total impedance Z_T . (3 marks)
 - (ii) Determine the current I_S . (2 marks)
 - (iii) Calculate V_R and V_C . (3 marks)
 - (iv) Find I_C . (2 marks)

TERBUKA

- Q6 (a) The voltage across a load is $v(t) = 160 \cos 377t$ V and the current through the element in the direction of the voltage drop is $i(t) = 4 \cos (377t + 45^\circ)$ A.

Find :

- (i) complex power. (4 marks)
 - (ii) apparent power. (2 marks)
 - (iii) real / average power. (2 marks)
 - (iv) reactive power. (2 marks)
 - (v) power factor and specify whether it is leading or lagging. (2 marks)
- (b) A 50 kW load operates from a 60 Hz, 10 kV_{rms} line with a power factor of 60% lagging. Compute the capacitance that must be placed in parallel with the load to achieve a 90% lagging power factor. (8 marks)

TERBUKA

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2017/2018
COURSE NAME : CIRCUIT THEORY

PROGRAMME : DAE
COURSE CODE : DAE 11103

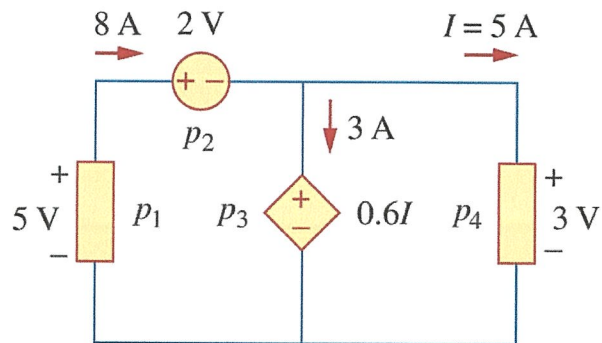


Figure Q1(c)

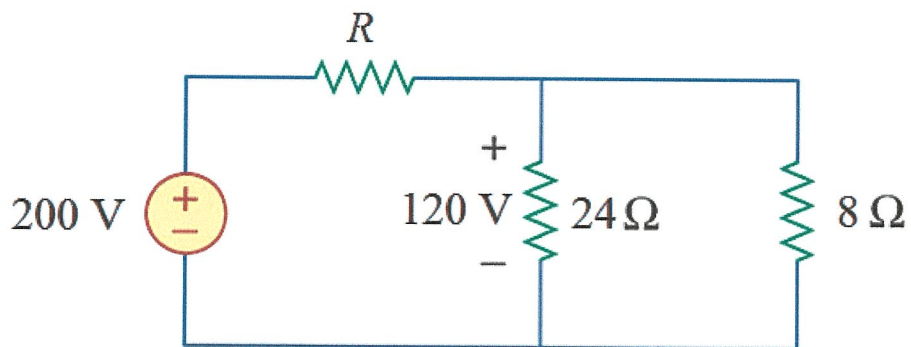


Figure Q1(d)

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2017/2018
COURSE NAME : CIRCUIT THEORY

PROGRAMME : DAE
COURSE CODE : DAE 11103

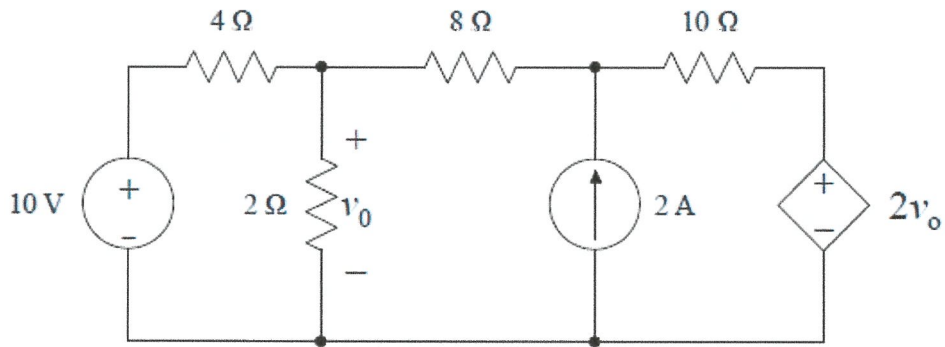


Figure Q2(a)

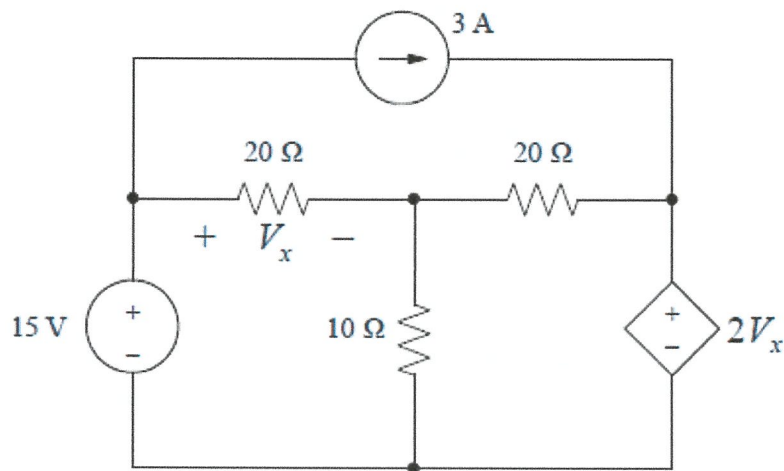


Figure Q2(b)

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2017/2018
COURSE NAME : CIRCUIT THEORY

PROGRAMME : DAE
COURSE CODE : DAE 11103

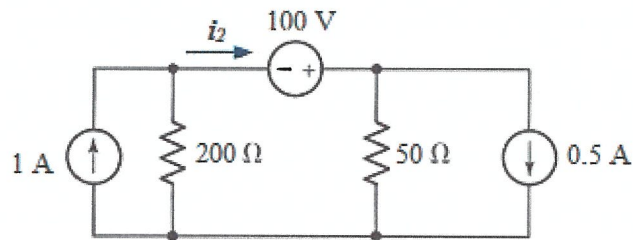


Figure Q3(a)

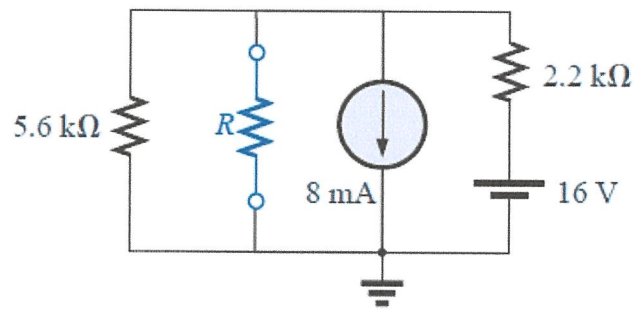


Figure Q3(b)

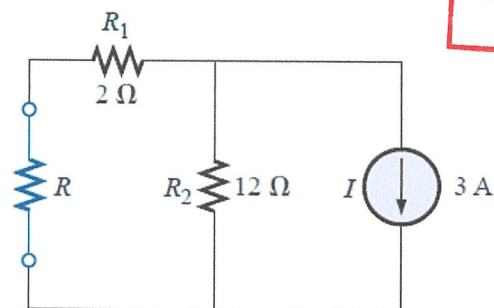


Figure Q3(c)

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2017/2018
COURSE NAME : CIRCUIT THEORY

PROGRAMME : DAE
COURSE CODE : DAE 11103

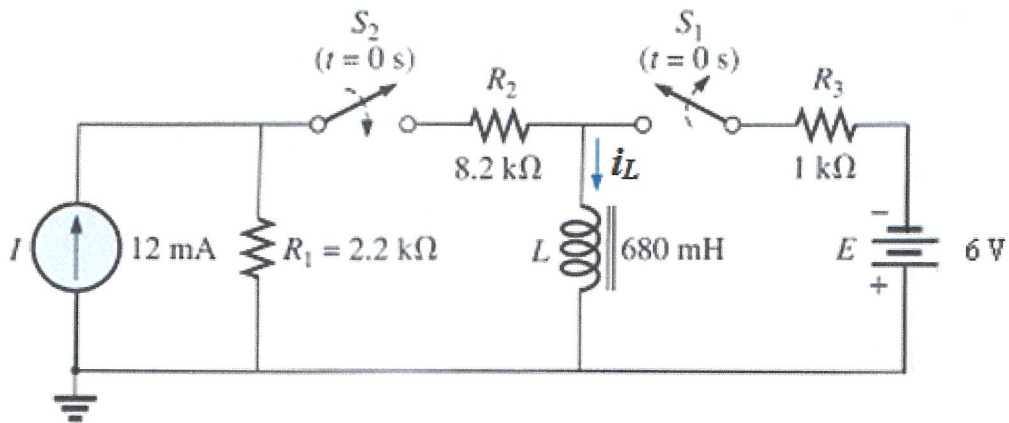


Figure Q4(b)

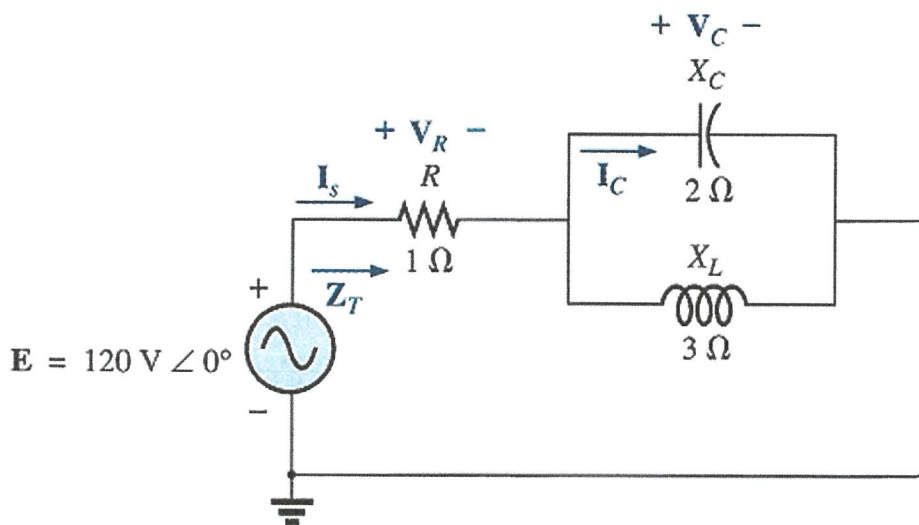


Figure Q5(b)

TERBUKA