



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2018/2019**

COURSE NAME : LOGIC SYSTEMS
COURSE CODE : DAE 21603
PROGRAMME CODE : DAE
EXAMINATION DATE : DECEMBER 2018 / JANUARY 2019
DURATION : 2 HOURS 30 MINUTES
INSTRUCTIONS :
1) **PART A: ANSWER ALL**
QUESTIONS ON OMR PAPER
2) **PART B: ANSWER FOUR (4)**
QUESTIONS ONLY
3) **ATTACH APPENDIX I, II, III**
AND IV WITH YOUR ANSWER
BOOKLET

TERBUKA

THIS QUESTION PAPER CONSISTS OF ~~FOURTEEN~~ (14) PAGES

PART A: PLEASE SELECT THE CORRECT ANSWER. ANSWER ALL QUESTIONS ON OMR PAPER. (20 marks)

- Q1** Which of the following is correct for a gated D-type flip-flop?
- A. The Q output is either SET or RESET as soon as the D input goes HIGH or LOW
 - B. The output complement follows the input when enabled
 - C. Only one of the inputs can be HIGH at a time
 - D. The output toggles if one of the inputs is held HIGH
- Q2** What is a trigger pulse?
- A. A pulse that starts a cycle of operation
 - B. A pulse that reverses the cycle of operation
 - C. A pulse that prevents a cycle of operation
 - D. None of the above
- Q3** When is a flip-flop said to be transparent?
- A. When the Q output is opposite the input
 - B. When the Q output follows the input
 - C. When you can see through the IC packaging
 - D. None of the above
- Q4** On a positive edge-triggered S-R flip-flop, the outputs reflect the input condition when _____
- A. The clock pulse is LOW
 - B. The clock pulse is HIGH
 - C. The clock pulse transitions from LOW to HIGH
 - D. The clock pulse transitions from HIGH to LOW
- Q5** Which statement BEST describes the operation of a negative-edge-triggered D flip-flop?
- A. The logic level at the D input is transferred to Q on NGT of CLK
 - B. The Q output is ALWAYS identical to the CLK input if the D input is HIGH
 - C. The Q output is ALWAYS identical to the D input when CLK = PGT
 - D. The Q output is ALWAYS identical to the D input
- Q6** Which of the following is correct for a D latch?
- A. The output toggles if one of the inputs is held HIGH
 - B. Q output follows the input D when the enable is HIGH
 - C. Only one of the inputs can be HIGH at a time
 - D. The output complement follows the input when enabled

TERBUKA

- Q7** A ripple counter's speed is limited by the propagation delay of:
- A. Each flip-flop
 - B. All flip-flops and gates
 - C. The flip-flops only with gates
 - D. Only circuit gates
- Q8** A 5-bit asynchronous binary counter is made up of five flip-flops, each with a 12 ns propagation delay. The total propagation delay (t_p (total)) is
- A. 12 ms
 - B. 24 ns
 - C. 48 ns
 - D. 60 ns
- Q9** A sequential circuit design is used to
- A. Count up
 - B. Count down
 - C. Decode an end count
 - D. Count in a random order
- Q10** As the number of flip flops are increased, the total propagation delay of
- A. Ripple counter increases but that of synchronous counter remains the same
 - B. Both ripple and synchronous counters increase
 - C. Both ripple and synchronous counters remain the same
 - D. Ripple counter remains the same but that of synchronous counter increases
- Q11** The main difference between a register and a counter is
- A. A register has no specific sequence of states
 - B. A counter has no specific sequence of states
 - C. A register has capability to store one bit of information but counter has n-bit
 - D. None of the above
- Q12** What is a fusing process?
- A. It is a process by which data is passed to the memory
 - B. It is a process by which data is read through the memory
 - C. It is a process by which programs are burnout to the diode/transistors
 - D. None of the above
- Q13** What is the major difference between DRAM and SRAM?
- A. Dynamic RAMs are always active; static RAMs must reset between data read/write cycles
 - B. SRAMs can hold data via a static charge, even with power off
 - C. The only difference is the terminal from which the data is removed—from the
 - D. FET Drain or Source
 - E. DRAMs must be periodically refreshed

- Q14** Which ROM can be erased by an electrical signal?
- A. ROM
 - B. Mask ROM
 - C. EPROM
 - D. EEPROM
- Q15** What does the term “random access” mean in terms of memory?
- A. Any address can be accessed in systematic order
 - B. Any address can be accessed in any order
 - C. Addresses must be accessed in a specific order
 - D. None of the above
- Q16** The inputs in the PLD is given through
- A. NAND gates
 - B. OR gates
 - C. NOR gates
 - D. AND gates
- Q17** The difference between a PAL & a PLA is
- A. PALs and PLAs are the same thing
 - B. The PAL has a programmable OR plane and a programmable AND plane, while the PLA only has a programmable AND plane
 - C. The PLA has a programmable OR plane and a programmable AND plane, while the PAL only has a programmable AND plane
 - D. The PAL has more possible product terms than the PLA
- Q18** Dynamic RAM is more preferable than static RAM, why?
- A. DRAM is of the lowest cost, lowest density
 - B. DRAM is of the highest cost, reduced size
 - C. DRAM is of the lowest cost, highest density
 - D. DRAM is more flexible and lowest storage capacity
- Q19** The advantages of RAMs are
- A. Non-destructive read out
 - B. Fast operating speed
 - C. Low power dissipation
 - D. All of the above
- Q20** CD-ROM is a
- A. Memory register
 - B. Magnetic memory
 - C. Semiconductor memory
 - D. Non-volatile memory

TERBUKA

PART B: ANSWER FOUR (4) QUESTIONS ONLY

- Q1** (a) State the difference between latches and flip-flop operation. (4 marks)
- (b) With the aid of truth tables, describe the differences between the following flip-flops.
- (i) RS flip flop (3 marks)
 - (ii) JK flip-flop. (3 marks)
 - (iii) D flip-flop. (3 marks)
- (c) The waveforms for input signals A and B shown in **Figure Q1(c)(i)** are applied to the circuit shown in **Figure Q1(c)(ii)**. Sketch the waveforms of P, Q, R and S of the circuit on **APPENDIX I**. Assumes that initially R=0 and S=1. (7 marks)
- Q2** (a) Design a synchronous counter using JK flip-flop to count 4 digits number. The count sequence is 2,0,3,1 and repeat. The JK excitation table is shown 8 in **Table 1**. Show all steps and the design should include the following :
- (i) State diagram (2 marks)
 - (ii) Excitation table (4 marks)
 - (iii) K-maps to generate minimal expression (4 marks)
 - (iv) Circuit implementation (4 marks)
- (b) **Figure Q2(b)** shown an astable multivibrator circuit using 555 timer. Determine the external resistors R1 and R2 to give output frequency of 10 kHz with duty cycle of 50 % if the external capacitor C is 3nF. (6 marks)
- Q3** (a) State **four (4)** modes of data movement in shift register. (4 marks)
- (b) (i) Draw a logic diagram for a 4-bit serial load shift register (SISO) constructed from edge-triggered D-type flip-flops. All the input and output must be labelled completely. (5 marks)
- (ii) Explain how the shift register in **Q3(b)(i)** can be cleared. (3 marks)

- (iii) For shift register in **Q3(b)(i)**, on the successive rising edges of the clock signal CLK, if the input takes on the values 1 0 1 0, show the contents of the shift register after each edge of the clock until 8th clock pulses in table provided in **APPENDIX II**. You may assume that the register contains all zeroes initially.

(8 marks)

- Q4** (a) With the aid of diagram, explain the difference between the synchronous and asynchronous counters.

(4 marks)

- (b) **Figure Q4(b)(i)** shows the block diagram of a 4-bit counter. Show how it can be configured as the following counter. You may refer to **Figure Q4(b)(ii)** for its internal circuitry. Draw the following counter circuit on **APPENDIX III**.

(i) MOD 6 (5 marks)

(ii) MOD 13 (5 marks)

- (c) For the **Figure Q4(c)**, the propagation delay, t_{pd} for each flip-flop is 40ns and t_{pd} for AND gate is 10ns. Determine the maximum input clock frequency (f_{max}) with a MOD-16 ripple counter.

(6 marks)

- Q5** (a) Several types of architecture are used in PLDs. Draw the block diagram of **three (3)** common types and describe their differences.

(12 marks)

- (b) Show how the PLA shown in **Figure Q5(b)** can be configured to implement the functions in (i) and (ii). Draw the circuit on **APPENDIX IV**. Label all inputs and outputs.

(i) $F1(W, X, Y) = \Sigma(1,2,3,5,7)$ (4 marks)

(ii) $F2(W, X, Y) = \Sigma(0,4,6,7)$ (4 marks)

TERBUKA

- Q6** (a) Define each basic memory operation terms below.
- (i) Write (2 marks)
 - (ii) Read (2 marks)
 - (iii) Address (2 marks)
- (b) A certain memory has a capacity of $4K \times 8$, determine
- (i) The number of data inputs and data outputs. (2 marks)
 - (ii) The number of address lines. (2 marks)
 - (iii) Its capacity in bytes. (2 marks)
- (c) Define each of the following terms.
- (i) RAM (2 marks)
 - (ii) ROM (2 marks)
 - (iii) EPROM (2 marks)
 - (iv) Internal Memory (2 marks)

-END OF QUESTIONS -

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2018/2019
 COURSE NAME : LOGIC SYSTEMS

PROGRAMME CODE : DAE
 COURSE CODE : DAE 21603

 


Figure Q1(c)(i)

 


Figure Q1(c)(ii)

Table 1 : JK FF's Excitation Table

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2018/2019
 COURSE NAME : LOGIC SYSTEMS

PROGRAMME CODE : DAE
 COURSE CODE : DAE 21603



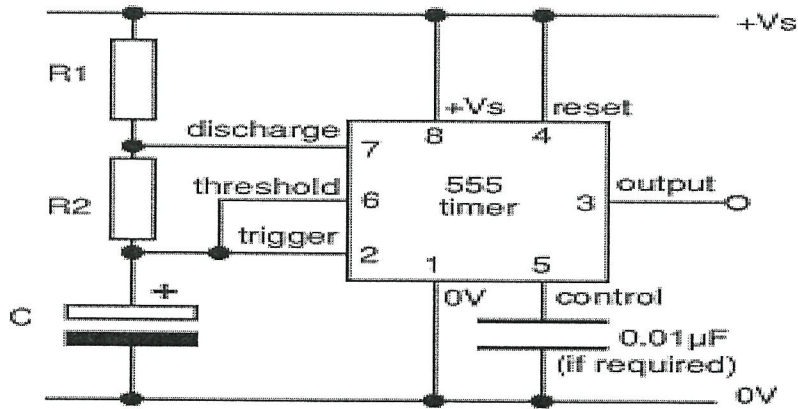


Figure Q2 (b)

 

(i)

 

(ii)

Figure Q4 (b)

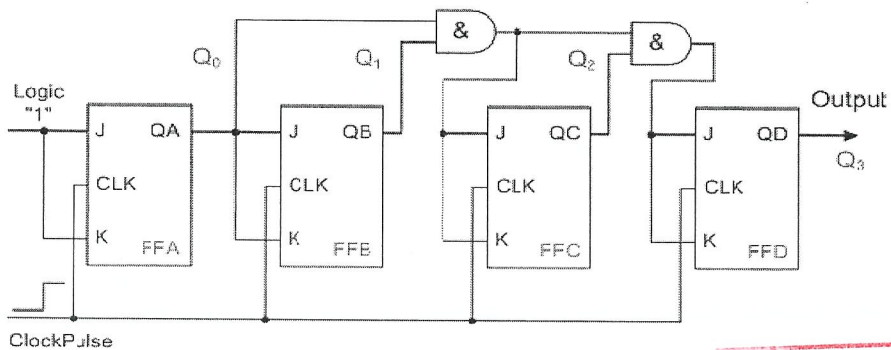


Figure Q4 (c)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2018/2019
COURSE NAME : LOGIC SYSTEMS

PROGRAMME CODE : DAE
COURSE CODE : DAE 21603

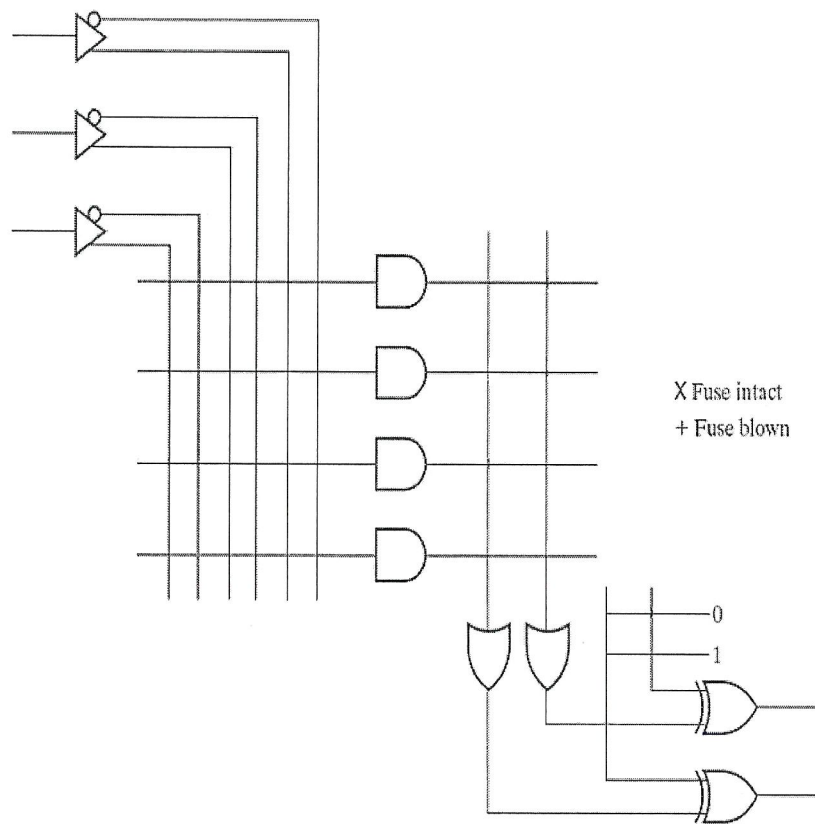



Figure Q5 (b)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION	: SEM I 2018/2019	PROGRAMME CODE	: DAE
COURSE NAME	: LOGIC SYSTEMS	COURSE CODE	: DAE 21603

APPENDIX I

 

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2018/2019
COURSE NAME : LOGIC SYSTEMS

PROGRAMME CODE : DAE
COURSE CODE : DAE 21603

APPENDIX II

Clock Pulse	Q₃	Q₂	Q₁	Q₀
1 st				
2 nd				
3 rd				
4 th				
5 th				
6 th				
7 th				
8 th				




FINAL EXAMINATION


SEMESTER / SESSION : SEM I 2018/2019
COURSE NAME : LOGIC SYSTEMS

PROGRAMME CODE : DAE
COURSE CODE : DAE 21603

APPENDIX III

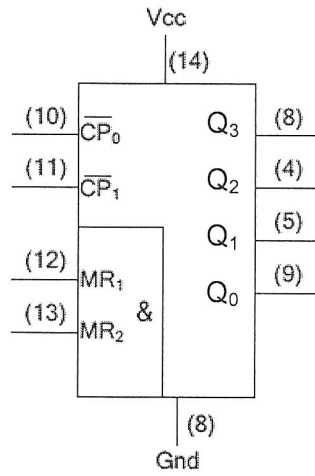

MOD 6

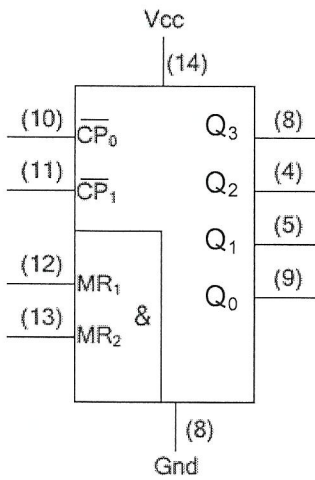

MOD 13


TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2018/2019
COURSE NAME : LOGIC SYSTEMS

PROGRAMME CODE : DAE
COURSE CODE : DAE 21603

APPENDIX IV

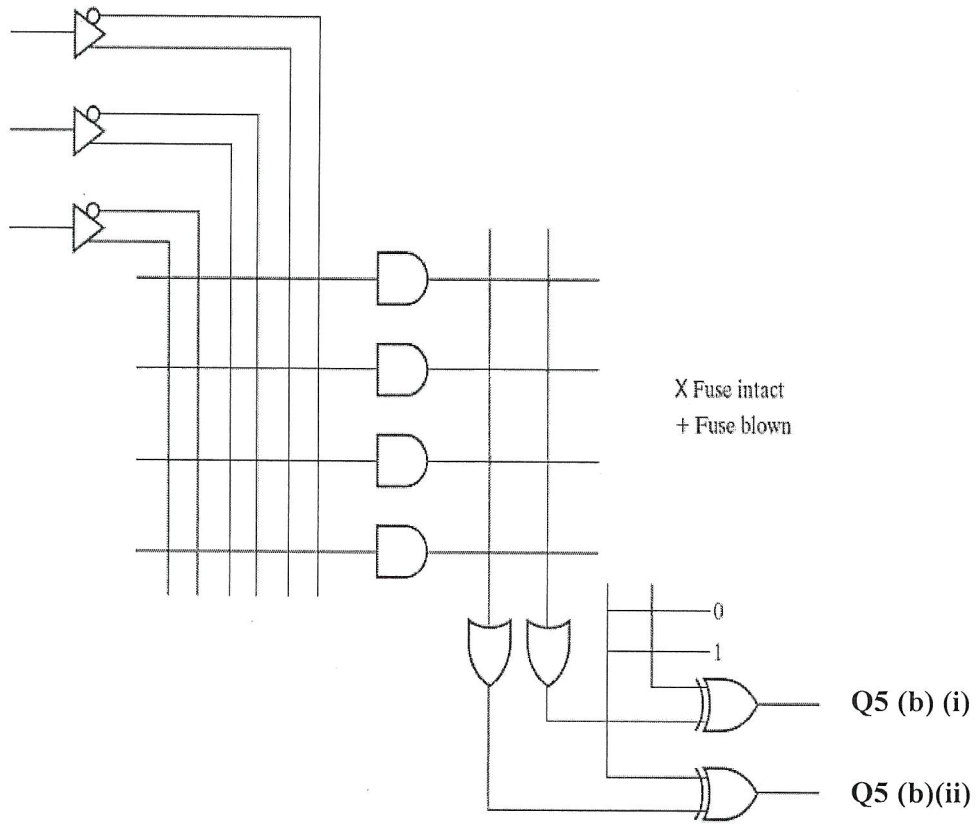

TERBUKA