



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER I  
SESSION 2019/2020**

COURSE NAME : ELECTRONICS II  
COURSE CODE : BWC 20203  
PROGRAMME CODE : BWC  
EXAMINATION DATE : DECEMBER 2019 / JANUARY 2020  
DURATION : 3 HOURS  
INSTRUCTION : ANSWER ALL QUESTIONS

**TERBUKA**

THIS QUESTION PAPER CONSISTS OF **EIGHT (8)** PAGES

- Q1**
- (a) Determine **THREE (3)** advantages of integrated circuit (ICs) over conventional circuit. (3 marks)
- (b) Determine the closed loop gain for each of the amplifier in **Figure Q1 (b) (i)** and **Figure Q1 (b) (ii)**. (6 marks)
- (c) Calculate the value of feedback resistance,  $R_f$  that will produce the indicated closed loop gain,  $A_{cl}$  in each amplifier in **Figure Q1 (c)**. (5 marks)
- (d) Determine the output voltage for the circuit in **Figure Q1 (d)** with a sinusoidal input of 3.0 mV. (6 marks)
- (e) (i) Determine the input and output resistances of the amplifier circuit in **Figure Q1 (e)**. The op-amp data sheet gives  $R_{in} = 2 \text{ M}\Omega$ ,  $R_{out} = 75 \text{ }\Omega$  and  $A_{ol} = 200,000$ . (6 marks)
- (ii) Calculate the close loop gain,  $A$  of the amplifier. (3 marks)
- Q2**
- (a) Describe **TWO (2)** types of active filters and draw an example of the circuit.
- (i) Active filter (2 marks)
- (ii) Passive filter (2 marks)
- (b) Calculate the capacitance values required to produce a 3 kHz critical frequency in the low pass filter as in **Figure Q2 (b)**. (8 marks)
- (c) **Figure Q2 (c)** shows a circuit for the combination of high pass and low pass filter. Determine,
- (i) the bandwidth of the circuit; (4 marks)
- (ii) center of the frequency. (4 marks)

TERBUKA

- (d) Calculate the resonance frequency,  $f_0$  and the band width,  $BW$  for the band pass filter circuit in **Figure Q2 (d)**. (5 marks)

**Q3** (a) Calculate the following codes;

(i)  $(11001)_2 + (101)_2 = 11110$  (2 marks)

(ii)  $(11010)_2 - (10101)_2 = 00101$  (2 marks)

(iii)  $(1101)_2 \times (1001)_2 = 1110101$  (2 marks)

(iv)  $(101101)_2 \div (110)_2 = 111$  (2 marks)

- (b) (i) Simplify the logic expression,  $A+B'C + (A(B+C'))$  and draw a schematic for the circuit that implements the simplified expression. (6 marks)

- (ii) Draw a schematic for a circuit that directly implements the logic function  $A+B'C+(A(B+C'))$ . (6 marks)

- (c) Show the behavior of the logic circuit in **Figure Q3 (c)** with a truth table. (6 marks)

**Q4** (a) Describe two differences between latches and flip-flop. (4 marks)

- (b) State the characteristic equations and the excitation tables for the SR and JK flip-flops. (6 marks)

- (c) A flip-flop 7474 integrated circuit is supplied with a waveform in their input,  $S$  and  $R$  as in **Figure Q4(c)**. Sketch the output diagram at  $Q$  and state the function at each sequence. (10 marks)

TERBUKA

– END OF QUESTIONS –

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020  
COURSE NAME : ELECTRONICS II

PROGRAMME CODE : BWC  
COURSE CODE : BWC 20203

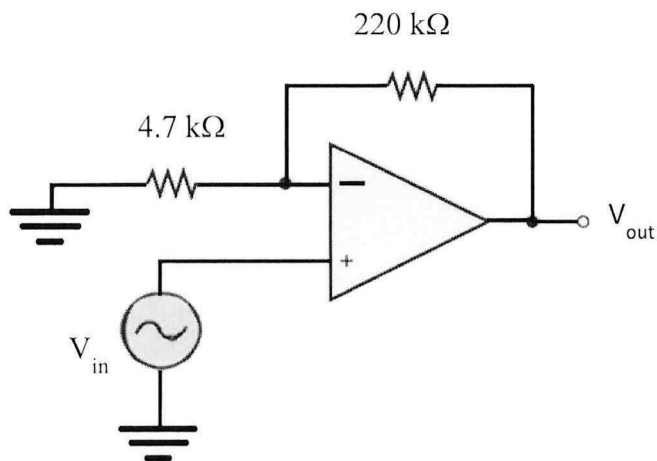


Figure Q1 (b) (i)

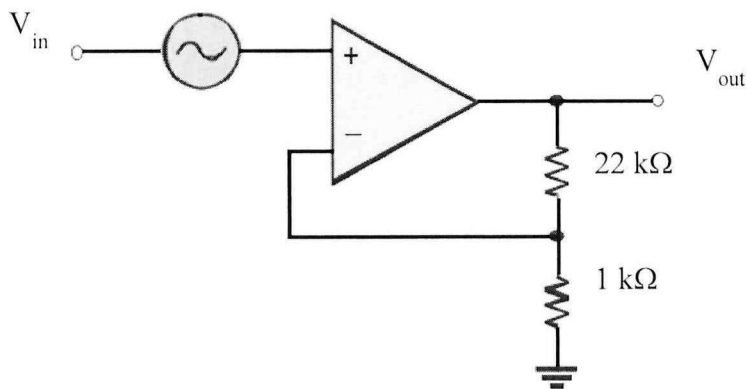


Figure Q1 (b) (ii)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020  
COURSE NAME : ELECTRONICS II

PROGRAMME CODE : BWC  
COURSE CODE : BWC 20203

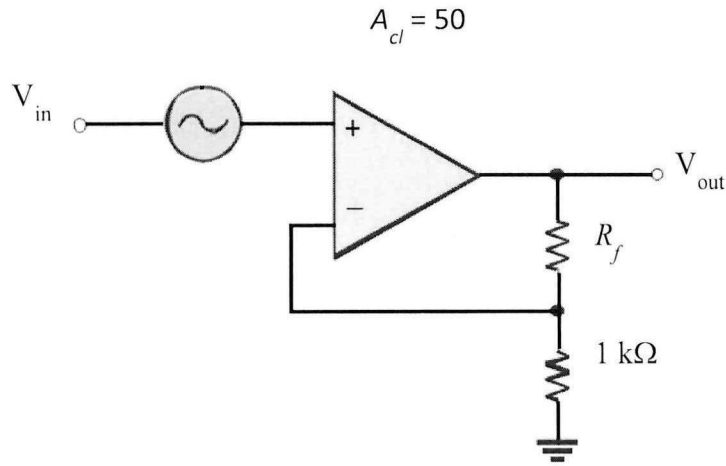


Figure Q1 (c)

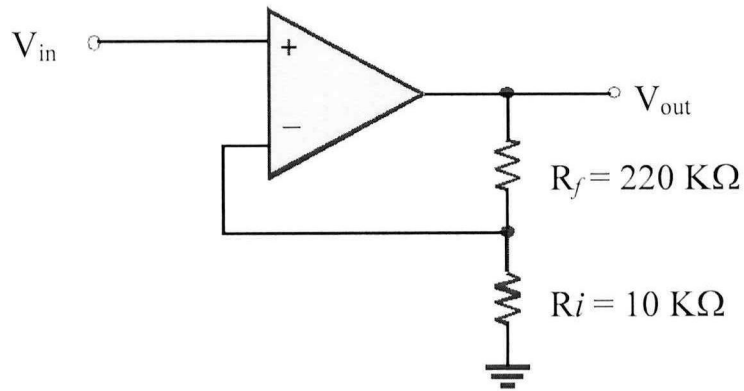


Figure Q1 (d)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020  
COURSE NAME : ELECTRONICS II

PROGRAMME CODE : BWC  
COURSE CODE : BWC 20203

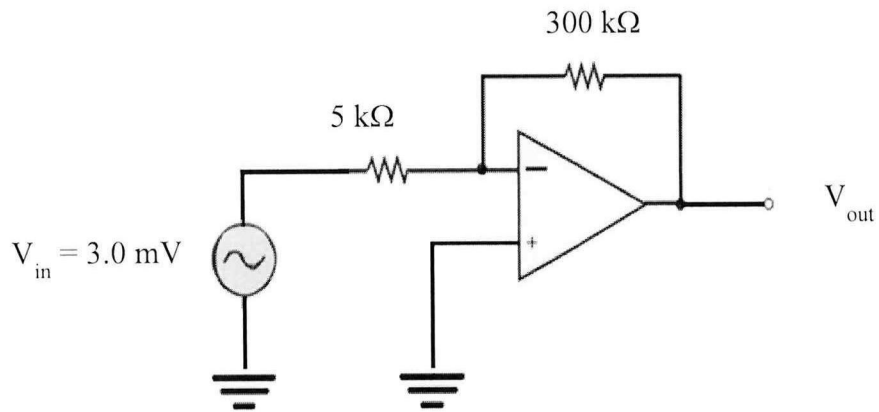


Figure Q1 (e)

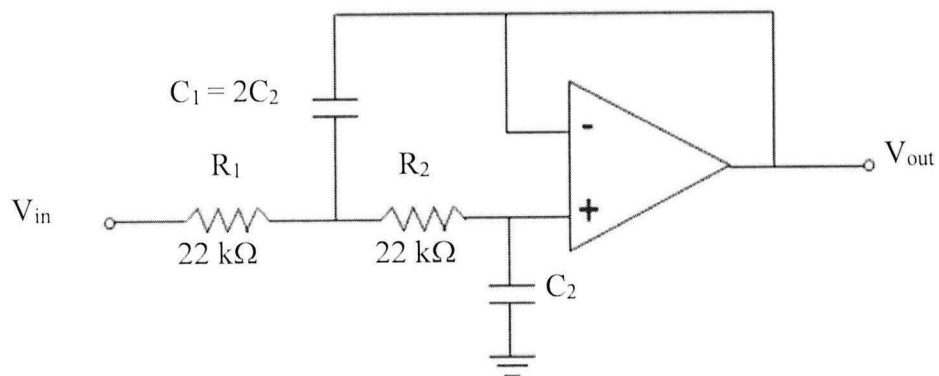


Figure Q2 (b)

TERBUKA



FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020  
COURSE NAME : ELECTRONICS II

PROGRAMME CODE : BWC  
COURSE CODE : BWC 20203

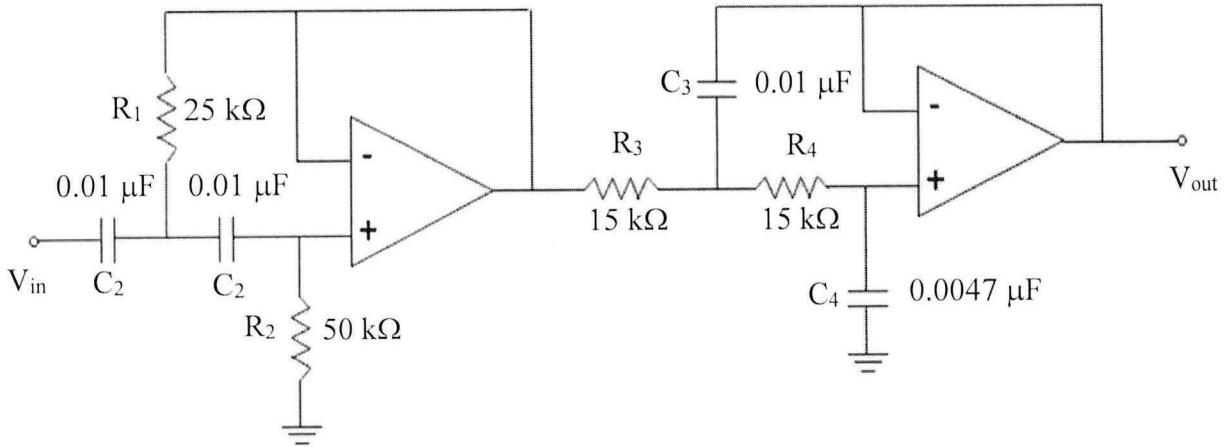


Figure Q2 (c)

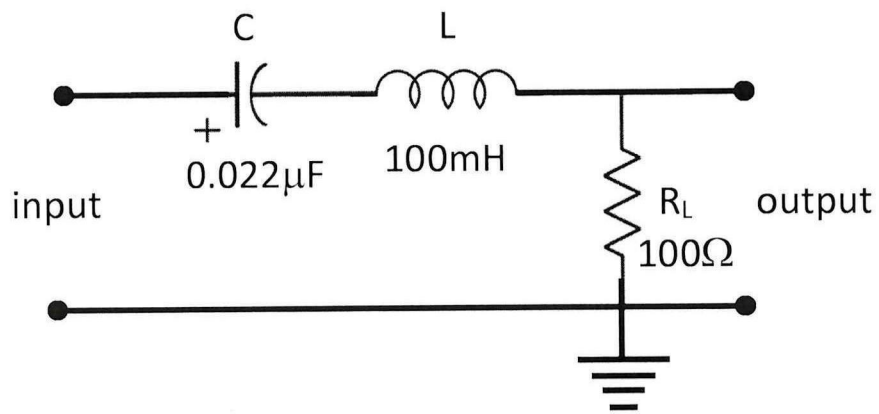


Figure Q2 (d)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2019/2020  
COURSE NAME : FIBER OPTICS

PROGRAMME CODE : BWC  
COURSE CODE : BWC 40703

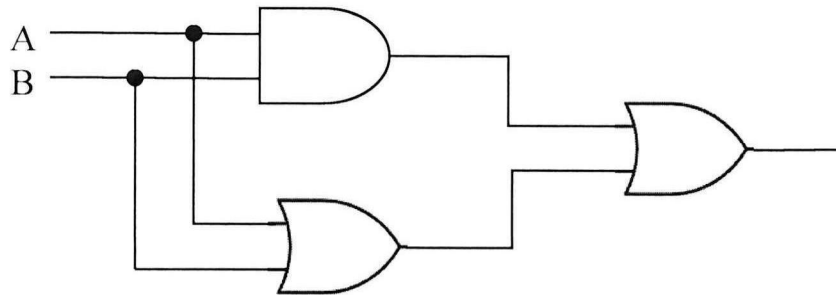


Figure Q3 (c)

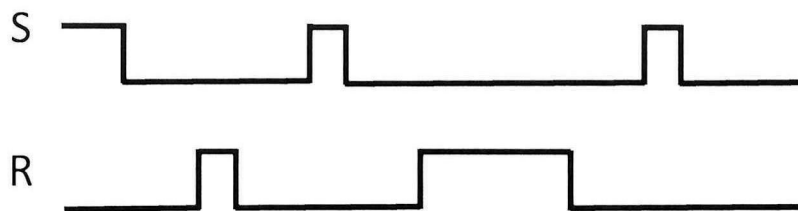
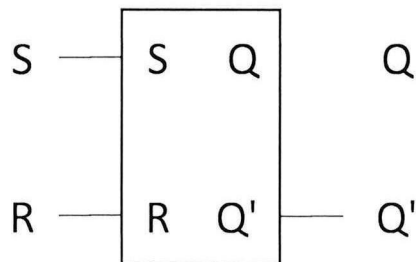


Figure Q4 (c)

TERBUKA