



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

PEPERIKSAAN AKHIR SEMESTER II SESI 2008/09

NAMA MATA PELAJARAN : SISTEM LOGIK

KOD MATAPELAJARAN : DEE 2223

KURSUS : 2 DET / DEE / DEX

TARIKH PEPERIKSAAN : APRIL 2009

JANGKA MASA : 3 JAM

ARAHAN : **BAHAGIAN A : JAWAB SEMUA SOALAN**
BAHAGIAN B : JAWAB TIGA (3) SOALAN SAHAJA DARIPADA LIMA (5) SOALAN.

PART A

- Q1** (a) Draw an active HIGH input R-S latch logic diagram and build its truth table. (3 marks)
- (b) Modify the logic diagram that you have drawn in part Q1(a) if a signal ENABLE is applied. (2 marks)
- (c) State the name of the new logic circuit that you have drawn in part Q1(b)? (1 marks)
- (d) Sketch the Q output waveform for the logic diagram from part Q1(b), when input waveforms EN, S and R as shown in Figure Q1(d) are applied. (2 marks)
- Q2** (a) Draw a logic diagram for four-bit asynchronous binary counter using negative edge-triggered J-K flip-flop and sketch the complete timing diagram using CLK input in Figure Q2(a). (3 marks)
- (b) Determine the maximum clock frequency at which the counter can be operated for a 4-bit asynchronous binary counter if each negative edge-triggered flip-flop has a propagation delay for 15ns. (2 marks)
- (c) Draw a logic diagram for four-bit synchronous binary counter using positive edge-triggered flip-flop and sketch the complete timing diagram using CLK input in Figure Q2(c). (3 marks)
- Q3** (a) Draw the logic symbol for a positive edge-triggered S-R and J-K flip-flop. (2 marks)
- (b) What is the difference between a latch and a flip-flop? Give one reason and one example using logic symbol. (2 marks)
- (c) Show how a negative Edge Triggered D Flip-Flop can be implemented using an S-R flip-flop and inverter. (1 marks)
- (d) The input waveforms in Figure Q3(d) are applied to CLK, D, PRE and CLR as indicated. Determine and draw the \bar{Q} output waveform. (3 marks)

- Q4** (a) State **THREE (3)** possible mode of register operation. (3 marks)
- (b) The circuit shown in Figure Q4(b)(i) is a 5 bits universal register. Sketch all the parallel output Q_0, Q_1, Q_2, Q_3 and Q_4 waveforms in Figure Q4(b)(ii), the states of the 5-bit register (SRG 5), if the data input given is 01101 and clock waveforms as shown in Figure Q4(b)(ii). The register initially contains all 0s. (5 marks)
- Q5** (a) Show how a NOR gate can be implemented by using only four NAND gates. (3 marks)
- (b) Show how a AND gate can be implemented by using only three NOR gates. (3 marks)
- (c) Sketch the output waveform, X for the circuit shown in Figure Q5(c), by referring to the given input waveforms A, B and C and output waveform Y. (2 marks)

PART B (Show all your steps)

- Q6** (a) Determine the Boolean expression of X for the circuit shown in Figure Q6(a). (4 marks)
- (b) Convert the Boolean expression from part Q6(a) into a standard SOP expression. (6 marks)
- (c) Use Karnaugh map to determine the minimum SOP expression for X. (10 marks)
- Q7** (a) With the 555 Timer IC and RC component, draw the complete schematic diagram for monostable (one-shot) operation and astable operation. (6 marks)
- (b) Determine the time width (t_w) for monostable (One-Shot) if given $E = 90V$, $R = 9k\Omega$ and $C = 10nF$ (3 marks)
- (c) Determine the external capacitor (C_{ext}) for monostable (One-Shot) if given $E = 12V$, $t_w = 0.5s$ and $R = 40k\Omega$ (3 marks)
- (d) For the astable multivibrator, if $R_1=1M\Omega$, $R_2= 470k\Omega$ and $C_1=0.001\mu F$, determine the frequency output, t_{H1} , t_{H2} and duty cycle, also draw the output waveform at pin 3. (8 marks)
- Q8** (a) Determine the output Q_0, Q_1, Q_2 and Q_3 of 74HC194 IC a 4-bit bidirectional universal shift register if given the data input waveforms is given as shown in Figure Q8(a). (14 marks)
- (b) If a 10-bit ring counter in Figure Q8(b) has the initial state 0101001111, determine the waveform for each of the Q outputs. (6marks)
- Q9** (a) Convert each of the BINARY code 0000, 0010, 0100, 0110, 0111 to Gray Code. (3 marks)
- (b) Design a J-K synchronous 3-bit up/down counter with a Gray code sequence from Q9(a). The counter should count up when an UP/DOWN control input is 1 and count down when the control input is 0. (17marks)

- Q10 (a) By referring to the logic schematic J-K flip-flop in Figure Q10(a)(i), determine the output \bar{Q} if the input waveforms CLK, J, K, Clear and Preset is given in Figure Q10(a)(ii). Q is initially 1. (10 marks)
- (b) Determine the waveforms at Q, $\bar{Q}(Q')$, CP and $\bar{CP}(CP')$ in Figure Q10(b) for a non-overlapping clock. (10 marks)

PEPERIKSAAN AKHIR

SEMESTER / SESI : SEMESTER II / 2008/2009
MATAPELAJARAN : SISTEM LOGIK

KURSUS : 2 DET/DEE/DIX
KOD MATAPELAJARAN : DBE2223

 


FIGURE Q1(d)

PEPERIKSAAN AKHIR

SEMESTER / SESI : SEMESTER II / 2008/2009
MATAPELAJARAN : SISTEM LOGIK

KURSUS : 2 DET / DEE / DEX
KOD MATAPELAJARAN : DEE2223

 


FIGURE Q2(a)

PEPERIKSAAN AKHIR

SEMESTER / SESI : SEMESTER II / 2008/2009
MATAPELAJARAN : SISTEM LOGIK

KURSUS : 2 DET / DEE / DEX
KOD MATAPELAJARAN : DER2223

 


FIGURE Q2 (c)

PEPERIKSAAN AKHIR

SEMESTER / SESI : SEMESTER II / 2008/2009
MATAPELAJARAN : SISTEM LOGIK

KURSUS : 2 DET / DEE / DEX
KOD MATAPELAJARAN : DIJE2223

 
 


FIGURE Q3(d)

PEPERIKSAAN AKHIR

SEMESTER / SESI : SEMESTER II / 2008/2009
 MATAPELAJARAN : SISTEM LOGIK

KURSUS : 2 DET/DEE/DEX
 KOD MATAPELAJARAN : DEE2223

 


FIGURE Q4 (b)(i)

PEPERIKSAAN AKHIR

SEMESTER / SESI : SEMESTER II / 2008/2009
MATAPELAJARAN : SISTEM LOGIK

KURSUS : 2 DET / DEE / DEX
KOD MATAPELAJARAN : DEE2223

 


FIGURE Q4 (b)(i)

PEPERIKSAAN AKHIR

SEMESTER / SESI : SEMESTER II / 2008/2009
MATAPELAJARAN : SISTEM LOGIK

KURSUS : 2 DET/DEE/DEX
KOD MATAPELAJARAN : DEF2223

 
 


FIGURE Q5 (c)

PEPERIKSAAN AKHIR

SEMESTER / SESI : SEMESTER II / 2008/2009
MATAPELAJARAN : SISTEM LOGIK

KURSUS : 2 DET / DHE / DEX
KOD MATAPELAJARAN : DEE2223

 


FIGURE Q6(a)

PEPERIKSAAN AKHIR

SEMESTER / SESI : SEMESTER II / 2008/2009
MATAPELAJARAN : SISTEM LOGIK

KURSUS : 2 DET / DEE / DEX
KOD MATAPELAJARAN : DEI2223

 


FIGURE Q8(a)

PEPERIKSAAN AKHIR

SEMESTER / SESI : SEMESTER II / 2008/2009
MATAPELAJARAN : SISTEM LOGIK

KURSUS : 2 DET / DFF / DEX
KOD MATAPELAJARAN : DKE2223

 


FIGURE Q8(b)

PEPERIKSAAN AKHIR

SEMESTER / SESI : SEMESTER II / 2008/2009
MATAPELAJARAN : SISTEM LOGIK

KURSUS : 2 DET / DEE / DEX
KOD MATAPELAJARAN : DEE2223

 


FIGURE Q10(a)(i)

 


FIGURE Q10(a)(ii)

PEPERIKSAAN AKHIR

SEMESTER / SESI : SEMESTER II / 2008/2009
MATA PELAJARAN : SISTEM LOGIK

KURSUS : 2 DET / DEB / DEX
KOD MATA PELAJARAN : DEE2223

 
 


FIGURE Q10(b)