



**UNIVERSITI TUN HUSSEIN ONN
MALAYSIA**

**PEPERIKSAAN AKHIR
SEMESTER II
SESI 2008/2009**

NAMA MATAPELAJARAN : ANALISIS & SINTESIS RANGKAIAN
ELEKTRIK

KOD MATAPELAJARAN : BEE 3113

KURSUS : 2 BEE

TARIKH PEPERIKSAAN : APRIL/MEI 2009

JANGKA MASA : 2 ½ JAM

ARAHAN : KERTAS SOALAN INI TERBAHAGI
KEPADA **DUA (2) BAHAGIAN**.
BAHAGIAN A: SILA JAWAB **TIGA (3)**
DARIPADA **LIMA (5) SOALAN**.
BAHAGIAN B : SILA JAWAB **SATU (1)**
DARIPADA **DUA (2) SOALAN**

KERTAS SOALAN INI MENGANDUNGI 13 MUKA SURAT.

PART A: ANSWER ONLY THREE (3) FROM FIVE (5) QUESTIONS GIVEN.**Q1** Please use Table Q1 for your reference.

(a) Determine the Laplace transform of the following function:

(i) $f(t) = \sin(\omega t + 90^\circ)$

(ii) $f(t) = e^{-6t} \sin 4t u(t)$

(iii) $f(t) = te^{2t} \sin 2t u(t)$

(iv) $f(t) = 2t^2 u(t) + 5e^{-3t-6} u(t-2)$

(v) $f(t) = 20 \cos 4(t-1)u(t)$

(10 marks)

(b) Obtain the Laplace transforms of the functions in Figure Q1(b)(i) and Figure Q1(b)(ii).

(10 marks)

(c) Determine the inverse Laplace transform of each of the following functions:

(i) $F(s) = \frac{2se^{-\pi}}{s^2 + 1}$

(2 marks)

(ii) $F(s) = \frac{8s^3}{s(s+1)}$

(3 marks)

- Q2** (a) For the circuit in Fig. Q2(a),
- (i) Find the initial voltage, $v(0^-)$ and current, $i(0^-)$ at $t < 0$. (3 marks)
 - (ii) Draw the circuit diagram at $t=0$. (2 marks)
 - (iii) Find $v_o(t)$ at $t > 0$ in the circuit. (6 marks)
 - (iv) Identify the output voltage in term of force and natural response. (1 mark)
- (b) The transfer function for a network is $H(s) = \frac{s+10}{s^2+4s+8}$.
- (i) Sketch the pole-zero plot of $H(s)$. (3 marks)
 - (ii) Determine the type of damping exhibited by the network. Justify if this is a stable network. (2 marks)
- (c) A system has a transfer function, $h_1(t) = u(t-1) - u(t-3)$ and an input of $x(t) = u(t) - u(t-1)$. Determine the output function, $y(t)$ using convolution integral. Show all the diagrams and steps. (8 marks)

- Q3** (a) A series RLC circuit with an input voltage of $5V \angle 0^\circ$ is to be designed to meet the following specifications:

A peak current of 500mA at resonance

A bandwidth of 120 Hz

A resonant frequency of 8400 Hz

- (i) Find the values of resistance, R , inductance, L , and capacitance, C in the circuit. (8 marks)
- (ii) Determine the quality factor, Q of the circuit (3 marks)
- (b) Based on Figure Q3 (b),
- (i) Determine the transfer function of voltage gain, $\frac{V_o}{V_i}$ (4 marks)
- (ii) Sketch the bode plot of voltage gain A_{vdB} versus frequency (8 marks)
- (iii) State the application of the circuit based on the frequency response (2 marks)

- Q4** (a) Given a filter configuration shown as Figure Q4(a),

- (i) Find the transfer function, $\frac{V_o(s)}{V_s(s)}$ (5 marks)
- (ii) Determine the type of filter (2 marks)
- (iii) If the Band Stop Filter is a standard series resonance circuit, Calculate the center frequency and bandwidth. Use $L = 100\text{mH}$, $C = 10\ \mu\text{F}$ and $R = 100\text{k}\Omega$ (8 marks)
- (b) For an emergency situation, an engineer needs to make an RC high-pass filter. He has one 10-pF capacitor, one 30-pF capacitor, one 1.8 k Ω resistor, and one 3.3-k Ω resistor available. Find the greatest cutoff frequency possible using these elements. (10 marks)

- Q5** (a) A two port network has the following ABCD parameter:

$$ABCD = \begin{bmatrix} 4 & 20\Omega \\ 0.1 \text{ S} & 2 \end{bmatrix}$$

The network is driven by a 50Volt dc source whose internal resistance is 10Ω . The output port is connected to the variable load resistance, R_L .

- (i) State the condition for maximum power transfer to the load (2 marks)
 - (ii) Determine the resistance load, R_L for maximum power transfer (7 marks)
 - (iii) Calculate the power maximum power transfer (7 marks)
- (b) Find the admittance parameters of the circuit in Figure Q5(b). (9 marks)

PART B: ANSWER ONE (1) QUESTION ONLY.

- Q6** (a) Given the waveform in Figure Q6(a), determine the type of symmetry that exists if the origin is selected at:
- (i) point t_1
 - (ii) point t_2
- (4 marks)

- (b) For the periodic functions in Figure Q6(b), determine the following:
- (i) Fundamental frequency, ω_0 in radians per second (2 marks)
 - (ii) The exponential Fourier coefficient, C_n (7 marks)
 - (iii) Voltage equation, $V(t)$ as a Fourier series (2 marks)

- (c) The voltage and current at the terminals of a network are given as:

$$v = 50 + 200 \cos (500t + 45^\circ) + 60 \sin 1000t \text{ V,}$$

$$i = 5 + 5 \sin (500t + 75^\circ) + 8 \cos (1000t - 30^\circ) \text{ A}$$

Known that the current is in the direction of the voltage drop across the terminals,

- (i) Find the average power at the terminals (4 marks)
- (ii) Obtain the rms value of the voltage, V_{rms} (3 marks)
- (iii) Determine the rms value of the current, I_{rms} (3 marks)

- Q7** (a) The Fourier Series for a function is given by equation:

$$f(t) = \sum_{\substack{n=-1 \\ n=\text{odd}}}^{\infty} \frac{-2}{n\pi} \sin \frac{n\pi}{2} \cos(n\omega_0 t) + \frac{6}{n\pi} \sin(n\omega_0 t)$$

- (i) Find the first four terms of the amplitude and phase spectra for the signal
(4 marks)
- (ii) Plot the amplitude and phase spectra found in part (a)(i)
(4 marks)
- (iii) Based on your result in part a(ii), what can you conclude about the magnitude of the n^{th} harmonic as $n \rightarrow \infty$?
(2 marks)
- (b) A voltage of $v(t) = 100 \cos \omega t + 30 \cos(3\omega t + 60^\circ)$ is connected to the circuit shown in Figure Q7 (b). What will be the current through 500Ω resistor, if the fundamental frequency is 10^4 rad/s ?
(7 marks)
- (c) A network in Figure Q7(c) represents a simple low pass filter. An input voltage, $v_i(t) = 5e^{-2t} u(t)$ is applied to the network. Find the Fourier transform of the output, $v_o(t)$.
(8 marks)

PEPERIKSAAN AKHIR

SEMESTER/SESI : SEMESTER 1/2008/09

KURSUS : 2 & 3 BEE

MATAPELAJARAN : ANALISIS & SINTESIS
RANGKAIAN ELEKTRIK

KOD M/P: BEE 3113

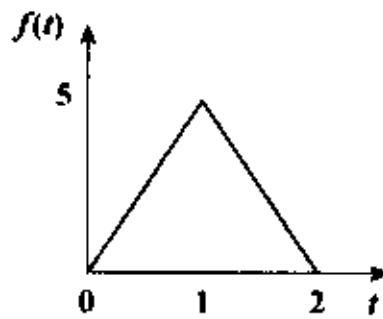


Figure Q1(b)(i)

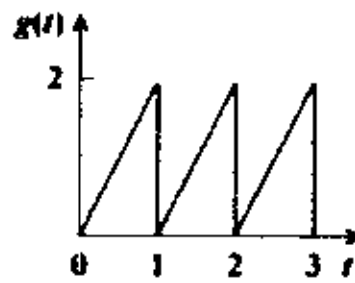


Figure Q1(b)(ii)

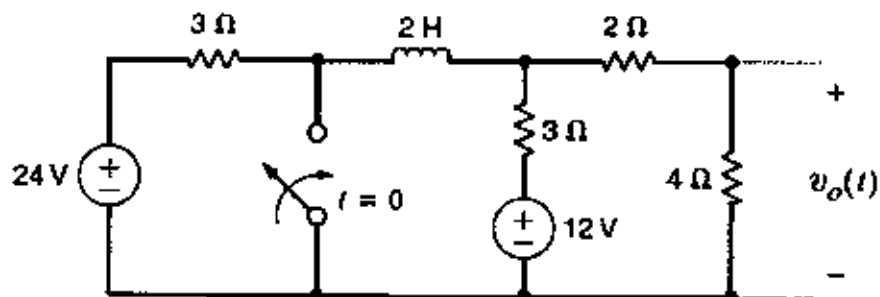


Figure Q2(a)

PEPERIKSAAN AKHIR

SEMESTER/SESI : SEMESTER II/2008/09

KURSUS : 2 BEE

MATAPELAJARAN : ANALISIS & SINTESIS
RANGKAIAN ELEKTRIK

KOD M/P: BEE 3113

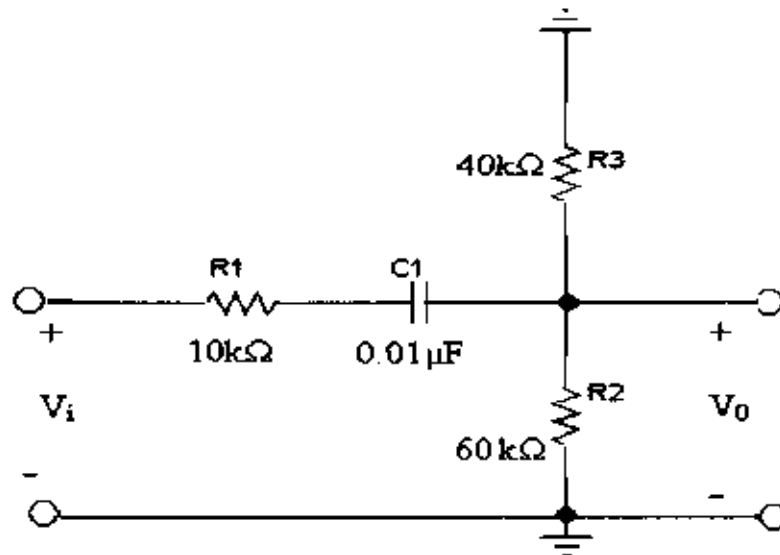


Figure Q3(b)

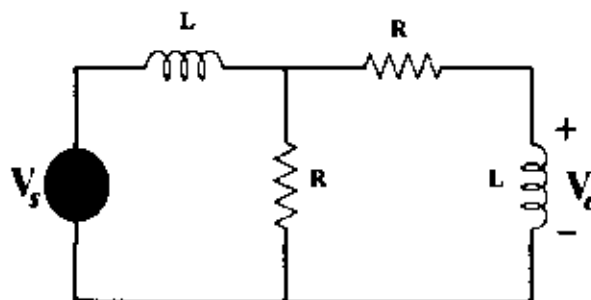


Figure Q4(a)

PEPERIKSAAN AKHIR

SEMESTER/SESI : SEMESTER II/2008/09

KURSUS : 2 BEE

MATAPELAJARAN : ANALISIS & SINTESIS
RANGKAIAN ELEKTRIK

KOD M/P: BEE 3113

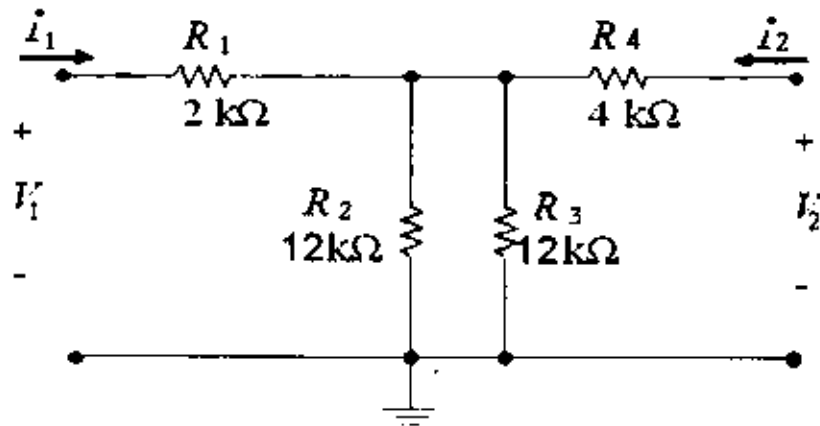


Figure Q5(b)

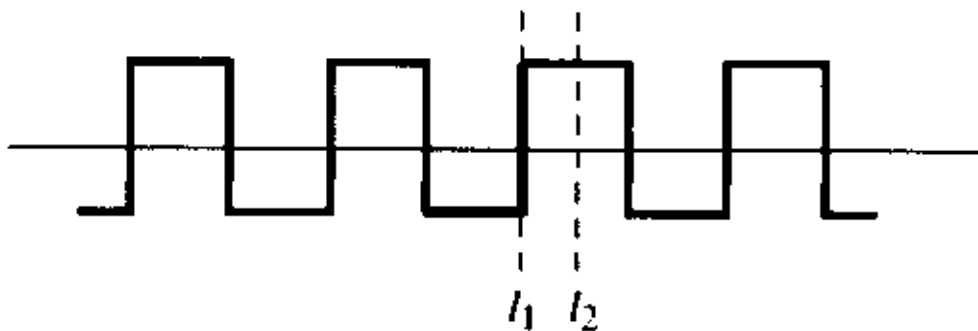


Figure Q6(a)

PEPERIKSAAN AKHIR

SEMESTER/SESI : SEMESTER II/2008/09

KURSUS : 2 BEE

MATAPELAJARAN : ANALISIS & SINTESIS
RANGKAIAN ELEKTRIK

KOD M/P: BEE 3113

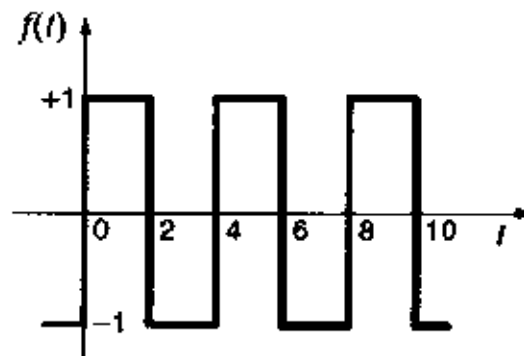


Figure Q6(b)

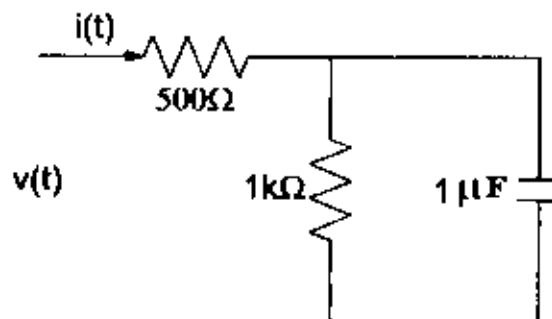


Figure Q7(b)

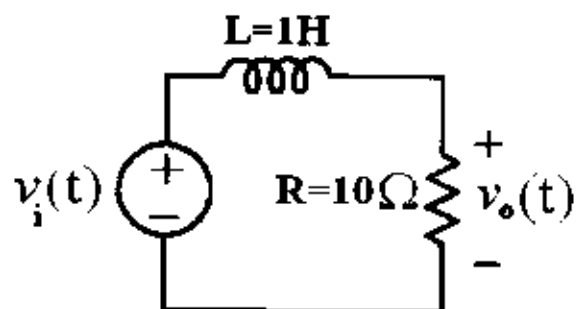


Figure Q7(c)

PEPERIKSAAN AKHIR

SEMESTER/SESI : SEMESTER II/2008/09

KURSUS : 2 BEE

MATAPELAJARAN : ANALISIS & SINTESIS
RANGKAIAN ELEKTRIK

KOD M/P: BEE 3113

Table 1: Properties of Laplace Transform

No.	f(t)	F(s)
1.	$\delta(t)$	1
2.	$u(t)$	$1/s$
3.	$tu(t)$	$1/s^2$
4.	$t^n u(t)$	$(n!)/s^{n+1}$
5.	$e^{-at} u(t)$	$1/(s+a)$
6.	$\sin \omega t u(t)$	$\omega/(s^2+\omega^2)$
7.	$\cos \omega t u(t)$	$s/(s^2+\omega^2)$
8.	$f(at)$	$\frac{1}{a} F\left(\frac{s}{a}\right)$
9.	$e^{-at} f(t)$	$F(s+a)$
10.	$f(t-a) u(t-a)$	$e^{-as} F(s)$
11.	$\frac{df}{dt}$ $\frac{d^n f}{dt^n}$	$sF(s) - f(0^-)$ $s^n F(s) - s^{n-1} f(s)$ $- s^{n-2} f'(0^-) \dots - f^{(n-1)}(0^-)$
12.	$\int_0^t f(t) dt$	$\frac{1}{s} F(s)$
13.	$tf(t)$	$-\frac{d}{ds} F(s)$
14.	$\frac{f(t)}{t}$	$\int_0^\infty F(s) ds$
15.	$f(t+nT)$	$\frac{F_1(s)}{1-e^{-sT}}$
16.	$f(0)$	$\lim_{s \rightarrow \infty} sF(s)$
17.	$f(\infty)$	$\lim_{s \rightarrow 0} sF(s)$
18.	$f_1(t) * f_2(t)$	$F_1(s) \cdot F_2(s)$

PEPERIKSAAN AKHIR

SEMESTER/SESI : SEMESTER II/2008/09

KURSUS : 2 BEE

MATAPELAJARAN : ANALISIS & SINTESIS
RANGKAIAN ELEKTRIK

KOD M/P: BEE 3113

Table 2: Trigonometric Integrals

$\sin(A \pm B) = \sin A \cos B \pm \cos A \sin B$
$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$
$\int_0^T \sin n\omega_0 t \, dt = 0$
$\int_0^T \cos n\omega_0 t \, dt = 0$
$\int_0^T \sin n\omega_0 t \cos m\omega_0 t \, dt = 0$
$\int_0^T \sin n\omega_0 t \sin m\omega_0 t \, dt = 0, \quad (m \neq n)$
$\int_0^T \cos n\omega_0 t \cos m\omega_0 t \, dt = 0, \quad (m \neq n)$
$\int_0^T \sin^2 n\omega_0 t \, dt = T/2$
$\int_0^T \cos^2 n\omega_0 t \, dt = T/2$

Table 3: Fourier Transform Pairs

Pair	$f(t)$	$F(\omega)$
1	$\delta(t)$	1
2	A	$2\pi A\delta(\omega)$
3	$\text{sgn}(t)$	$2/j\omega$
4	$u(t)$	$\pi\delta(\omega) + 1/j\omega$
5	$e^{-a}u(t)$	$1/(a + j\omega), a > 0$
6	$e^a u(-t)$	$1/(a - j\omega), a > 0$
7	$e^{-a t }$	$2a/(a^2 + \omega^2), a > 0$
8	$e^{j\omega_0 t}$	$2\pi\delta(\omega - \omega_0)$
9	$\cos(\omega_0 t)$	$\pi[\delta(\omega + \omega_0) + \delta(\omega - \omega_0)]$
10	$\sin(\omega_0 t)$	$j\pi[\delta(\omega + \omega_0) - \delta(\omega - \omega_0)]$