



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

FINAL EXAMINATION SEMESTER II SESSION 2008/09

SUBJECT'S NAME : ELECTRICAL CIRCUIT THEORY

SUBJECT'S CODE : BEE 1113

COURSE : 1 BEE

EXAMINATION DATE : APRIL 2009

DURATION : 3 HOURS

**INSTRUCTION : PART A
ANSWER ALL QUESTIONS**

**PART B
ANSWER FOUR (4) QUESTIONS
OUT OF SIX (6) QUESTIONS**

THIS QUESTION PAPER CONSISTS OF THIRTEEN (13) PAGES

PART A – Question 1 to Question 4 (60 marks)

- Q1** (a) A resistor with a current of 2 A through it in an amplifier circuit converts 1000 J of electrical energy in 90 s. What is the voltage across the resistor? (3 marks)
- (b) Explain how a parallel-plate capacitor stores the energy when it is connected to an electrical source. You may include diagram in your answer. (8 marks)
- Q2** (a) Using the node voltage technique to the circuit given in Figure Q2(a), calculate
- (i) node voltages v_1 and v_2 . (7 marks)
- (ii) current i_β . (3 marks)
- (b) Referring to the circuit given in Figure Q2(b), it is found that the current $i = 4$ mA when $R = 2$ k Ω and $i = 3$ mA when $R = 4$ k Ω .
- (i) Determine the Thevenin equivalent circuit. (6 marks)
- (ii) Specify the value of R to cause $i = 2$ mA. (2 marks)
- (iii) Calculate the maximum power transfer to R . (3 marks)
- (iv) Determine the maximum possible value of the current i . (2 marks)
- Q3** Given portable lighting equipment for a mine is located at point A, located 100 m from its DC supply. The mine lights used a total of 5 kW and operates at 120 V.
- (a) State the parameters that affect the resistance value of wire. (3 marks)
- (b) Determine the maximum cross-sectional area required of the copper wires if the power loss in copper wire is not more than 5% of power required by the mine lights. Given the resistivity of copper wire, $\rho = 1.7 \times 10^{-4}$ Ωm . (7 marks)
- (c) Suppose a worker that using the portable light moves further away from point A, what happen to the portable lighting wire resistance? Give **ONE (1)** reason for your answer. (4 marks)

- Q4** (a) For first-order circuit analysis, what is the difference between a natural response analysis and a step response analysis? (6 marks)
- (b) Referring to Figure Q4(b), redraw the circuit for
- (i) $t < 0$. (3 marks)
- (ii) $t > 0$. (3 marks)

PART B – Question 5 to Question 10 (40 marks)

- Q5** An electroplating bath, as shown in Figure Q5, is to plate silver uniformly into objects such as kitchen ware and plates. A current of 600 A flows for 20 minutes and each coulomb transports 1.118 milligrams of silver.
- (a) Calculate the supply voltage required if the process absorbs 14.4 MJ of energy. (2 marks)
- (b) What is the weight of silver deposited in grams? (8 marks)
- Q6** (a) Referring to the circuit in Figure Q6, calculate current i_a using mesh-current technique. (8 marks)
- (b) Suppose a wire is connected in parallel with the 12 A source, determine the current supplied by the dependent source. (2 marks)
- Q7** (a) Referring to the circuit in Figure Q7, determine the reading on both ammeter and voltmeter using the superposition technique. (7 marks)
- (b) Explain what will happen if the ammeter in Figure Q7 is connected in parallel with 20 k Ω resistor. (3 marks)

Q8 Referring to circuit in Figure Q8, the voltage supply is given as $v(t) = 4\cos 3t$ V.

- (a) How do inductor voltage expressed in term of inductor current? (2 marks)
- (b) Find the equivalent inductance in term of L. (4 marks)
- (c) Given the value of $L = 0.04$ H, calculate the value of current $i(t)$. (4 marks)

Q9 A typical charging circuit for control system is given in Figure Q9.

- (a) What is the response produced by this circuit? (1 mark)
- (b) Determine $v(t)$ for $t \geq 0$. (6 marks)
- (c) If the $4 \text{ k}\Omega$ resistor becomes short-circuit, does the initial capacitor voltage change? Give **ONE (1)** reason for your answer. (3 marks)

Q10 A second-order RLC circuit with double switches, T1 and T2, is given in Figure Q10.

- (a) What happen when switch T2 is closed? (2 marks)
- (b) Calculate both initial inductor current and initial capacitor voltage. (2 marks)
- (c) Determine the solution produce by this circuit, final inductor current and final capacitor voltage. (6 marks)

FINAL EXAMINATION

SEMESTER/SESSION : II/2008/09

COURSE

: I BEE

SUBJECT'S NAME : ELECTRICAL CIRCUIT THEORY

SUBJECT'S CODE

: BEE 1113

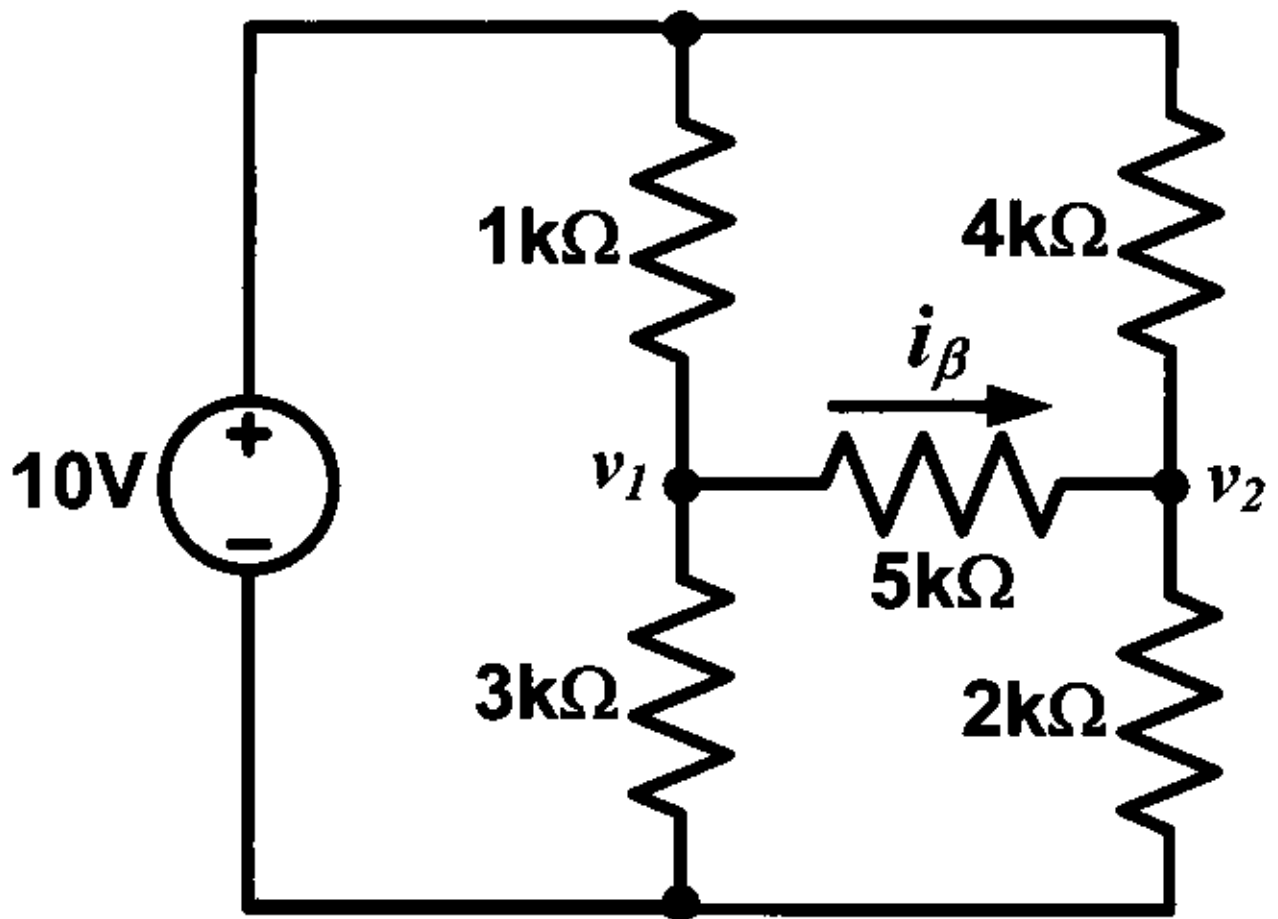


FIGURE Q2(a)

FINAL EXAMINATION

SEMESTER/SESSION : II/2008/09

COURSE

: I BEE

SUBJECT'S NAME : ELECTRICAL CIRCUIT THEORY

SUBJECT'S CODE

: BEE 1113

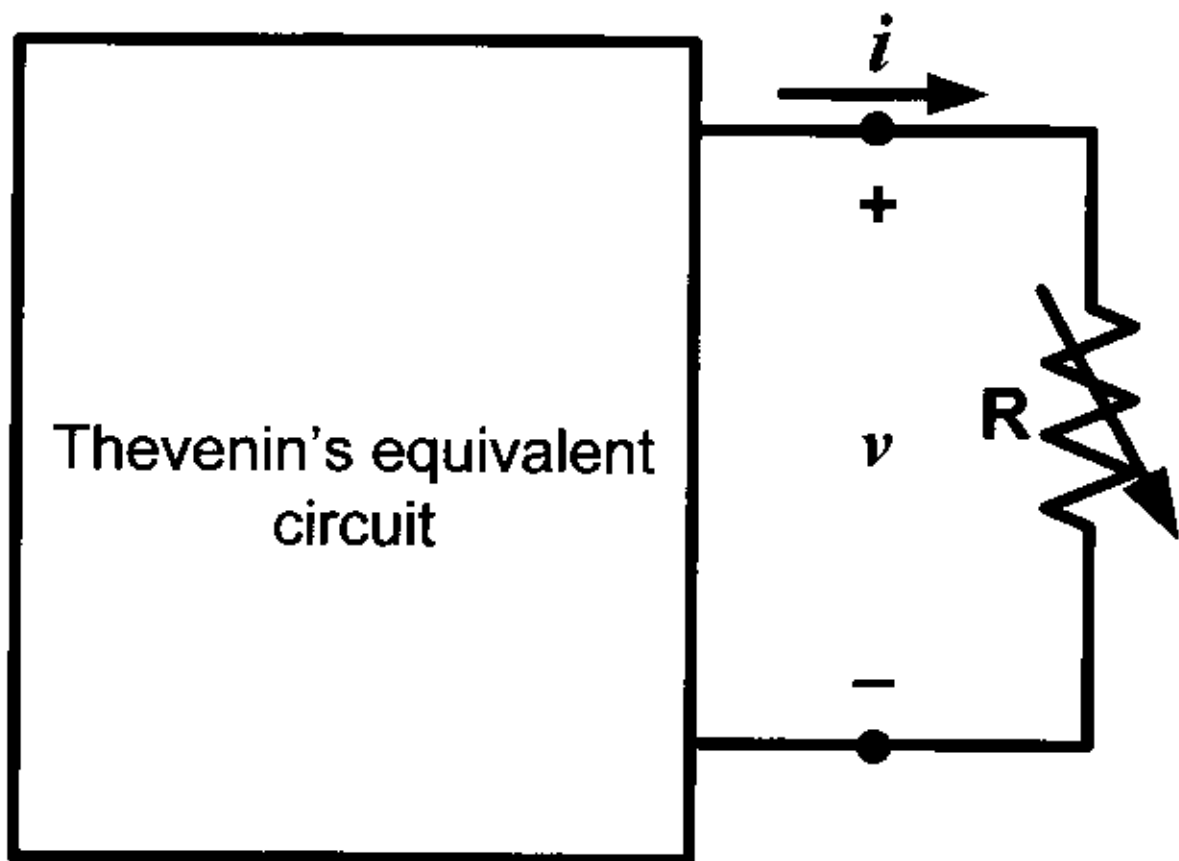


FIGURE Q2(b)

FINAL EXAMINATION

SEMESTER/SESSION : II/2008/09

COURSE :

I BEE

SUBJECT'S NAME : ELECTRICAL CIRCUIT THEORY

SUBJECT'S CODE :

BEE 1113

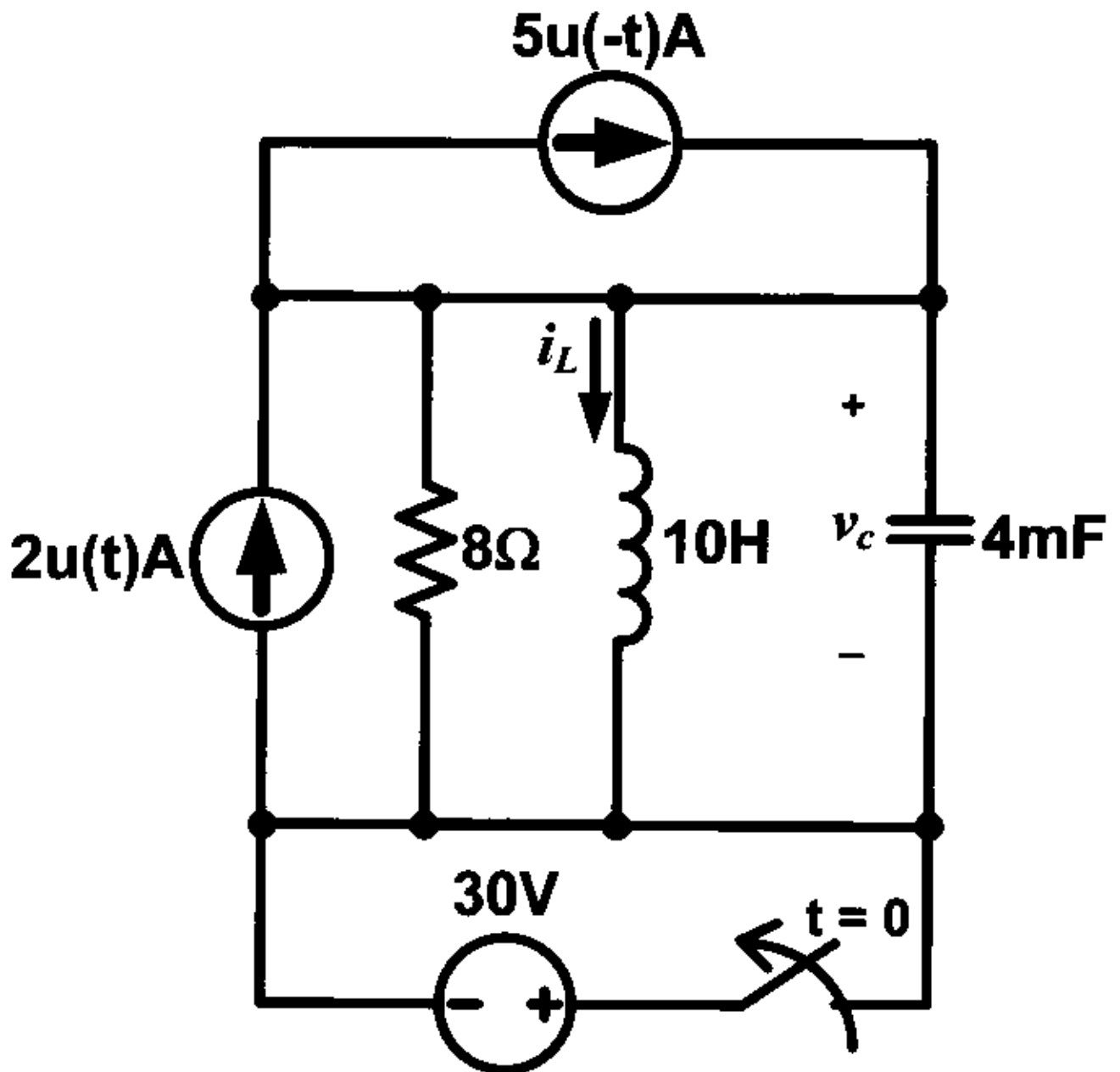


FIGURE Q4(b)

FINAL EXAMINATION

SEMESTER/SESSION : II/2008/09

COURSE

: I BEE

SUBJECT'S NAME : ELECTRICAL CIRCUIT THEORY

SUBJECT'S CODE

: BEE 1113

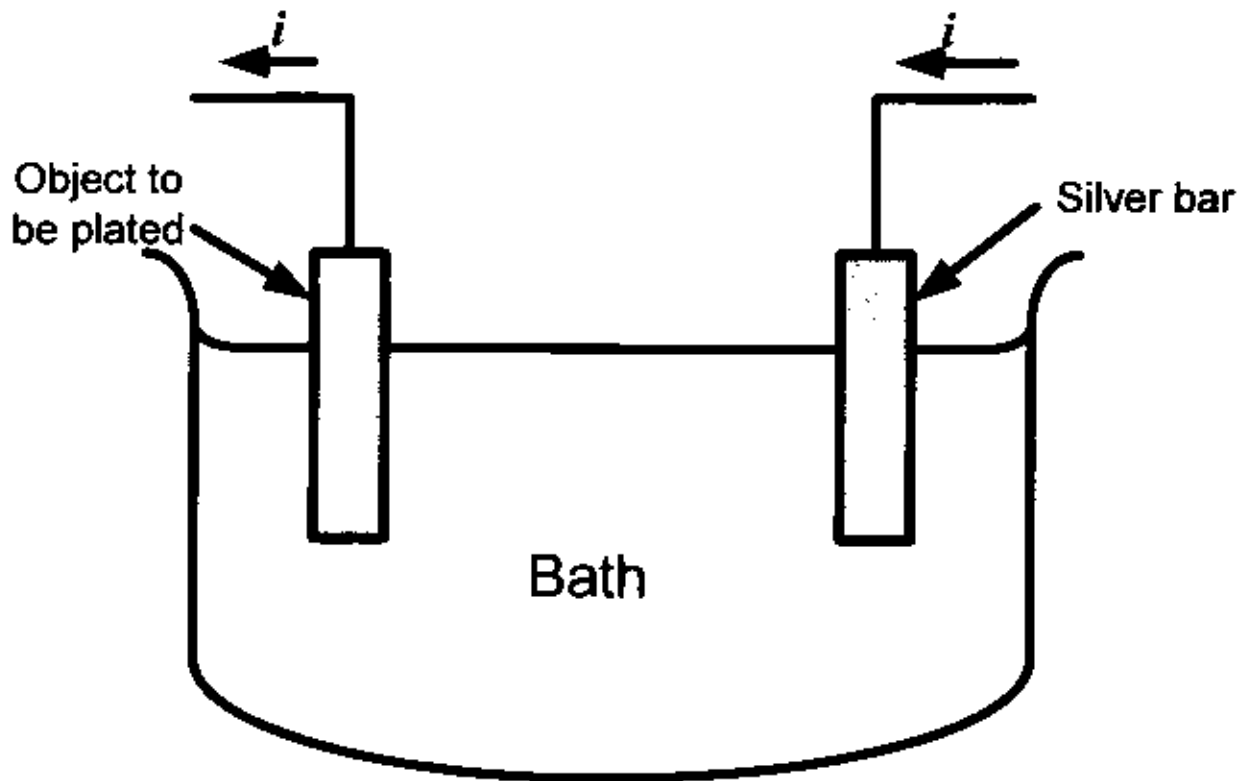


FIGURE Q5

FINAL EXAMINATION

SEMESTER/SESSION : II/2008/09

COURSE

: 1 BEE

SUBJECT'S NAME : ELECTRICAL CIRCUIT THEORY

SUBJECT'S CODE

: BEE 1113

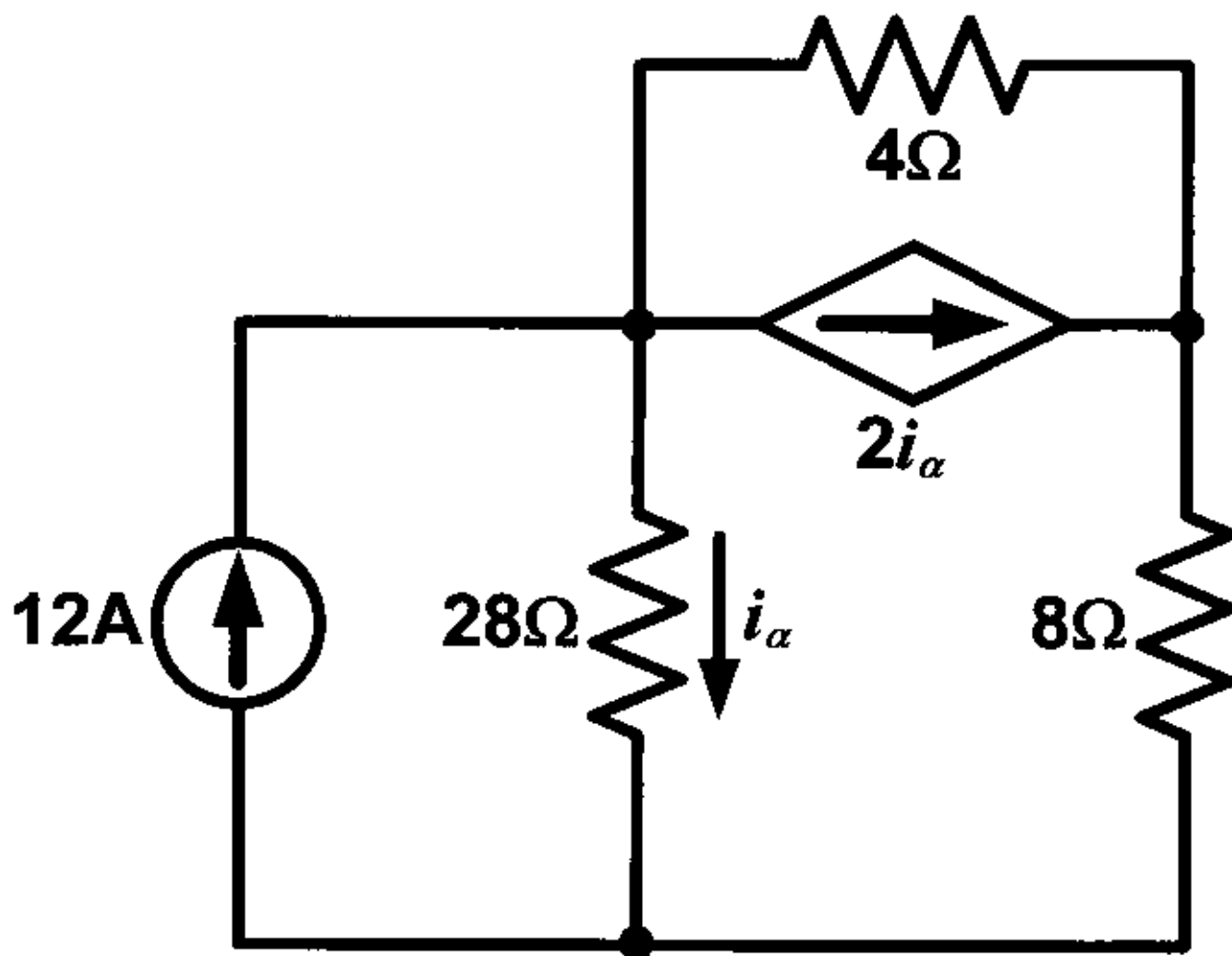


FIGURE Q6

FINAL EXAMINATION

SEMESTER/SESSION : II/2008/09

COURSE

: I BEE

SUBJECT'S NAME : ELECTRICAL CIRCUIT THEORY

SUBJECT'S CODE

: BEE 1113

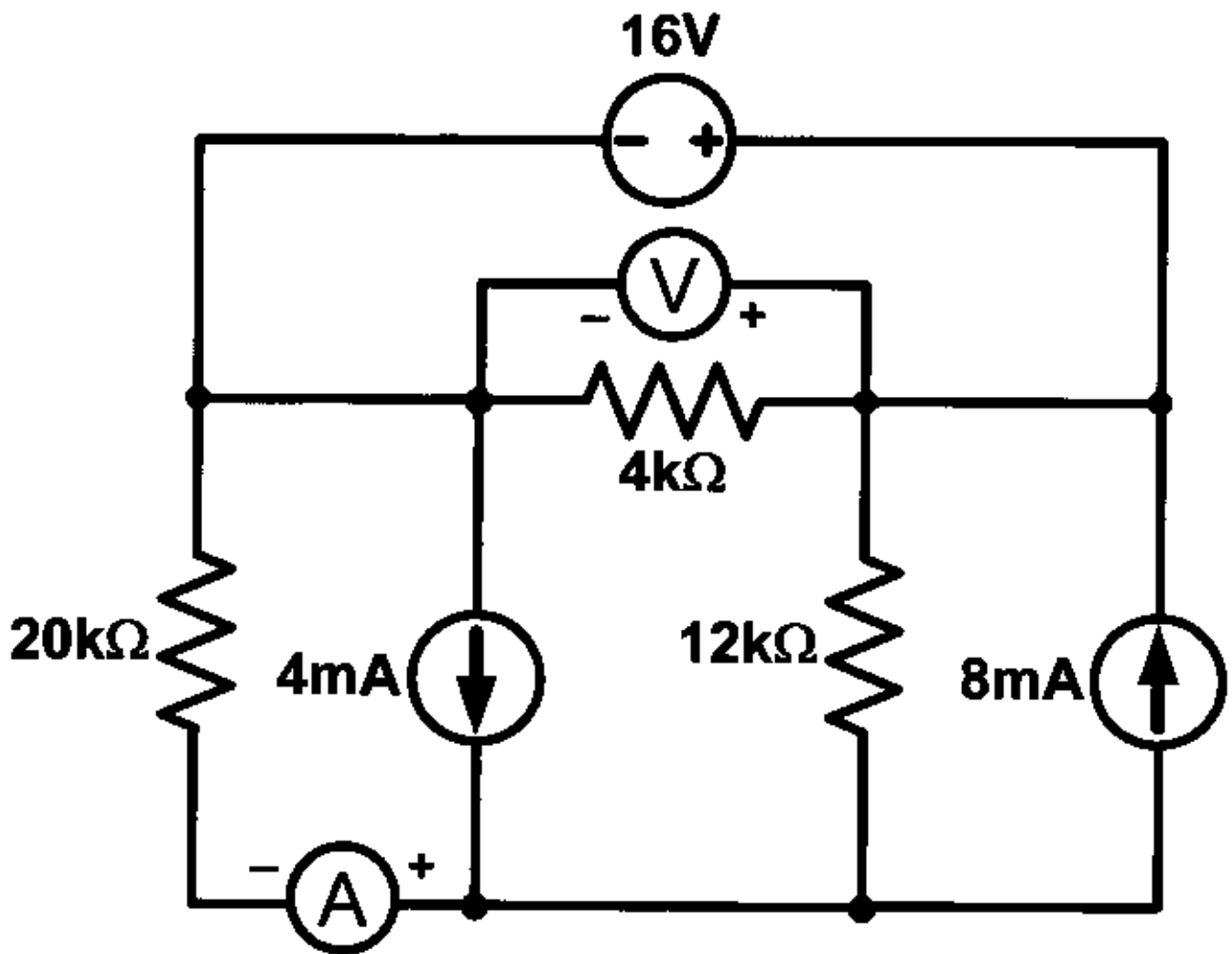


FIGURE Q7

FINAL EXAMINATION

SEMESTER/SESSION : 11/2008/09

COURSE : I BEE

SUBJECT'S NAME : ELECTRICAL CIRCUIT THEORY

SUBJECT'S CODE

: BEE 1113

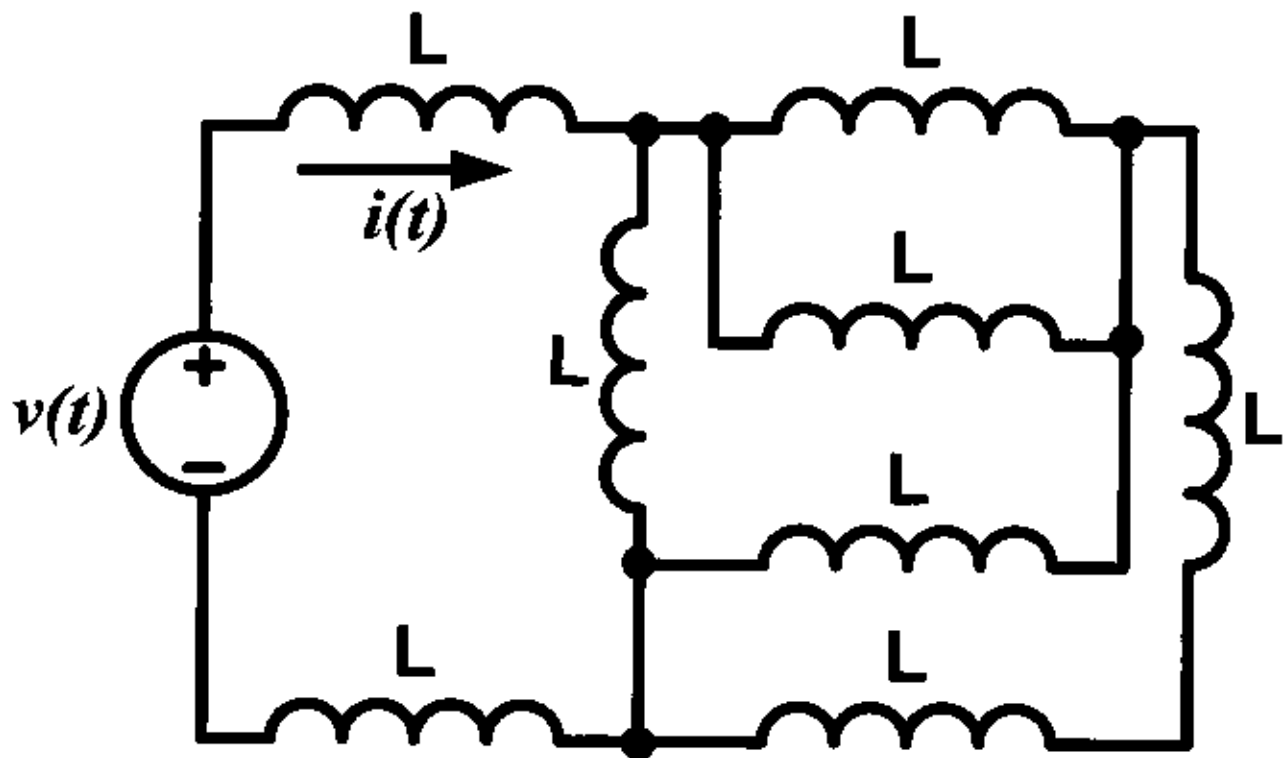


FIGURE Q8

FINAL EXAMINATION

SEMESTER/SESSION : II/2008/09

COURSE

: I BEE

SUBJECT'S NAME : ELECTRICAL CIRCUIT THEORY

SUBJECT'S CODE

: BEE 1113

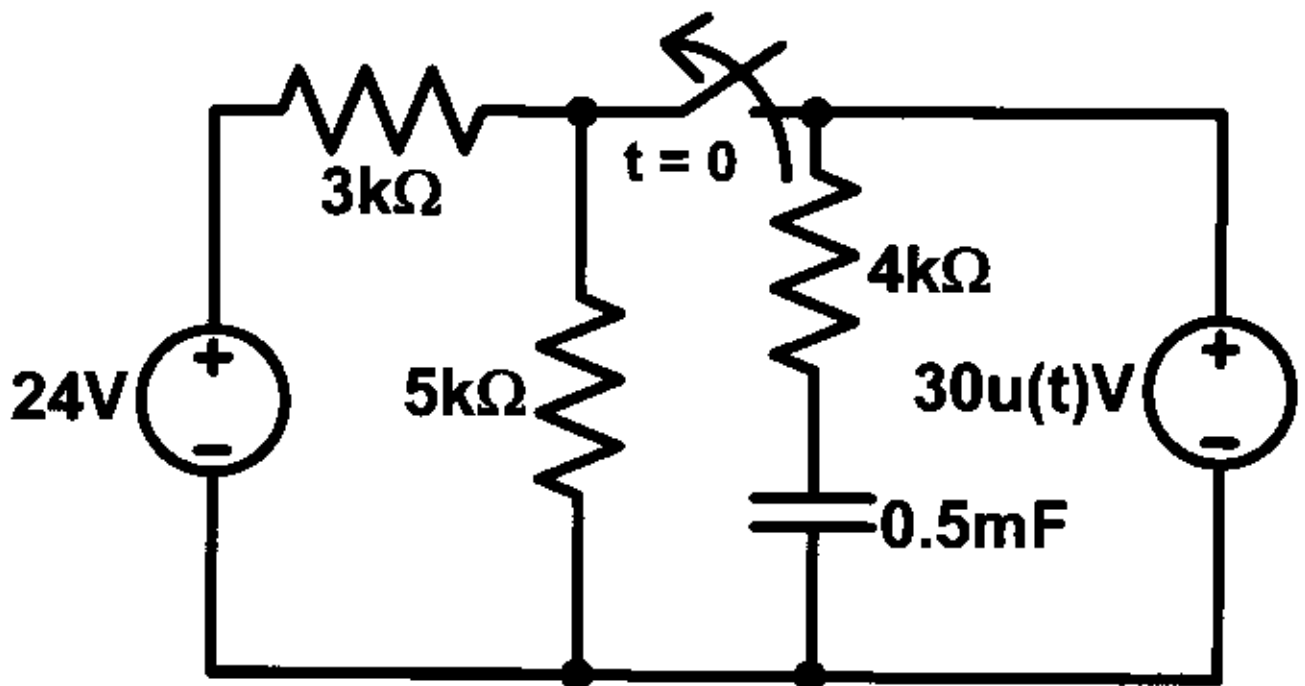


FIGURE Q9

FINAL EXAMINATION

SEMESTER/SESSION : II/2008/09

COURSE

: I BEE

SUBJECT'S NAME : ELECTRICAL CIRCUIT THEORY

SUBJECT'S CODE

: BEE 1113

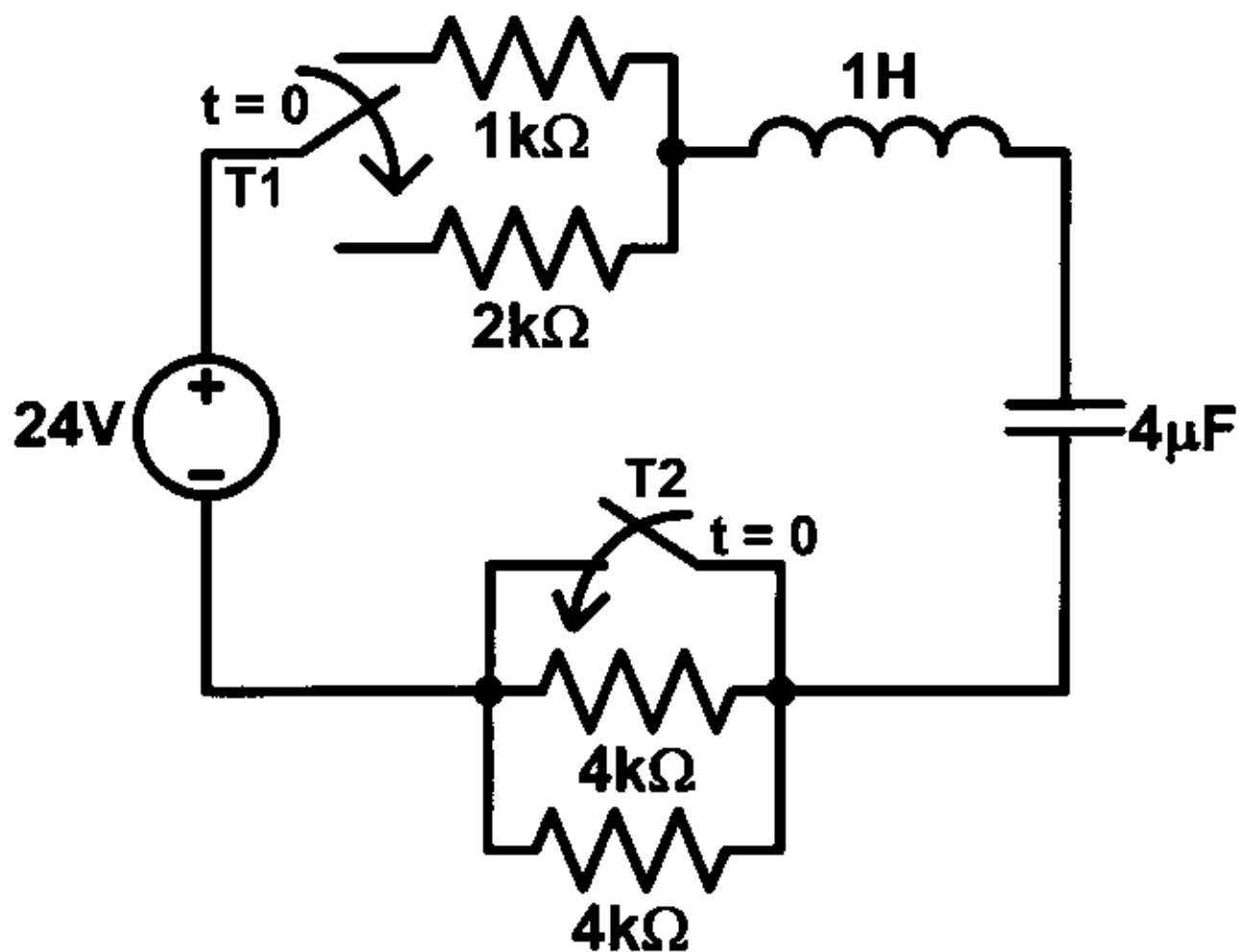


FIGURE Q10