



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

PEPERIKSAAN AKHIR SEMESTER II SESI 2008/2009

NAMA MATA PELAJARAN : SISTEM KUASA ELEKTRIK

KOD MATA PELAJARAN : DEK 3213

KURSUS : 3 DEE/DET/DEX

TARIKH PEPERIKSAAN : APRIL/MEI 2009

JANGKAMASA : 2 1/2 JAM

**ARAHAN : JAWAB EMPAT (4) SOALAN SAHAJA
DARIPADA ENAM (6) SOALAN**

KERTAS SOALAN INI MENGANDUNGI LAPAN (8) MUKA SURAT

- Q1 (a)** Briefly describe the load and Fault terms. (4 marks)
- (b)** Give the definition of one-line diagram and state the advantages of the one-line diagram. (7 marks)
- (c)** Briefly describe (use diagram to assist your explanation),
- (i) The Radial System
 - (ii) The Ring Main System
- (14 marks)
- Q2 (a)** A 3-phase transformer 10 KVA, 440 V has a reactance of 4Ω . Determine the per-unit reactance if the base value
- (i) 15 KVA and 415 V
 - (ii) 5 KVA and 600 V
- (4 marks)
- (b)** An interconnected system with its rated value is shown as in Figure Q2(b). Obtain the per-unit reactance and the base value for this system is chosen to be 11 kV and 50 MVA at the generator (G_2). Draw the equivalent impedance diagram (per-unit).
- Ratings:
- $G_1 - 40 \text{ MVA}, 13.8 \text{ kV}, X = 20\%$.
 - $G_2 - 50 \text{ MVA}, 11 \text{ kV}, X = 35\%$
 - $T_1 - 40 \text{ MVA}, 13.8 / 69 \text{ kV}, X = 8\%$
 - $T_2 - 50 \text{ MVA}, 69 / 11 \text{ kV}, X = 9\%$
 - $T_3 - 30 \text{ MVA}, 64 / 34.5 \text{ kV}, X = 7\%$
 - $X_{TA} = j8 \Omega$
 - $X_{TB} = j10 \Omega$
 - $X_{TC} = j6 \Omega$
- (21 marks)

Q3 A three-phase 50 Hz double circuit line is composed of ACSR Pelican conductors arranged as shown in Figure Q3. Calculate;

- (a) inductive reactance in Ω/km per phase.
- (b) capacitive reactance in $\Omega.\text{km}$ per phase to neutral.
($k = 8.85 \times 10^{-12} \text{F/m}$)

(25 marks)

Q4 (a) Most of the faults that occur on power systems are unsymmetrical faults. One of them is line to earth fault. Prove the equation below if fault occurs at line 'a' by using equation of symmetrical voltage and current.

$$I_{a1} = \frac{E_a}{Z_1 + Z_2 + Z_0}$$

(14 marks)

- (b) Calculate the three-phase fault current and the corresponding fault level in MVA by using a base of 100 MVA if fault occurs at point F in Figure Q4(b).

(11 marks)

Q5 (a) The protection schemes must have high sensitivity in its operation when a fault occurs under minimum fault conditions. Several consequences of fault have been identified and they can be summarized as follows: When a fault occurs under minimum fault conditions there are several consequences of fault that have been identified. Explain three of the consequences.

(9 marks)

- (b) In the system protection components there have their design criteria that have been considered such as Reliability, Selectivity, Speed, Economy and Simplicity. Explain all of the design criteria's.

(10 marks)

- (c) By referring to the Figure Q5(c). There are three major components which are commonly constituted in a power system protection scheme: circuit breaker, transducers and relays. Explain operation of the system when the fault occurs in the system.

(6 marks)

- Q6 (a) One circuit of a single-phase transmission line is composed of three solid 0.4 cm radius wires in side X . The return circuit is composed of two solid 0.6 cm radius wires in side Y . The arrangement of conductors is shown as Figure Q6(a). Calculate the inductance in H/m for;

- (i) side X
- (ii) side Y
- (iii) The complete line

(15 marks)

- (b) A three-phase fault occurs at point F in the system of Figure Q6(b). Calculate the fault MVA for the system. The reactances are all in percentage. Choose 50 MVA as a base value.

(10 marks)

PEPERIKSAAN AKHIR

SEMESTER/SESI : SEMESTER II/2008/09
 MATAPELAJARAN : SISTEM KUASA ELEKTRIK

KURSUS : 3 DEE/DET/DEX
 KOD MP : DEK 3213

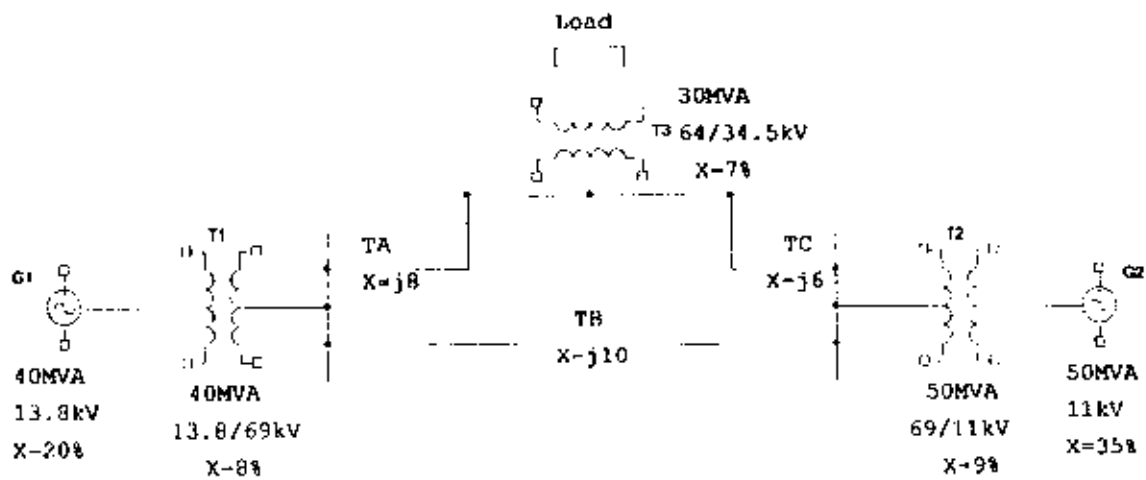


Figure Q2(b)

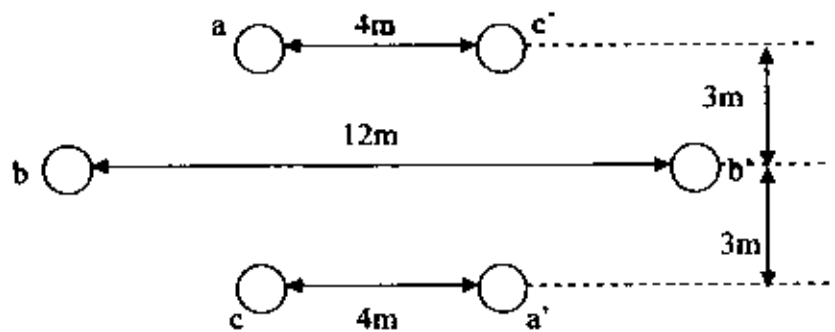


Figure Q3

PEPERIKSAAN AKHIR

SEMESTER/SESI : SEMESTER II/2008/09
 MATAPELAJARAN : SISTEM KUASA ELEKTRIK

KURSUS : 3 DEE/DET/DEX
 KOD MP : DEK 3213

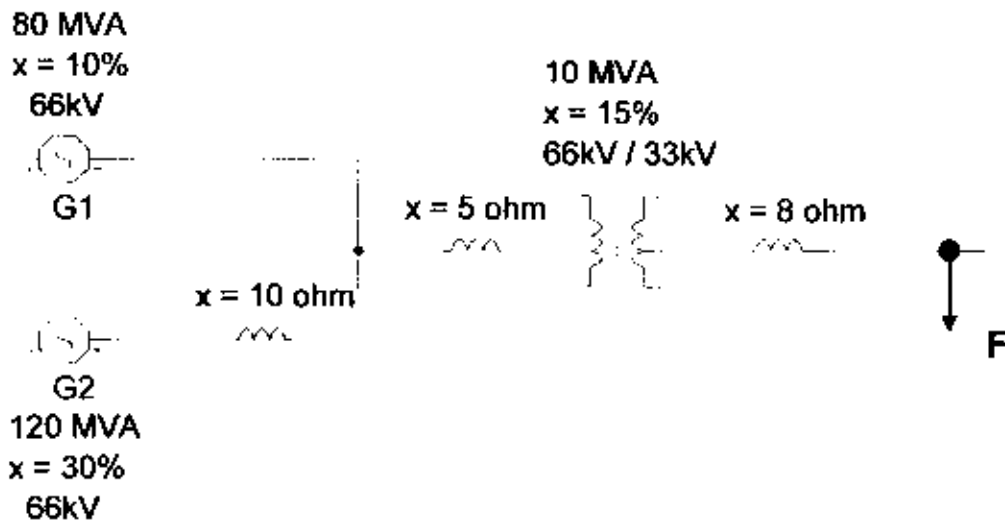


Figure Q4(b)

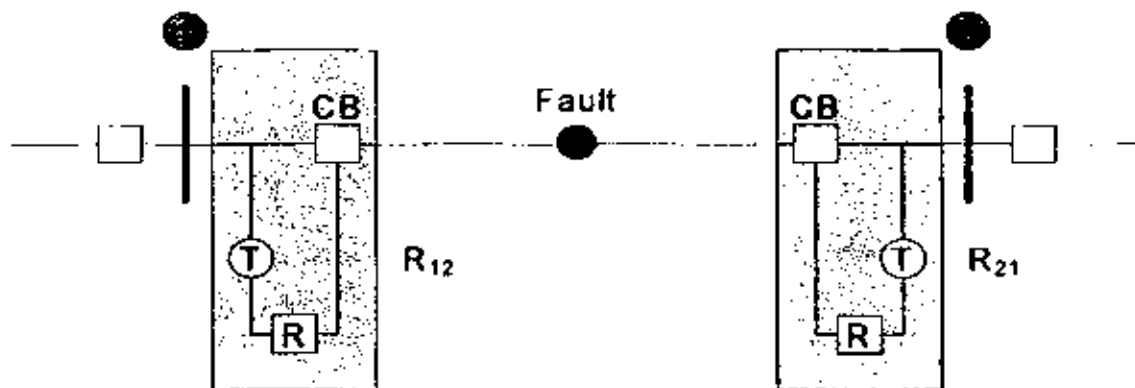


Figure Q5(c)

PEPERIKSAAN AKHIR

SEMESTER/SESI : SEMESTER II/2008/09
 MATAPELAJARAN : SISTEM KUASA ELEKTRIK

KURSUS : 3 DEE/DET/DEX
 KOD MP : DEK 3213

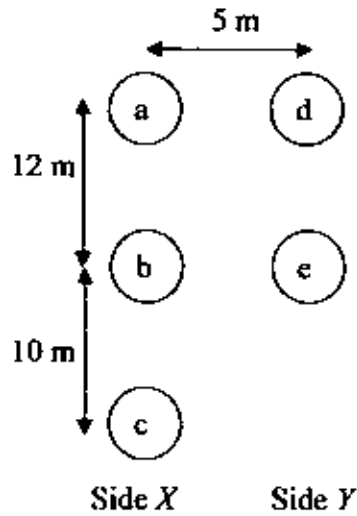


Figure Q6(a)

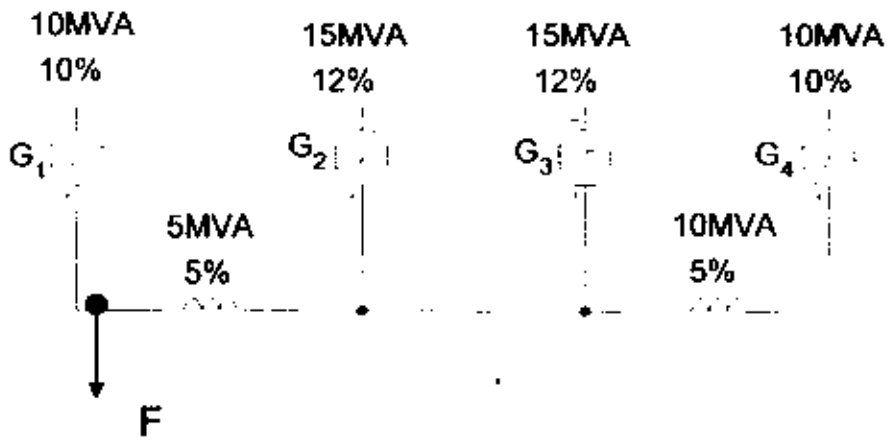


Figure Q6(b)

PEPERIKSAAN AKHIR

SEMESTER/SESI : SEMESTER II/2008/09
 MATAPELAJARAN : SISTEM KUASA ELEKTRIK

KURSUS : 3 DEE/DET/DEX
 KOD MP : DEK 3213

TABLE A3
Electrical characteristics of bare aluminum conductors steel-reinforced (ACSR)†

Code word	Aluminum area, mm ²	Stranding Al/Al	Layers of aluminum	Gross dia, mm, in	Resistance			GMR D _g , ft	Resistance per conductor 1-ft span @ 90 Hz	
					D _g , 20°C, Ω/1,000 ft	A _c , 60 Hz			Inductive X _L , Ω/ft	Capacitive X _C , MΩ/ft
						30°C, Ω/ft	90°C, Ω/ft			
Wardag	904,800	18/7	2	0.909	0.0646	0.6428	0.8431	0.0196	0.878	0.1090
Paruhay	595,800	26/7	2	0.643	0.0640	0.4455	0.8795	0.0217	0.490	0.1074
Gairah	520,000	26/7	2	0.680	0.0655	0.5070	0.8972	0.0226	0.438	0.1067
Meriah	335,400	18/1	2	0.464	0.0612	0.3707	0.8057	0.0215	0.489	0.1065
Lihat	330,400	26/7	2	0.721	0.0607	0.3787	0.8006	0.0215	0.441	0.1043
Orhah	330,400	26/7	2	0.741	0.0604	0.3719	0.8287	0.0216	0.445	0.1029
Chaladad	307,300	18/1	2	0.728	0.0483	0.2845	0.8272	0.0214	0.489	0.1081
Tua	307,300	26/7	2	0.752	0.0480	0.2822	0.8241	0.0214	0.441	0.1016
Pekona	277,000	18/1	2	0.814	0.0281	0.1957	0.8148	0.0264	0.441	0.1005
Pikler	477,000	24/7	2	0.846	0.0286	0.1942	0.8124	0.0264	0.432	0.0992
Hawk	417,000	26/7	2	0.857	0.0287	0.1931	0.8120	0.0265	0.430	0.0988
Hia	477,000	26/7	2	0.893	0.0285	0.1919	0.8107	0.0264	0.431	0.0980
Opay	450,500	18/1	2	0.879	0.0290	0.1978	0.8144	0.0264	0.433	0.0981
Paruhak	450,500	26/7	2	0.914	0.0298	0.1948	0.8282	0.0264	0.423	0.0959
Dora	450,500	26/7	2	0.927	0.0297	0.1943	0.8280	0.0264	0.430	0.0966
Rosok	486,000	24/7	2	0.970	0.0295	0.1905	0.8209	0.0267	0.419	0.0980
Greenback	696,000	36/7	2	0.900	0.0288	0.1924	0.8156	0.0275	0.412	0.0946
Drinks	795,000	26/7	2	1.108	0.0216	0.1178	0.7281	0.0275	0.399	0.0935
Tern	795,000	26/7	2	1.043	0.0217	0.1169	0.7289	0.0276	0.406	0.0926
Hah	654,000	24/7	2	1.166	0.0181	0.0997	0.6882	0.0272	0.395	0.0977
Oradual	924,000	48/7	2	1.166	0.0181	0.0997	0.6882	0.0272	0.390	0.0970
Bludak	1,083,800	48/7	2	1.312	0.0187	0.0924	0.7021	0.0262	0.390	0.0885
Bludak	1,113,000	48/7	2	1.369	0.0186	0.0911	0.7081	0.0261	0.385	0.0874
Biluh	1,113,000	54/7	2	1.399	0.0185	0.0902	0.7082	0.0261	0.379	0.0867
Biluh	1,173,000	54/7	2	1.416	0.0185	0.0889	0.7082	0.0261	0.372	0.0847
Biluh	1,279,000	54/7	2	1.482	0.0183	0.0791	0.6751	0.0260	0.371	0.0827
Biluh	1,379,000	54/7	2	1.537	0.0181	0.0745	0.6745	0.0260	0.368	0.0825
Pesant	1,481,000	48/7	2	1.466	0.0180	0.0673	0.6973	0.0246	0.364	0.0823
Badokak	1,481,000	54/7	2	1.502	0.0180	0.0673	0.6973	0.0246	0.364	0.0814
Flora	1,600,000	48/7	2	1.545	0.0180	0.0673	0.6973	0.0246	0.364	0.0811
Lapang	1,600,000	54/7	2	1.545	0.0180	0.0673	0.6973	0.0246	0.364	0.0811
Falosa	1,600,000	54/7	2	1.545	0.0180	0.0673	0.6973	0.0246	0.364	0.0811
Dubud	2,155,000	84/18	4	1.792	0.0080	0.0276	0.6918	0.0260	0.344	0.0778

Table Q3