



## **UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

### **PEPERIKSAAN AKHIR SEMESTER II SESI 2008/2009**

**NAMA MATA PELAJARAN : ASAS ELEKTRIK DAN ELEKTRONIK**

**KOD MATA PELAJARAN : DKE 3273**

**KURSUS : 3 DDM, DDT, DDX**

**TARIKH PEPERIKSAAN : APRIL 2009**

**JANGKA MASA : 2½ JAM**

**ARAHAN : JAWAB EMPAT (4) SOALAN SAHAJA DARIPADA ENAM (6) SOALAN**

- Q1** (a) Define Ohm's law. (2 marks)
- (b) Three lamps have the following rated values: 60 W 240 V, 100 W 200 V, and 40 W 100 V. Calculate the power dissipated by each if they are connected in series across a 240 V supply. (23 marks)
- Q2** (a) From the circuit of Figure Q2(a), calculate:-  
(i) total resistance ( $R_T$ ), total current ( $I_T$ ), and total power ( $P_T$ ). (10 marks)  
(ii) voltage drop at resistors  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$ . (8 marks)  
(iii) currents,  $I_1$  and  $I_2$ . (4 marks)
- (b) Give TWO (2) comparisons between parallel circuits and series circuits. (3 marks)
- Q3** (a) Define magnetomotive force (MMF). (3 marks)
- (c) An iron ring of mean length 60 cm has an air gap of 2 mm and a winding of 300 turns. If the relative permeability of iron used in the ring is 400 when a current of 1.5A flows through it, find the flux density.  
( $\mu_0 = 4\pi \times 10^{-7}$ ) (12 marks)
- (d) State FIVE (5) points of similarities between magnetic circuits and electric circuits. (10 marks)

- Q4** (a) From the circuit shown in Figure Q4(a), solve for the following:-
- (i)  $Z_T$ . (3 marks)
  - (ii)  $I_T$ ,  $I_R$ ,  $I_C$ , and  $I_L$ . (5 marks)
  - (iii)  $V_R$ ,  $V_C$ , and  $V_L$ . (9 marks)
  - (iv)  $\theta_Z$ . (3 marks)
  - (v) phasor diagram for equivalent circuit. (3 marks)
- (b) State the purpose of phasor diagram. (2 marks)
- Q5** (a) List **FIVE (5)** types of the transformer. (5 marks)
- (b) An ideal transformer has a primary coil current of 32 A and an applied voltage of 240 V. The secondary coil current is 2 A. Calculate:-
- (i) power input of primary coil,  $P_P$ . (3 marks)
  - (ii) power output of secondary coil,  $P_S$ . (3 marks)
  - (iii) secondary coil voltage,  $V_S$ . (3 marks)
  - (iv) turns ratio. (3 marks)
- (c) State the type of the transformer used in Q5(b). Briefly explain your answer. (3 marks)
- (d) Give **THREE (3)** comparisons between step-up and step-down transformers. (5 marks )

- Q6** (a) Draw simple circuit diagrams to show how a transistor can be connected in:-  
(i) common base configuration. (2 marks)  
(ii) common emitter configuration. (2 marks)  
(iii) common collector configuration. (2 marks)

(b) With the aid of suitable diagram, briefly explain the principle of a rectifier circuit used to produce half-wave rectification. (7 marks)

(c) Explain the action of the SCR (thyristor) in terms of the two transistor model. (8 marks)

(d) State **TWO (2)** functions for each of the following components in electronic circuits.  
(i) diode  
(ii) transistor (4 marks)

**PEPERIKSAAN AKHIR**


SEMESTER/SESI : II / 2008/09

KURSUS

: 3 DDM/T/X

MATA PELAJARAN : ASAS ELEKTRIK  
DAN ELEKTRONIK

KOD MATA PELAJARAN : DKE 3273

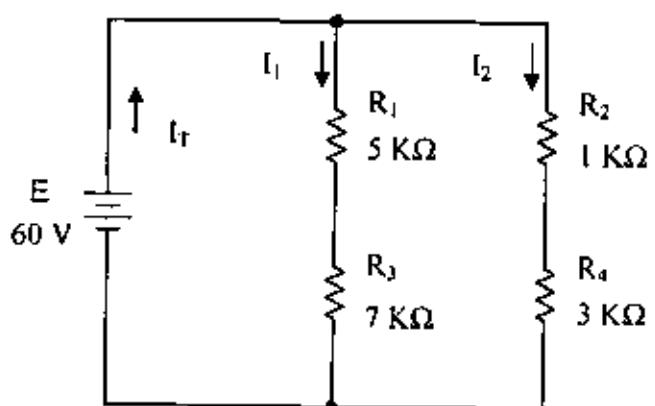

**FIGURE Q2(a)**

PEPERIKSAAN AKHIR

SEMESTER/SESI : II / 2008/09

KURSUS

: 3 DDM/T/X

MATA PELAJARAN

: ASAS ELEKTRIK  
DAN ELEKTRONIK

KOD MATA PELAJARAN

: DKE 3273

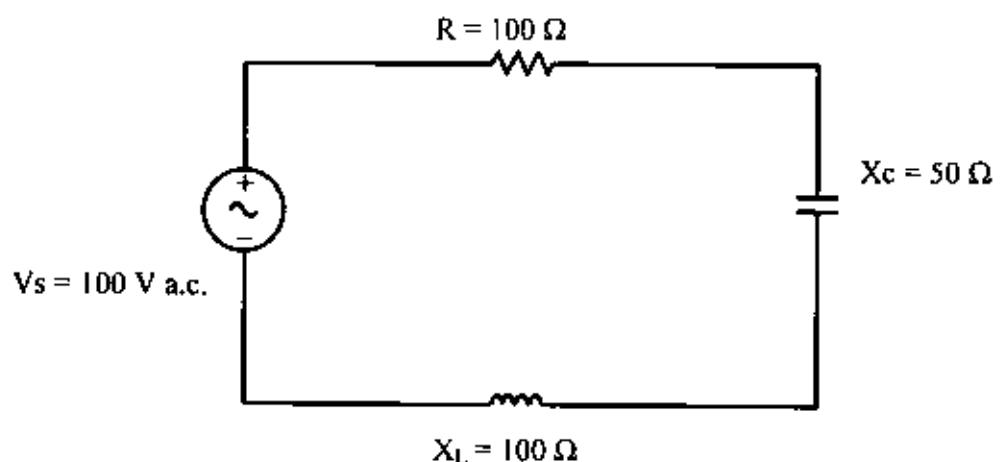


FIGURE Q4 (a)