



# UNIVERSITI TUN HUSSEIN ONN MALAYSIA

## FINAL EXAMINATION SEMESTER II SESSION 2009/2010

COURSE NAME : LOGIC SYSTEM  
COURSE CODE : DEE 2233  
PROGRAMME : 2 DET / DEE / DEX  
EXAMINATION DATE : APRIL/MAY 2010  
DURATION : 3 HOURS  
INSTRUCTION : **PART A : ANSWER ALL QUESTIONS**  
**PART B : ANSWER THREE (3)**  
QUESTION ONLY

THIS PAPER CONSISTS OF SIXTEEN (16) PAGES

**PART A**

- Q1** (a) Draw an active LOW input R-S latch logic diagram and build its truth table. (3 marks)
- (b) Modify the logic diagram that you have drawn in part Q1(a) if a signal ENABLE is applied. (2 marks)
- (c) Sketch the Q output waveform for the logic diagram at in part Q1(b), when the input waveforms EN, S and R as shown in Figure Q1(c) are applied. (3 marks)
- Q2** (a) Draw the logic symbol for a negative edge-triggered S-R flip-flop and J-K flip-flop. (2 marks)
- (b) What is the difference between a latch and a flip-flop? Give **ONE (1)** reason by sketching using logic symbol. (2 marks)
- (c) Show how a Positive Edge Triggered D Flip-Flop can be implemented using an S-R flip-flop and inverter. (2 marks)
- (d) The input waveforms in Figure Q2(d) are applied to CLK, D, PRE and CLR as indicated. Determine and draw the output waveform. (2 marks)
- Q3** (a) Draw a logic diagram for three-bit asynchronous binary counter using positive edge-triggered J-K flip-flop and sketch the complete timing diagram using CLK input in Figure Q3(a). (3 marks)
- (b) Determine the maximum clock frequency at which the counter can be operated for a 3-bit asynchronous binary counter if each negative edge-triggered flip-flop has a propagation delay for 15 ns. (2 marks)
- (c) Draw a logic diagram for three-bit synchronous binary counter using negative edge-triggered flip-flop and sketch the complete timing diagram using CLK input in Figure Q3(c). (3 marks)

- Q4**
- (a) Show how a NOR gate can be implemented by using only **FOUR (4)** NAND gates. (2.5 marks)
  - (b) Show how an AND gate can be implemented by using only **THREE (3)** NOR gates. (2.5 marks)
  - (c) Sketch the output waveform, X for the circuit shown in Figure **Q4(c)**, by referring to the given input waveforms A, B and C and output waveform Y. (3 marks)
- Q5**
- (a) State **FOUR (4)** possible mode of register operation and draw **TWO (2)** logic diagram from the possible mode of register operation. (4 marks)
  - (b) Determine the state of the shift register of Figure **Q5(b)** after each clock pulse for the given RIGHT/LEFT' control input waveform in Figure **Q5(b)**. Assume  $Q_0 = 1$ ,  $Q_1 = 1$ ,  $Q_2 = 0$ ,  $Q_3 = 1$  and that the serial data-input line is LOW. (4 marks)

**PART B** (Show all your steps)


- Q6** (a) Using the IC 555 Timer and RC component, draw the complete schematic diagram for Monostable (One-Shot) operation and Astable operation. (6 marks)
- (b) Determine **TIME WIDTH** ( $t_w$ ) for monostable (One-Shot) if given **ENERGY** ( $E$ ) = 9V, **RESISTANCE** ( $R$ ) = 9k $\Omega$  and **CAPACITOR** ( $C$ ) = 1nF (3 marks)
- (c) Determine **CAPACITOR EXTERNAL** ( $C_{ext}$ ) for monostable (One-Shot) if given **ENERGY** ( $E$ ) = 12V, **TIME WIDTH** ( $t_w$ ) = 0.1s and **RESISTANCE** ( $R$ ) = 39k $\Omega$  (3 marks)
- (d) For the astable multivibrator, if  $R_1=1\text{ M}\Omega$ ,  $R_2=470\text{ k}\Omega$  and  $C_1=0.001\text{ }\mu\text{F}$ , determine the frequency output, **TIME HIGH** ( $t_{HI}$ ), **TIME LOW** ( $t_{LO}$ ) and duty cycle. (8 marks)
- Q7** (a) Convert each of the BCD code 0000, 0010, 0100, 0110, 0111 to Gray Code. (3 marks)
- (b) Design a J-K synchronous 3-bit up/down counter with a Gray code sequence from part Q7 (a). The counter should count up when an  $\overline{\text{UP/DOWN}}$  control input is 1 and count down when the control input is 0. (17marks)
- Q8** (a) Determine the output  $Q_0, Q_1, Q_2$  and  $Q_3$  of 74HC194 IC a 4-bit bidirectional universal shift register if given the data input waveforms as shown in Figure Q8 (a). (14 marks)
- (b) If a 10-bit ring counter in Figure Q8 (b) has the initial state 0101001111, determine the waveform for each of the Q outputs. (6marks)

- Q9** (a) Determine the Boolean expression of X for the circuit in Figure **Q9** (a). (4 marks)
- (b) Convert the Boolean expression from part **Q9** (a) into a standard SOP expression. (show all your steps) (6 marks)
- (c) Use Karnaugh map to determine the minimum SOP expression for X. (show all your steps) (10 marks)
- 
- Q10** (a) By referring to the logic schematic J-K flip-flop in Figure **Q10** (a), determine the output  $\bar{Q}$  if the input waveforms CLK, J, K, Clear and Preset Q is initially 1. (10 marks)
- (b) Determine the waveforms at Q,  $\bar{Q}$  (Q'), CP and  $\bar{CP}$  (CP') in Figure **Q10** (b) for a non-overlapping clock. (10 marks)

**FINAL EXAMINATION**

SEMESTER / SESSION : SEMESTER II / 2009/2010  
COURSE NAME : LOGIC SYSTEM

PROGRAMME : 2 DET / DEE / DEX  
COURSE CODE : DEE2223

 

**Figure Q1(d)**

**FINAL EXAMINATION**

SEMESTER / SESSION : SEMESTER II / 2009/2010  
 COURSE NAME : LOGIC SYSTEM

PROGRAMME : 2 DET / DEE / DEX  
 COURSE CODE : DEE2223

 


Figure Q2(d)

**FINAL EXAMINATION**

SEMESTER / SESSION : SEMESTER II / 2009/2010  
COURSE NAME : LOGIC SYSTEM

PROGRAMME : 2 DET / DEE / DEX  
COURSE CODE : DEE2223

 


Figure Q3 (a)

**FINAL EXAMINATION**

SEMESTER / SESSION : SEMESTER II / 2009/2010  
 COURSE NAME : LOGIC SYSTEM

PROGRAMME : 2 DET / DEE / DEX  
 COURSE CODE : DEE2223

 


Figure Q3 (c)

**FINAL EXAMINATION**

SEMESTER / SESSION : SEMESTER II / 2009/2010  
 COURSE NAME : LOGIC SYSTEM

PROGRAMME : 2 DET / DEE / DEX  
 COURSE CODE : DEE2223

 


Figure Q4 (c)

**FINAL EXAMINATION**

SEMESTER / SESSION : SEMESTER II / 2009/2010  
 COURSE NAME : LOGIC SYSTEM

PROGRAMME : 2 DET / DEE / DEX  
 COURSE CODE : DEE2223

 
 


Figure Q5 (b)

**FINAL EXAMINATION**

SEMESTER / SESSION : SEMESTER II / 2009/2010  
 COURSE NAME : LOGIC SYSTEM

PROGRAMME : 2 DET / DEE / DEX  
 COURSE CODE : DEE2223

 


Figure Q8(a)

**FINAL EXAMINATION**

SEMESTER / SESSION : SEMESTER II / 2009/2010  
 COURSE NAME : LOGIC SYSTEM

PROGRAMME : 2 DET / DEE / DEX  
 COURSE CODE : DEE2223

 


Figure Q8(b)

**FINAL EXAMINATION**

SEMESTER / SESSION : SEMESTER II / 2009/2010  
COURSE NAME : LOGIC SYSTEM

PROGRAMME : 2 DET / DEE / DEX  
COURSE CODE : DEE2223

 


Figure Q9 (a)

**FINAL EXAMINATION**

SEMESTER / SESSION : SEMESTER II / 2009/2010  
 COURSE NAME : LOGIC SYSTEM

PROGRAMME : 2 DET / DEE / DEX  
 COURSE CODE : DEE2223

 
 


Figure Q10(a)

**FINAL EXAMINATION**

SEMESTER / SESSION : SEMESTER II / 2009/2010  
 COURSE NAME : LOGIC SYSTEM

PROGRAMME : 2 DET / DEE / DEX  
 COURSE CODE : DEE2223

 
 


Figure Q10 (b)