



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESSION 2010/2011**

**COURSE NAME** : ELECTRICAL AND  
ELECTRONIC TECHNOLOGY

**COURSE CODE** : BEX 17003 / BEE 1803

**PROGRAMME** : 1 Bachelor of Mech. Eng. (Hons)

**EXAMINATION DATE** : APRIL/MAY 2011

**DURATION** : 2 1/2 HOURS

**INSTRUCTIONS** : **ANSWER FOUR (4)**  
QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF EIGHT (8) PAGES

- Q1**
- (a) With the aid of diagrams, explain  
 (i) Kirchhoff's current law  
 (ii) Kirchhoff's voltage law  
 (6 marks)
- (b) Find the current,  $I$  and voltage,  $V_{ab}$  in the circuit of **Figure Q1(b)**.  
 (7 marks)
- (c) Use the nodal or mesh analysis to find the voltages across the  $40\Omega$ ,  $10\Omega$  and  $20\Omega$  resistors for the circuit in **Figure Q1(c)**.  
 (12 marks)
- Q2**
- (a) Describe the steps to apply superposition principle to circuits that have more than one source.  
 (5 marks)
- (b) For the circuit in **Figure Q2(b)**, find the current  $I$ , using the superposition principle.  
 (7 marks)
- (c) For the circuit in **Figure Q2(c)**:
- (i) find the Thevenin's equivalent circuit with respect to the terminals a,b  
 (8 marks)
- (ii) use source transformation to obtain the Norton's equivalent circuit  
 (3 marks)
- (iii) find the value of the load resistor to be connected to terminals a,b so that maximum power can be transferred to it  
 (2 marks)
- Q3**
- (a) Write a brief description of the following: capacitor, inductor and mutual inductance.  
 (6 marks)
- (b) Find the equivalent capacitance for the circuit in **Figure Q3(b)**. Calculate the voltage across, the charge, and energy stored in each of those capacitors.  
 (14 marks)

- (c) Find the voltage across terminal a-b of the circuit in **Figure Q3(c)** if the current  $i(t) = 0.5 \cos 314t$  A.

(5 marks)

- Q4** (a) For the circuit in **Figure Q4(a)**, find:

- (i) the total circuit impedance
- (ii) the current  $i(t)$
- (iii) the voltage across the capacitor,  $V_c(t)$

(9 marks)

- (b) For the circuit in **Figure Q4(b)**,  $V_s(t) = 450\cos(314t)$  and  $Z_L = (7 + j1) \Omega$ :

- (i) calculate the complex power and draw the power triangle
- (ii) find the required parallel capacitor needed to improve the power factor to unity

(11 marks)

- (c) Explain why large companies need to correct their power factor. Explain the technique used to improve the power factor of a given load.

(5 marks)

- Q5** (a) Sketch the typical voltage/current characteristics for a rectifier diode and a zener diode.

(4 marks)

- (b) Briefly explain how EACH of the diodes in part Q5(a) operates under forward and reverse bias conditions.

(4 marks)

- (c) Sketch the circuit of a full-wave bridge rectifier with transformer input and a reservoir capacitor. Briefly explain how this circuit achieves full rectification.

(7 marks)

- (d) Draw the truth table for EACH of the following types of 2-input logic gate.


- (i) OR
- (ii) NOR
- (iii) AND

(6 marks)


- (e) For the logic circuit shown in **Figure Q5(e)** state the possible inputs to give an output of logic 1 from the circuit  
(4 marks)
- Q6**
- (a) With the aid of diagrams, explain how the speed of DC series and shunt wound motors may be controlled.  
(6 marks)
- (b) A 300V DC series motor runs at 15 revs/sec and takes an armature current of 30A. If the armature resistance is  $0.5 \Omega$ , calculate the torque developed by the motor.  
(4 marks)
- (c) Describe with sketches two different ways of starting a single-phase induction motor.  
(6 marks)
- (d) A 5 kW, 240V, 50Hz induction motor has a running power factor of 0.7 lagging and an efficiency of 80%. Calculate the current drawn by the motor.  
(4 marks)
- (e) List three advantages of fluorescent lighting units as compared to incandescent lamps.  
(3 marks)
- (f) A fluorescent tube fixture takes 1A when connected to a 120V source. A wattmeter in the circuit reads 80 watts. What is the operating power factor of this unit.  
(2 marks)

**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2010/2011      PROGRAMME : 1 BDD  
COURSE : ELECTRICAL AND ELECTRONIC TECHNOLOGY  
COURSE CODE: BEX17003 / BEE1803

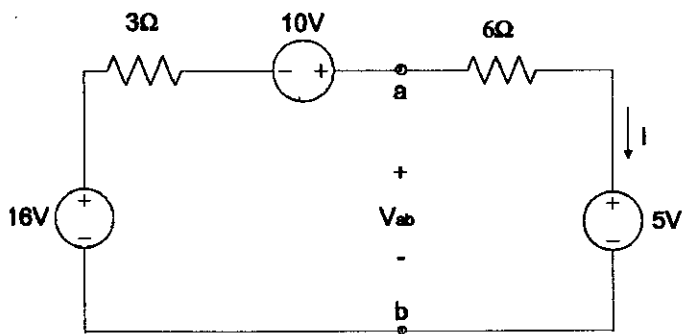


**FIGURE Q1(b)**

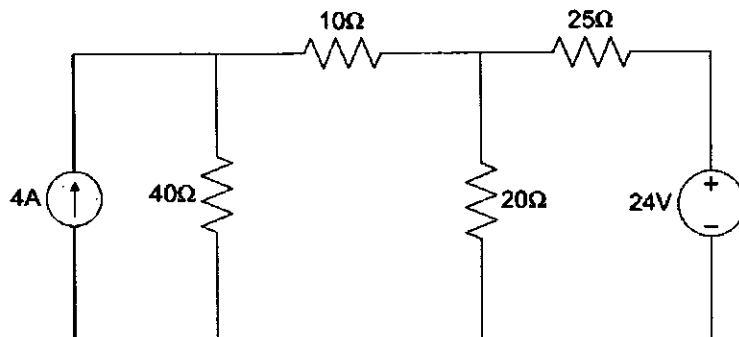


**FIGURE Q1(c)**

**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2010/2011      PROGRAMME : 1 BDD  
COURSE : ELECTRICAL AND ELECTRONIC TECHNOLOGY  
COURSE CODE: BEX17003 / BEE1803

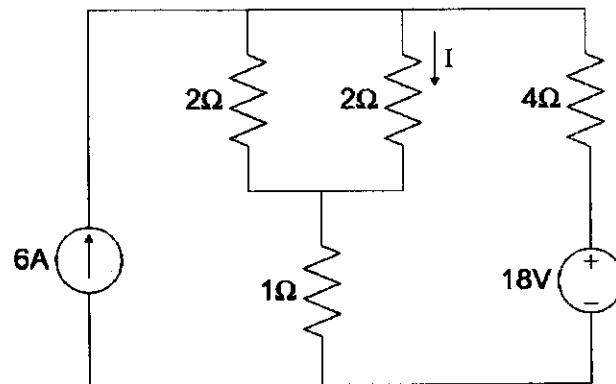


**FIGURE Q2(b)**

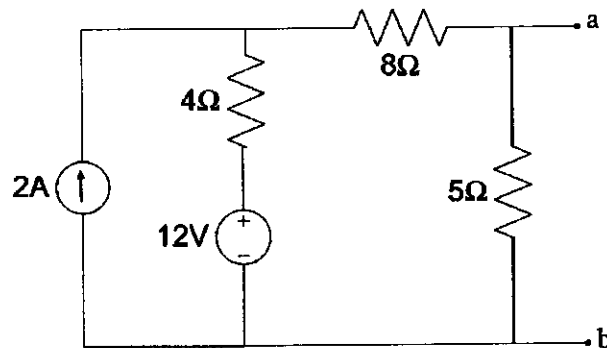


**FIGURE Q2(c)**

**FINAL EXAMINATION**


SEMESTER / SESSION : SEM II / 2010/2011      PROGRAMME : 1 BDD  
 COURSE : ELECTRICAL AND ELECTRONIC TECHNOLOGY  
 COURSE CODE: BEX17003 / BEE1803

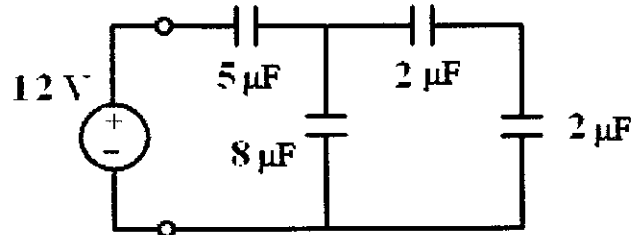

**FIGURE Q3(b)**

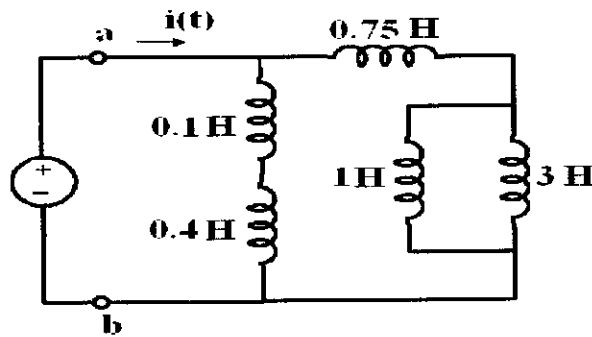


**FIGURE Q3(c)**

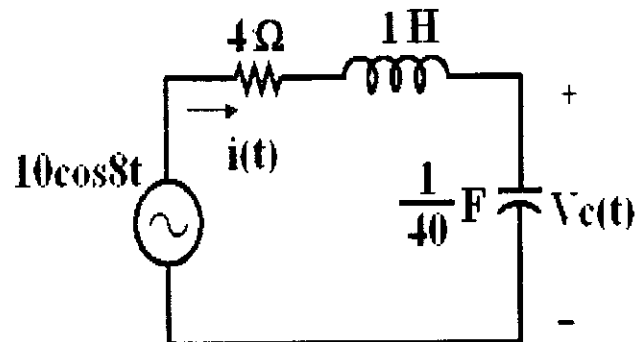


**FIGURE Q4(a)**

**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2010/2011      PROGRAMME : 1 BDD  
COURSE : ELECTRICAL AND ELECTRONIC TECHNOLOGY  
COURSE CODE: BEX17003 / BEE1803

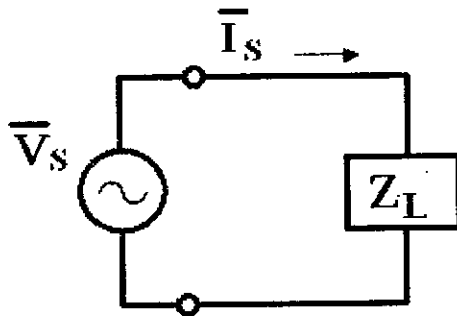

**FIGURE Q4(b)**

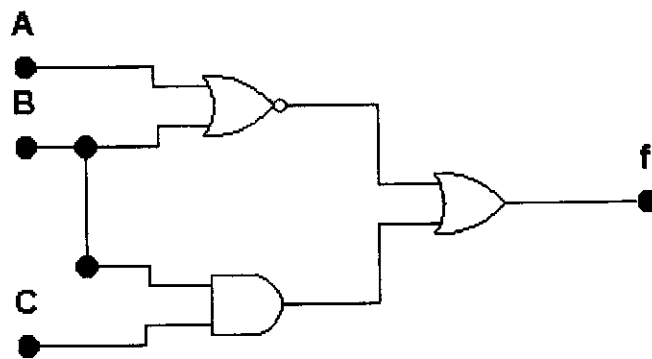

**FIGURE Q5(e)**