

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2010/2011**

COURSE	: ELECTRICAL TECHNOLOGY
COURSE CODE	: BEE 1123/10403
PROGRAMME	: 1 BEE
EXAMINATION DATE	: APRIL/MAY 2011
DURATION	: 2 HOURS 30 MINUTES
INSTRUCTION	: ANSWER ALL QUESTIONS

THIS PAPER CONSIST OF NINE (9) PAGES

CONFIDENTIAL

- Q1** (a) (i) Briefly define peak-to-peak, V_{pp} , peak, V_p , and root mean square value, V_{rms} , of a sine wave voltage. (3 marks)
- (ii) Illustrate the sine wave value in Q1 (a) (i) in a sine wave diagram and express the equation that shows the relationship between the root mean square, V_{rms} , and peak-to-peak voltage values, V_{pp} , with the peak voltage values, V_p . (4 marks)
- (b) Consider the sine wave voltages shown in Figure Q1(b). The frequency of each signal is $f = 50$ Hz.
- (i) State the time domain expression for each voltage in the form of $V_m \cos(\omega t + \phi)$. (4 marks)
- (ii) Determine the instantaneous value of each voltage in Figure Q1(b) if the phase angle, θ equal to 45° (3 marks)
- (iii) Sketch the phasor diagrams for all the sine wave voltage in Figure Q1(b). (4 marks)
- (iv) Determine the phase relationship between V_1 and V_2 and between V_1 and V_3 (2 marks)
- (c) Solve the following complex number and leaves the result in polar form.
- (i) $\frac{15\angle 45^\circ}{-3-j4} + j2$
- (ii) $\frac{8\angle -20^\circ}{(2+j)(3-j4)} + \frac{10}{-5+j12}$ (5 marks)
- Q2** (a) Explain briefly what is Lenz's law. (1 mark)

- (b) Figure Q2(b) shows the variation of X_L and X_C for a series RCL circuits with frequency, f . Based on the graph, explain how the circuit behaves at:
- (i) High frequency
 - (ii) Low frequency
- (4 marks)
- (c) Figure Q2(c) is a series circuit with the input voltage, $v_s(t) = 240 \cos(314t + 30^\circ)$ V, $R = 100 \Omega$, $L = 0.3$ H and $C = 40 \mu\text{F}$. Assume the frequency is 50 Hz. Determine:
- (i) the total equivalent impedance of the circuit, Z_{eq} in polar form. (3 marks)
 - (ii) the steady-state current of the circuit, $i_I(t)$. (3 marks)
 - (iii) the phasor voltage across each element. (3 marks)
 - (iv) Construct a phasor diagram showing all the current and the voltages in the circuit. (2 marks)
- (d) Let say R, L and C in Figure Q2(c) is connected in parallel to each other. Assume the frequency is 50 Hz. Determine:
- (i) the total equivalent impedance of the circuit, Z_{eq} in polar form. (2 marks)
 - (ii) the steady-state current of the circuit, $i_I(t)$. (2 marks)
 - (iii) the phasor current across each element (3 marks)
 - (iv) Construct a phasor diagram showing all the current and the voltages in the circuit. (2 marks)

Q3 (a) Define the following terms:

- (i) Average power
- (ii) Apparent power
- (iii) Complex power
- (iv) Reactive power
- (v) Power factor

(5 marks)

(b) Consider the circuit shown in Figure Q3(b). Determine I by using:

- (i) Nodal analysis

(6 marks)

- (ii) Mesh analysis

(8 marks)

(c) In the circuit of Figure Q3(c), if $V_{ab} = 440\angle 10^\circ V$, $V_{bc} = 440\angle 250^\circ V$, $V_{ca} = 440\angle 130^\circ V$, find:

- (i) The line currents, I_a , I_b and I_c .
- (ii) The phase voltage at the load side.

(6 marks)

Q4 (a) The model of a real transformer is constructed by considering all the losses that occurs in a transformer.

- (i) Explain briefly the losses that occur in a transformer.

(4 marks)

- (ii) Draw and label the equivalent circuit of a real transformer.

(2 marks)

(b) A 15 kVA 2200/110 V transformer has the following parameters:

$$\begin{array}{llll} R_p & = 1.75 \Omega & X_p & = 2.6 \Omega & R_c & = 10000 \Omega \\ R_s & = 0.0045 \Omega & X_s & = 0.0075 \Omega & X_m & = 1550 \Omega \end{array}$$

By using equivalent circuit referred to the primary, calculate:

- (i) the primary voltage of the transformer at rated load with 0.8 lagging power factor.
 - (ii) the efficiency and voltage regulation of the transformer. (9 marks)
- (c) A 220 V shunt DC motor has an armature resistance of 0.15Ω and a field resistance of 70Ω . The motor draw a 7 A of line current while running light (no load) at 1150 rpm. The line current at full load is 46 A.
- (i) Determine the motor speed at full load condition.
 - (ii) At full load condition, if the field circuit resistance is increase to 100Ω , calculate the new speed of this DC shunt motor. Assume that the line current remain the same.

(10 marks)

FINAL EXAMINATION

SEMESTER/SESSION	: SEM II/2010/11	PROGRAMME	: 1 BEE
COURSE	: ELECTRICAL TECHNOLOGY	COURSE CODE	: BEE 1223 / BEE 10403

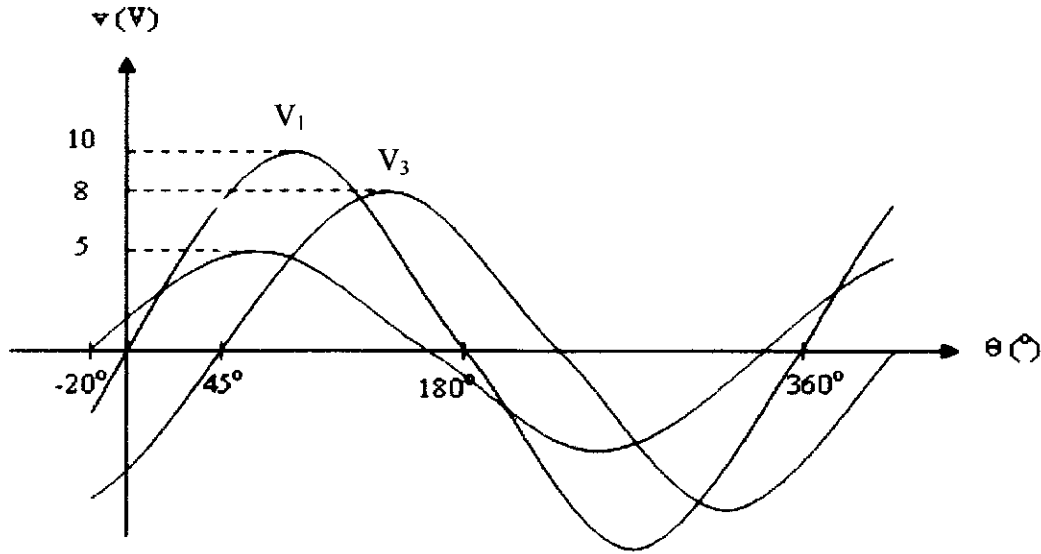


Figure Q1(b)

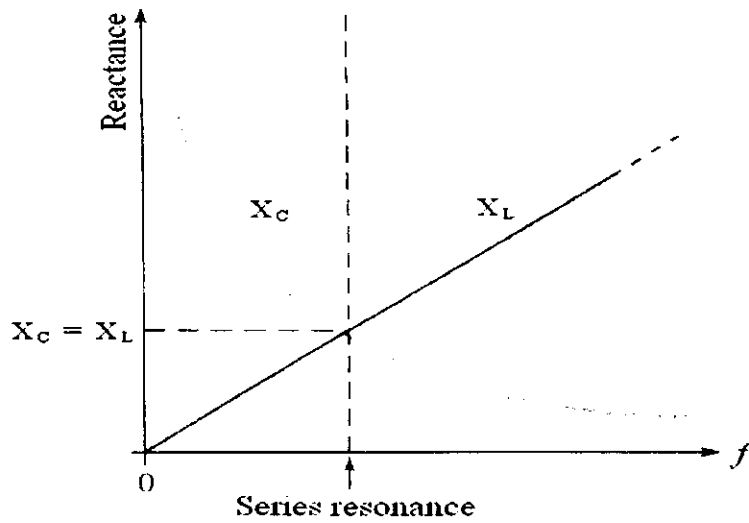


Figure Q2(b)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/2010/11
 COURSE : ELECTRICAL TECHNOLOGY

PROGRAMME : 1 BEE
 COURSE CODE : BEE 1223 / BEE 10403

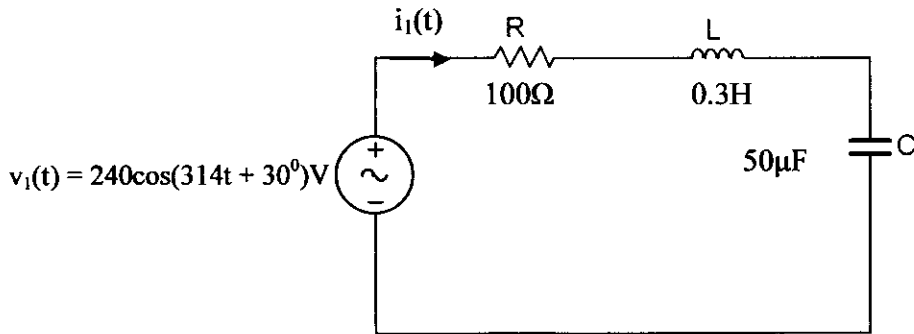


Figure Q2(c)

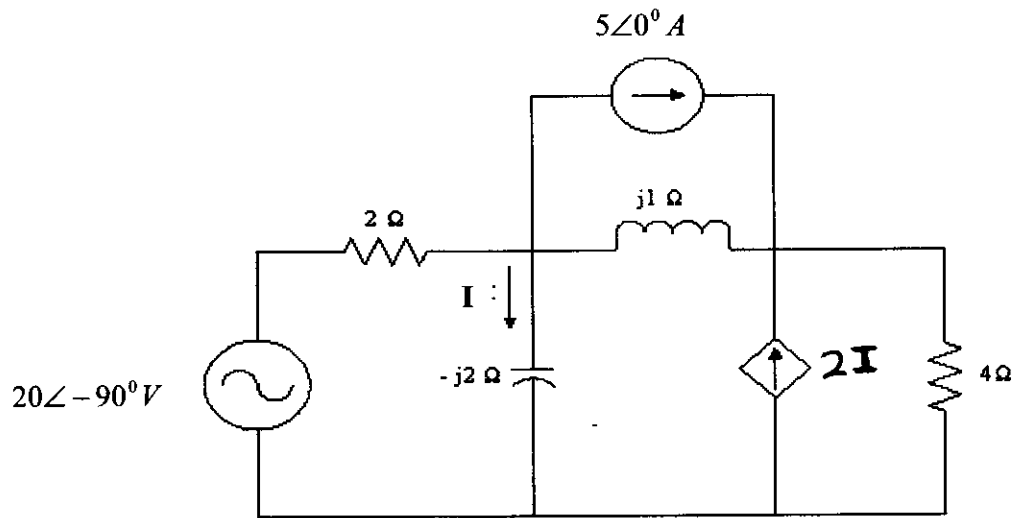


Figure Q3(b)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/2010/11
 COURSE : ELECTRICAL TECHNOLOGY

PROGRAMME : 1 BEE
 COURSE CODE : BEE 1223 / BEE 10403

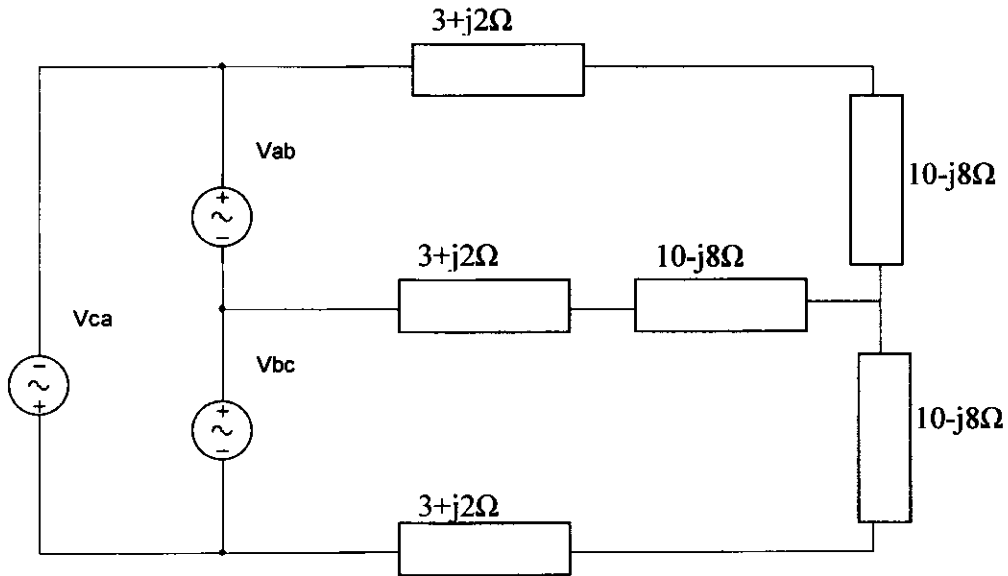


Figure Q3(c)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/2010/11
 COURSE : ELECTRICAL TECHNOLOGY

PROGRAMME : 1 BEE
 COURSE CODE : BEE 1223 / BEE 10403

Formulae

Trigonometric identities

$$\begin{aligned} \sin(\omega t \pm 180^\circ) &= -\sin \omega t \\ \cos(\omega t \pm 180^\circ) &= -\cos \omega t \\ \sin(\omega t \pm 90^\circ) &= \pm \cos \omega t \\ \cos(\omega t \pm 90^\circ) &= \mp \sin \omega t \end{aligned}$$

The delta to wye (Δ -Y) and wye to delta (Y- Δ) conversion formulas

Delta to wye conversion (Δ - Y)	Wye to delta conversion (Y - Δ)	Superposition of Y and Δ network
$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$ $R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$ $R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$	$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$ $R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$ $R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$	

Transformer voltage regulation

$$VR = \frac{V_{s,nl} - V_{s,fl}}{V_{s,fl}} \times 100\%$$

Transformer Efficiency

$$\eta = \frac{P_{out}}{P_{out} + P_{loss}} \times 100\%$$

Terminal voltage equation for DC shunt motor

$$V_t = E_a + I_a R_a$$