



# UNIVERSITI TUN HUSSEIN ONN MALAYSIA

## FINAL EXAMINATION SEMESTER I SESSION 2010/2011

COURSE NAME : POWER ELECTRONICS  
COURSE CODE : BEE 4113  
PROGRAMME : 4 BEE  
EXAMINATION DATE : NOVEMBER / DISEMBER 2010  
DURATION : 2 ½ HOURS  
INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS ONLY

THIS EXAMINATION PAPER CONSISTS OF (8) PAGES

- Q1 (a) Define the power electronics and what is the goal of power electronics. (4 marks)
- (b) Semiconductor power devices such as BJT, GTO and IGBT have power dissipation during turn on and turn off. Therefore it is important to consider this matter in designing a power electronic circuit. Figure Q1(b) has shown the switching characteristic of a typical semiconductor power device. If it is given that  $t_{c(on)} = 4ns$ ,  $t_{c(off)} = 6ns$ ,  $t_{on} = 3\mu s$ , and operates at switching frequency of  $100kHz$ . If the total average power dissipation,  $P_T$  is 1.75 watt, current flow through the switch is 5 A and switch on-state voltage is 1 V. Calculate;
- the average power dissipated during on-state,  $P_{ON}$ .
  - the average switching power loss,  $P_S$ .
  - the input voltage (voltage across the switch during off-state),  $V_d$ .
  - what is the new switching frequency if it is required to reduce the average power dissipated  $P_{ON}$  as in Q1(b)(i) by 50%.
- (10 marks)
- (c) Figure Q1(c) is a half-wave uncontrolled rectifier has a  $120 V_{rms}$  source at 60Hz. The load  $R=500\Omega$ ,  $C=100\mu F$ . Assume  $\alpha$  and  $\theta$  equal to 48 and 93 degrees respectively. Determine
- expression for output voltage,  $V_o$
  - peak-to-peak ripple voltage,  $\Delta V_o$
  - capacitor current,  $I_c$
  - Peak diode current,  $I_{D,peak}$
- (11 marks)
- Q2 (a) (i) State the requirement or condition to turn ON of Silicon Controlled Rectifier (SCR). (2 marks)
- (ii) Crest factor is a parameter to measure the performance of a rectifier circuit. A large value of crest factor will give indication that the circuit is not efficient in delivering energy. Calculate the value of crest factor for a given output waveform in Figure Q2(a)(ii). (5 marks)
- (b) Figure Q2 (b) is a single phase half-wave uncontrolled rectifier circuit connected to resistive and inductive load (RL load). The output current will flow in the circuit even in -ve input cycle of voltage source.
- Draw the waveform of output voltage,  $V_o$  and output current,  $I_o$  of the circuit if the extinction angle,  $\beta$  is  $200^\circ$ .
  - If the output current is Discontinuous Current Mode (DCM), explain with the aid of suitable diagram to overcome this problem. (6 marks)

- (c) Figure Q2 (c) shows a single phase half-wave controlled rectifier which has a resistive load of  $R = 10\Omega$ . The voltage at the secondary transformer is 240V and the firing angle  $\alpha = 60^\circ$ .
- Calculate the values of average voltage output,  $V_{avg}$  and RMS voltage output,  $V_{rms}$ .
  - Determine the average load current,  $I_{avg}$  and rms load current,  $I_{rms}$
  - Determine the average output power
  - Determine the new firing angle  $\alpha$ , if the rectifier is connected to the load which consumes half than maximum possible average output voltage
  - Draw the output voltage,  $V_o$  and current waveforms,  $I_o$  for the new firing angle,  $\alpha$ .
- (12 marks)
- Q3 (a) State two (2) advantages and disadvantages of PWM switching scheme. (4 marks)
- (b) Figure Q3(b) shows a single phase, half-bridge inverter with a resistive load  $R = 4\Omega$  and the input voltage is 24 volt DC. The inverter operates at a frequency of 50 Hz. Determine;
- the rms output voltage,  $V_{rms}$  at fundamental frequency.
  - the output power,  $P_o$
  - the average current of each transistor
- (9 marks)
- (c) A single phase, full-bridge inverter supplies has a resistive load of  $12\Omega$  in series with an inductive load of 25 mH and a capacitive load of 500  $\mu\text{F}$ . The inverter operates at a frequency of 60 Hz.
- Determine the value of the fundamental rms output voltage if the fundamental rms output load current is  $I_{orms} = 10\text{ A}$
  - Determine the value of the DC voltage source required to establish a load current in Q3(c)(i)
  - If the output voltage is to be in quasi-square wave, calculate the angle  $\alpha$  of inverter when the fundamental output voltage is 100 V.
  - Find the THD<sub>v</sub> of the output voltage in Q3(c)(i).
- (12 marks)
- Q4 (a) Pulse Frequency Modulation (PFM) is not preferred for switching technique in DC to DC converter. State three (3) disadvantages of PFM (3 marks)
- (b) Figure Q4 (b) shows the design of a boost converter to provide an output voltage of 15V from a 5V voltage source. The load is 30W. The minimum inductor current must be no less than 75% of the average value. The output voltage ripple must be less than 1.5%. The switching frequency is 10 kHz.

- (i) Formulate the expression of the output voltage,  $V_o$ .
- (ii) Calculate the duty ratio of the converter,  $D$
- (iii) Determine the minimum inductor current,  $I_{Lmin}$  afterwards calculate the value of inductor,  $L$
- (iv) Determine the minimum value of capacitor.

(10 marks)

- c). An engineer are requires to design and analyze a DC to DC converter that shown in Figure Q4(c) with the following specifications:

DC input voltage : 24 V  
 Output voltage : 20 V  
 Load : 33 W  
 Ripple output voltage :  $\leq 1\%$   
 Switching frequency : 25 kHz

The converter is expected to operate in Continuous Current Mode (CCM). Assuming all the components used are ideal:

- (i) Determine the duty cycle,  $D$
- (ii) Determine the minimum value of the inductor,  $L_{min}$  to provide Continuous Current Mode (CCM) operation
- (iii) Calculate the value of capacitor,  $C$
- (iv) Sketch the waveforms of  $V_L$ ,  $i_L$ ,  $i_D$  and input current  $I_s$  of the converter during ON-state and OFF-state conditions,
- (v) What is the output voltage of the converter if the new duty cycle is 0.65?
- (vi) Explain your answer Q4(c)(v) relate to  $V_o$

(12 marks)

- Q5 (a)** Figure Q5(a) shows a single phase full wave ac voltage controller with resistor load. If the firing angle,  $\alpha=30^\circ$ , plot the waveform (in one period) of:

- (i)  $V_{sw}$
- (ii)  $I_o$ , and
- (iii)  $V_o$

(9 marks)

- (b) If Figure Q5(a) employed for controlling the power flow from 240 Vrms, 50 Hz source into a load circuit consisting of a resistor load,  $R = 15 \Omega$  and inductor load,  $L = 50 \text{ mH}$ .


- (i) Calculate the control range of the firing angle,  $\alpha$ .
- (ii) Determine the maximum value of RMS load current,  $I_{orms}$
- (iii) Determine the maximum value of output power,  $P_o$  and power factor,  $PF$
- (iv) Derive the maximum value of RMS thyristor current,  $I_{TM}$

(16 marks)



**FINAL EXAMINATION**

SEMESTER/SESSION : I/2010/2011  
 COURSE NAME : POWER ELECTRONICS

PROGRAMME : 4 BEE  
 COURSE CODE : BEE 4113

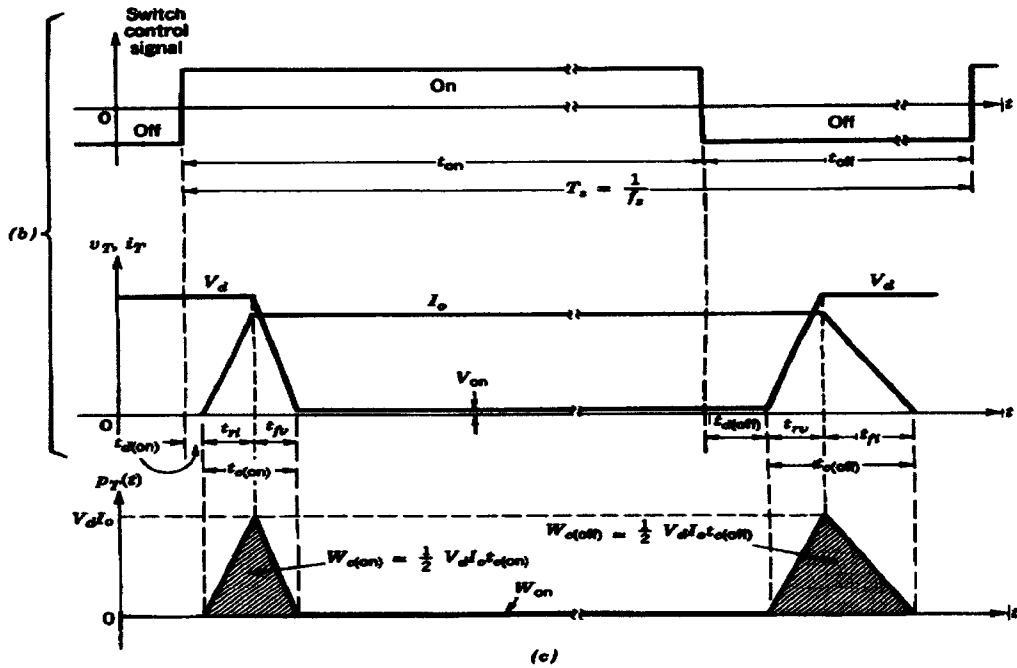

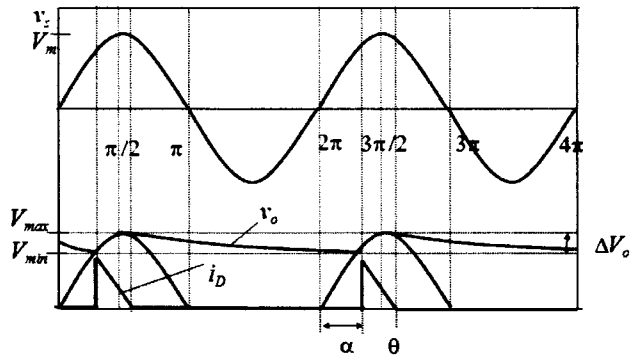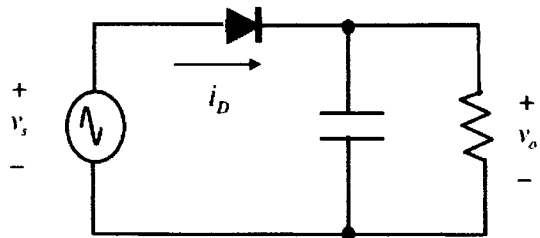**Figure Q1(b)**

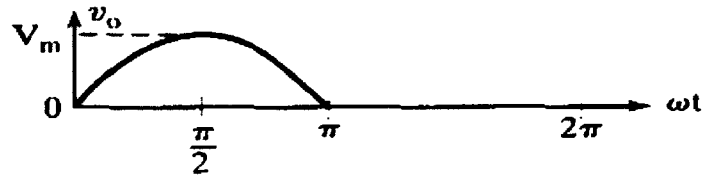


**Figure Q1(c)**


**FINAL EXAMINATION**

SEMESTER/SESSION : I/2010/2011  
 COURSE NAME : POWER ELECTRONICS


PROGRAMME : 4 BEE  
 COURSE CODE : BEE 4113



**Figure Q2(a)(ii)**

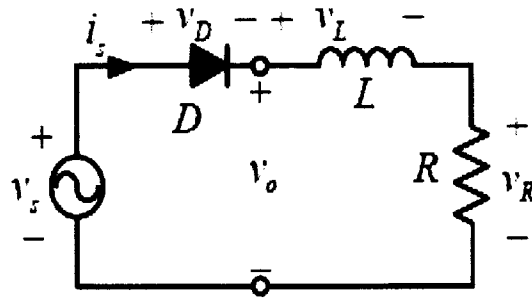

**Figure Q2(b)**

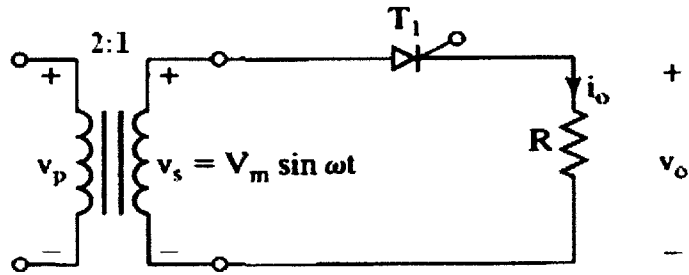


**Figure Q2(c)**


**FINAL EXAMINATION**

SEMESTER/SESSION : I/2010/2011  
 COURSE NAME : POWER ELECTRONICS


PROGRAMME : 4 BEE  
 COURSE CODE : BEE 4113

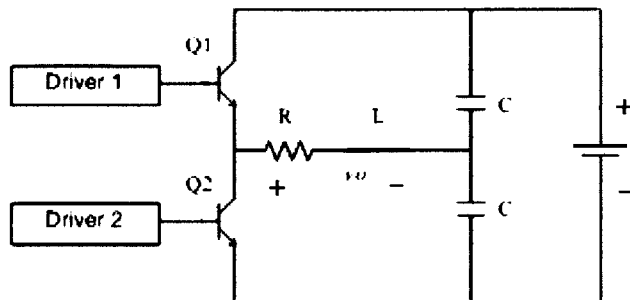

**Figure Q3(b)**

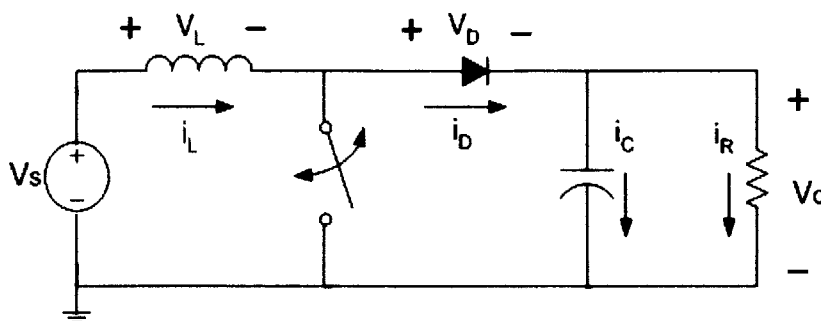

**Figure Q4(b)**

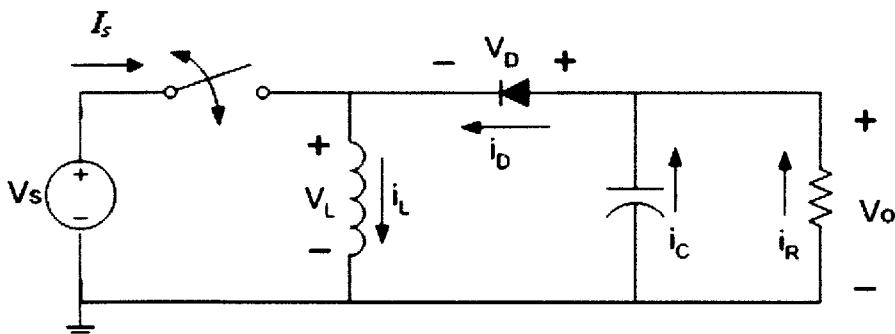


**Figure Q4(c)**

## FINAL EXAMINATION

SEMESTER/SESSION : I/2010/2011  
COURSE NAME : POWER ELECTRONICS

PROGRAMME : 4 BEE  
COURSE CODE : BEE 4113

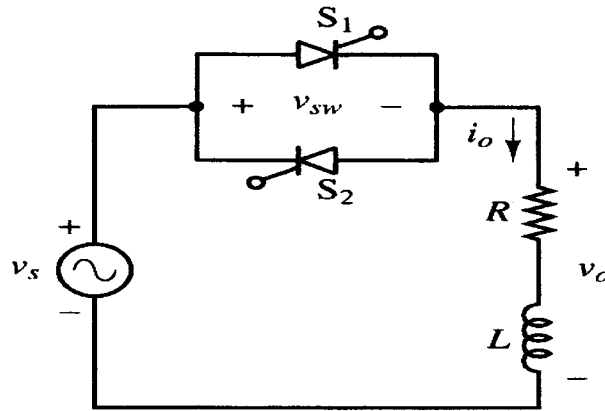

**Figure Q5(a)**