

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2010/2011**

COURSE NAME : POWER ELECTRONICS
COURSE CODE : BEE 4113
PROGRAMME : 4 BEE
EXAMINATION DATE : APRIL / MAY 2011
DURATION : 2 HOURS 30 MINUTES
INSTRUCTIONS : ANSWER **FOUR (4)** QUESTIONS ONLY

THIS EXAMINATION PAPER CONSISTS OF (6) PAGES

CONFIDENTIAL

- Q1** (a) (i) What is a converter and state the types of power converter? (4 marks)
- (ii) The diode cannot be used in high frequency application if the reverse recovery time (t_r) and reverse recovery charge (Q_r) of power diode is high. State the three effects of reverse recovery for a diode. (3 marks)
- (iii) Power electronic switches are used in power electronic converters to convert one level of signal to another level. In general, it can be categorized into three types, which are: Uncontrolled, Semi-Controlled and Fully Controlled. List the power electronic switches used for each type of those converters. (3 marks)
- (b) A 240V single-phase half-wave rectifier are connected in series with a diode and a load resistor 100Ω as shown in Figure Q1(b). Calculate the current flowing through the load and its power consumed. (6 marks)
- (c) The switching characteristic of a typical semiconductor power device is shown in Figure Q1(c). It is given that $t_{c(on)} = 4ns$, $t_{c(off)} = 6ns$, $t_{on} = 3\mu s$, and operates at switching frequency of $50kHz$. If the total average power dissipation, P_T is 1.75watt, current flow through the switch is 5A and switch on-state voltage is 1V. Calculate:
- (i) The average power dissipated during on-state, P_{ON} .
- (ii) The average switching power loss, P_S .
- (iii) The input voltage (voltage across the switch during off-state), V_d . (9 marks)
- Q2** A single phase full-wave controlled rectifier has a resistive load of $R = 12.5\Omega$, the voltage at the primary transformer is 240V with ratio 2:1, and the firing angle of thyristor is 30° .
- (i) Draw the circuit explain in this question.
- (ii) Derive and find the average output voltage.
- (iii) Determine the average load current
- (iv) Determine average output power
- (v) Determine the new firing angle, α . if the rectifier is connected to the load which consumes 50% less than maximum possible average output voltage
- (vi) Draw the input voltage, output voltage and output current waveforms for the new firing angle α . (25 marks)

- Q3** (a) (i) List three common types of inverter and draw its block diagram.
(ii) State the advantages and disadvantages of PWM switching scheme.
(10 marks)
- (b) A single phase, full-bridge inverter supplies a load of 10Ω in series with an inductance of 15 mH . The inverter is supplied from a 100 volts DC source. The inverter is operates at the frequency of 100 Hz .
- (i) Calculate the rms value of the fundamental output voltage of a square-wave waveform.
(ii) Determine the power absorbed by the load resistor due to the fundamental component.
(iii) Find the total harmonics distortion (THD) of the load current. Consider up to 7^{th} order harmonics.
(iv) If the output voltage is to be in quasi-square wave, calculate the angle α of inverter when the fundamental rms output voltage is 50 V .
(15 marks)
- Q4** (a) Explain briefly two modes of operation in DC-DC Converters based on inductor current.
(4 marks)
- (b) Design a boost converter to provide an output of 36V from constant dc source supply for continuous current mode with duty cycle 0.666 . The load is 100W and the output voltage ripple must be less than 1% . Assuming for the ideal components and the switching frequency is 25 kHz .
- (i) Using volt-second balance technique, prove that the output voltage of the buck-boost converter is

$$V_o = \frac{V_s}{1-D}$$
- (ii) Determine the dc input voltage.
(iii) Determine the capacitor size
(iv) Find the average inductor current
(v) Derive the expression of the minimum inductor current I_{Lmin} , during the switch is closed
(vi) Derive and determine minimum inductor L_{min} , for continuous current mode operation
(21 marks)

- Q5** (a) Figure Q5(a) employed for controlling the power flow from 240 Vrms, 50 Hz source into a load circuit consisting of a resistor load, $R = 7 \Omega$ and the average output voltage is 160V.
- (i) Derive the average output voltage and find the firing angle.
 - (ii) Determine the RMS output voltage.
- (9 marks)
- (b) If an inductance load is added in series connection with R load in question Q5(a), $L = 100 \text{ mH}$.
- (i) Calculate the control range of the firing angle, α .
 - (ii) Determine the maximum value of RMS load current, I_{orms}
 - (iii) Determine the maximum value of output power, P_o and power factor, PF
 - (iv) Derive the maximum value of RMS thyristor current, I_{TM}
- (16 marks)

FINAL EXAMINATION

SEMESTER/SESSION : II/2010/2011
 COURSE NAME : POWER ELECTRONICS

PROGRAMME : 4 BEE
 COURSE CODE : BEE 4113

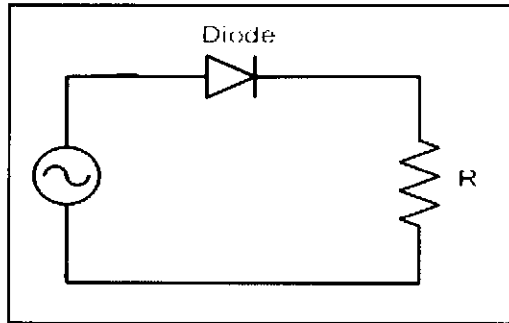


Figure Q1 (b)

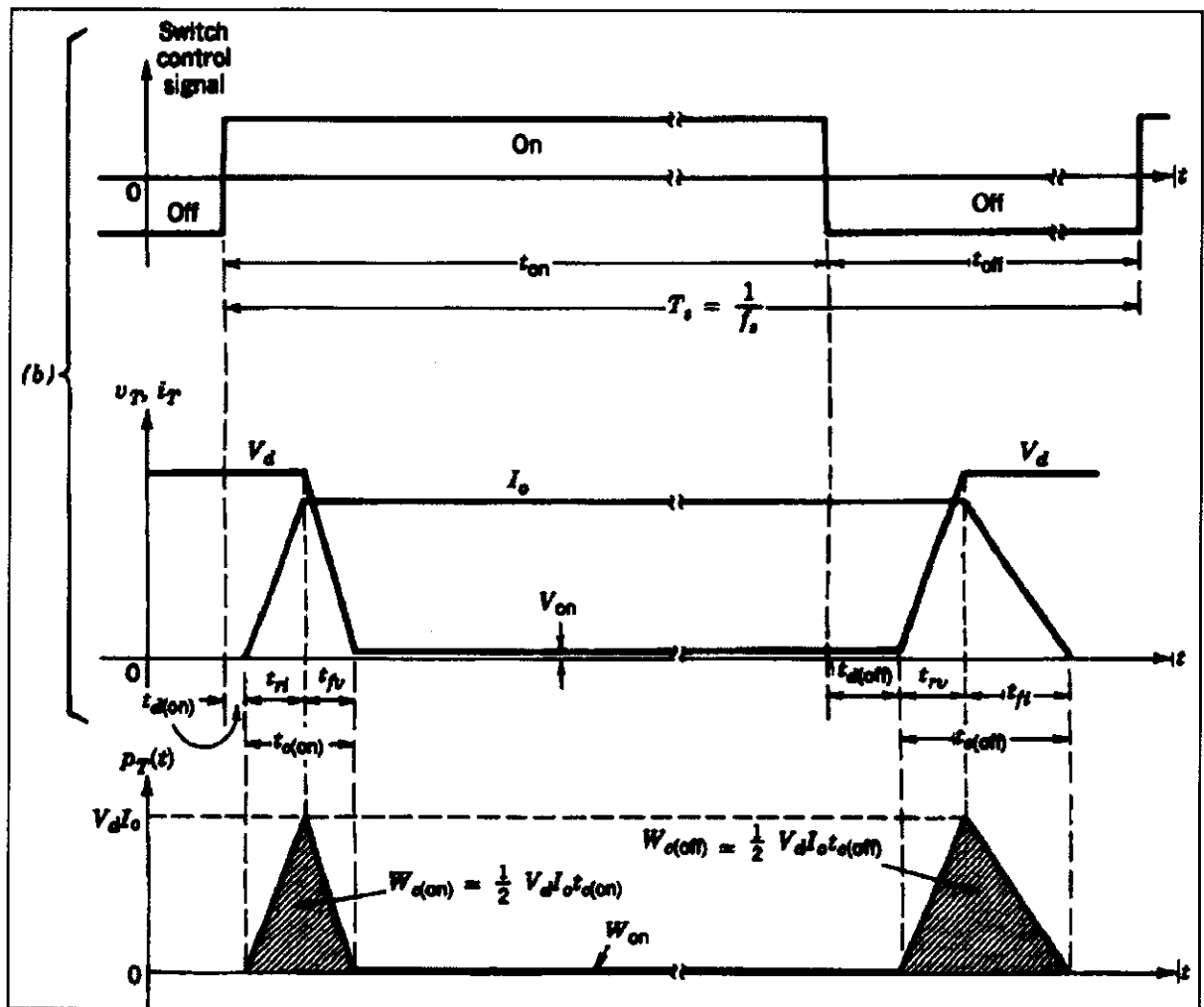


Figure Q1(c)

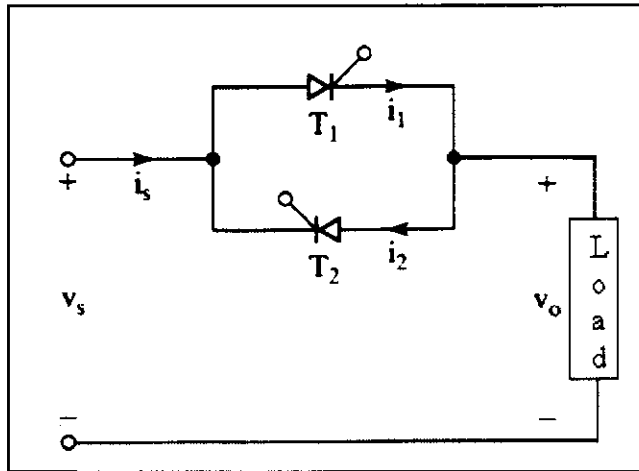


Figure Q5(a)