



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2012/2013**

COURSE NAME : DIGITAL SYSTEM DESIGN
COURSE CODE : BEE 3133/BEX31503
PROGRAMME : 3 BEE
EXAMINATION DATE : JUNE 2013
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF **SIX (6)** PAGES

- Q1** (a) In 1965, Gordon Moore predict that the transistor would continue to shrink
- (i) Identify THREE (3) advantages on electronic device capabilities based on this prediction. (3 marks)
 - (ii) Moore's Law has proved remarkably accurate for more than half a century, but it is expected that the growth will slow by the end of 2013. Predict TWO (2) restrictions that should be considered in Moore's Law. (3 marks)
- (b) Based on VHDL code in Figure Q1 (b), construct its schematic circuit. (7 marks)
- (c) By using 'Case Statement', compose the VHDL code for 5-to-1 multiplexer circuit in Figure Q1 (c). (7 marks)
- Q2** (a) A sequence detector consists of a single-input and single-output. This sequence detector will produce an output of '1' if the input sequence detects 101 patterns.
- (i) Develop a Moore-type state diagram for the sequence detector. (3 marks)
 - (ii) Produce state-assigned table for the detector. (4 marks)
 - (iii) Construct the schematic circuitry of sequence detector. (6 marks)
- (b) Consider a stick diagram in Figure Q2 (b).
- (i) Produce the electrically equivalent transistor-level. (4 marks)
 - (ii) Illustrate the Euler path for transistor level in Q2 (b)(i). (3 marks)

- Q3** (a) Given a function $f(x_1, x_2, x_3, x_4) = \sum m(0, 1, 3, 4, 7, 11, 13, 15) + D(9, 12, 14)$.
By using K-Map, produce the minimum-cost SOP function. (5 marks)
- (b) Given a function of $f(A,B,C,D) = \sum (0,1,4,5,10,12,14)$. By using tabular method of simplification:
- Construct the First, Second and Third List table. (9 marks)
 - Construct Essential Prime Implicant (EPI) cover table. (4 marks)
 - Produce the minimum cost implementation. (2 marks)
- Q4** (a) For nFET transistor, assume that $k_n' = 100 \times 10^{-6} \text{ A/V}^2$, $W/L = 0.25 \mu\text{m}/0.2 \mu\text{m}$, $V_{DD} = 5\text{V}$, and $V_{TN} = 1\text{V}$.
- Investigate the maximum current flow in the nFET. (5 marks)
 - Decide the aspect ratio needed to obtain a maximum current of 8mA and $W = 5 \mu\text{m}$. (5 marks)
- (b) t_{LH} defines as a time needed for the output arise from the 10% V_{DD} to 90% V_{DD} in digital waveform. Given $t_{LH} = t_{90\%} - t_{10\%}$, where $t_x = \tau_p \ln\left(\frac{1}{1 - \frac{V_x}{V_{DD}}}\right)$, produce the t_{LH} value. (10 marks)
- Q5** (a) Given a simple circuit in Figure Q5(a).
- Determine a fault table for the circuit to show the coverage of the various stuck-at-0 and stuck-at-1 faults by the eight possible tests. (10 marks)
 - Predict the minimal test set for this circuit. (4 marks)
- (b) Based on the logic circuit in Figure Q5(b) predict the tests that can detect each of these faults:
- $w_2/0$
 - $b/1$
 - $d/1$
- (6 marks)

-END OF QUESTION-

FINAL EXAMINATION

SEMESTER / SESSION : SEM II/ 20122013 PROGRAMME : 3 BEE
COURSE NAME : DIGITAL SYSTEM DESIGN COURSE CODE : BEE 3133/BEX31503

```
Library ieee;
use ieee.std_logic_1164.all;

entity dec3to8 is
port ( Wa : in std_logic_vector ( 2 downto 0);
      Ena : in std_logic;
      Ya : out std_logic_vector (0 to 7));
end dec3to8;

architecture structural of dec3to8 is
signal s : std_logic_vector (0 to 1);

component dec2to4
port ( w : in std_logic_vector ( 1 downto 0);
      En : in std_logic;
      y : out std_logic_vector(0 to 3));
end component;

Begin
s(0) <= not Wa(2) and Ena;
s(1) <= Wa(2) and Ena;
D1 : dec2to4 port map ( w(1)=>Wa(1), w(0)=>Wa(0), En => s(0), y(0)=>Ya(0),
                      y(1)=> Ya(1),y(2)=> Ya(2),y(3)=> Ya(3));
D2 : dec2to4 port map ( Wa(1 downto 0), s(1), Ya(4 to 7));
End structural;
```

FIGURE Q1(b)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II/ 20122013 PROGRAMME : 3 BEE
 COURSE : DIGITAL SYSTEM DESIGN COURSE CODE : BEE 3133/BEX31503

 


FIGURE Q1(c)

 


FIGURE Q2(b)

 


FIGURE Q5(a)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II/ 20122013

PROGRAMME : 3 BEE

COURSE : DIGITAL SYSTEM DESIGN

COURSE CODE : BEE 3133/BEX31503

 


FIGURE Q5(b)