



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2012/2013**

COURSE NAME : ELECTRIC MACHINES AND DRIVES /
ELECTRICAL MACHINES

COURSE CODE : BEE 4123 / BEX 42403 / BEF 24103

PROGRAMME : BEE / BEF

EXAMINATION DATE : JUNE 2013

DURATION : 2 ½ HOURS

INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF NINE (9) PAGES

- Q1** (a) Explain clearly the differences between fringing flux and leakage flux. (4 marks)
- (b) An electromagnet of rectangular cross-section shown in Figure Q1(b) has a tightly wound coil with 500 turns. The inner and the outer radius of the magnetic core are 10 cm and 12.5 cm, respectively and its thickness being 2 cm. The length of the air-gap is 1 mm. If the current, I in the coil is 3 A and produces a flux density, B of 1.2 T in the air-gap (no fringing effect), determine:
- The magnetic field intensity in the magnetic core, H_c and in the air-gap, H_g
 - The relative permeability of the magnetic material of the core, μ_r
 - The total reluctance, \mathcal{R}_{total} of the magnetic core and air-gap
- (7 marks)
- (c) The toroidal (circular cross section) core shown in Figure Q1(c) is made from cast steel. Its magnetization curve as shown in Figure Q1(d),
- Calculate the coil current required to produce a core flux density of 1.2 tesla at the mean radius of the toroid
 - Determine the core flux, in Wb. Assume uniform flux density in the core
 - If a 2-mm-wide air gap is made in the toroid (cross $A-A'$), determine the new coil current required to maintain a core flux density of 1.2 T. Assume fringing effects of 5%
- (14 marks)
- Q2** (a) Draw the connection of transformer for short circuit test and open circuit test together with their necessary meters. (6 marks)
- (b) A 5500 kVA 240/13.8 kV single-phase transformer has a values of the excitation branch, $R_c=2500 \Omega$ and $X_m=250 \Omega$ referred to the primary of the transformer. The short circuit test performed on the high-voltage side of the transformer and the data recorded are as follows:
- $$V_{SC} = 550 \text{ V} \quad I_{SC} = 20 \text{ A} \quad P_{SC} = 450 \text{ W}$$
- Determine the type of the transformer.
 - Determine the values of series impedance R_{eq} and X_{eq} .
 - Draw the equivalent circuit referred to the high voltage side of the transformer. Label all the components correctly.
 - Determine the full-load voltage regulation at 0.8 lagging power factor.

- (v) Determine the output power of the transformer.
- (vi) Determine the core loss and copper loss of the transformer.
- (vii) From result (b)(vi), explain the relationship between the values of the excitation branch and the results.

(19 marks)

- Q3** (a) Sketch and explain briefly power flow diagram of an induction motor. (8 marks)

- (b) A 3 phase, 450V, 50Hz, 4 pole, Δ -connected induction motor has the following parameter referred to the stator.

$$R_1 = 0.15\Omega$$

$$X_1 = 0.6\Omega$$

$$X_m = 35\Omega$$

$$R_2 = 0.35\Omega$$

$$X_2 = 0.6\Omega$$

The rotor is running at 1450 rpm and the rotational loss is 1800W. Based on the information given,

- (i) Draw the equivalent circuit.
- (ii) Find the stator current, I_f .
- (iii) Calculate the power factor, pf .
- (iv) Input power, P_{IN} .
- (v) Stator copper loss, P_{SCL} .
- (vi) Air gap power, P_{AG} .
- (vii) Converted power, P_{CONV} .
- (viii) Output Power, P_{OUT} .
- (ix) Calculate the induced and load torque.
- (x) Determine the value of external resistance required in each phase of the rotor when the maximum torque occurs at the starting point.

(17 marks)

- Q4** (a) Sketch and explain the principle operation of a 3-phase, 2-pole DC excited synchronous motor. (5 marks)

- (b) A three-phase wye-connected synchronous motor has specifications as follow:

Line Voltage = 415 V, 50 Hz	Armature Resistance, $R_A = 0.3$ ohms
Power Factor = 0.8 leading	Synchronous Reactance, $X_S = 4$ ohms
Output Power = 20 Hp	Friction and Windage Losses = 15 kW
Pole = 2	Core Losses = 20 kW

Based on Figure Q4(b) and information given, answer the following questions.

- (i) Sketch and label a single-phase equivalent circuit of synchronous motor.
- (ii) By considering the related factor, estimate the value of three-phase copper losses, P_{copper} and armature current, I_A at unity power factor and full-load condition.
- (iii) Calculate the required value of three-phase internal generated voltage, E_A and identify the required field current, I_F .
- (iv) Sketch and label phasor diagram of the motor at unity power factor and full-load condition.
- (v) Compute the motor efficiency, η_m at unity power factor and full-load condition by considering copper losses, P_{copper} effect.
- (vi) Determine the maximum torque, τ_m at unity power factor and full-load condition by considering copper losses, P_{copper} effect.
- (vii) Determine the maximum torque, τ_m at 0.8 leading power factor by considering copper losses, P_{copper} effect.
- (viii) Sketch and label phasor diagram of the motor at 0.8 leading power factor.

(20 marks)

- Q5** (a) Sketch and explain briefly equivalent circuit of shunt DC motor with its starting resistor in order to avoid any excess current. (8 marks)
- (b) A 50hp, 250V, 1200r/min dc shunt motor with compensating windings has an armature resistance of 0.06Ω . Its field circuit has a total resistance $R_{adj} + R_F$ of 50Ω , which produces a no-load speed of 1200r/min. There are 1200turns per pole on the shunt field windings.
- (i) Find the speed of this motor when its input currents are 100A, 200A, and 300A
 - (ii) Plot the torque-speed characteristics of this motor at all conditions calculated from (i) and
 - (iii) List three (3) methods to control the speed of the motor
- (17 marks)

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/ 20122013
 COURSE : ELECTRIC MACHINES AND DRIVES/
 ELECTRICAL MACHINES

PROGRAMME : BEE/BEF
 COURSE CODE :
 BEE4123/BEX42403/BEF24103

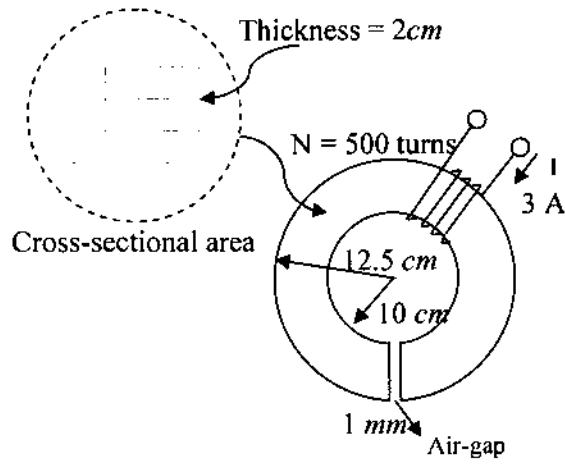


FIGURE Q1(b)

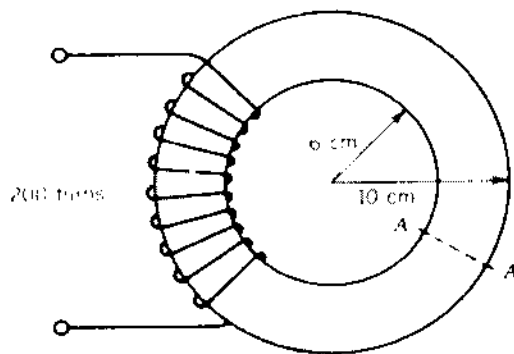


FIGURE Q1(c)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/ 20122013

PROGRAMME : BEE/BEF

COURSE : ELECTRIC MACHINES AND DRIVES/
ELECTRICAL MACHINES

COURSE CODE :
BEE4123/BEX42403/BEF24103

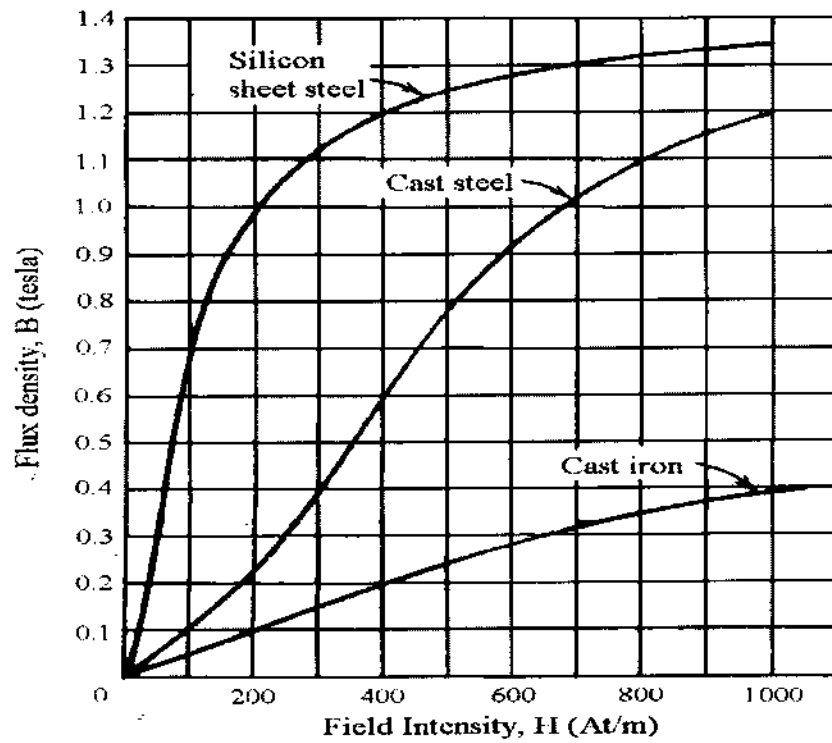


FIGURE Q1(d)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/ 20122013

PROGRAMME : BEE/BEF

COURSE : ELECTRIC MACHINES AND DRIVES/
ELECTRICAL MACHINES

COURSE CODE :
BEE4123/BEX42403/BEF24103

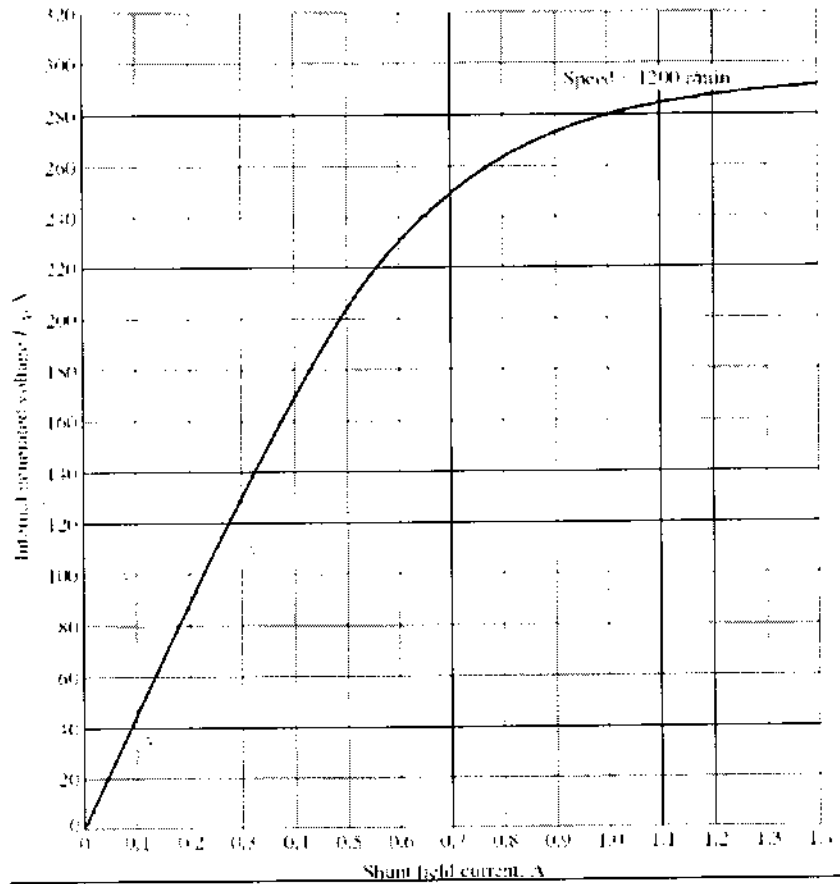


FIGURE Q4(b)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/ 20122013

PROGRAMME : BEE/BEF

COURSE : ELECTRIC MACHINES AND DRIVES/
ELECTRICAL MACHINESCOURSE CODE :
BEE4123/BEX42403/BEF24103**Formulae****Magnet:**

$$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$$

Synchronous machine:

$$P_{conv} = \tau_{ind} \omega_m = 3E_A I_A \cos \gamma$$

$$P = \frac{3V_\phi E_A \sin \delta}{X_S}$$

$$\tau_{ind} = \frac{3V_\phi E_A \sin \delta}{\omega_m X_S}$$

Induction motor:

$$P_{conv} = 3I_2^2 R_2 \left(\frac{1-s}{s} \right)$$

$$P_{AG} = 3I_2^2 \frac{R_2}{s}$$

$$\tau_{ind} = \frac{P_{AG}}{\omega_{sync}}$$

$$\tau_{load} = \frac{P_{OUT}}{\omega_m}$$

$$\tau_{ind} = \frac{3V_{TH}^2 \frac{R_2}{s}}{\omega_{sync} \left[\left(R_{TH} + \frac{R_2}{s} \right)^2 + (X_{TH} + X_2)^2 \right]}$$

$$s_{max} = \frac{R_2}{\sqrt{R_{TH}^2 + (X_{TH} + X_2)^2}}$$

DC motor:

$$E_A = K\phi\omega$$

$$\tau_{ind} = K\phi I_A$$

$$P_{conv} = E_A I_A = \tau_{ind} \omega_m$$

$$I_F^* = I_F + \frac{N_{SE}}{N_F} I_A - \frac{\mathfrak{I}_{AR}}{N_F}$$

$$\omega = \frac{V_T}{K\phi} - \frac{R_A}{(K\phi)^2} \tau_{ind}$$