



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2012/2013**

COURSE NAME : ELECTRICAL TECHNOLOGY
COURSE CODE : BEE 10403 / BEX 10303 / BEE 1223
PROGRAMME : BEB/BEC/BED/BEE/BEH/BEU
EXAMINATION DATE : JUNE 2013
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF SIX (6) PAGES

- Q1** (a) Given the sinusoid $v_s = 5\sin(4\pi t - 60^\circ)V$. Determine its:
- (i) amplitude (1 marks)
 - (ii) angular frequency (1 marks)
 - (iii) period (2 marks)
 - (iv) frequency (2 marks)
 - (v) v_s at $t = 2.5\text{ms}$ (2 marks)
- (b) Simplify the following expression:
- $$\frac{(240\angle 75^\circ + 160\angle -30^\circ)(60 - j80)}{(67 + j84)(20\angle 32^\circ)}$$
- (4 marks)
- (c) Find a single sinusoid corresponding to each of these phasors:
- (i) $V_1 = 40\angle -60^\circ V$ (2 marks)
 - (ii) $V_2 = 6 + j8, \omega = 40$ (2 marks)
- (d) Calculate the phase angle between $i_1 = -4\sin(277t + 25^\circ)$ and $i_2 = 5\cos(277t - 40^\circ)$. Determine if i_1 lead or lags i_2 ? Draw a phasor diagram showing i_1 and i_2 . (4 marks)

- Q2**
- (a) Using your own words to explain the resonance conditions. (4 marks)
- (b) Based on the R-L circuit shown in **Figure Q2(b)**; Calculate the current, I , in the circuit. Give your answer in polar form. (6 marks)
- (c) Referring to **Figure Q2(b)**, if a capacitor with capacitance of 500nF is now connected in parallel with the inductor, find
- (i) the total impedance of the circuit, Z (3 marks)
- (ii) the resonant frequency of the circuit (3 marks)
- (iii) the current, I , flowing in the circuit during the resonant frequency (4 marks)
-
- Q3**
- (a) In your own words and with the aid of an appropriate diagram, explain the principle of mutual induction. (5 marks)
- (b) A magnetic material has a magnetic field strength of 1000 At/m and a flux density of 480 mT. Given that the permeability at free space is $4\pi \times 10^{-7}$, calculate:
- (i) the relative permeability of the material (5 marks)
- (ii) the magnetomotive force (m.m.f) required to produces the above flux density in an air-gap of 1 mm width (5 marks)
- (iii) the current flow in 1000 turns to produce m.m.f in **Figure Q3(b)(ii)** (5 marks)

- Q4** (a) Describe the **TWO (2)** advantages of three phase system (compared to single phase systems) and give your reason. (4 marks)
- (b) A delta-connected 415 V, 50 Hz, 3-phase supply is connected to a Y-connected balanced load. Each phase of the load consists of a resistance of 25Ω and inductance 0.1 H, connected in series. Given the phase angle of V_{AB} is zero:
- (i) find line to neutral voltage, V_{an} (3 marks)
- (ii) calculate the line current drawn from the supply, I_{aA} (3 marks)
- (iii) sketch a phasor diagram showing V_{AB} , V_{an} and I_{aA} (2 marks)
- (c) A balanced positive sequence wye-connected 120 Hz, 3-phase supply has phase voltages of $V_Y = 100V$. This source is connected to a delta-connected balanced load through wires having impedance of $Z_{line} = 0.2+j0.4 \Omega$. Given that the impedance of each phase of the load is $Z_{\Delta} = 25-j8 \Omega$ and the phase angle of V_{an} is -15° :
- (i) calculate line to line voltage at the load, V_{AB} (2 marks)
- (ii) calculate current in each phase of the load, I_{AB} (4 marks)
- (iii) sketch a phasor diagram showing V_{AB} and I_{AB} (2 marks)

- Q5 (a) Explain briefly **TWO (2)** losses that occur in a transformer. (4 marks)
- (b) A 100 kVA transformer has 400 turns on the primary and 80 turns on the secondary. The primary and secondary resistance are 0.3Ω and 0.01Ω , respectively. While the corresponding leakage reactances are given by 1.1Ω and 0.035Ω , respectively. Given that the supply voltage is 2200 V.
- (i) Calculate the equivalent impedance referred to the primary circuit (5 marks)
- (ii) Determine the voltage regulation and the secondary terminal voltage for full load having a power factor of 0.8 lagging (5 marks)
- (c) An ideal transformer, connected to a 240V main, supplies a 12V, 150 W lamp.
- (i) Calculate the transformer turns ratio (3 marks)
- (ii) Determine the current taken from the supply (3 marks)

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER/SESSION : II / 2012/2013

PROGRAMME : BEB/BEC/BED/BEE

BEH/BEU

COURSE NAME : ELECTRICAL TECHNOLOGY

COURSE CODE : BEE 10403/

BEX 10303/BEE 1223

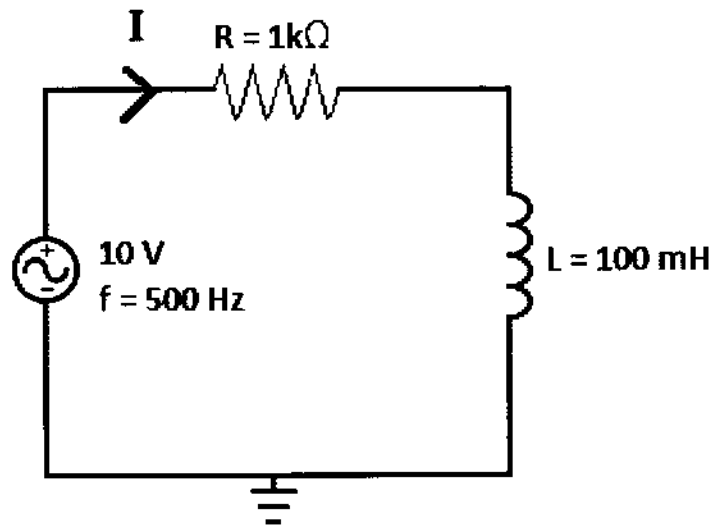


FIGURE Q2(b)