

**CONFIDENTIAL**



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESSION 2012/2013**

**COURSE NAME : VLSI DESIGN**  
**COURSE CODE : BED 30303**  
**PROGRAMME : BED**  
**EXAMINATION DATE : JUNE 2013**  
**DURATION : 2 ½ HOURS**  
**INSTRUCTION : ANSWER FIVE (5) QUESTIONS ONLY.**

**THIS QUESTION PAPER CONSISTS OF SEVEN (7) PAGES**

**CONFIDENTIAL**

**Q1** For the following function

$$G = \overline{ab + cd + e}$$

- (a) Design a static CMOS circuit using minimum number of transistors to realize the function. (10 marks)
- (b) Draw the most compact stick diagram layout for the function. (10 marks)

**Q2** (a) A 2-input multiplexer (2:1 MUX) can be realized by using a pair of transmission gate as shown in **Figure Q2(a)**.

(i) Obtain the equation for output Y of **Figure Q2(a)**. (2 marks)

(ii) State the advantage of using transmission gate in designing a logic circuit. (3 marks)

(b) A 4-input multiplexer (4:1 MUX) can be constructed using two 2-input multiplexers as shown in **Figure Q2(b)**. Design the 4-input multiplexer using the transmission gate method. Draw the circuit at transistor level. (15 marks)

- Q3** (a) A Half Adder circuit is shown in gate level in **Figure Q3(a)**. For this circuit:
- (i) State the Boolean equations for the output S and  $C_{out}$ . (2 marks)
  - (ii) Draw the circuit for sum (S) at transistor level using static CMOS. (8 marks)
- (b) A Carry Look-Ahead circuit is usually used along with a Full Adder circuit.
- (i) Complete the truth table shown in **Figure Q3(b)** to include two terms Generate (G) and Propagate (P) that is used in the Carry Look-Ahead circuit and obtain the general equation for G and P. (4 marks)
  - (ii) Based on the truth table on **Figure Q3(b)**, acquire the equations for S and  $C_o$ ; and then rewrite the equations S and  $C_o$  in term of Generate (G) and Propagate (P) . (6 marks)
- Q4** (a) A Full Adder circuit at transistor level is shown in **Figure Q4(a)**. Acquire the Boolean equations for X,  $C_o$ , Y and S (8 marks)
- (b) A block diagram of a 2-to-4 decoder is shown in **Figure Q4(b)**.
- (i) Construct the truth table for the decoder and obtain the equation for each output. (4 marks)
  - (ii) Design a dynamic 2-to-4 NOR decoder and draw the full circuit at transistor level. (8 marks)


- Q5**
- (a) In VLSI design, IC designing process can be described in the behavioural, structural and physical domains. Describe these domains.  
(6 marks)
  - (b) Explain the following two most common style of physical clocking networks in VLSI design.
    - (i) H tree  
(3 marks)
    - (ii) Balanced tree  
(3 marks)
  - (c) One aspect in optimization of VLSI design is in reducing circuit delay. Discuss about RC delay and propose techniques to improve the delay imposed by the resistance of a wire.  
(8 marks)

- END OF QUESTION -


**FINAL EXAMINATION**

SEMESTER/SESSION : SEMESTER II/2012/2013  
 COURSE : VLSI DESIGN

PROGRAMME: BED  
 COURSE CODE: BED 30303

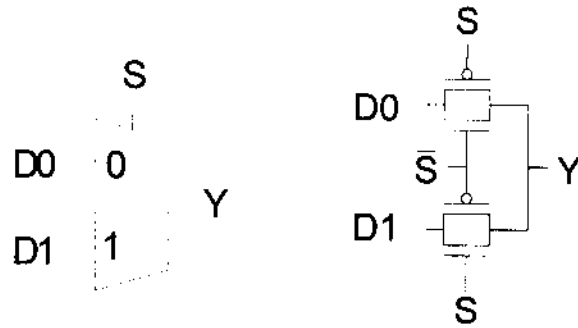

**FIGURE Q2(a)**

 


**FIGURE Q2(b)**

**FINAL EXAMINATION**

SEMESTER/SESSION : SEMESTER II/2012/2013  
 COURSE : VLSI DESIGN

PROGRAMME: BED  
 COURSE CODE: BED 30303

 

**FIGURE Q3(a)**


A	B	$C_1$	S	$C_0$	P	G
0	0	0	0	0		
0	0	1	1	0		
0	1	0	1	0		
0	1	1	0	1		
1	0	0	1	0		
1	0	1	0	1		
1	1	0	0	1		
1	1	1	1	1		

**FIGURE Q3(b)**


**FINAL EXAMINATION**

SEMESTER/SESSION : SEMESTER II/2012/2013  
 COURSE : VLSI DESIGN

PROGRAMME: BED  
 COURSE CODE: BED 30303

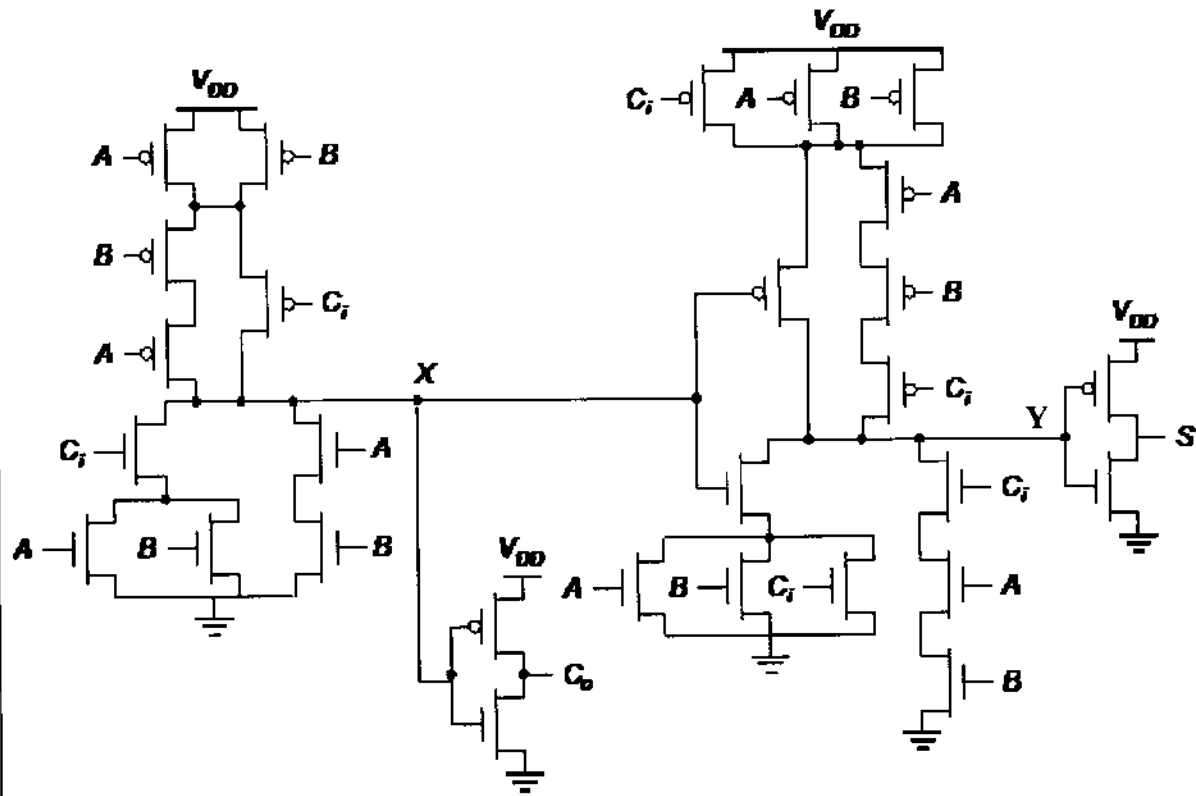

**FIGURE Q4(a)**

 

**FIGURE Q4(b)**