

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2013/2014**

COURSE NAME : ELECTRIC NETWORK
ANALYSIS & SYNTHESIS
COURSE CODE : BEE 3113
PROGRAMME : BEE
EXAMINATION DATE : JUNE 2014
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF **SIX (6)** PAGES

CONFIDENTIAL


- Q1** (a) Explain the term transfer function of any electric network. Briefly describe the meanings of pole and zero. (4 marks)

- (b) Given a function of a system is

$$h(t) = \frac{250}{3} (25e^{-100t} - e^{-4t})u(t)$$

- (i) Find the transfer function, $H(s)$ of this system. (4 marks)
- (ii) Sketch a pole-zero map of the transfer function, $H(s)$. (3 marks)
- (iii) By using semilog graph paper, draw the magnitude response of $H(s)$. (6 marks)
- (iv) From the magnitude response plotted in Question **(b)(iii)**, identify the type of filter this system produced, maximum gain (in dB) and its operating frequency range. (3 marks)

- Q2** (a) Explain the difference between natural response and forced response of any electric network. (4 marks)
- (b) The switch in the circuit in Figure **Q2(b)** has been closed for a very long time before opening at $t = 0$ s.
- (i) Show that the initial condition for capacitor, $v_o(0) = 70$ V. (5 marks)
- (ii) Construct the s-domain circuit for $t > 0$ s. Include all the initial conditions for energy storage elements if available. Name the type of response exists during this time. (3 marks)
- (iii) Analyse the circuit to obtain $V_o(s)$, $i_L(t)$ and $v_o(t)$. (10 marks)

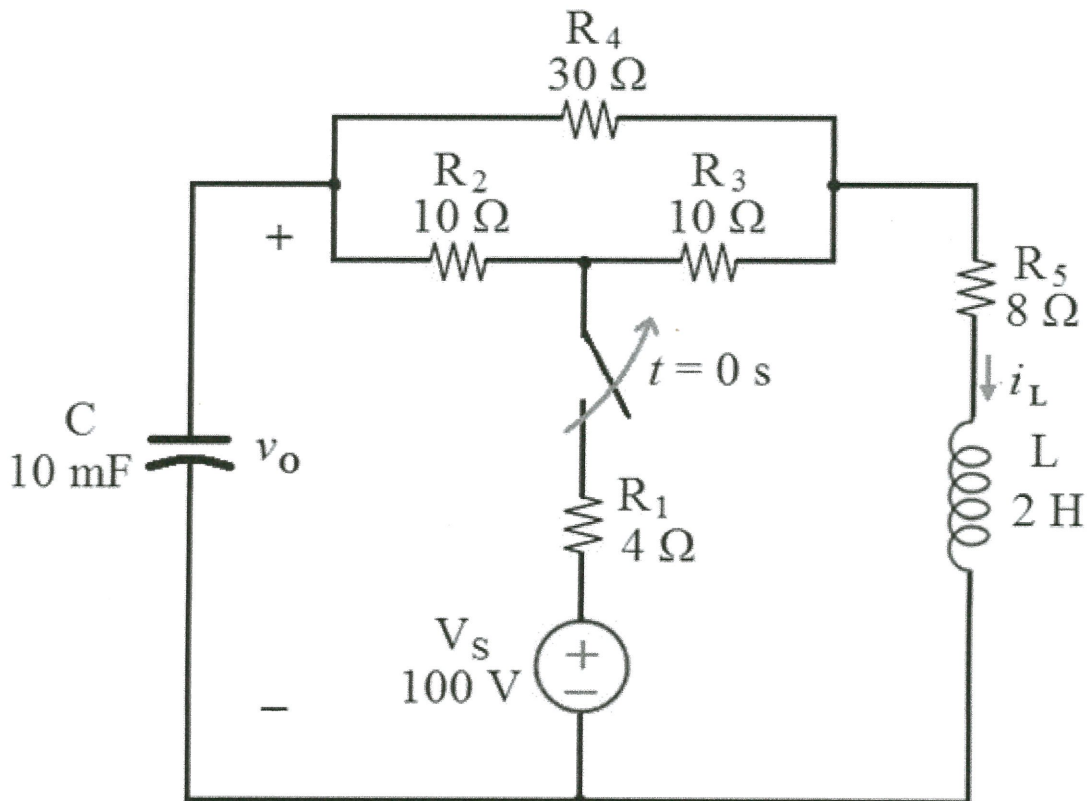**FIGURE Q2(b)**

Q3 (a) Describe only **THREE (3)** out of four basic types of filter and sketch its frequency response. (6 marks)

(b) The electric network in Figure **Q3(b)** behaves as filter for specified frequency range.

(i) Explain how the resonant phenomenon could be materialized in an electric network. (2 marks)

(ii) Prove that its resonant frequency, ω_0 is

$$\omega_0 = \frac{1}{\sqrt{CL}} \sqrt{1 - \frac{L}{CR^2}}$$

(6 marks)

(iii) Given that the resistor, R is 1Ω and the capacitance is twice of inductance, calculate the value of L and C to produce the resonant frequency of 100 rad/s .

(4 marks)

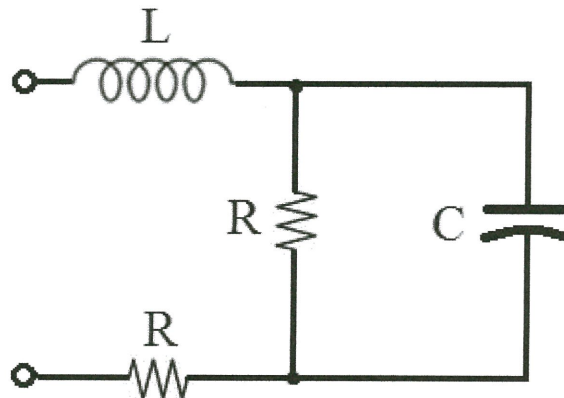


FIGURE Q3(b)

Q4 (a) Explain **ONE (1)** advantage of using two-port network in circuit analysis. (2 marks)

(b) In an experiment on a two-port network, the following observations are recorded:

- with port 1 open-circuited and $V_2 = 10$ V, it is found that $V_1 = 25$ mV and $I_2 = 5$ mA
- with port 2 short-circuited and $V_1 = 20$ V, it is found that $I_1 = 10$ mA and $I_2 = 1$ A.

Obtain the Y-parameter of the two-port network. Determine whether this is a reciprocal network.

(10 marks)

(c) The hybrid parameter model of the circuit shown in Figure **Q4(c)** is

$$\begin{bmatrix} A \Omega & 0.1 \\ B & 0.6 S \end{bmatrix}$$

Determine A and B .

(8 marks)

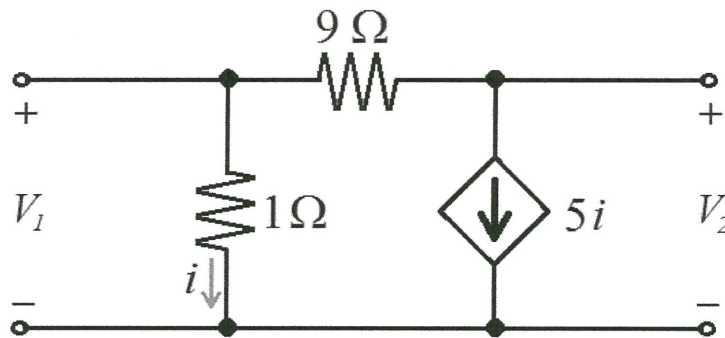
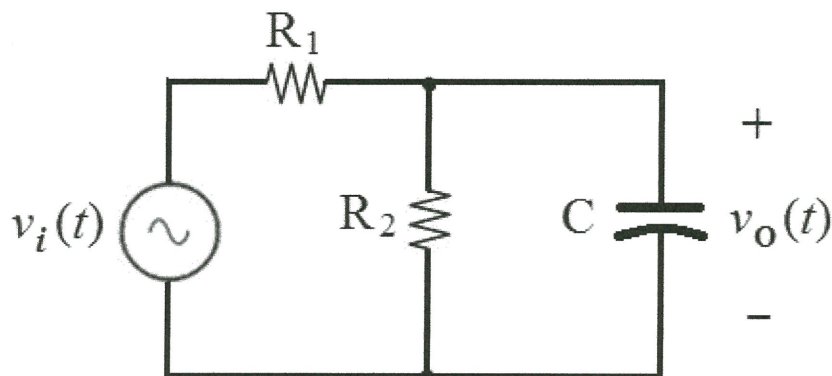


FIGURE Q4(c)

- Q5** (a) Explain briefly the importance of Fourier Transform over Fourier series. (2 marks)
- (b) The input voltage in the circuit in Figure **Q5(b)** is $v_i(t) = 30e^{-|t|}$ V.
- (i) Sketch the input signal, $v_i(t)$. By using the definition of Fourier Transform, determine the Fourier Transform of $v_i(t)$. (6 marks)
- (ii) Express the transfer function of the circuit in terms of R_1 , R_2 and C . What can be concluded from this transfer function in terms of circuit's behaviour as the frequency of the input signal is varied? (6 marks)
- (iii) Determine $v_o(t)$ if the values of resistors R_1 and R_2 are 20Ω and 80Ω respectively, while the value of capacitor C is 0.125 F. (6 marks)

**FIGURE Q5(b)**

- END OF QUESTION -