

CONFIDENTIAL



UTHM
Universiti Tun Hussein Onn Malaysia

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2013/2014**

COURSE NAME	: ELECTRICAL AND ELECTRONIC TECHNOLOGY
COURSE CODE	: BDA 14303 / BEX17003
PROGRAMME	: 1 BDA
EXAMINATION DATE	: JUNE 2014
DURATION	: 3 HOURS
INSTRUCTION	: ANSWER ALL QUESTIONS. <u>PART A:</u> MULTIPLE CHOICE QUESTION. WRITE ANSWER IN THE ANSWER SHEET (PAGE 8) <u>PART B:</u> STRUCTURED QUESTION. ANSWER IN THE PROVIDED SPACE.

THIS QUESTION PAPER CONSISTS OF NINETEEN (19) PAGES

CONFIDENTIAL

PART A: MULTIPLE CHOICE QUESTION**(1 mark each)**

Q1 An electric heater draws 10 A from a 120V line. Determine the resistance of the heater.

(a) 1200Ω (c) 120Ω


(b) 12Ω (d) 1.2Ω

Q2 A toaster is connected to a 240V line. If the resistance is 1000Ω , calculate the power consumption.

(a) $0.24W$ (c) $4.167W$

(b) $57.6W$ (d) Undetermined

Figure Q3 is for question **Q3**, **Q4** and **Q5**

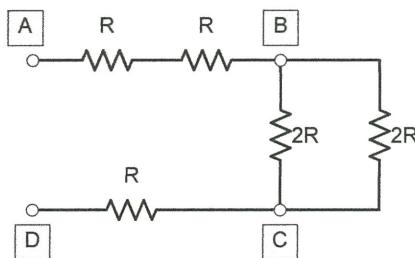**FIGURE Q3**

Q3 Determine the total resistance for the circuit in Figure Q3 at terminal A-C?

(a) $2 R$ (c) $2.5 R$

(b) $3 R$ (d) None above

Q4 Determine the total resistance for the circuit in Figure Q3 at terminal B-D?


(a) $2 R$ (c) $2.5 R$

(b) $3 R$ (d) None above

Q5 Determine the total resistance for the circuit in Figure Q3 at terminal A-D?


(a) $3 R$ (c) $3.5 R$

(b) $4 R$ (d) None above

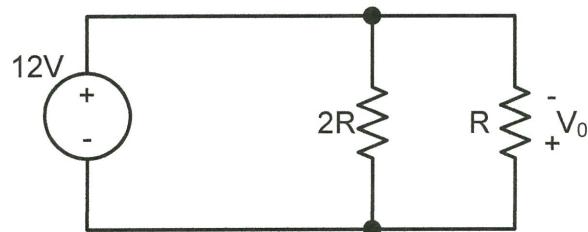**FIGURE Q6**


Q6 Determine the V_0 for circuit in Figure Q6.

- | | |
|--------------------|-------------------|
| (a) 12 V | (c) Less than 12V |
| (b) More than 12 V | (d) None above |

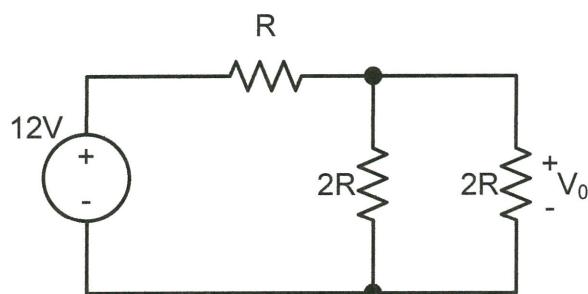**FIGURE Q7**


Q7 Determine the V_0 for circuit in Figure Q7.

- | | |
|---------|----------------|
| (a) 6 V | (c) 12V |
| (b) 3 V | (d) None above |

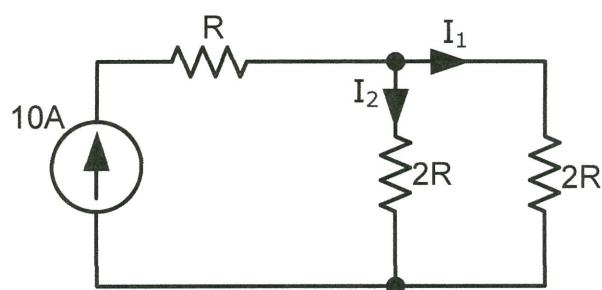**FIGURE Q8**


Q8 Determine the I_2 for circuit in Figure Q8.

- | | |
|----------|----------------|
| (a) 10 A | (c) -10 A |
| (b) 5 A | (d) None above |

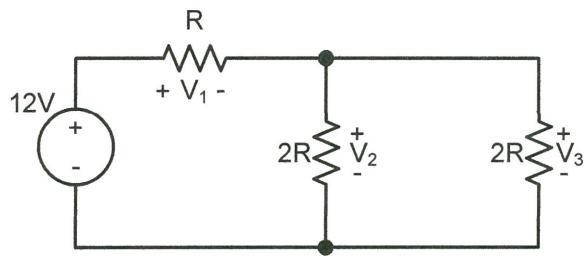**FIGURE Q9**


Q9 Deduce the relation between V_1 , V_2 and V_3 for the circuit in Figure Q9.

- | | |
|-----------------------|-----------------------|
| (a) $V_1 > V_2 > V_3$ | (c) $V_1 = V_2 = V_3$ |
| (b) $V_1 < V_2 = V_3$ | (d) None above |

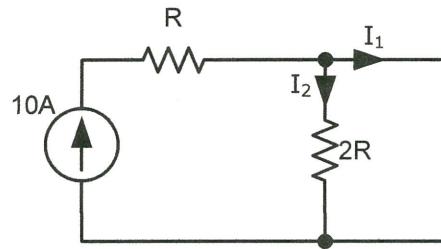**FIGURE Q10**

Q10 Determine the I_2 for circuit in Figure Q10.

- | | |
|----------|----------------|
| (a) 10 A | (c) -10 A |
| (b) 5 A | (d) None above |

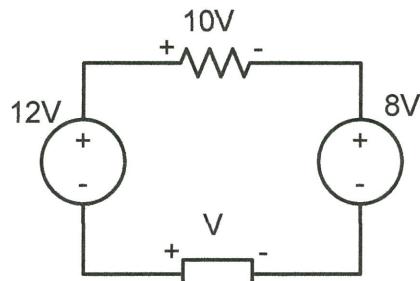**FIGURE Q11**

Q11 Determine V for circuit in Figure Q11.

- | | |
|----------|----------|
| (a) 30 V | (c) 10 V |
| (b) 14 V | (d) 6 V |

Q12 Determine which of the circuit below will give $V_{ab}=7V$.

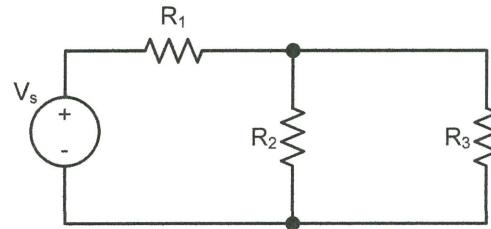
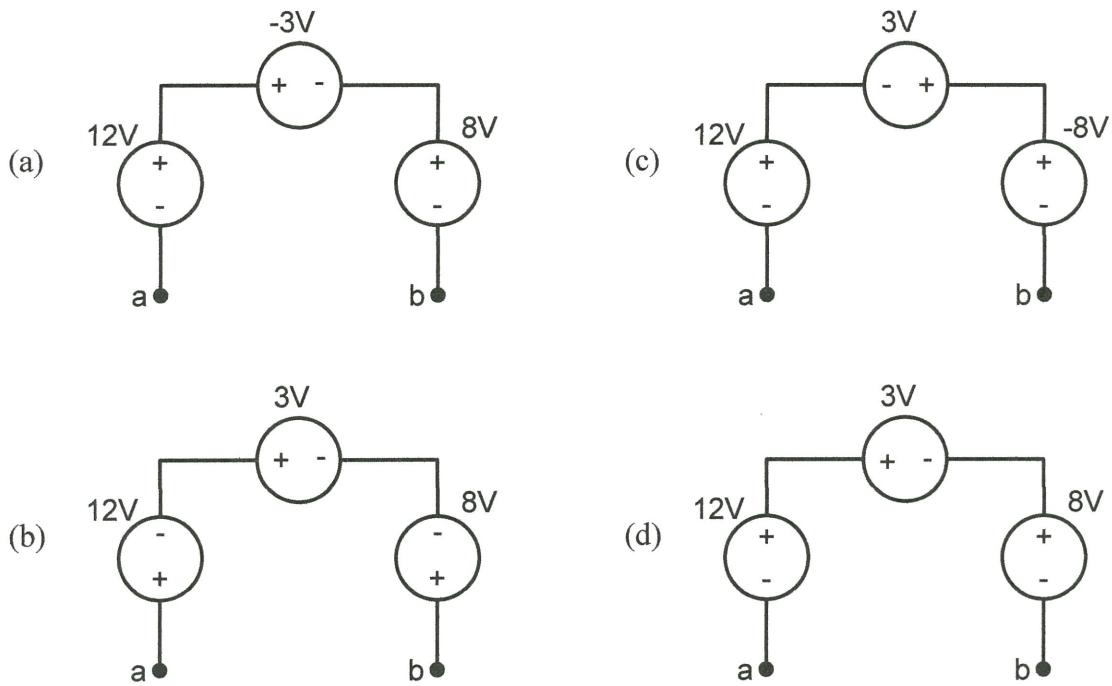


FIGURE Q13

Q13 Which of the value below will decrease if the value of R_3 for circuit in Figure Q13 decreases?

- | | |
|---------------------------|--------------------------|
| (a) Current through R_3 | (c) Voltage across R_1 |
| (b) Voltage across R_3 | (d) None above |

Q14 Which of the following is the correct method for obtaining Thevenin resistance?

- | | |
|---|---|
| (a) Both voltage and current source are 'open' | (c) Voltage source are 'open' and current source are 'shorted'. |
| (b) Voltage source are 'shorted' and current source are 'open'. | (d) Both voltage and current source are 'shorted' |

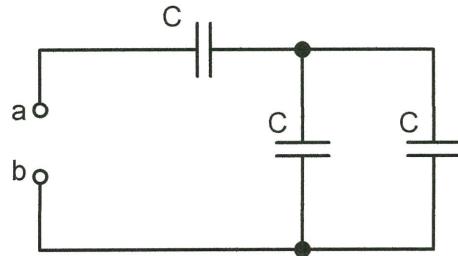


FIGURE Q15

Q15 Determine the total capacitance for circuit in Figure Q15.

- | | |
|-----------|----------------|
| (a) 0.5 C | (c) 1.5 C |
| (b) 1 C | (d) None above |

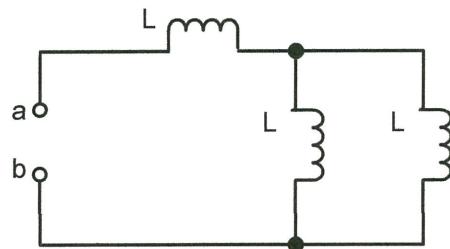


FIGURE Q16

Q16 Determine the total inductance for circuit in Figure Q16.

- | | |
|-----------|----------------|
| (a) 0.5 L | (c) 1.5 L |
| (b) 1 L | (d) None above |

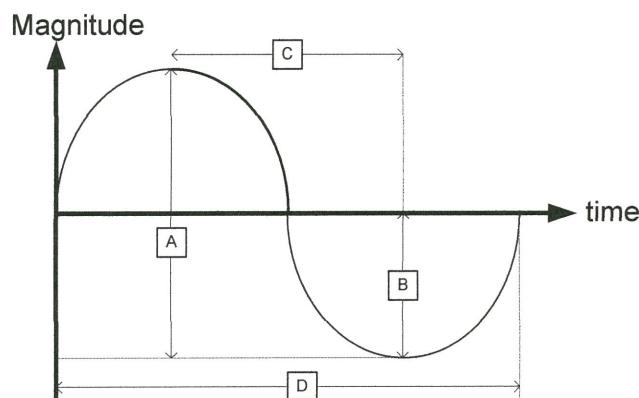


FIGURE Q17

17. Figure Q17 shows a typical alternate current waveform. Identify the amplitude.

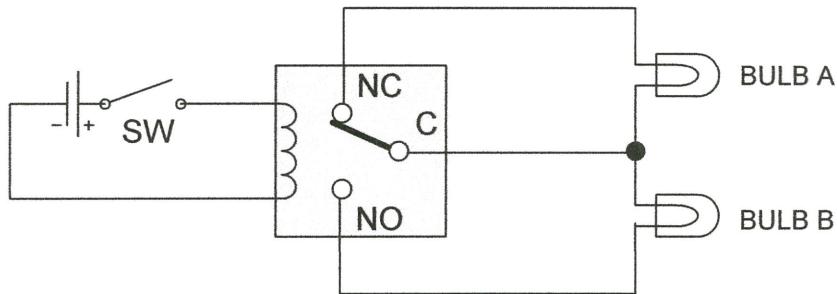


FIGURE 18

Q18 Deduce what happen to both bulb in circuit in Figure Q18 when switch ‘SW’ is closed

- | | |
|-------------------------------|-------------------------------|
| (a) Both ‘ON’ | (c) Bulb A ‘OFF’; Bulb B ‘ON’ |
| (b) Bulb A ‘ON’; Bulb B ‘OFF’ | (d) Both ‘OFF’ |

Q19 A transformer **CANNOT** be used to change the value of

- | | |
|-------------|----------------|
| (a) Voltage | (c) Current |
| (b) Power | (d) None above |

Q20 Determine which of the following electric motor is **NOT** an alternate current motor?

- | | |
|---------------------|-----------------------|
| (a) Stepper motor | (c) Synchronous motor |
| (b) Induction motor | (d) None above |

PART A (ANSWER SHEET)

Q1

Q11

Q2

Q12

Q3

Q13

Q4

Q14

Q5

Q15

Q6

Q16

Q7

Q17

Q8


Q18

Q9

Q19

Q10

Q20

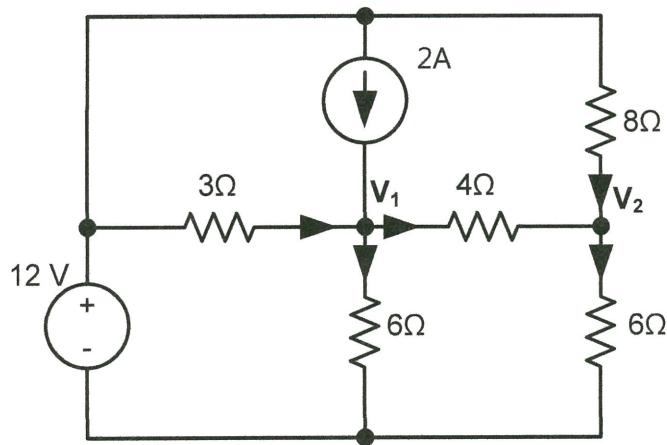PART B: STRUCTURED QUESTION**FIGURE Q21**

Q21 (a) Applying KCL at node V_1 for circuit in Figure Q21 gives:

(5 marks)

(b) Applying KCL at node V_2 for circuit in Figure Q21 gives:

(5 marks)

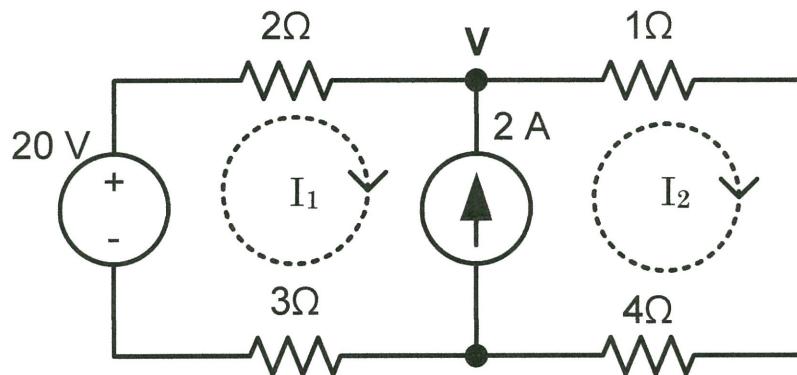


FIGURE Q22

Q22 (a) Calculate I_1 for circuit in Figure Q22.

(5 marks)

(b) Calculate V for circuit in Figure Q22.

(5 marks)

Q23 Calculate V_L for circuit in Figure Q23, Show all steps.

(10 marks)

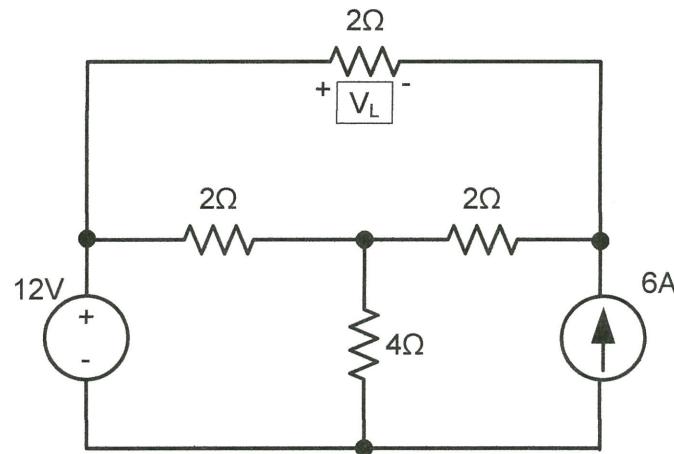


FIGURE Q23

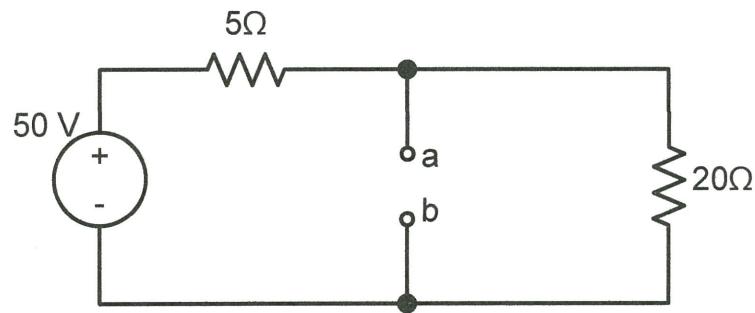


FIGURE Q24

Q24 (a) Calculate the R_{TH} across terminal a-b for circuit in Figure Q24.


(4 marks)

(b) Calculate the V_{TH} across terminal a-b for circuit in Figure Q24.

(4 marks)

(c) Calculate the value of R at terminal A-B for maximum power transfer

(2 marks)

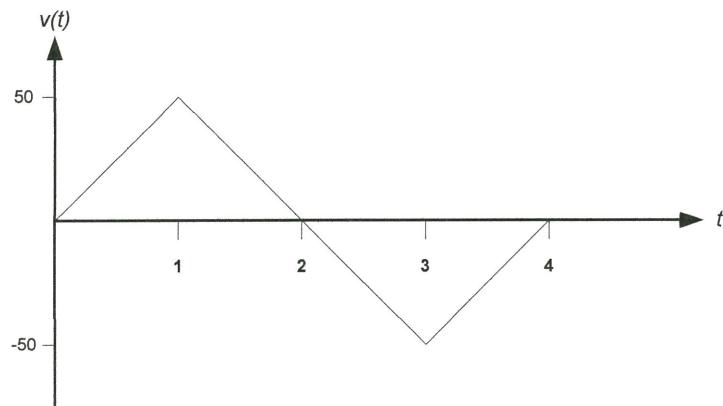**FIGURE Q25**

(10 marks)

- Q25** Determine the current through a $200 \mu\text{F}$ capacitor whose voltage is shown in Figure Q25. Sketch the current waveform.

- Q26** (a) Sketch a basic transformer structure. Identify and label the core, primary winding and secondary winding.

(2 marks)



- (b) Differentiate between a step-up transformer and a step-down transformer.

(2 marks)




- (c) An ideal transformer is rated at 2400/120V, 9.6kVA, and has 50 turns on the secondary side. Calculate:

- (i) The turn ratio
- (ii) The number of turns on the primary side
- (iii) The current rating for primary and secondary winding

(6 marks)

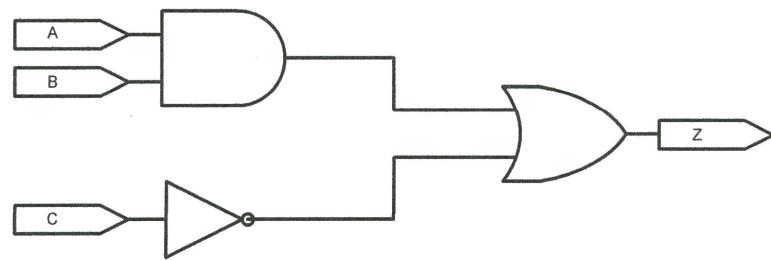

**FIGURE Q27**

- Q27** (a) Analyze the logic circuit in Figure Q27 and obtain the Boolean expression for Z
(4 marks)

- (b) Analyze the logic circuit in Figure Q27 and fill in the truth table below.
(6 marks)

A	B	C	Z

Q28 Given a sinusoid

$$v(t) = 12 \cos(50t + 10^\circ)$$

Find the:

- (a) Amplitude
- (b) Phase
- (c) Period
- (d) Frequency

(10 marks)

LIST OF FORMULA

OHMS LAW

$$V = IR$$


JOULE'S LAW

$$P = IV$$

KIRCHHOFF LAW

$$\sum_{k=1}^n i_k = 0$$

$$\sum_{v=1}^n v_k = 0$$

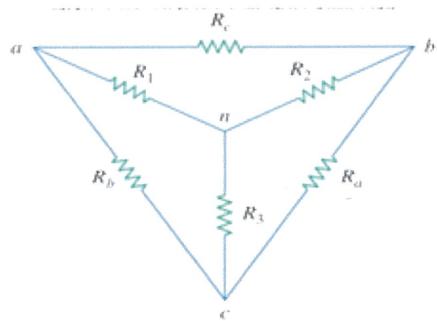WYE-DELTA TRANSFORMATION

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

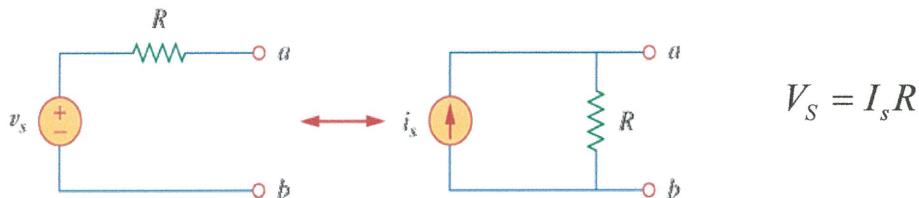SOURCE TRANSFORMATION**THEVENIN AND NORTON EQUIVALENT CIRCUIT**

$$R_{TH} = R_N$$

$$IN = \frac{V_{TH}}{R_{TH}}$$

$$P = i^2 R_L = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L \quad \text{When } R_L \neq R_{TH}$$

$$P_{\max} = \frac{V_{TH}^2}{4R_{TH}} \quad \text{When } R_L = R_{TH}$$

CAPACITOR AND INDUCTOR

$$C = \frac{\epsilon A}{d} \quad v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt + v(t_0)$$

$$i = C \frac{dv}{dt} \quad w = \frac{1}{2} Cv^2$$

$$L = \frac{N^2 \mu A}{l} \quad v = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0) \quad w = \frac{1}{2} Li^2$$

$$\tau = RC \quad \tau = \frac{L}{R}$$

PHASOR REALTIONSHIP

$$v(t+T) = v(t)$$

$$f = \frac{1}{T}$$

$$z = x + jy = r\angle\phi = r(\cos\phi + j\sin\phi)$$

ALTERNATING CURRENT POWER CALCULATION

$$P(t) = v(t)i(t) \quad \text{Instantaneous power}$$

$$P = \frac{1}{2} \operatorname{Re}[VI^*] = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad \text{Average power}$$

$$i_{RMS} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

$$P_{RMS} = I_{RMS}^2 R = \frac{V_{RMS}^2}{R}$$

TRANSFORMERS

$$\frac{V_P}{V_S} = \frac{N_P}{N_S}$$

LOGIC GATES

Name	Graphic symbol	Algebraic function	Truth table															
AND		$x = A \cdot B$ or $x = AB$	<table border="1"> <tr> <td>A</td> <td>B</td> <td>x</td> </tr> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </table>	A	B	x	0	0	0	0	1	0	1	0	0	1	1	1
A	B	x																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$x = A + B$	<table border="1"> <tr> <td>A</td> <td>B</td> <td>x</td> </tr> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </table>	A	B	x	0	0	0	0	1	1	1	0	1	1	1	1
A	B	x																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$x = A'$	<table border="1"> <tr> <td>A</td> <td>x</td> </tr> <tr> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> </tr> </table>	A	x	0	1	1	0									
A	x																	
0	1																	
1	0																	
Buffer		$x = A$	<table border="1"> <tr> <td>A</td> <td>x</td> </tr> <tr> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> </tr> </table>	A	x	0	0	1	1									
A	x																	
0	0																	
1	1																	
NAND		$x = (AB)'$	<table border="1"> <tr> <td>A</td> <td>B</td> <td>x</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </table>	A	B	x	0	0	1	0	1	1	1	0	1	1	1	0
A	B	x																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$x = (A + B)'$	<table border="1"> <tr> <td>A</td> <td>B</td> <td>x</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </table>	A	B	x	0	0	1	0	1	0	1	0	0	1	1	0
A	B	x																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
Exclusive-OR (XOR)		$x = A \oplus B$ or $x = A'B + AB'$	<table border="1"> <tr> <td>A</td> <td>B</td> <td>x</td> </tr> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </table>	A	B	x	0	0	0	0	1	1	1	0	1	1	1	0
A	B	x																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
Exclusive-NOR or equivalence		$x = (A \oplus B)'$ or $x = A'B' + AB$	<table border="1"> <tr> <td>A</td> <td>B</td> <td>x</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </table>	A	B	x	0	0	1	0	1	0	1	0	0	1	1	1
A	B	x																
0	0	1																
0	1	0																
1	0	0																
1	1	1																