

CONFIDENTIAL



UTHM
Universiti Tun Hussein Onn Malaysia

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2015/2016**

COURSE NAME : ANALOG ELECTRONICS

COURSE CODE : BEL 10203

PROGRAMME CODE : BEJ

EXAMINATION DATE : JUNE / JULY 2016

DURATION : 3 HOURS



INSTRUCTION : ANSWERS ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF **SIX (6)** PAGES

CONFIDENTIAL

- Q3** (a) Illustrate the basic construction of an *n-p-n* BJT transistors during **ACTIVE** mode. Label all the various minority and majority carriers. (3 marks)
- (b) A voltage divider bias circuit for an *n-p-n* BJT transistor having $\beta = 150$ is to be used in a Common Emitter (C-E) configuration. The quiescent point (Q-point) is to be $I_{CQ} = 1 \text{ mA}$, $V_{CEQ} = 12 \text{ V}$. The supply voltage, V_{CC} is 20 V. Assume $V_E = 0.1V_{CC}$ and $\beta R_E \geq 10R_2$.
- (i) Design the voltage divider bias circuit with bypass capacitor C_E . (Hint: Find all the resistors value). (6 marks)
 - (ii) Establish the DC load line and mark the Q point. (2 marks)
- (c) A load resistance, R_L of 10 k Ω and a source resistance, R_s , of 2.2 k Ω is applied to the Common Emitter (C-E) configuration from the circuit designed in part Q3(b). Assuming the transistor AC output resistance $r_o = \infty$,
- (i) construct the AC equivalent circuit. (2 marks)
 - (ii) calculate the input and output impedance, Z_i and Z_o . (3 marks)
 - (iii) determine the loaded voltage gain, A_v . (2 marks)
 - (iv) analyze the overall gain from the signal source to the output voltage, A_{vs} . (2 marks)

- Q4** (a) Distinguish the structure and transfer characteristics of a depletion-mode and enhancement-mode MOSFET. (4 marks)
- (b) **Figure Q4(b)(i)** shows a voltage divider bias FET circuit. Determine the required values for R_S and R_D if the FET transfer characteristics curve with the defined Q-point is as shown in **Figure Q4(b)(ii)** and the following values are given: $V_{DD} = +18$ V, $R_1 = 2.1 \text{ M}\Omega$, $R_2 = 270 \text{ k}\Omega$, and $V_{DS} = 7$ V. (6 marks)
- (c) Synthesize the effect of increasing the source resistor, R_S to the Q-point in **Figure Q4(b)(ii)**. (2 marks)
- (d) Solve and analyze the input impedance, Z_i , output impedance, Z_o , and the output voltage of the amplifier in part Q4(b) if the input signal $V_i = 2\text{mV}$ (peak) and the ac output impedance $r_d = \infty$ are applied to the circuit. (8 marks)

  **Figure Q4(b)(i)****Figure Q4(b)(ii)**

Q5 The circuit shown in **Figure Q5** has the following parameters:

$I_{DSS} = 10\text{mA}$; pinch-off voltage, $V_p = -6\text{V}$; $r_d = \infty$;
stray capacitances: $C_{gd} = 8\text{pF}$, $C_{gs} = 12\text{ pF}$, $C_{ds} = 3\text{ pF}$ and
input and output wiring capacitances: $C_{wi} = 4\text{pF}$ and $C_{wo} = 6\text{pF}$

- (a) determine the operating point of the amplifier. (6 marks)
- (b) calculate the input and output impedance. (3 marks)
- (c) find the midband voltage gain, $A_V = \frac{V_o}{V_i}$. (3 marks)
- (d) draw the low- and high-frequency AC equivalent circuits. (2 marks)
- (e) analyze the overall high cut-off frequency. (4 marks)
- (f) sketch the bode-plot of high frequency response. (2 marks)

 


Figure Q5

- END OF QUESTION -

SIGNIFICANT EQUATIONS

1 Semiconductor Diodes $W = QV$, $1 \text{ eV} = 1.6 \times 10^{-19} \text{ J}$, $I_D = I_s(e^{V_D/nV_T} - 1)$, $V_T = kT/q$, $T_K = T_C + 273^\circ$, $k = 1.38 \times 10^{-23} \text{ J/K}$, $V_K \approx 0.7 \text{ V (Si)}$, $V_K \approx 0.3 \text{ V (Ge)}$, $V_K \approx 1.2 \text{ V (GaAs)}$, $R_D = V_D/I_D$, $r_d = 26 \text{ mV}/I_D$, $r_{av} = \Delta V_d/\Delta I_d|_{\text{pt. to pt.}}$, $P_D = V_D I_D$, $T_C = (\Delta V_Z/V_Z)/(T_1 - T_0) \times 100\%/\text{^oC}$

2 Diode Applications Silicon: $V_K \approx 0.7 \text{ V}$, germanium: $V_K \approx 0.3 \text{ V}$, GaAs: $V_K \approx 1.2 \text{ V}$; half-wave: $V_{dc} = 0.318V_m$; full-wave: $V_{dc} = 0.636V_m$

3 Bipolar Junction Transistors $I_E = I_C + I_B$, $I_C = I_{C_{\text{majority}}} + I_{C_{\text{O minority}}}$, $I_C \equiv I_E$, $V_{BE} = 0.7 \text{ V}$, $\alpha_{dc} = I_C/I_E$, $I_C = \alpha I_E + I_{CBO}$, $\alpha_{ac} = \Delta I_C/\Delta I_E$, $I_{CEO} = I_{CBO}/(1 - \alpha)$, $\beta_{dc} = I_C/I_B$, $\beta_{ac} = \Delta I_C/\Delta I_B$, $\alpha = \beta/(\beta + 1)$, $\beta = \alpha/(1 - \alpha)$, $I_C = \beta I_B$, $I_E = (\beta + 1)I_B$, $P_{C_{\text{max}}} = V_{CE}I_C$

4 DC Biasing—BJTs In general: $V_{BE} = 0.7 \text{ V}$, $I_C \equiv I_E$, $I_C = \beta I_B$; fixed-bias: $I_B = (V_{CC} - V_{BE})/R_B$, $V_{CE} = V_{CC} - I_C R_C$, $I_{C_{\text{sat}}} = V_{CC}/R_C$; emitter-stabilized: $I_B = (V_{CC} - V_{BE})/(R_B + (\beta + 1)R_E)$, $R_i = (\beta + 1)R_E$, $V_{CE} = V_{CC} - I_C(R_C + R_E)$, $I_{C_{\text{sat}}} = V_{CC}/(R_C + R_E)$; voltage-divider: exact: $R_{Th} = R_1 \parallel R_2$, $E_{Th} = R_2 V_{CC}/(R_1 + R_2)$, $I_B = (E_{Th} - V_{BE})/(R_{Th} + (\beta + 1)R_E)$, $V_{CE} = V_{CC} - I_C(R_C + R_E)$, approximate: $\beta R_E \geq 10R_2$, $V_B = R_2 V_{CC}/(R_1 + R_2)$, $V_E = V_B - V_{BE}$, $I_C \equiv I_E = V_E/R_E$; voltage-feedback: $I_B = (V_{CC} - V_{BE})/(R_B + \beta(R_C + R_E))$; common-base: $I_B = (V_{EE} - V_{BE})/R_E$; switching transistors: $t_{on} = t_r + t_d$, $t_{off} = t_s + t_f$; stability: $S(I_{CO}) = \Delta I_C/\Delta I_{CO}$; fixed-bias: $S(I_{CO}) = \beta + 1$; emitter-bias: $S(I_{CO}) = (\beta + 1)(1 + R_B/R_E)/(1 + \beta + R_B/R_E)$; voltage-divider: $S(I_{CO}) = (\beta + 1)(1 + R_{Th}/R_E)/(1 + \beta + R_{Th}/R_E)$; feedback-bias: $S(I_{CO}) = (\beta + 1)(1 + R_B/R_C)/(1 + \beta + R_B/R_C)$, $S(V_{BE}) = \Delta I_C/\Delta V_{BE}$; fixed-bias: $S(V_{BE}) = -\beta/R_B$; emitter-bias: $S(V_{BE}) = -\beta/(R_B + (\beta + 1)R_E)$; voltage-divider: $S(V_{BE}) = -\beta/(R_{Th} + (\beta + 1)R_E)$; feedback bias: $S(V_{BE}) = -\beta/(R_B + (\beta + 1)R_C)$, $S(\beta) = \Delta I_C/\Delta \beta$; fixed-bias: $S(\beta) = I_{C_1}/\beta_1$; emitter-bias: $S(\beta) = I_{C_1}(1 + R_B/R_E)/(R_1(1 + \beta_1 + R_B/R_E))$; voltage-divider: $S(\beta) = I_{C_1}(1 + R_{Th}/R_E)/(R_1(1 + \beta_1 + R_{Th}/R_E))$; feedback-bias: $S(\beta) = I_{C_1}(1 + R_B/R_C)/(R_1(1 + \beta_1 + R_B/R_C))$, $\Delta I_C = S(I_{CO}) \Delta I_{CO} + S(V_{BE}) \Delta V_{BE} + S(\beta) \Delta \beta$

5 BJT AC Analysis $r_e = 26 \text{ mV}/I_E$; CE fixed-bias: $Z_i \equiv \beta r_e$, $Z_o \equiv R_C A_v = -R_C/r_e$; voltage-divider bias: $Z_i = R_1 \parallel R_2 \parallel \beta r_e$, $Z_o \equiv R_C A_v = -R_C/r_e$; CE emitter-bias: $Z_i \equiv R_B \parallel \beta R_E$, $Z_o \equiv R_C A_v = -R_C/R_E$; emitter-follower: $Z_i \equiv R_B \parallel \beta R_E$, $Z_o \equiv r_e A_v = 1$; common-base: $Z_i \equiv R_E \parallel r_e$, $Z_o \equiv R_C A_v = R_C/r_e$; collector feedback: $Z_i \equiv r_e/(1/\beta + R_C/R_F)$, $Z_o \equiv R_C \parallel R_F$, $A_v = -R_C/r_e$; collector dc feedback: $Z_i \equiv R_{F_1} \parallel \beta r_e$, $Z_o \equiv R_C \parallel R_{F_2}$, $A_v = -(R_{F_2} \parallel R_C)/r_e$; effect of load impedance: $A_v = R_i A_{v_{NL}}/(R_L + R_o)$, $A_i = -A_v Z_i/R_L$; effect of source impedance: $V_i = R_i V_s/(R_i + R_s)$, $A_{v_s} = R_i A_{v_{NL}}/(R_i + R_s)$, $I_s = V_s/(R_s + R_i)$; combined effect of load and source impedance: $A_v = R_i A_{v_{NL}}/(R_L + R_o)$, $A_{v_s} = (R_i/(R_i + R_s))(R_L/(R_L + R_o)) A_{v_{NL}}$, $A_i = -A_v R_i/R_L$, $A_{i_s} = -A_{v_s} (R_s + R_i)/R_L$; cascode connection: $A_v = A_{v_1} A_{v_2}$; Darlington connection: $\beta_D = \beta_1 \beta_2$; emitter-follower configuration: $I_B = (V_{CC} - V_{BE})/(R_B + \beta D R_E)$, $I_C \equiv I_E \equiv \beta D I_B$, $Z_i = R_B \parallel \beta_1 \beta_2 R_E$, $A_i = \beta_D R_B/(R_B + \beta D R_E)$, $A_v \equiv 1$, $Z_o = r_{e_1}/\beta_2 + r_{e_2}$; basic amplifier configuration: $Z_i = R_1 \parallel R_2 \parallel Z_i'$, $Z_i' = \beta_1(r_{e_1} + \beta_2 r_{e_2})$, $A_i = \beta_D(R_1 \parallel R_2)/(R_1 \parallel R_2 + Z_i')$, $A_v = \beta_D R_C/Z_i'$, $Z_o = R_C \parallel r_{o_2}$; feedback pair: $I_{B_1} = (V_{CC} - V_{BE_1})/(R_B + \beta_1 \beta_2 R_C)$, $Z_i = R_B \parallel Z_i'$, $Z_i' = \beta_1 r_{e_1} + \beta_1 \beta_2 R_C$, $A_i = -\beta_1 \beta_2 R_B/(R_B + \beta_1 \beta_2 R_C)$, $A_v = \beta_2 R_C/(r_e + \beta_2 R_C) \cong 1$, $Z_o \equiv r_{e_1}/\beta_2$.

6 Field-Effect Transistors $I_G = 0 \text{ A}$, $I_D = I_{DSS}(1 - V_{GS}/V_P)^2$, $I_D = I_S$, $V_{GS} = V_P(1 - \sqrt{I_D/I_{DSS}})$, $I_D = I_{DSS}/4$ (if $V_{GS} = V_P/2$), $I_D = I_{DSS}/2$ (if $V_{GS} \approx 0.3 V_P$), $P_D = V_{DS} I_D$, $r_d = r_o/(1 - V_{GS}/V_P)^2$; MOSFET: $I_D = k(V_{GS} - V_T)^2$, $k = I_{D(\text{on})}/(V_{GS(\text{on})} - V_T)^2$

7 FET Biasing Fixed-bias: $V_{GS} = -V_{GG}$, $V_{DS} = V_{DD} - I_D R_D$; self-bias: $V_{GS} = -I_D R_S$, $V_{DS} = V_{DD} - I_D(R_S + R_D)$, $V_S = I_D R_S$; voltage-divider: $V_G = R_2 V_{DD}/(R_1 + R_2)$, $V_{GS} = V_G - I_D R_S$, $V_{DS} = V_{DD} - I_D(R_D + R_S)$; common-gate configuration: $V_{GS} = V_{SS} - I_D R_S$, $V_{DS} = V_{DD} + V_{SS} - I_D(R_D + R_S)$; special case: $V_{GS_0} = 0 \text{ V}$: $I_{L_0} = I_{DSS}$, $V_{DS} = V_{DD} - I_D R_D$, $V_D = V_{DS}$, $V_S = 0 \text{ V}$. enhancement-type MOSFET: $I_D = k(V_{GS} - V_{GS(\text{Th})})^2$, $k = I_{D(\text{on})}/(V_{GS(\text{on})} - V_{GS(\text{Th})})^2$; feedback bias: $V_{DS} = V_{GS}$, $V_{GS} = V_{DD} - I_D R_D$; voltage-divider: $V_G = R_2 V_{DD}/(R_1 + R_2)$, $V_{GS} = V_G - I_D R_S$; universal curve: $m = |V_P|/I_{DSS} R_S$, $M = m \times V_G/|V_P|$, $V_G = R_2 V_{DD}/(R_1 + R_2)$

8 FET Amplifiers $g_m = y_{fs} = \Delta I_D/\Delta V_{GS}$, $g_{m0} = 2I_{DSS}/|V_P|$, $g_m = g_{m0}(1 - V_{GS}/V_P)$, $g_m = g_{m0} \sqrt{I_D/I_{DSS}}$, $r_d = 1/y_{os} = \Delta V_{DS}/\Delta I_D|_{V_{GS}=\text{constant}}$; fixed-bias: $Z_i = R_G$, $Z_o \equiv R_D$, $A_v = -g_m R_D$; self-bias (bypassed R_S): $Z_i = R_G$, $Z_o \equiv R_D$, $A_v = -g_m R_D$; self-bias (unbypassed R_S): $Z_i = R_G$, $Z_o = R_D$, $A_v \equiv -g_m R_D/(1 + g_m R_S)$; voltage-divider bias: $Z_i = R_1 \parallel R_2$, $Z_o = R_D$, $A_v = -g_m R_D$; source follower: $Z_i = R_G$, $Z_o = R_S \parallel 1/g_m$, $A_v \equiv g_m R_S/(1 + g_m R_S)$; common-gate: $Z_i = R_S \parallel 1/g_m$, $Z_o \equiv R_D$, $A_v = g_m R_D$; enhancement-type MOSFETs: $g_m = 2k(V_{GSQ} - V_{GS(\text{Th})})$; drain-feedback configuration: $Z_i \equiv R_F/(1 + g_m R_D)$, $Z_o \equiv R_D$, $A_v \equiv -g_m R_D$; voltage-divider bias: $Z_i = R_1 \parallel R_2$, $Z_o \equiv R_D$, $A_v \equiv -g_m R_D$.

9 BJT and JFET Frequency Response $\log_{10}a = 2.3 \log_{10}\alpha, \log_{10}1 = 0, \log_{10}a/b = \log_{10}\alpha - \log_{10}b, \log_{10}1/b = -\log_{10}b$, $\log_{10}ab = \log_{10}a + \log_{10}b, G_{dB} = 10 \log_{10}P_2/P_1, G_{dBm} = 10 \log_{10}P_2/1 \text{ mW} |_{R=100 \Omega}, G_{dB} = 20 \log_{10}V_2/V_1$, $G_{dBR} = G_{dB_1} + G_{dB_2} + \dots + G_{dB_n}, P_{o_HFF} = 0.5P_{o_{mid}}$, BW = $f_1 - f_2$; low frequency (BJT): $f_{L_S} = 1/2\pi(R_s + R_i)C_S$, $f_{L_C} = 1/2\pi(R_o + R_L)C_C, f_{L_E} = 1/2\pi R_E C_E, R_e = R_E \parallel (R'_s/\beta + r_e), R'_s = R_s \parallel R_1 \parallel R_2$; FET: $f_{L_G} = 1/2\pi(R_{sig} + R_i)C_G$, $f_{L_C} = 1/2\pi(R_o + R_L)C_C, f_{L_S} = 1/2\pi R_{eq} C_S, R_{eq} = R_S \parallel 1/g_m(r_d \approx \infty \Omega)$; Miller effect: $C_{M_i} = (1 - A_v)C_f, C_{M_o} = (1 - 1/A_v)C_f$; high frequency (BJT): $f_{H_i} = 1/2\pi R_{Th_i} C_i, R_{Th_i} = R_s \parallel R_1 \parallel R_2 \parallel R_i, C_i = C_{w_i} + C_{be} + (1 - A_v)C_{bc}, f_{H_o} = 1/2\pi R_{Th_o} C_o$, $R_{Th_o} = R_C \parallel R_L \parallel r_o, C_o = C_{W_o} + C_{ce} + C_{M_o}, f_B = 1/2\pi \beta_{mid} r_e(C_{be} + C_{bc}), f_T = \beta_{mid} f_B$; FET: $f_{H_i} = 1/2\pi R_{Th_i} C_i, R_{Th_i} = R_{sig} \parallel R_G, C_i = C_{W_i} + C_{gs} + C_{M_P}, C_{M_i} = (1 - A_v)C_{gd} f_{H_o} = 1/2\pi R_{Th_o} C_o, R_{Th_o} = R_D \parallel R_L \parallel r_d, C_o = C_{W_o} + C_{ds} + C_{M_o}, C_{M_o} = (1 - 1/A_v)C_{gd}$; multistage: $f_1 = f_1/\sqrt{2^{1/n} - 1}, f_2' = (\sqrt{2^{1/n}} - 1)f_2$; square-wave testing: $f_{B_i} = 0.35/t_r, \% \text{ tilt} = P\% = ((V - V')/V) \times 100\%$, $f_{L_o} = (P/\pi)f_s$

10 Operational Amplifiers CMRR = A_d/A_c ; CMRR(log) = $20 \log_{10}(A_d/A_c)$; constant-gain multiplier: $V_o/V_1 = -R_f/R_1$; noninverting amplifier: $V_o/V_1 = 1 + R_f/R_1$; unity follower: $V_o = V_1$; summing amplifier: $V_o = -[(R_f/R_1)V_1 + (R_f/R_2)V_2 + (R_f/R_3)V_3]$; integrator: $v_o(t) = -(1/R_1 C_1) \int v_1 dt$

11 Op-Amp Applications Constant-gain multiplier: $A = -R_f/R_1$; noninverting: $A = 1 + R_f/R_1$; voltage summing: $V_o = -[(R_f/R_1)V_1 + (R_f/R_2)V_2 + (R_f/R_3)V_3]$; high-pass active filter: $f_{oL} = 1/2\pi R_1 C_1$; low-pass active filter: $f_{oH} = 1/2\pi R_1 C_1$

12 Power Amplifiers

Power in: $P_i = V_{CC} I_{CQ}$
 power out: $P_o = V_{CE} I_C = I_C^2 R_C = V_{CE}^2 / R_C \text{ rms}$
 $= V_{CE} I_C / 2 = (I_C^2 / 2) R_C = V_{CE}^2 / (2 R_C) \text{ peak}$
 $= V_{CE} I_C / 8 = (I_C^2 / 8) R_C = V_{CE}^2 / (8 R_C) \text{ peak-to-peak}$
 efficiency: $\eta = (P_o/P_i) \times 100\%$; maximum efficiency: Class A, series-fed = 25%; Class A, transformer-coupled = 50%; Class B, push-pull = 78.5%; transformer relations: $V_2/V_1 = N_2/N_1 = I_1/I_2, R_2 = (N_2/N_1)^2 R_1$; power output: $P_o = [(V_{CE_{max}} - V_{CE_{min}})(I_{C_{max}} - I_{C_{min}})]/8$; class B power amplifier: $P_i = V_{CC}[(2/\pi)I_{peak}]$; $P_o = V_L^2(\text{peak})/(2R_L)$; $\eta = (\pi/4)[V_L(\text{peak})/V_{CC}] \times 100\%$; $P_Q = P_{2Q}/2 = (P_i - P_o)/2$; maximum $P_o = V_{CC}^2/2R_L$; maximum $P_i = 2V_{CC}^2/\pi^2 R_L$; maximum $P_{2Q} = 2V_{CC}^2/\pi^2 R_L$; % total harmonic distortion (% THD) = $\sqrt{D_2^2 + D_3^2 + D_4^2 + \dots} \times 100\%$; heat-sink: $T_J = P_D \theta_{JA} + T_A, \theta_{JA} = 40^\circ\text{C/W}$ (free air); $P_D = (T_J - T_A)/(\theta_{JC} + \theta_{CS} + \theta_{SA})$

13 Linear-Digital ICs Ladder network: $V_o = [(D_0 \times 2^0 + D_1 \times 2^1 + D_2 \times 2^2 + \dots + D_n \times 2^n)/2^n] V_{ref}$
 555 oscillator: $f = 1.44(R_A + 2R_B)C$; 555 monostable: $T_{high} = 1.1R_A C$; VCO: $f_o = (2/R_1 C_1)[(V^+ - V_C)/V^+]$; phase-locked loop (PLL): $f_o = 0.3/R_1 C_1, f_L = \pm 8f_o/V, f_C = \pm (1/2\pi)\sqrt{2\pi f_L/(3.6 \times 10^3)C_2}$

14 Feedback and Oscillator Circuits $A_f = A/(1 + \beta A)$; series feedback: $Z_f = Z_s(1 + \beta A)$; shunt feedback: $Z_f = Z_s/(1 + \beta A)$; voltage feedback: $Z_{vf} = Z_o/(1 + \beta A)$; current feedback: $Z_{cf} = Z_o(1 + \beta A)$; gain stability: $dA_f/A_f = 1/(1 + \beta A)(dA/A)$; oscillator: $\beta A = 1$; phase shift: $f = 1/2\pi RC\sqrt{6}, \beta = 1/29, A > 29$; FET phase shift: $|A| = g_m R_L, R_L = R_D r_d / (R_D + r_d)$; transistor phase shift: $f = (1/2\pi RC)[1/\sqrt{6} + 4(R_C/R)]$, $f_{fp} > 23 + 29(R_C/R) + 4(R/r_C)$; Wien bridge: $R_3/R_4 = R_1/R_2 + C_2/C_1, f_o = 1/2\pi\sqrt{R_1 C_1 R_2 C_2}$; tuned: $f_o = 1/2\pi\sqrt{LC_{eq}}, C_{eq} = C_1 C_2 / (C_1 + C_2)$, Hartley: $L_{eq} = L_1 + L_2 + 2M, f_o = 1/2\pi\sqrt{L_{eq}C}$

15 Power Supplies (Voltage Regulators) Filters: $r = V_o(\text{rms})/V_{dc} \times 100\%, \text{V.R.} = (V_{ML} - V_{FL})/V_{FL} \times 100\%, V_{dc} = V_m - V_{r(p-p)}/2, V_r(\text{rms}) = V_r(p-p)/2\sqrt{3}, V_r(\text{rms}) = (I_{dc}/4\sqrt{3})(V_{dc}/V_m)$; full-wave, light load $V_r(\text{rms}) = 2.4I_{dc}/C, V_{dc} = V_m - 4.17I_{dc}/C, r = (2.4I_{dc}CV_{dc}) \times 100\% = 2.4/R_L C \times 100\%, I_{peak} = T/T_1 \times I_{dc}$; RC filter: $V'_{dc} = R_L V_{dc} / (R + R_L), X_C = 2.653/C$ (half-wave), $X_C = 1.326/C$ (full-wave), $V'_r(\text{rms}) = (X_C/\sqrt{R^2 + X_C^2})$; regulators: $IR = (I_{ML} - I_{FL})/I_{FL} \times 100\%, V_L = V_Z(1 + R_1/R_2), V_o = V_{ref}(1 + R_2/R_1) + I_{adj}R_2$

16 Other Two-Terminal Devices Varactor diode: $C_T = C(0)/(1 + |V_r/V_T|)^n, TC_C = (\Delta C/C_o(T_1 - T_0)) \times 100\%$; photodiode: $W = hf, \lambda = \nu/f, 1 \text{ fm} = 1.496 \times 10^{-10} \text{ W}, 1 \text{ Å} = 10^{-10} \text{ m}, 1 \text{ fc} = 1 \text{ lm}/\text{ft}^2 = 1.609 \times 10^{-9} \text{ W/m}^2$

17 pnpn and Other Devices Diac: $V_{BR_1} = V_{BR_2} \pm 0.1 V_{BR_2}$; UJT: $R_{BB} = (R_{B_1} + R_{B_2})|_{I_E=0}, V_{B_{B_1}} = \sqrt{V_{B_{B_1}}|_{I_E=0}}$, $\eta = R_{B_1}/(R_{B_1} + R_{B_2})|_{I_E=0}, V_P = \eta V_{BB} + V_D$; phototransistor: $I_C = h_f I_A$; PUT: $\eta = R_{B_1}/(R_{B_1} + R_{B_2})V_P = R V_{BB} + V_D$