



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2015/2016**

COURSE NAME : ELECTRIC CIRCUIT ANALYSIS II
COURSE CODE : BEF 12503
PROGRAMME CODE : BEV
EXAMINATION DATE : JUNE / JULY 2016
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF SEVEN (7) PAGES

- Q1** (a) Define the basic of capacitor and inductor elements in electrical circuit. Describe the definitions with a proper figure and equations. (8 marks)
- (b) A 24V DC supply is connected to a passives element in the circuit as shown in **Figure Q1(b)**,
- (i) determine the current i_T and i_L , (4 marks)
 - (ii) determine the voltage across 10Ω resistor, (2 marks)
 - (iii) determine the energy stored in the capacitor and the inductor., (4 marks)
 - (iv) conclude the relationship of the energy stored in capacitor and the inductor based on the results obtained in **Q1(b)(iii)**. (2 marks)
- Q2** (a) **Figure Q2(a)** shows a capacitor, $C= 0.5\mu\text{F}$ is being charged through a $10\text{k}\Omega$ resistor from a 100V DC source.
- (i) Rewrite an expression of the current, i_C the capacitor voltage, V_C and the resistor voltage, V_R when switch S is changed from A to B. (6 marks)
 - (ii) Calculate the current flowing and the current drop rate at $t=0^+$. (4 marks)
 - (iii) Determine the capacitor voltage rise rate and the resistor voltage drop rate at $t=0^+$. (4 marks)
 - (iv) Analyze the energy stored by the capacitor when it is fully charged. (2 marks)
 - (v) Based on the results in **Q2(a)(i)**, describe an expression of i_C , V_C and V_R when switch S is changed from B to C. (4 marks)

- **Q3** (a) A series circuit consists of 50Ω resistor, an inductor of 0.5 H , and a capacitor of $250 \mu\text{F}$ are connected to a 240 V , 50 Hz single-phase supply.
- (i) Sketch the phasor domain circuit. (4 marks)
 - (ii) Calculate the impedance, Z of the circuit. (3 marks)
 - (iii) Analyze the voltage source, V_s , voltage drop across resistor V_R , V_L and V_C of the circuit. (8 marks)
 - (iv) Construct the phase angle of the circuit. (3 marks)
 - (v) Conclude the relationship of phasor current and the voltage supply based on the result obtained in **Q3(a)(iv)**. (2 marks)
- Q4** (a) A single-phase sinusoidal AC voltage supply is defined as $v_s(t) = 10 \sin(1000t)$ as shown in **Figure Q4(a)** connected to the linear circuit.
- (i) Find the complex impedance of the inductor and the capacitor. (2 marks)
 - (ii) Draw the phasor domain circuit. (3 marks)
 - (iii) Use the Voltage Divider Rule, to determine the capacitor voltage, $V_C(t)$. (2 marks)
 - (iv) Use the Ohms Law, calculate the $i_R(t)$, $i_C(t)$ and $i(t)$. (3 marks)
- (b) A single-phase sinusoidal current supply is defined as $i_s(t) = 125 \sin(100t)$ shown in **Figure Q4(b)** is connected to passive elements.
- (i) Determine the complex impedance of the inductor and the capacitor. (2 marks)
 - (ii) Construct the phasor domain circuit. (2 marks)

- (iii) Use the Current Divider Rule, find the output current $i_o(t)$. (2 marks)
- (iv) Calculate the $i_l(t)$ of the circuit. (2 marks)
- (v) Illustrate the phasor angle of the circuit. (2 marks)

Q5 (a) The purely inductor circuit as shown in **Figure Q5(a)**.

- (i) Describe an expression of $i(t)$, $v(t)$ and $p(t)$ of the circuit (3 marks)
- (ii) Illustrate the power triangle for purely inductive load. (2 marks)

(b) The AC voltage supply is defined as $v_s(t) = 100 \cos(1000t)$ V as shown in **Figure Q5(b)** is connected to R-L-C loads.

- (i) Calculate the load current, $I(\omega)$. (2 marks)
- (ii) Use the Ohms Law, find the voltage phasors, $V_R(\omega)$, $V_L(\omega)$ and $V_C(\omega)$. (3 marks)
- (iii) Compute the complex power of each elements, the source S_V , the resistor S_R , the inductor S_L and the capacitor S_C . (4 marks)
- (iv) Determine the average power for the resistor, inductor, capacitor and source, P_V . (4 marks)
- (v) Conclude the relationship of total power absorbed by all elements based on the results obtained in **Q5(b)(iii)**. (2 marks)

- END OF QUESTIONS

FINAL EXAMINATION

SEMESTER/SESSION : II / 2015/2016
COURSE : ELECTRIC CIRCUIT ANALYSIS II

PROGRAMME CODE : BEV
COURSE CODE : BEF12503

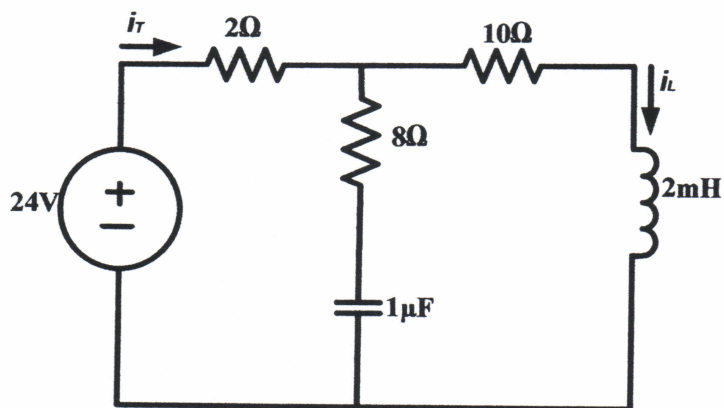


FIGURE Q1(b)

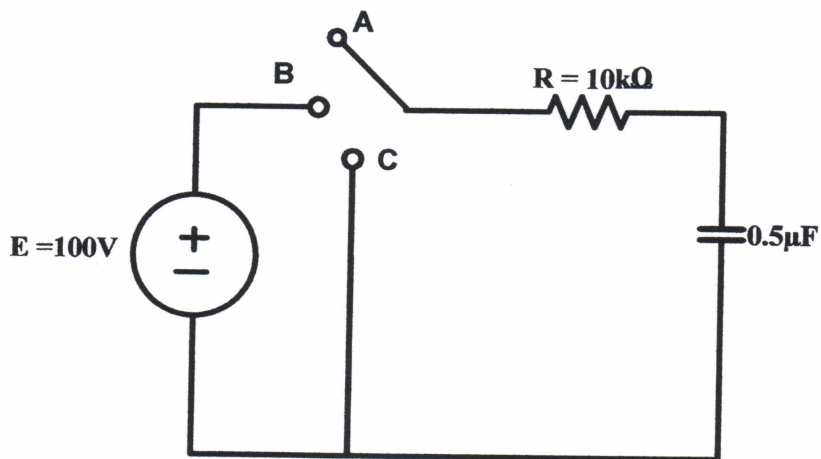


FIGURE Q2(a)

FINAL EXAMINATION

SEMESTER/SESSION : II / 2015/2016
COURSE : ELECTRIC CIRCUIT ANALYSIS II

PROGRAMME CODE : BEV
COURSE CODE : BEF12503

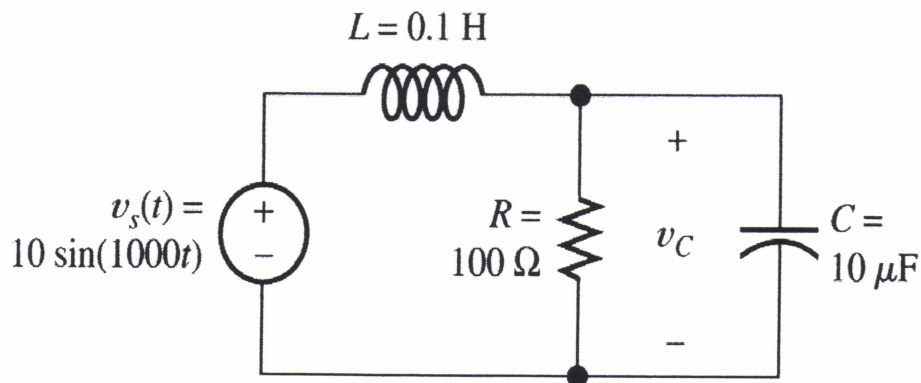


FIGURE Q4(a)

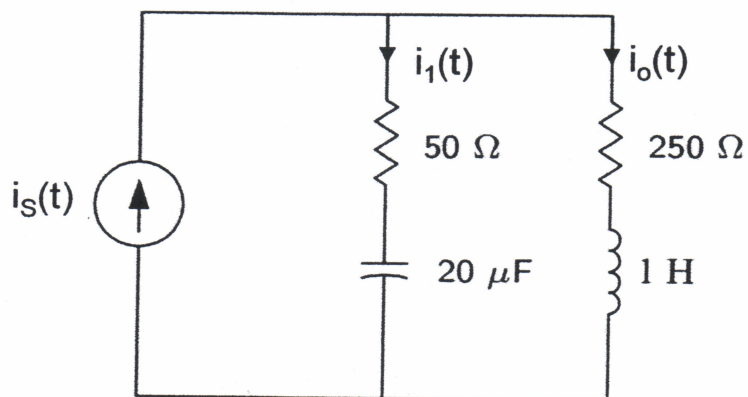


FIGURE Q4(b)

FINAL EXAMINATION -

SEMESTER/SESSION : II / 2015/2016
COURSE : ELECTRIC CIRCUIT ANALYSIS II

PROGRAMME CODE : BEV
COURSE CODE : BEF12503

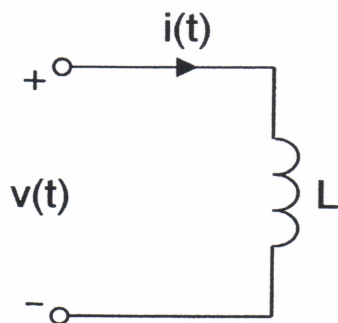


FIGURE Q5(a)

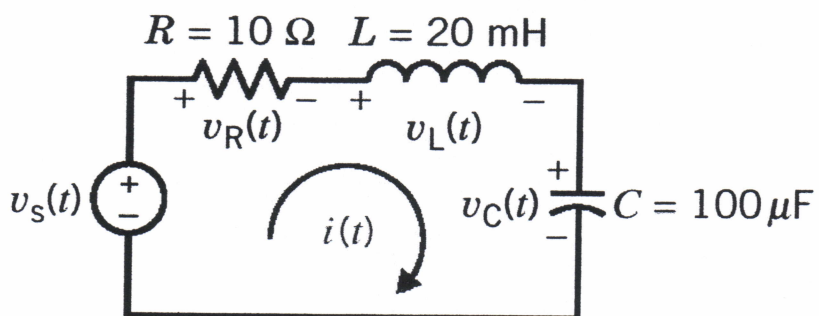


FIGURE Q5(b)