



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESSION 2015/2016**

COURSE NAME : ELECTRICAL TECHNOLOGY  
COURSE CODE : BEE 10403  
PROGRAMME CODE : BEJ / BEV  
EXAMINATION DATE : JUNE / JULY 2016  
DURATION : 3 HOURS  
INSTRUCTION : ANSWERS ALL QUESTIONS

DR. DIRMAN HANAFI  
Penyerasan  
Tahap Kejuruteraan Mechatronik & Robotik  
Jurusan Elektrik dan Elektronik  
Universiti Tun Hussein Onn Malaysia

**THIS QUESTION PAPER CONSISTS OF SIX (6) PAGES**

**Q1** Analyze the following based on the Resistor (R), Inductor (L), Capacitor (C) circuit as in **Figure Q1**.

- (a) Phase difference between current flows at  $L$  series with  $C_2$  branch, at  $R$  branch and at  $C_1$ .  
(13 marks)
- (b) Phase difference between complex power of  $C_1$ ,  $L$  series with  $C_2$  branch and  $R$  branch.  
(7 marks)

**Q2** A balanced  $120 V_{rms}$  wye connected three-phase source with positive phase sequence is connected to two balanced three-phase loads connected in parallel. Load #1 is wye connected with  $Z_Y = (30 + j40)\Omega$  and Load #2 is delta connected with  $Z_\Delta = (60 - j45)\Omega$ . The line impedance per phase is  $Z_{line} = (2 + j4)\Omega$ . (Please refer to **Figure Q2**).

- (a) Draw the per phase equivalent circuit.  
(4 marks)
- (b) Analyze the value of the total complex power supplied by the three-phase source.  
(6 marks)
- (c) Analyze the value of the total three-phase power delivered to each load.  
(10 marks)

**Q3** The magnetic circuit as shown in **Figure Q3** has the following dimensions:  $A_c = 16 \text{ cm}^2$ ,  $l = 40 \text{ cm}$ ,  $l_g = 0.5 \text{ mm}$  and  $N = 350$  turns. The core is made of a material with the  $B$ - $H$  relationship given in **Table Q3**. For  $B = 1.0 \text{ T}$  in the core.

- (a) Draw the electric equivalent circuit that represents the magnetic circuit from **Figure Q3**.  
(3 marks)
- (b) Determine the flux  $\phi$  and the total flux linkage  $\lambda$ , where  $\lambda = N\phi$ .  
(4 marks)
- (c) Determine the required current to set this flux if there is no air gap.  
(7 marks)
- (d) Identify the required current related to the presence of an air gap.  
(6 marks)

- Q4** (a) Sketch the approximate transformer model that is (please label your sketch appropriately):
- (i) Referred to the primary. (1 mark)
  - (ii) Referred to the secondary. (1 mark)
  - (iii) With no excitation branch, referred to the primary. (1 mark)
  - (iv) With no excitation branch, referred to the secondary. (1 mark)

- (b) The results of open circuit and short circuit test on a 25 kVA 440/220V 60 Hz transformer are as follow:

Open circuit test

Primary open circuited with instrumentation on the low voltage side  $V_{oc} = 220V$ ,  $I_{oc} = 9.6A$  and  $P_{oc} = 710W$ .

Short circuit test

Secondary short circuited  $V_{sc} = 42V$ ,  $I_{sc} = 57A$  and  $P_{sc} = 1030W$ .

Evaluate the parameters of the exact equivalent circuit referred to the high voltage side. (Assume  $X_p = a^2 X_s$  and  $R_p = a^2 R_s$ ).

(6 marks)

- (c) (i) Define voltage regulation (VR) of a transformer. (2 marks)
- (ii) Considering the simplified transformer equivalent circuit where the effect of excitation branch to voltage regulation is ignored, demonstrate with phasor diagrams, the effect of various power factors of the load to the VR of a transformer. (2 marks)
- (iii) A 1 $\phi$ , 10 kVA, 2200/220 V, 60 Hz transformer with approximate equivalent circuit referred to the high side, has the following parameters:  
 $R_{eq,p} = 10.4\Omega$ ,  $R_c = 48.4k\Omega$ ,  $X_{eq,p} = 31.3\Omega$ ,  $X_m = 8.94k\Omega$   
 where all the symbols carry their usual standard meanings. Determine the voltage regulation for 75% full load, 0.6 power factor lagging. Assume the load voltage to be at rated value.  
 [Hint: due to the approximation of the equivalent circuit,  $V_p = E_1$ , where  $V_p$  and  $E_1$  are the voltages at the input and across the parallel magnetizing branch ( $R_c || X_m$ ) respectively] (6 marks)

- Q5** (a) (i) Name various power losses in a DC motor. (2 marks)
- (ii) Sketch with power flow diagram for a DC generator and a DC motor (please label your diagrams appropriately). (3 marks)
- (iii) A four pole, 40 kW, DC motor operating at 1500 rpm has a generated emf of 124 V. If the speed is reduced to 80 % of its original value, and the pole flux is doubled. Develop the induced emf and frequency of the rectangular wave in the armature winding. (5 marks)
- (b) (i) Diagram equivalent circuits (with appropriate labelling) for separately excited DC motor and shunt DC motor. (5 marks)
- (ii) A 250 V shunt DC motor has an armature resistance of  $0.25 \Omega$  and a field resistance of  $125 \Omega$ . At no load, the motor takes a line current of 5.0 A while running at 1200 rpm. If the line current at full load is 52 A, calculate the full load speed. (5 marks)

**-END OF QUESTIONS -**

DR. DIRMAN HANAFI  
Lecturer  
Laboratory of Robotics & Mechatronics  
Faculty of Electrical Engineering  
Universitas Islam Sumatera Utara Medan

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2015/2016  
 COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : BEJ/BEV  
 COURSE CODE : BEE 10403

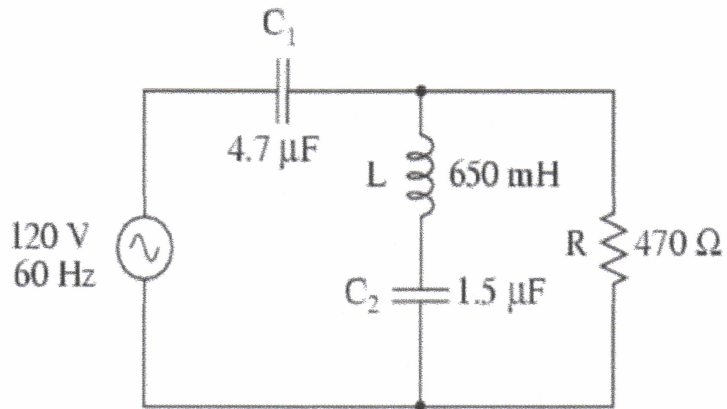


Figure Q1


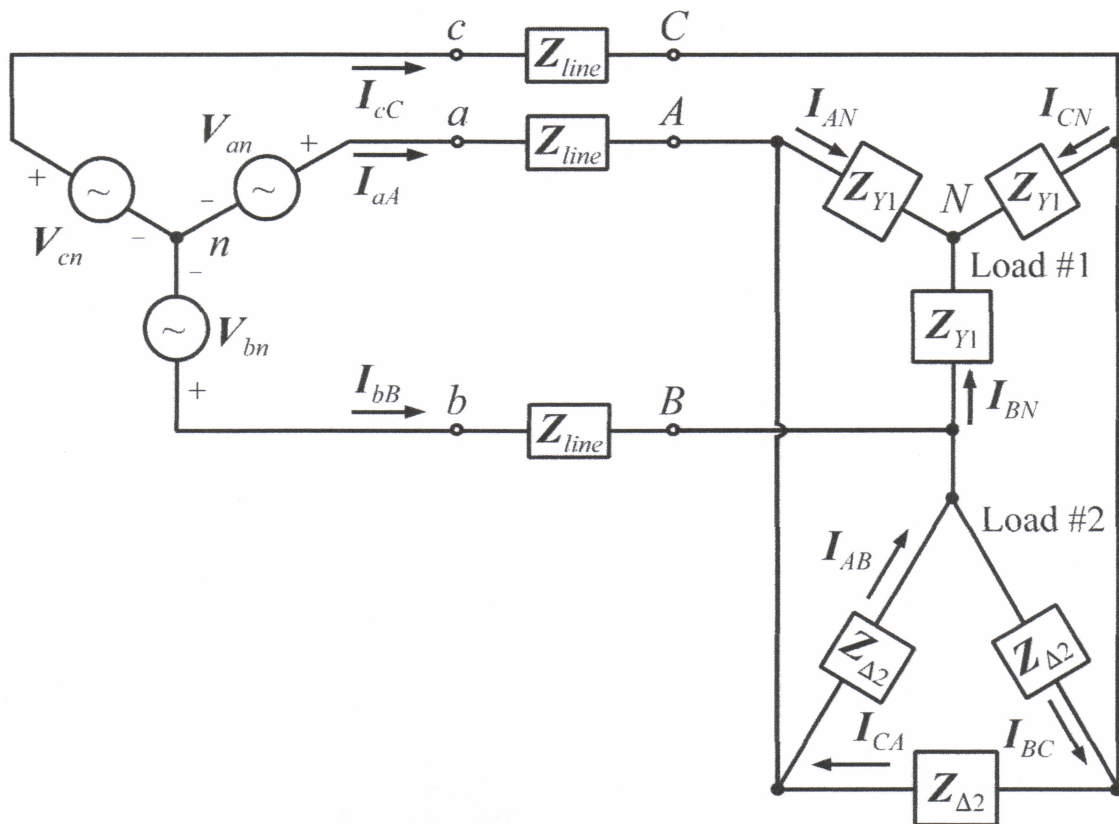


Figure Q2

**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2015/2016  
 COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : BEJ/BEV  
 COURSE CODE : BEE 10403

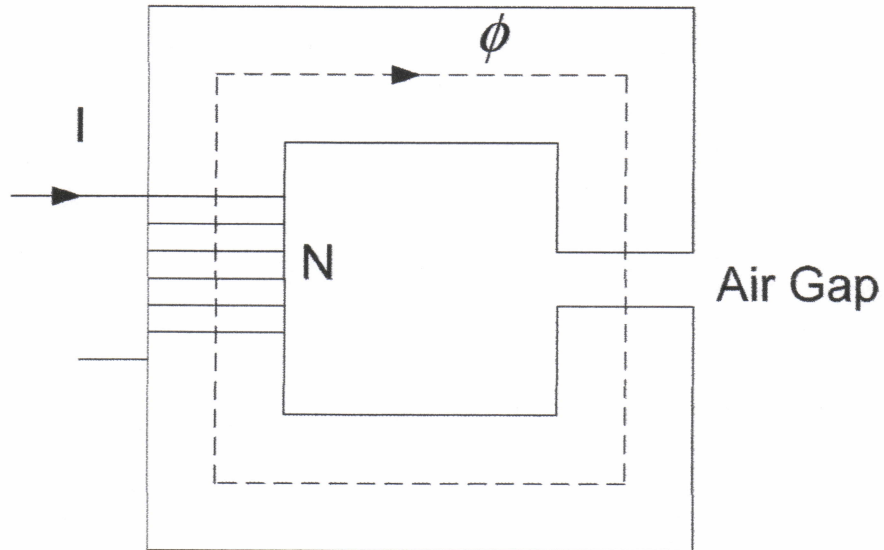

**Figure Q3**

**Table Q3**

B (Tesla)	H (A.T)
0.6	12.5
0.8	15.0
1.0	20.0
1.2	31.0
1.4	55.0

DR. DIRMAN HANARI  
 Dosen  
 Jurusan Kejuruteraan Mekanik & Robotik  
 Fakulti Kejuruteraan Elektrik dan Elektronik  
 Universiti Tun Hussein Onn Malaysia