

**CONFIDENTIAL**



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESSION 2015/2016**

COURSE NAME : ENGINEERING MATHEMATICS II  
COURSE CODE : BEE11403 / BWM10303  
PROGRAMME : BEJ / BEV  
EXAMINATION DATE : JUNE / JULY 2016  
DURATION : 3 HOURS  
INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF **EIGHT (8)** PAGES

**CONFIDENTIAL**

**Q1** (a) A  $RC$  series circuit can be described by the following differential equation

$$RC \frac{dV}{dt} + V = Ee^{-\frac{t}{RC}}$$

with initial condition  $V(0) = 1$ . If  $R = 10 \Omega$ ,  $C = 0.1 \text{ F}$ , and  $E = 15 \text{ V}$ , find the voltage  $V$  in the  $RC$  series circuit by the method of integrating factor for solving linear differential equation.

(10 marks)

(b) A  $RLC$  series circuit can be modelled by

$$L \frac{d^2i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = E'(t).$$

Given zero initial current,  $i'(0) = 4$ ,  $R = 2 \Omega$ ,  $L = 1 \text{ H}$ ,  $C = 0.1 \text{ F}$ , and  $E = \frac{37}{3} \sin 3t$ .

Find the current  $i$  in the  $RLC$  series circuit by the method of undetermined coefficient.

(15 marks)

**Q2** (a) The network circuit in **Figure Q2(a)** with  $R = 10\Omega$ ,  $L = 1.25H$ , and  $C = 0.002F$  can be modelled by the following system of first-order differential equations.

$$\begin{pmatrix} \frac{di_1}{dt} \\ \frac{di_2}{dt} \end{pmatrix} = \begin{pmatrix} -42 & -8 \\ 8 & -8 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix}$$

(i) Evaluate the eigenvalues for the above homogeneous system. (2 marks)

(ii) Find the corresponding eigenvectors for the above homogeneous system (6 marks)

(iii) Formulate the general solution for the homogenous system. (1 mark)

(iv) If  $i_1(0) = 0$ ,  $i_2(0) = 3$ , show that the currents

$$i_1 = -24t + 600t^2 - 8400t^3 + \dots \text{ and}$$

$$i_2 = 3 - 24t + 0t^2 + 1600t^3 + \dots$$

$$\text{by using } e^t = \sum_{m=0}^{\infty} \frac{t^m}{m!} = 1 + t + \frac{t^2}{2!} + \frac{t^3}{3!} + \dots$$

(3 marks)

- (b) (i) By substituting  $i_1 = a_0 + a_1t + a_2t^2 + a_3t^3 + \dots$ ,  $i_2 = b_0 + b_1t + b_2t^2 + b_3t^3 + \dots$  into the homogeneous system in Q2(a), then collecting the same power of  $t$ , solve for  $a_1, a_2, a_3, b_1, b_2, b_3$ , in terms of  $a_0$  and  $b_0$ . (8 marks)
- (ii) By substituting back  $a_1, a_2, a_3, b_1, b_2, b_3$ , that obtained in Q2 (b) (i), then deduce the general solution for the homogeneous system in Q2(a) (4 marks)
- (iii) If  $i_1(0) = 0, i_2(0) = 3$ , show that the currents  $i_1, i_2$  are same with Q2(a)(iv). (1 mark)

- Q3** (a) Consider an RC circuit shown in **Figure Q3(a)**. At time  $t > 0$  second, the switch is changed from position Q to P, held there for 2 seconds, then switch back to Q. Given that  $C = 0.1$  F,  $R = 1 \Omega$  and voltage source,  $E(t)$  of 4 V is applied to the circuit. Suppose the capacitor in the circuit initially has zero charge,  $q(0) = 0$  and  $i(0) = 0$ .
- (i) Show that the circuit can be governed by the differential equation 
$$\frac{dq}{dt} + 10q = 4 - 4H(t - 2).$$
 (3 marks)
- (i) Solve the differential equation in Q3(a)(i) by applying Laplace transform. (9 marks)
- (ii) Calculate the output voltage,  $E_{out}$  on the capacitor. (1 mark)
- (b) For the RL circuit in **Figure Q3(b)**, with  $R = 4 \Omega$ ,  $C = 2$  H and the source of this circuit is  $4e^{-3t}u(t)$  V, where  $u(t)$  is unit step function.
- (i) Solve for the current,  $i(t)$  by using Laplace transform given the initial current  $i(0) = 1$  A. (8 marks)
- (ii) Find the voltage across the capacitor and resistor by using  $i(t)$  that obtained in Q3(b) (i). (4 marks)

- Q4** (a) Given the periodic graph in Figure Q3 for the interval  $[-3\pi, 3\pi]$ .
- (i) Write down the periodic function. (3 marks)
- (ii) Explain whether the above periodic function is an odd function, even function or neither odd nor even function. (2 marks)
- (iii) Determine the Fourier series expansion to represent the above periodic function. (10 marks)
- (b) By applying Kirchhoff's voltage law, the RC-circuit shown in **Figure Q4(b)** can be governed by the first order ODE given by

$$\frac{dV_c}{dt} + 10V_c = 150,$$

where  $V_c$  is the voltage across the capacitor. Compose the general solution for the voltage across the capacitor by using Fourier transform. (10 marks)

- END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2015/2016  
 COURSE NAME : ENGINEERING  
 MATHEMATICS III

PROGRAMME : BEV, BEJ  
 COURSE CODE: BEE11403/ BWM20403

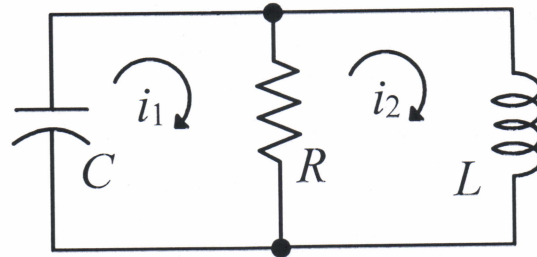


Figure Q2(a)

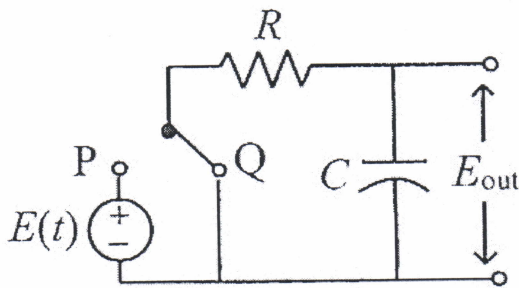


Figure Q3 (a)

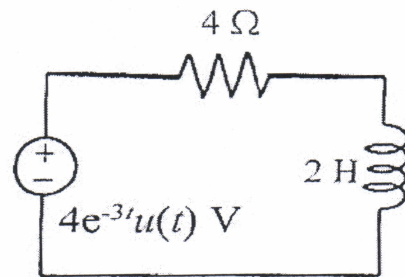


Figure Q3 (b)

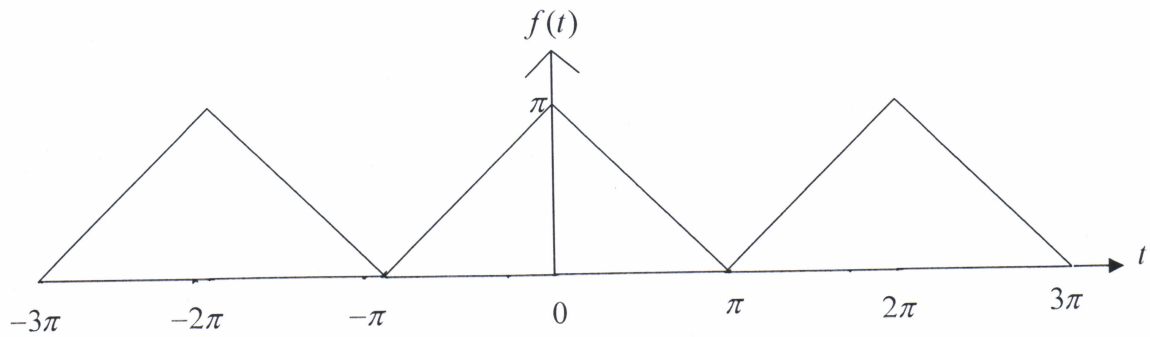


Figure Q4 (a)

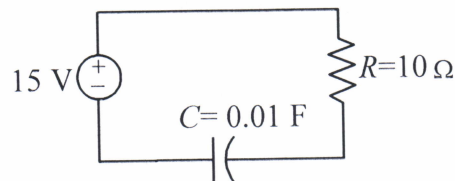


Figure Q4 (b)

**FINAL EXAMINATION**

SEMESTER/SESSION: SEM II/2015/2016  
 COURSE NAME : ENGINEERING  
 MATHEMATICS II

PROGRAMME : BEV, BEJ  
 COURSE CODE: BEE11403/ BWM10303

**FORMULAS**

**Electrical Formula**

1. Voltage drop across resistor,  $R$  (Ohm's Law):  $V_R = iR$
2. Voltage drop across inductor,  $L$  (Faraday's Law):  $V_L = L \frac{di}{dt}$
3. Voltage drop across capacitor,  $C$  (Coulomb's Law):  $V_C = \frac{1}{C} \int i dt$  or  $i = C \frac{dV_C}{dt}$   
 or  $V_C = \frac{q}{C}$
4. Linear equation:  $\frac{dy}{dt} + p(t)y = q(t)$   
 $I = e^{\int p(t)dt}$   
 $I y = \int I q(t)dt + C$

**Second-order Differential Equation**

The roots of characteristic equation and the general solution for differential equation  $ay''(t) + by'(t) + cy(t) = 0$ .

Characteristic equation: $am^2 + bm + c = 0$ .		
Case	The roots of characteristic equation	General solution
1.	Real and different roots: $m_1$ and $m_2$	$y = Ae^{m_1 t} + Be^{m_2 t}$
2.	Real and equal roots: $m = m_1 = m_2$	$y = (A + Bx)e^{mt}$
3.	Complex roots: $m_1 = \alpha + \beta i$ , $m_2 = \alpha - \beta i$	$y = e^{\alpha t} (A \cos \beta t + B \sin \beta t)$

**Homogeneous System of first-order differential equation**

$I' = AI$

**Eigenvalues**

$|A - \lambda I| = 0$

**Eigenvectors**

$(A - \lambda I)V = 0$

$I = AV_1 e^{\lambda_1 t} + BV_2 e^{\lambda_2 t}$

**FINAL EXAMINATION**

SEMESTER/SESSION: SEM II/2015/2016  
 COURSE NAME : ENGINEERING  
 MATHEMATICS II

PROGRAMME : BEV, BEJ  
 COURSE CODE: BEE11403 /BWM10303

**Laplace Transform**

$$\mathcal{L}\{f(t)\} = \int_0^{\infty} f(t)e^{-st} dt = F(s)$$

$f(t)$	$F(s)$	$f(t)$	$F(s)$
$a$	$\frac{a}{s}$	$\int_0^t f(\tau) d\tau$	$\frac{F(s)}{s}$
$e^{at}$	$\frac{1}{s-a}$	$H(t-a)$	$\frac{e^{-as}}{s}$
$\sin at$	$\frac{a}{s^2+a^2}$	$f(t-a)H(t-a)$	$e^{-as}F(s)$
$\cos at$	$\frac{s}{s^2+a^2}$	$\delta(t-a)$	$e^{-as}$
$\sinh at$	$\frac{a}{s^2-a^2}$	$f(t)\delta(t-a)$	$e^{-as}f(a)$
$\cosh at$	$\frac{s}{s^2-a^2}$	$\int_0^t f(u)g(t-u) du$	$F(s) \cdot G(s)$
$t^n,$ $n = 1, 2, 3, \dots$	$\frac{n!}{s^{n+1}}$	$y(t)$	$Y(s)$
$e^{at} f(t)$	$F(s-a)$	$y'(t)$	$sY(s) - y(0)$
$t^n f(t),$ $n = 1, 2, 3, \dots$	$(-1)^n \frac{d^n}{ds^n} F(s)$	$y''(t)$	$s^2Y(s) - sy(0) - y'(0)$

**Fourier Series**

Fourier series expansion of periodic function with period $2L/2\pi$	Half Range series
$a_0 = \frac{1}{L} \int_{-L}^L f(x) dx$	$a_0 = \frac{2}{L} \int_0^L f(x) dx$
$a_n = \frac{1}{L} \int_{-L}^L f(x) \cos \frac{n\pi x}{L} dx$	$a_n = \frac{2}{L} \int_0^L f(x) \cos \frac{n\pi x}{L} dx$
$b_n = \frac{1}{L} \int_{-L}^L f(x) \sin \frac{n\pi x}{L} dx$	$b_n = \frac{2}{L} \int_0^L f(x) \sin \frac{n\pi x}{L} dx$
$f(x) = \frac{1}{2} a_0 + \sum_{n=1}^{\infty} a_n \cos \frac{n\pi x}{L} + \sum_{n=1}^{\infty} b_n \sin \frac{n\pi x}{L}$	$f(x) = \frac{1}{2} a_0 + \sum_{n=1}^{\infty} a_n \cos \frac{n\pi x}{L} + \sum_{n=1}^{\infty} b_n \sin \frac{n\pi x}{L}$

**FINAL EXAMINATION**

SEMESTER/SESSION: SEM II/2015/2016  
 COURSE NAME : ENGINEERING  
 MATHEMATICS II

PROGRAMME : BEV, BEJ  
 COURSE CODE: BEE11403 /BWM10303

**Table of Fourier Transform**  $\mathcal{F}\{f(t)\} = \int_{-\infty}^{\infty} f(t) e^{-i\omega t} dt$

$f(t)$	$F(\omega)$	$f(t)$	$F(\omega)$
$\delta(t)$	1	$\text{sgn}(t)$	$\frac{2}{i\omega}$
$\delta(t - \omega_0)$	$e^{-i\omega_0\omega}$	$H(t)$	$\pi\delta(\omega) + \frac{1}{i\omega}$
1	$2\pi\delta(\omega)$	$e^{-\omega_0 t} H(t)$ for $\omega_0 > 0$	$\frac{1}{\omega_0 + i\omega}$
$e^{i\omega_0 t}$	$2\pi\delta(\omega - \omega_0)$	$t^n e^{-\omega_0 t} H(t)$ for $\omega_0 > 0$	$\frac{n!}{(\omega_0 + i\omega)^{n+1}}$
$\sin(\omega_0 t)$	$i\pi[\delta(\omega + \omega_0) - \delta(\omega - \omega_0)]$	$e^{-at} \sin(\omega_0 t) H(t)$ for $a > 0$	$\frac{\omega_0}{(a+i\omega)^2 + \omega_0^2}$
$\cos(\omega_0 t)$	$\pi[\delta(\omega + \omega_0) + \delta(\omega - \omega_0)]$	$e^{-at} \cos(\omega_0 t) H(t)$ for $a > 0$	$\frac{a+i\omega}{(a+i\omega)^2 + \omega_0^2}$
$\int_0^t f(u)g(t-u) du$	$F(\omega) \cdot G(\omega)$		
$\sin(\omega_0 t) H(t)$	$\frac{\pi}{2} i[\delta(\omega + \omega_0) - \delta(\omega - \omega_0)] + \frac{\omega_0}{\omega_0^2 - \omega^2}$		
$\cos(\omega_0 t) H(t)$	$\frac{\pi}{2} [\delta(\omega + \omega_0) + \delta(\omega - \omega_0)] + \frac{i\omega}{\omega_0^2 - \omega^2}$		