



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2016/2017**

TERBUKA

COURSE NAME : ELECTRICAL TECHNOLOGY
COURSE CODE : BEE 10403
PROGRAMME CODE : BEJ
EXAMINATION DATE : JUNE 2017
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF SIX (6) PAGES

- Q1** A balanced three-phase system (abc sequence) is connected in wye-wye connection with phase voltage at 100V. The line impedance and load impedance are $5 - j2 \Omega$ and $10 + j8 \Omega$, respectively.
- (a) Calculate the line current for each line. (4 marks)
 - (b) Calculate the total complex power, average power and reactive power at the source. (4 marks)
 - (c) Calculate the total complex power, average power and reactive power at the load. (4 marks)
 - (d) Calculate the total complex power, average power and reactive power at the line. (4 marks)
 - (e) Prove that the system is balanced based on your findings. (4 marks)
- Q2**
- (a) Describe the differences between permanent magnet and electromagnet. (5 marks)
 - (b) Using an appropriate diagram from a specific rule, explain how to determine the direction of current flowing in a conductor and the magnetic field. (5 marks)
 - (c) A closed magnetic circuit of cast steel contains a 7 cm long path of cross-sectional area 1.5 cm^2 and a 2 cm path of cross-sectional area of 0.5 cm^2 . A coil of 300 turns is wound around the 7 cm length of the circuit and a current of 0.5 A flows. If the relative permeability of the cast steel is 750, determine the flux density in the 7 cm path of the cast steel. (10 marks)
- Q3**
- (a) Sketch the approximate transformer model that is (please label your sketch appropriately):
 - (i) Referred to the primary. (1 mark)
 - (ii) Referred to the secondary. (1 mark)
 - (iii) With no excitation branch, referred to the primary. (1 mark)
 - (iv) With no excitation branch, referred to the secondary. (1 mark)

TERBUKA (1 mark)

- (b) A 500 kVA 30kV/240V transformer has the following parameters:

$$R_p = 0.5 \Omega \quad X_p = 0.4 \Omega \quad R_c = 20 k\Omega$$

$$R_s = 2 m\Omega \quad X_s = 4 m\Omega \quad X_m = 5 k\Omega$$

By using the equivalent circuit referred to the primary as that illustrated in **Figure Q3(b)**, compute the primary voltage of the transformer at the rated load with 0.85 lagging power factor.

(16 marks)

- Q4** (a) (i) Name various power losses in a DC machine. (2 marks)
- (ii) Suggest **two (2)** methods to increase the turning force (or torque) of a DC motor. (3 marks)
- (iii) A four pole, 40 kW, DC machine operating at 1500 rpm has a generated emf of 124 V. If the speed is reduced to 80% of its original value, and the pole flux is doubled, develop: Induced emf and frequency of the rectangular wave in the armature winding. (5 marks)
- (b) A 24 V shunt DC machine in **Figure Q4(b)** has an armature resistance of 0.5Ω and a field resistance of 100Ω . At no load, the motor takes a line current of 0.5 A while running at 2500 rpm. If the line current at full load is 4 A,
- (i) Find the field current and the induced voltage when there is no load. (5 marks)
- (ii) Find the full load speed and the speed regulation of the DC motor. (5 marks)

TERBUKA

- Q5** (a) Briefly explain about
- (i) The working principle of synchronous motor. (5 marks)
 - (ii) The differences between synchronous machine and induction machine. (3 marks)
- (b) A synchronous motor that connected to 3980 V, 3-phase line develops an excitation voltage E_o of 1790 V (line to neutral) when the DC exciting current is 25 A as illustrated in **Figure Q5(b)**. The synchronous reactance is 22Ω and the torque angle is 30° . Show the answers of the following questions in polar forms with **TWO (2)** decimal places.
- (i) Compute the voltage across the synchronous reactance. (3 marks)
 - (ii) Compute the ac line current. (2 marks)
 - (iii) Compute the power factor of the motor. (2 marks)
 - (iv) Compute the input power. (2 marks)
 - (v) Sketch the phasor diagram. (3 marks)

- END OF QUESTIONS -

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2016/2017
COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : BEJ
COURSE CODE : BEE 10403

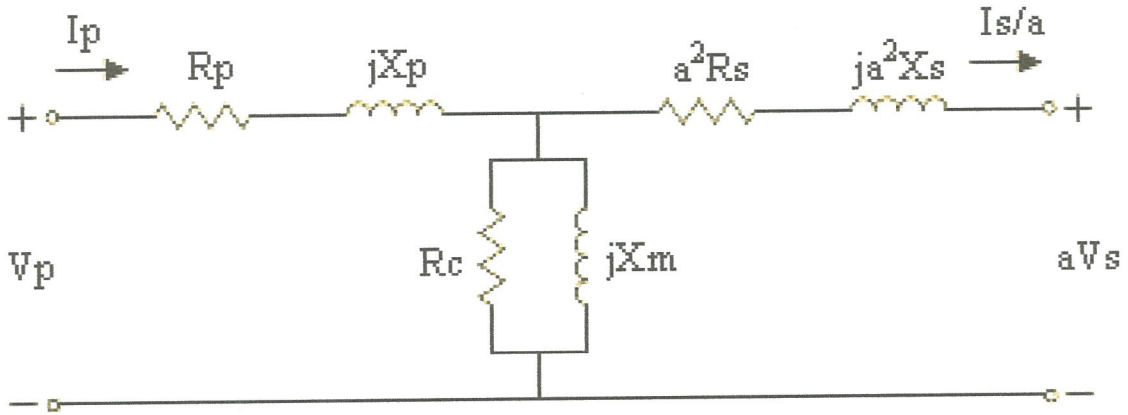


Figure Q3(b)

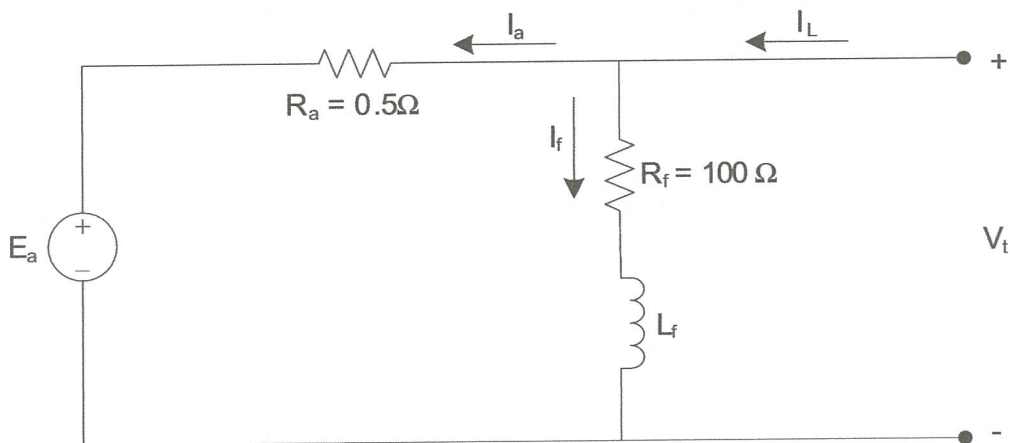


Figure Q4(b)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2016/2017
 COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : BEJ
 COURSE CODE : BEE 10403

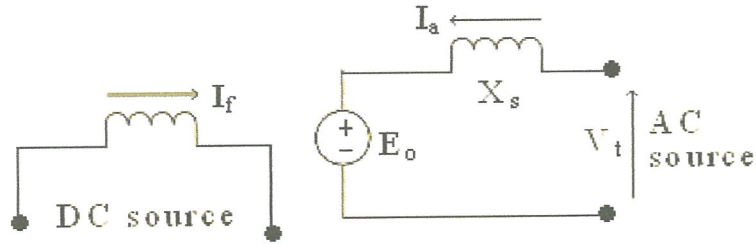


Figure Q5(b)

List of Formulae and Constant

1. $\beta = \mu H$ (unit: Tesla, T)
2. $\text{mmf (or } F_m) = NI = HI$ (unit: Ampere-turns, At)
3. $S \text{ (or } R) = l/\mu A = \text{mmf}/\phi$ (unit: Ampere-turns/weber, At/Wb)
4. $\phi_{\max} = B_{\max} a_{\text{area}}$ (unit: Weber, Wb)
5. $E = 4.44 fN\phi_m$ (unit: Volt, V)
6. $a = \frac{v_p}{v_e} = \frac{e_p}{e_s} = \frac{N_p}{N_s}$ (unit: -)
7. Permeability of vacuum, $\mu_0 = 4\pi \times 10^{-7} \text{ Wb/At.m (or H/m)}$

TERBUKA