



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2017/2018**

COURSE NAME : ELECTRICAL MACHINES
COURSE CODE : BEF 24103
PROGRAMME CODE : BEV
EXAMINATION DATE : JUNE / JULY 2018
DURATION : 3 HOURS
INSTRUCTION : ANSWERS ALL QUESTIONS

TERBUKA

THIS QUESTION PAPER CONSISTS OF FIVE (5) PAGES

- Q1** (a) List **five (5)** significance of transformer in daily life. (5 marks)
- (b) A single-phase 15,000VA, 7.2/0.24 kV distribution transformer has impedance which referred to the primary of $50 + j100 \Omega$. The R_C and X_M components of the excitation branch referred to the primary side are $350 \text{ k}\Omega$ and $70 \text{ k}\Omega$, respectively. The primary voltage of the transformer is 8000 V and the load impedance Z_L of $3 + j2 \Omega$ is connected to its secondary side.
- (i) Construct the equivalent circuit of the transformer. (3 marks)
- (ii) Determine the secondary current, secondary voltage, actual secondary voltage and voltage regulation of the transformer. (6 marks)
- (iii) Examine the phasor diagram of the transformer. (3 marks)
- (iv) Predict the output power of the transformer if the efficiency and total power loss are 95 % and 330 W, correspondingly. (3 marks)
- Q2** (a) Demonstrate the power flow and power losses diagram for AC motor. (4 marks)
- (b) Examine the generation of induced torque in current carrying loop based on a simple loop in a uniform magnetic field. (6 marks)
- (c) A ferromagnetic core shown in **Figure Q2(b)** has a number of turns, depth, and relative permeability of 3000 turns, 7 cm and 1500 H/m, respectively.
- (i) Illustrate the equivalent magnetic circuit of the core. (2 marks)
- (ii) Determine the input current if the flux produced is 0.05 Wb. (6 marks)
- (iii) Estimate the flux density at right side of the core if the number of turns is increased to 500 turns. (2 marks)

TERBUKA

- Q3** (a) State **five (5)** qualitative description of induced torque generation in induction motor. (5 marks)
- (b) A 415 V, 22 hp, 50 Hz, four-pole, Y-connected induction motor has the following impedances in ohms per phase referred to the stator (primary) circuit:
- | | | |
|----------------------|--|---------------------|
| $R_1 = 0.641 \Omega$ | $R_2 = 0.332 \Omega$ | |
| $X_1 = 1.106 \Omega$ | $X_2 = 0.464 \Omega$ | $X_M = 26.3 \Omega$ |
| Slip = 3.3% | $P_{\text{rot+core}} = 1414 \text{ W}$ | |
- (i) Calculate the synchronous speed, rotor mechanical speed, total current and resulting stator current. (6 marks)
- (ii) Compute the power factor, power converted and power output of the motor. (6 marks)
- (iii) Evaluate the induced torque, load torque and efficiency of the motor. (3 marks)
- Q4** (a) Explain briefly synchronous reactance determination in three-phase generator. (8 marks)
- (b) A 480 V, 200 kVA, 0.8 pf lagging, 50 Hz, two-pole, Y-connected synchronous generator has a synchronous reactance of 0.25Ω and an armature resistance of 0.03Ω . Its friction and windage losses are 6 kW, and its core losses are 4 kW. The field circuit has a DC voltage of 200 V, and the maximum current is 10 A. The resistance of the field circuit is adjustable over the range from 20Ω to 200Ω . The Open Circuit Characteristics (OCC) of this generator is shown in **Figure Q4 (b)**.
- (i) Choose the field current when generator is running at no load condition. (1 mark)
- (ii) Calculate the internal induced voltage and field current when generator is running at full load condition. (5 marks)
- (iii) Formulate the input pf power of the generator. (3 marks)
- (iv) Estimate the torque and efficiency of the generator. (3 marks)

TERBUKA

- Q5** (a) Explain clearly **two (2)** methods to control the speed of shunt DC motor. (10 marks)
- (b) A 200 V shunt DC motor has armature resistance, field resistance and rotational loss of 0.1Ω , of 240Ω and 236 W , respectively. The full-load line current is 9.8A when the motor running at 1450 rpm .
- (i) Calculate the armature current and the internal generated voltage. (3 marks)
- (ii) Estimate the mechanical power converted and power output. (2 marks)
- (iii) Predict the load torque of the motor. (2 marks)
- (iv) Evaluate the full-load efficiency. (2 marks)
- (v) Determine the KW rating of the motor, if a DC motor drives a 200kW generator having an efficiency of 85% . (1 marks)

- END OF QUESTIONS -

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2017/2018
COURSE NAME : ELECTRICAL MACHINES

PROGRAMME CODE : BEV
COURSE CODE : BEF 24103

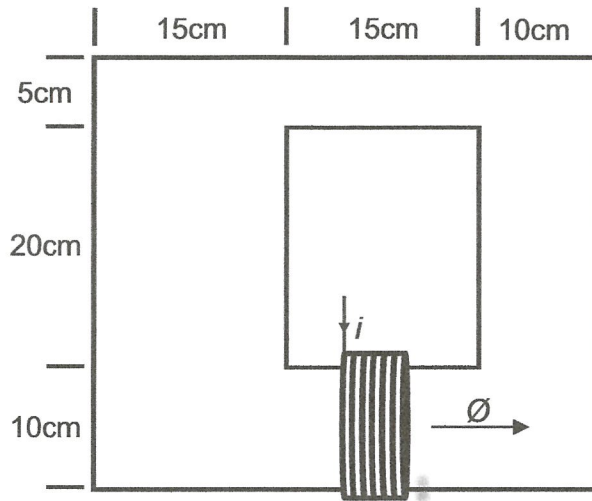


Figure Q2(b)

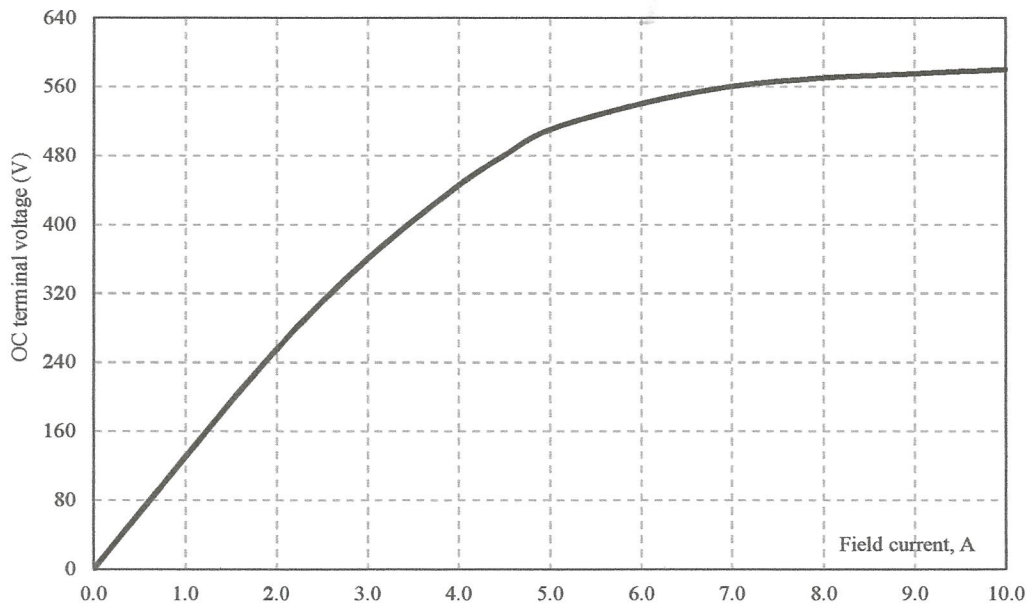


Figure Q4(b)

TERBUKA