



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2014/2015**

COURSE NAME	:	ELECTRICAL PRINCIPLES I
COURSE CODE	:	BNR 10203
PROGRAMME	:	1BND
EXAMINATION DATE	:	DECEMBER 2014 / JANUARY 2015
DURATION	:	3 HOURS
INSTRUCTION	:	ANSWER FIVE (5) QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF TWENTY TWO (22) PAGES

- Q1** (a) (i) Define current and charge? (3 marks)
- (ii) Calculate the current flows when a charge of 2 C passes through a given point each second. (1 mark)
- (iii) Determine the total charge entering a terminal between $t = 1$ s and $t = 2$ s if the current passing the terminal is $i = (3t^2 - t)$ A. (2 marks)
- (iv) A current of 3.2A flows through a conductor. Calculate how much charge passes through any cross-section of the conductor in 20 s. (2 marks)

- (b) If the current flowing through an element is given by

$$i(t) = \begin{cases} 3tA, & 0 \leq t < 6 \text{ s} \\ 18A, & 6 \leq t < 10 \text{ s} \\ -12A, & 10 \leq t < 15 \text{ s} \\ 0, & t \geq 15 \text{ s.} \end{cases}$$

Plot the charge stored in the element over $0 < t < 20$ s.

(8 marks)

- (c) Compute the power absorbed or supplied by each component of the circuit in Figure 1(c). (4 marks)

- Q2** (a) Compute the current I_A , I_B , I_C and I_D in Figure **Q2(a)**. (4 marks)
- (b) The light bulb in Figure Q2(b) is rated 120 V, 0.75 A. Calculate V_s to make the light bulb operate at the rated conditions. (6 marks)
- (c) Compute the equivalent resistance for the circuit in Figure **Q2(c)** by using *delta* network to *wye* network transformation and use it to find current i . (10 marks)

- Q3** (a) Calculate the node voltages in the circuit of Figure **Q3(a)**.
(12 marks)
- (b) By inspection, compute the mesh-current equations for the circuit in Figure **Q3(b)**.
(8 marks)
- Q4** (a) Using superposition theorem, compute V_o in the circuit of Figure **Q4(a)**.
(6 marks)
- (b) Determine v_x in the circuit of Figure **Q4(b)** using source transformation.
(7 marks)
- (c) Calculate the Norton equivalent at terminals $a-b$ of the circuit in Figure **Q4(c)**.
(7 marks)
- Q5** (a) The voltage across a $4 \mu\text{F}$ capacitor is shown in Figure **Q5(a)**. Compute the current waveform.
(5 marks)
- (b) Compute C_{eq} in the circuit of Figure **Q5(b)** if all capacitors are $4 \mu\text{F}$.
(5 marks)
- (c) If the voltage waveform in Figure **Q5(c)** is applied to a 50-mH inductor, compute the inductor current $i(t)$. Assume $i(0) = 0$.
(6 marks)
- (d) Compute the equivalent inductance looking into the terminals of the circuit in Figure **Q5(d)**.
(4 marks)
- Q6** (a) In the circuit shown in Figure **Q6(a)**.
- $$v(t) = 56e^{-200t}\text{V}, \quad t > 0$$
- $$i(t) = 8e^{-200t}\text{mA}, \quad t > 0$$

- (i) Determine the values of R and C .
 - (ii) Compute the time constant τ .
 - (iii) Determine the time required for the voltage to decay half of its initial value at $t = 0$.
(5 marks)
- (b) For the circuit in Figure Q6(b), calculate i_o for $t > 0$.
(6 marks)
- (c) Express the signals in Figure Q6(c) in terms of step functions.
(3 marks)
- (d) Calculate v_o in the circuit of Figure Q6(d) when $v_s = 6u(t)$. Assume that $v_o(0) = 1V$.
(6 marks)

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES I

COURSE CODE: BNR 10203

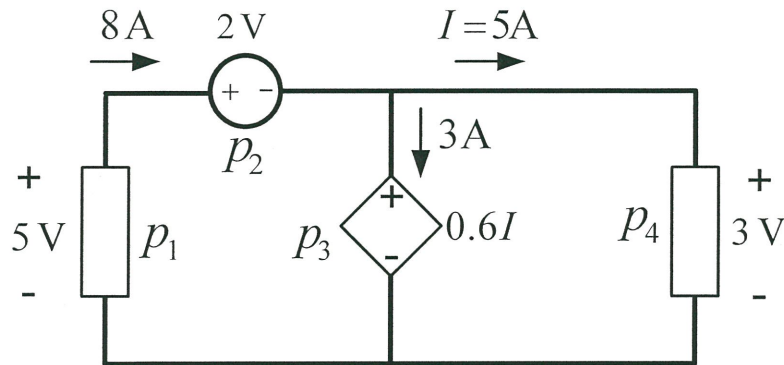


FIGURE Q1(c)

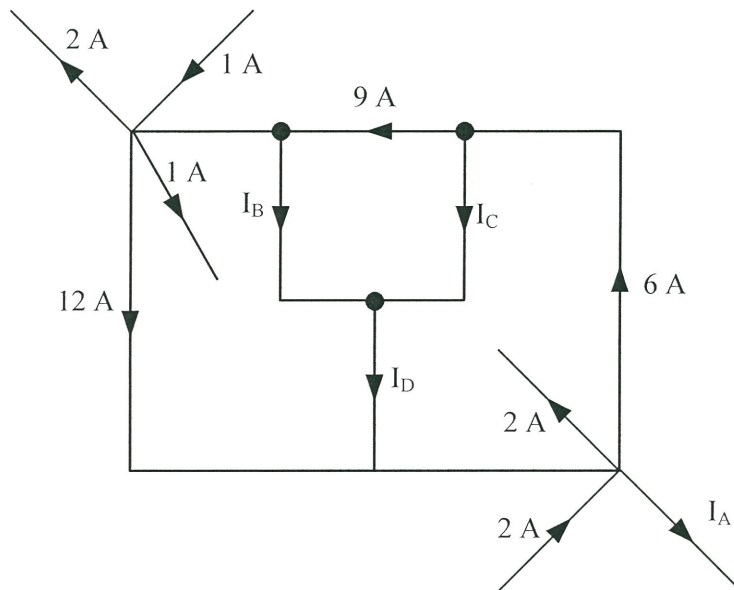


FIGURE Q2(a)

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES I

COURSE CODE: BNR 10203

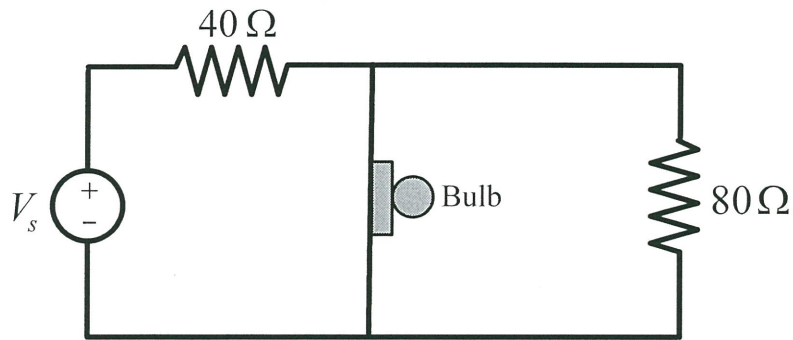


FIGURE Q2(b)

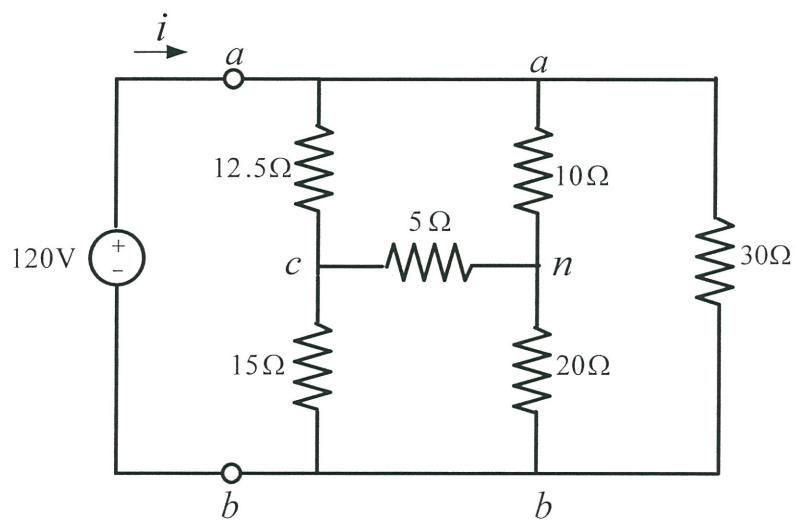


FIGURE Q2(c)

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES I

COURSE CODE: BNR 10203

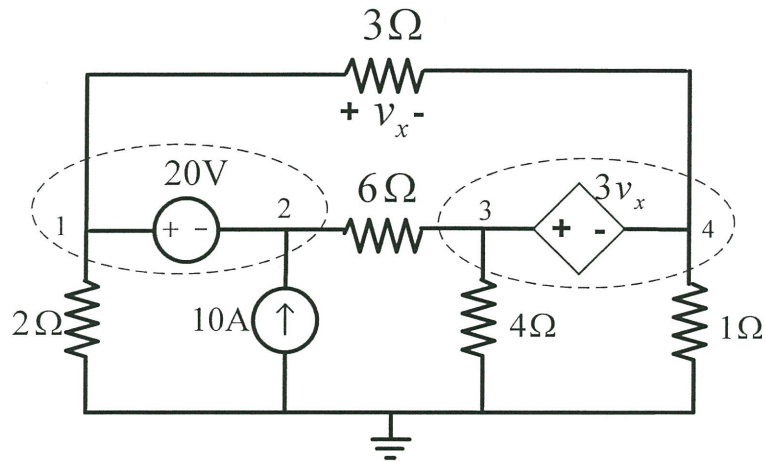


FIGURE Q3(a)

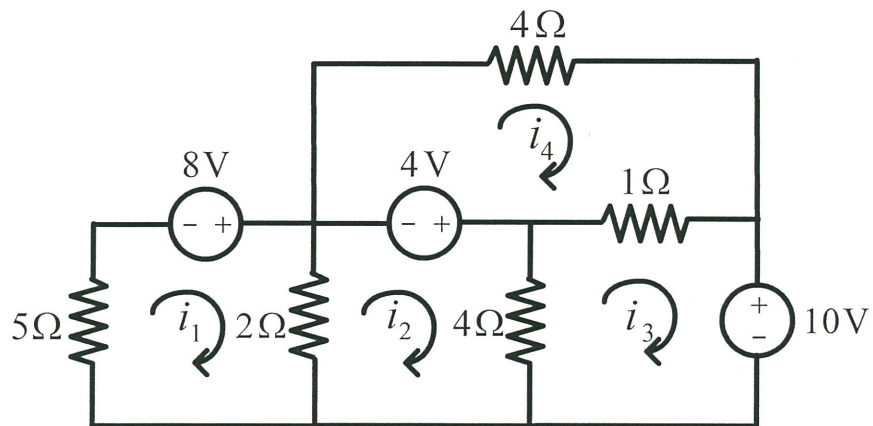


FIGURE Q3(b)

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES I

COURSE CODE: BNR 10203

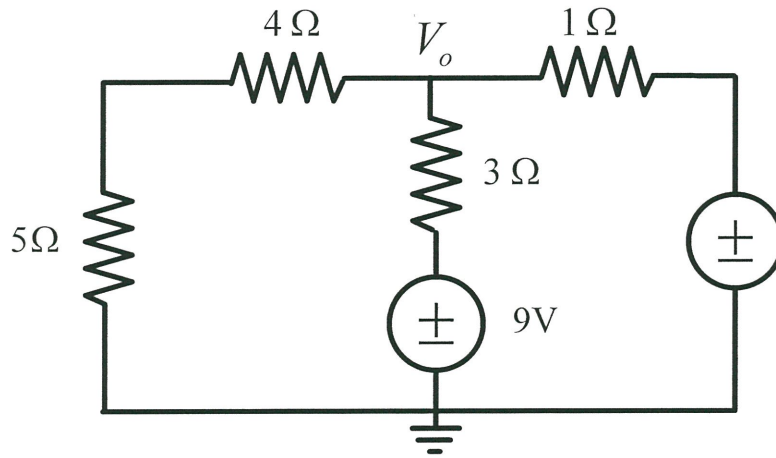


FIGURE Q4(a)

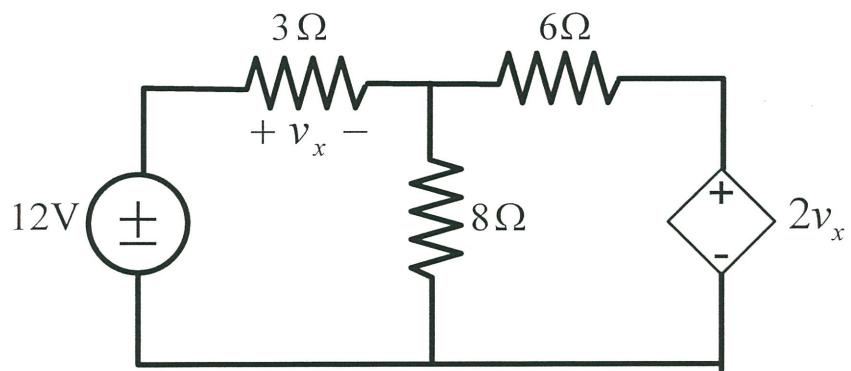


FIGURE Q4(b)

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES I

COURSE CODE: BNR 10203

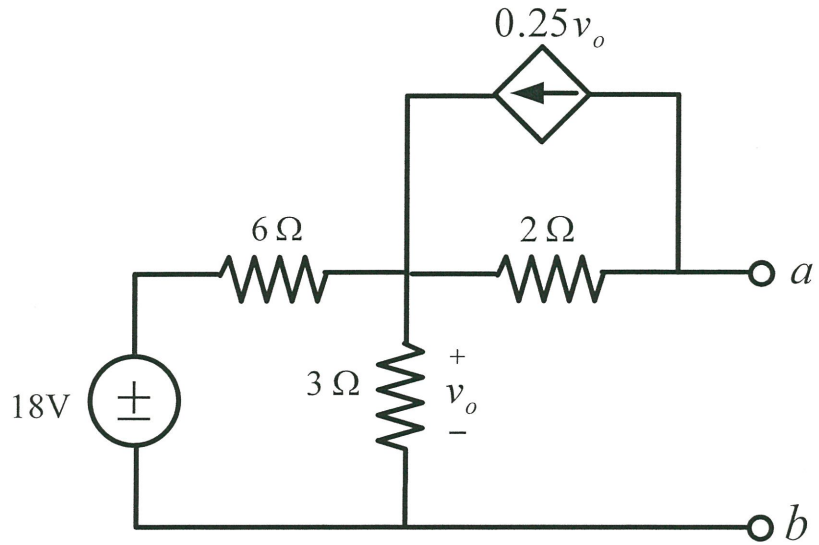


FIGURE Q4(c)

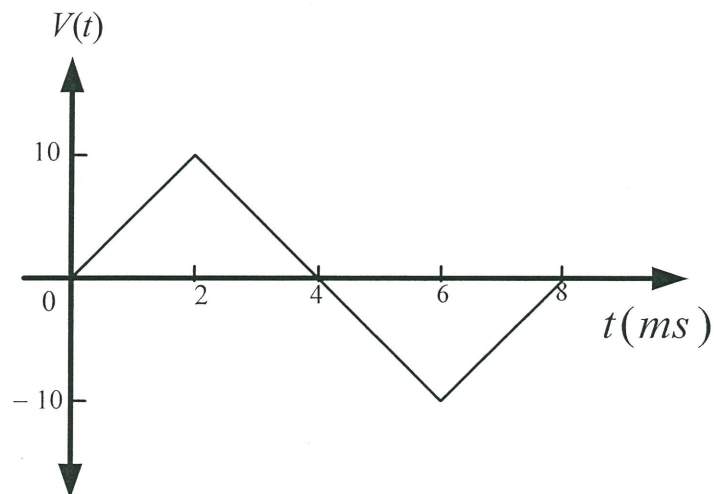


FIGURE Q5(a)

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES I

COURSE CODE: BNR 10203

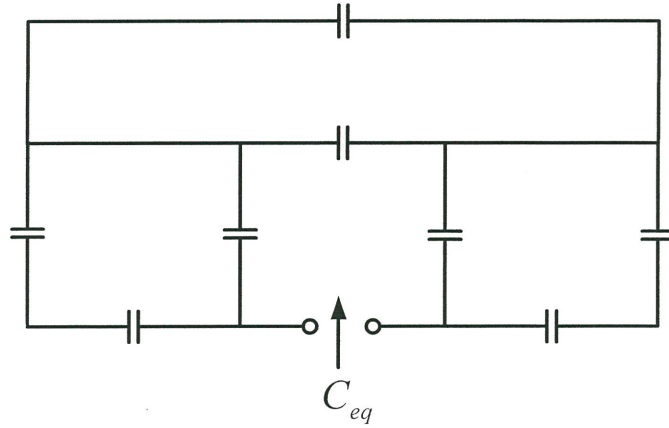


FIGURE Q5(b)

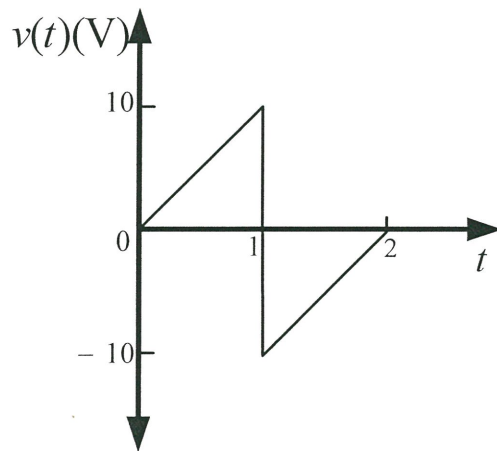


FIGURE Q5(c)

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES I

COURSE CODE: BNR 10203

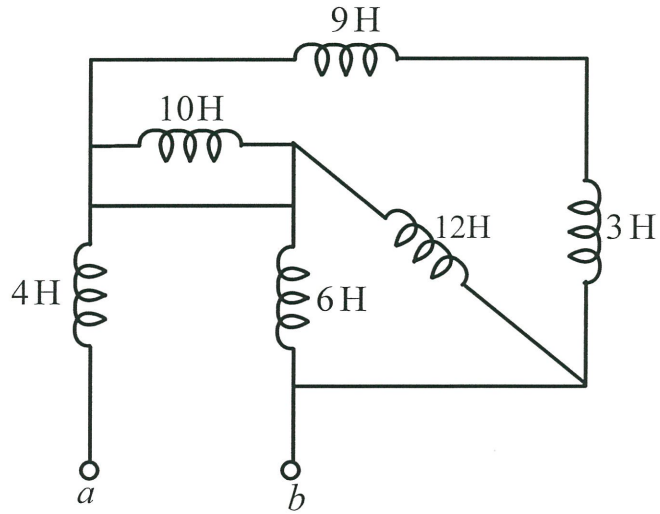


FIGURE Q5(d)

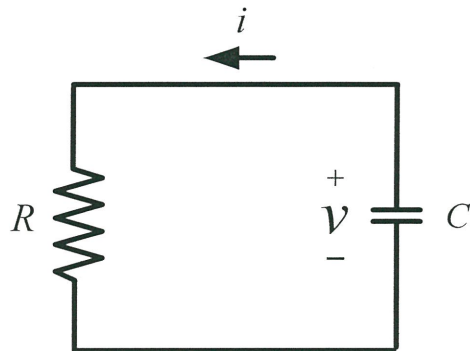


FIGURE Q6(a)

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES I

COURSE CODE: BNR 10203

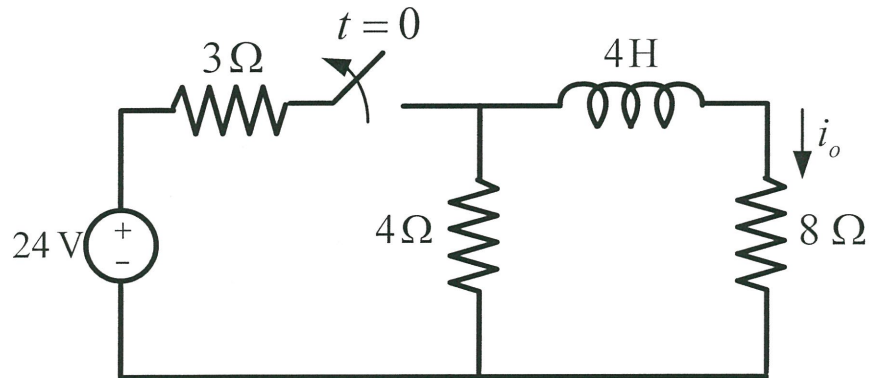


FIGURE Q6(b)

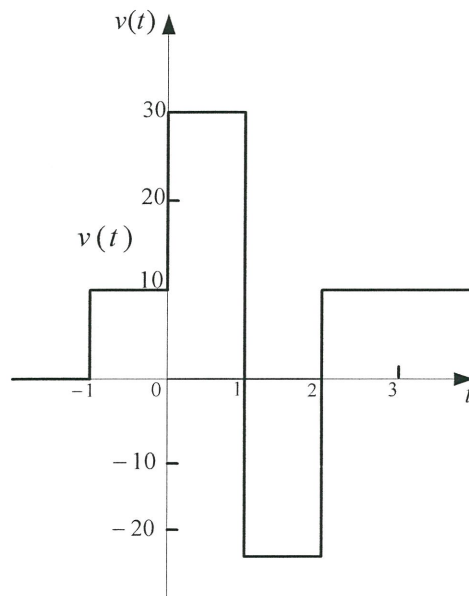


FIGURE Q6(c)


FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015

PROGRAMME : I BND

COURSE NAME : ELECTRICAL PRINCIPLES I

COURSE CODE: BNR 10203

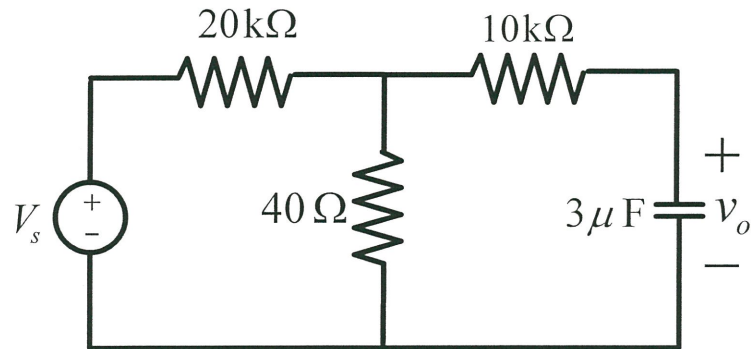**FIGURE Q6(d)**

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES I

COURSE CODE: BNR 10203

FORMULAS

The voltage division principle for two resistors in series is


$$v_1 = \frac{R_1}{R_1 + R_2} v$$

$$v_2 = \frac{R_2}{R_1 + R_2} v$$

The current division principle for two resistors in parallel is

$$i_1 = \frac{R_2}{R_1 + R_2} i$$

$$i_2 = \frac{R_1}{R_1 + R_2} i$$

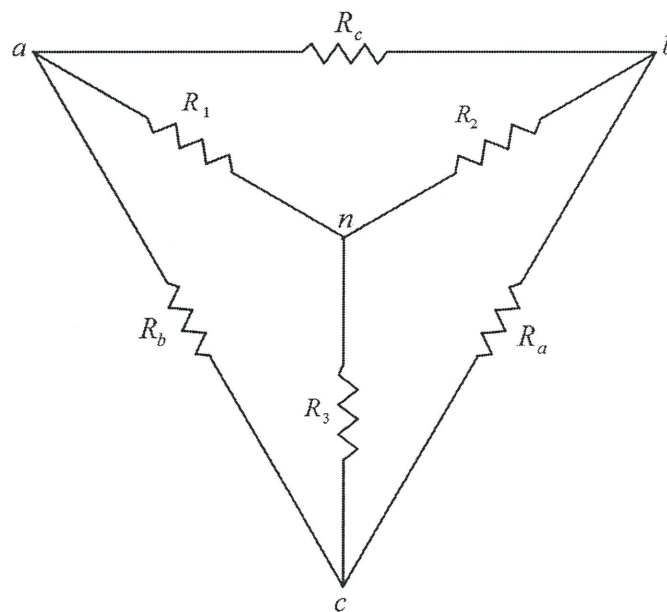

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015
 COURSE NAME : ELECTRICAL PRINCIPLES I

PROGRAMME : 1 BND
 COURSE CODE: BNR 10203

Delta to Wye-Conversion

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

Wye to Delta Conversion

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

The number of branches b , the number of nodes n , and the number of independent loops l in a network are related as

$$b = l + n - 1$$

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015
 COURSE NAME : ELECTRICAL PRINCIPLES I

PROGRAMME : 1 BND
 COURSE CODE: BNR 10203

The power delivered to the load is:

$$P = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

For maximum power dissipated in R_L , P_{max} , for a given R_{TH} , and V_{TH} ,

$$R_L = R_{TH} \quad \Rightarrow \quad P_{max} = \frac{V_{Th}^2}{4R_L}$$

CAPACITORS

The current-voltage relationship of capacitor according to above convention is

$$i = C \frac{dv}{dt}$$

$$v = \frac{1}{C} \int_{t_0}^t i dt + v(t_0)$$

The energy, w , stored in the capacitor is

$$w = \frac{1}{2} C v^2$$

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015
 COURSE NAME : ELECTRICAL PRINCIPLES I

PROGRAMME : 1 BND
 COURSE CODE: BNR 10203

INDUCTORS




The current-voltage relationship of an inductor:

$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

The energy, w , stored by an inductor:

$$w = \frac{1}{2} L i^2$$

Current and voltage relationship for R, L, C

Circuit element	Units	Voltage	Current	Power
 Resistance	ohms (Ω)	$v = Ri$ (Ohm's law)	$i = \frac{v}{R}$	$p = vi = i^2 R$
 Inductance	henries (H)	$v = L \frac{di}{dt}$	$i = \frac{1}{L} \int v dt + k_1$	$p = vi = Li \frac{di}{dt}$
 Capacitance	farads (F)	$v = \frac{1}{C} \int i dt + k_2$	$i = C \frac{dv}{dt}$	$p = vi = Cv \frac{dv}{dt}$

FINAL EXAMINATION



SEMESTER/SESSION: SEM I/2014/2015
 COURSE NAME : ELECTRICAL PRINCIPLES I

PROGRAMME : 1 BND
 COURSE CODE: BNR 10203

Important characteristics of the basic elements.


Relation	Resistor (R)	Capacitor (C)	Inductor (L)
<i>v-i:</i>	$v = iR$	$v = \frac{1}{C} \int_{t_0}^t i dt + v(t_0)$	$v = L \frac{di}{dt}$
<i>i-v:</i>	$i = \frac{v}{R}$	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int_{t_0}^t v dt + i(t_0)$
<i>p or w</i>	$p = i^2 R = \frac{v^2}{R}$	$w = \frac{1}{2} C v^2$	$w = \frac{1}{2} L i^2$
<i>Series</i>	$R_{eq} = R_1 + R_2$	$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{eq} = L_1 + L_2$
<i>Parallel</i>	$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{eq} = C_1 + C_2$	$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$
<i>At dc:</i>	Same	Open circuit	Short circuit
<i>Circuit variable that cannot change abruptly:</i>	Not applicable	<i>v</i>	<i>i</i>

An op amp integrator

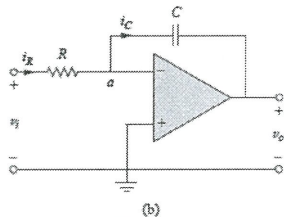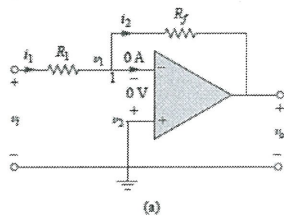

$$v_o = -\frac{1}{RC} \int_0^t v_i(t) dt$$

An op amp differentiator

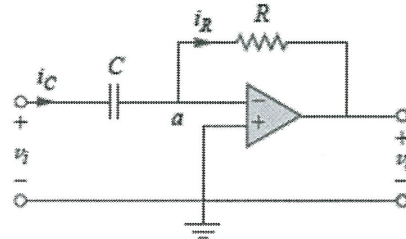


$$v_o = -RC \frac{dv_i}{dt}$$

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015
 COURSE NAME : ELECTRICAL PRINCIPLES I


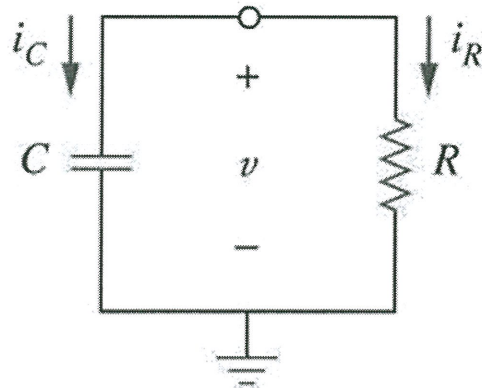
PROGRAMME : 1 BND
 COURSE CODE: BNR 10203



$$\text{KCL} \Rightarrow i_R + i_C = 0 \rightarrow \frac{v}{R} + C \frac{dv}{dt} = 0$$

A RC source-free circuit
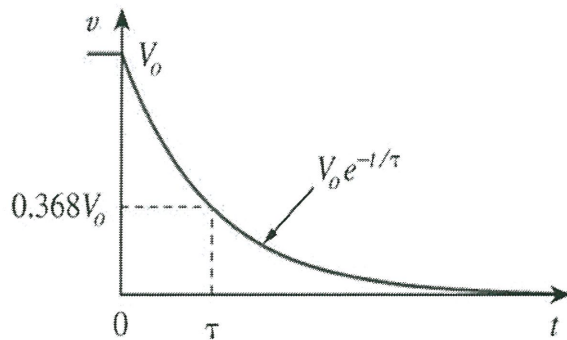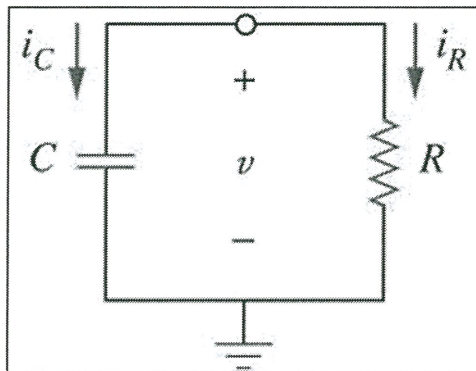
$$v(t) = V_0 e^{-t/\tau} \rightarrow \tau = RC$$



FINAL EXAMINATION


SEMESTER/SESSION: SEM I/2014/2015

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES I

COURSE CODE: BNR 10203

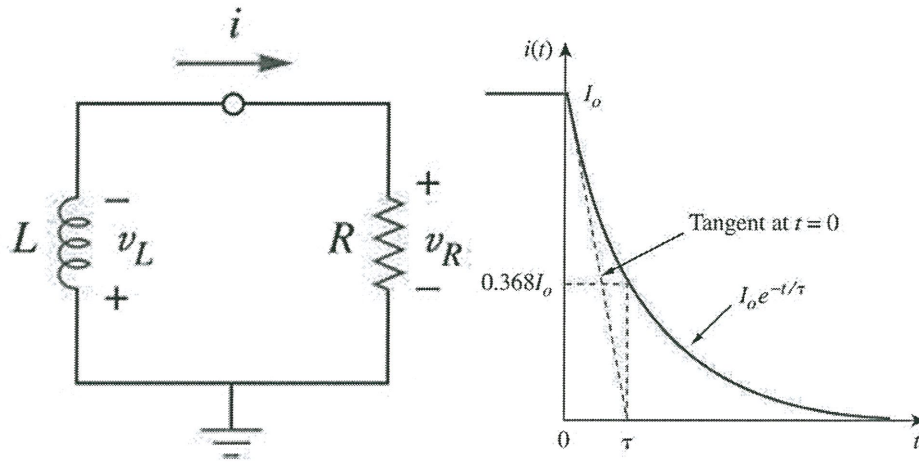A first-order RL circuit consists of an inductor L (or its equivalent) and a resistor or its equivalent



$$v_L + v_R = 0$$

$$L \frac{di}{dt} + iR = 0$$

Inductors law

Ohms law

A RL source-free circuit

$$i(t) = I_0 e^{-t/\tau}$$

$$\text{where } \tau = \frac{L}{R}$$

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015


PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES I


COURSE CODE: BNR 10203

The unit step function $u(t)$ is 0 for negative values of t and 1 for positive values of t .

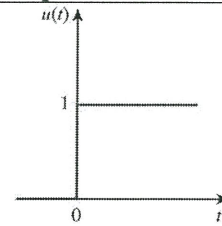
$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$


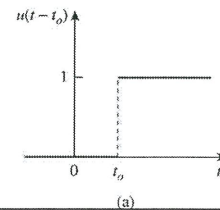
$$u(t - t_o) = \begin{cases} 0, & t < t_o \\ 1, & t > t_o \end{cases}$$



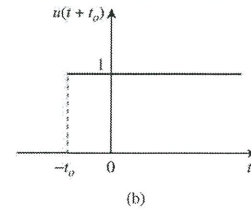
$$u(t + t_o) = \begin{cases} 0, & t < -t_o \\ 1, & t > -t_o \end{cases}$$




Represent an abrupt change for:

1. voltage source.

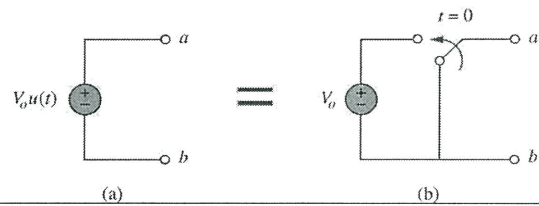

2. for current source:

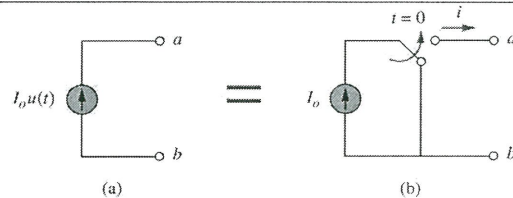

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2014/2015

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES I

COURSE CODE: BNR 10203

Summary of basic op amp circuits.

<u>Op amp circuit</u>	<u>Name/output-input relationship</u>
	<p>Inverting amplifier</p> $v_o = -\frac{R_2}{R_1}v_i$
	<p>Noninverting amplifier</p> $v_o = \left(1 + \frac{R_2}{R_1}\right)v_i$
	<p>Voltage follower</p> $v_o = v_i$
	<p>Summer</p> $v_o = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2 + \frac{R_f}{R_3}v_3\right)$
	<p>Difference amplifier</p> $v_o = \frac{R_2}{R_1}(v_2 - v_1)$