

# UNIVERSITI TUN HUSSEIN ONN MALAYSIA

# FINAL EXAMINATION **SEMESTER II SESSION 2017/2018**

COURSE NAME

: INDUSTRIAL ELECTRONIC

COURSE CODE

BND 22303 / BND 30603

PROGRAMME CODE :

BND

EXAMINATION DATE : JUNE / JULY 2018

**DURATION** 

: 3 HOURS

INSTRUCTION : ANSWERS FOUR (4) QUESTIONS ONLY



THIS QUESTION PAPER CONSISTS OF SIX (6) PAGES

- (a) For an ideal op amp, which of the following statements are not true? Q1(i)The differential voltage across the input terminals is zero. (ii) The current into the input terminals is zero. The current from the output terminal is zero. (iii) The input resistance is zero. (iv) (v)The output resistance is zero. (2 marks) Determine  $v_o$  for each of the op amp circuits in Figure Q1(b). (8 marks) Obtain  $v_o$  in the op amp circuit of Figure Q1(c). (15 marks) Describe the layer representation of a Silicon Controlled Rectifier (SCR).  $\mathbf{Q2}$ (2 marks) Illustrate the TWO (2) transistor electrical equivalent circuits of the SCR. (3 marks) Briefly explain and illustrate the characteristic curves of the SCR. (10 marks) Referring to Figure Q2(d), determine and redraw the circuit for gate triggering signal of SCR by the following applications: DC signals (i) (ii) AC signals (10 marks) Differentiate the function OR and OR LD in a ladder logic diagram construction. Q3(4 marks) Construct the ladder logic diagrams for the following Boolean logic equations:
  - (i) A = (01.02' + 03).04 + (05.06')
  - (ii) B = (07' . 08) + (08 + 09' . (10 . 11')) . 12
  - (iii) C = 13' + (14 + 15', (16 + 17'), 18 + 19), 20'

(9 marks)

(c) Construct the instruction list (mnemonic code) for the ladder diagram as shown in **Figure Q3(c)**.

(12 marks)

Q4 (a) Illustrate the basic components of Programmable Logic Controller (PLC).

(5 marks)

- (b) In the **Figure Q4(b)**, a tank will be filled with two chemicals, mixed, and then drained. When the Start button is pressed, the program will start Pump 1. Pump 1 runs for 10 seconds, filling the tank with the first chemical, then shuts off. The program then starts Pump 2 to fills the tank with second chemical until float switch is triggered then shut off automatically. At the same time, the program starts the mixer motor to mixes these two chemicals for 60 seconds. The program then opens the drain valve and starts Pump 3. Pump 3 shuts off after 15 seconds and the process stops. A manual Stop switch is also available in the system.
  - (i) Identify the input and output.

(5 marks)

(ii) Describe the process flow by motion diagram.

(5 marks)

(iii) Construct the PLC ladder diagram for the system.

(10 marks)

- Q5 (a) Briefly explain the operation of double acting cylinder with 3/2 way directional valve. (6 marks)
  - (b) A pneumatic system is operated at a pressure of 1000 kPa. Calculate the diameter of cylinder required to move a load at 500 N of force.

(5 marks)

- (c) A hydraulic cylinder is to be used to move a work parts in a manufacturing operation through a distance of 30 mm in 6 seconds. A force of 15 kN is required to move the work parts. Determine the required working pressure and hydraulic liquid flow rate if a cylinder with a piston diameter as follows:
  - (i) 50 mm.
  - (ii) 120 mm.

(7 marks)

- END OF QUESTIONS -



HAIRLULATUAN BIN INCEROR Pensyman Fakulti Teknologi <mark>6</mark> cjurute. Bon Universiti Tun Hosasin Oms Markysto

## FINAL EXAMINATION

SEMESTER/SESSION

: SEM II / 2017/2018

PROGRAMME CODE :


**BND** 

COURSE

INDUSTRIAL ELECTRONIC

COURSE CODE

BND 22303 / BND 30603

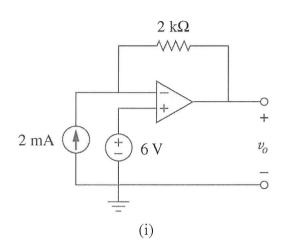

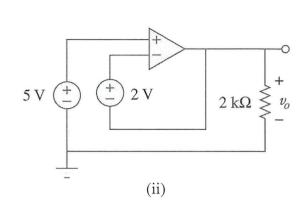


Figure Q1(b)

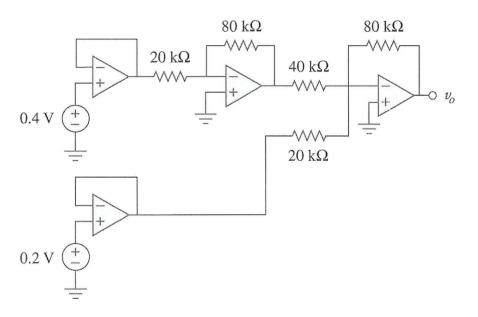


Figure Q1(c)



#### FINAL EXAMINATION

SEMESTER/SESSION

: SEM II / 2017/2018

PROGRAMME CODE :

BND

COURSE

INDUSTRIAL ELECTRONIC

COURSE CODE

BND 22303 /

BND 30603

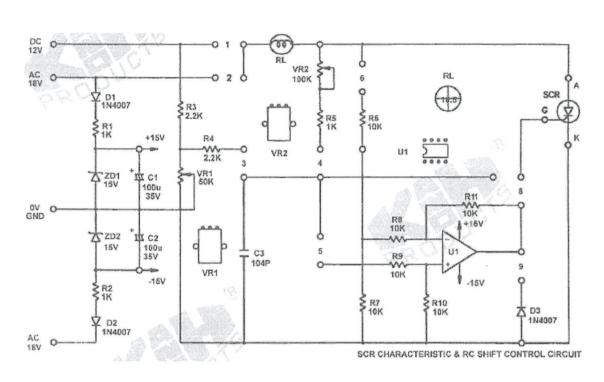


Figure Q2(d)

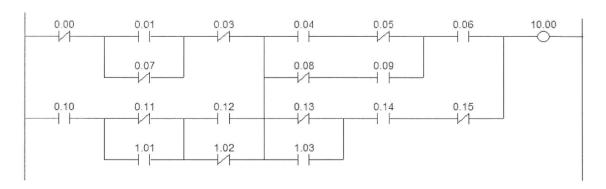


Figure Q3(c)



### FINAL EXAMINATION

SEMESTER/SESSION : SEM II / 2017/2018

PROGRAMME CODE : BND

COURSE

: INDUSTRIAL ELECTRONIC


COURSE CODE : BND 22303 /

BND 30603

**Process Control** Start

Pump 1

Pump 2

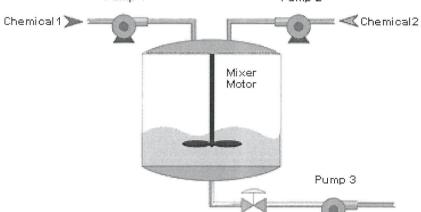

Stop

Figure Q4(b)

Drain Valve

TERBUKA