



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2012/2013**

COURSE NAME : LOGIC SYSTEMS
COURSE CODE : DAE 21603
PROGRAMME : 2 DAE
EXAMINATION DATE : OCTOBER 2012
DURATION : 2½ HOURS
INSTRUCTIONS : **ANSWER FOUR (4)**
QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF NINE (9) PAGES

- Q1**
- (a) Give the truth table of the RS flip-flop. Realize the RS flip-flop using:
 (i) NAND Gates only
 (ii) NOR Gates only.
 (6 marks)
- (b) A D flip-flop is sometimes used to delay a binary waveform. A D flip-flop with timing diagram for input data and clock input are as shown in Figure Q1(b).
 (i) Draw the Q output waveform on the space provided.
 (ii) By referring to the timing diagram, explain the operation of the D flip-flop.
 (6 marks)
- (c) Figure Q1(c) shows a 7476 JK flip-flop and timing diagram showing the clock input and two asynchronous inputs. By considering the input for both J and K are always HIGH and Q is initially LOW:
 (i) Draw the Q output waveform.
 (ii) Explain the operation of this JK flip-flop.
 (9 marks)
- (d) Show how to create the following flip flops from JK flip flop:
 (i) D flip flop
 (ii) T flip flop
 (4 marks)
- Q2**
- (a) What are the essential differences between synchronous and asynchronous counters.
 (4 marks)
- (b) (i) Construct a 4 bit ripple counter and explain its operation with the help of timing diagrams
 (ii) Convert the 4 bit ripple counter to a MOD 9 counter.
 (10 marks)
- (c) Explain the operation of the up/down counter shown in Figure Q2(c) by analysing the inputs to the clock of the flip-flop. Sketch logic and timing diagrams for both up and down sequence.
 (11 marks)

- Q3** (a) Determine the number of flip-flops needed to construct a shift register capable of storing:
- (i) a 6-bit binary number
 - (ii) decimal numbers up to 32
 - (iii) hexadecimal numbers up to F.
- (5 marks)
- (b) Figure Q3(b) shows a 4-bit serial input register and timing diagrams showing the clock and data inputs. Draw the output waveforms for four clock transitions.
- (8 marks)
- (c) With the aid of logic circuits and tables showing the sequence of states, describe the differences between a Ring counter and a Johnson counter.
- (12 marks)
-
- Q4** (a) What are the basic **five** (5) steps taken to create and load a digital circuit into a PLD?
- (5 marks)
- (b) Name **three** (3) advantages of constructing a digital circuit prototype using a PLD instead of standard logic devices.
- (3 marks)
- (c) Several types of architecture are used in PLDs. Draw the block diagram of three common types and describe their differences.
- (6 marks)
- (d) For the functions shown on the K-maps in Figure Q4(d):
- (i) Minimize the functions X, Y, Z and write down the minimized expressions.
 - (ii) Implement them on the PAL shown in Figure Q4(d)(ii). Label the inputs and outputs.
- (11 marks)

- Q5** (a) Figure Q5(a) shows a simplified view of a typical computer system.
- (i) Name the semiconductor memory devices used.
 - (ii) Explain the differences between the three storage devices.
- (8 marks)
- (b) Compare the characteristics of RAM, ROM and EPROM.
- (6 marks)
- (c) List and explain two types of RAM.
- (5 marks)
- (d) List and describe the three major operations in a flash memory.
- (6 marks)
-
- Q6** (a) Show the following connections:
- (i) Use JK flip-flops to divide a digital signal frequency by 8.
 - (ii) Use D-type flip-flops to divide a digital signal frequency by 4.
- (8 marks)
- (b) The logic diagram and Dual-In-Line Package for IC 7493 is given in Figure Q6(b). Do the following and show all steps.
- (i) Name the three standard MOD counters that can be implemented.
 - (ii) Design a 7493-based Mod-13 counter. If the input clock frequency is 2 kHz, what is the output frequency of this counter?
- (11 marks)
- (c) Determine the maximum input clock frequency (f_{max}) for the counter shown in Figure Q6(c) if the propagation delay, t_{pd} for each flip-flop is 50 ns and t_{pd} for AND gate is 20 ns. Compare this with a MOD-16 ripple counter.
- (6 marks)

FINAL EXAMINATION

SEMESTER / SESSION : SEMESTER I/ 2012/2013
 COURSE : LOGIC SYSTEMS

PROGRAMME : 2 DAE
 COURSE CODE : DAE 21603

 


Figure Q1(b)

 
 


Figure Q1(c)

FINAL EXAMINATION

SEMESTER / SESSION : SEMESTER I / 2012/2013
 COURSE : LOGIC SYSTEMS

PROGRAMME : 2 DAE
 COURSE CODE : DAE 21603

 


Figure Q2(c)

 
 


Figure Q3(b)

FINAL EXAMINATION

SEMESTER / SESSION : SEMESTER I/ 2012/2013
 COURSE : LOGIC SYSTEMS

PROGRAMME : 2 DAE
 COURSE CODE : DAE 21603

X	AB	00	01	11	10
CD		00	01	11	10
00					1
01		1	1		1
11		1	1		1
10					

Y	AB	00	01	11	10
CD		00	01	11	10
00		1	1	1	1
01			1		
11			1		1
10		1			1

Z	AB	00	01	11	10
CD		00	01	11	10
00				1	
01		1	1	1	
11		1	1	1	
10		1		1	1

Figure Q4(d)

 


Figure Q4(d)(ii)

FINAL EXAMINATION

SEMESTER / SESSION : SEMESTER I / 2012/2013
 COURSE : LOGIC SYSTEMS

PROGRAMME : 2 DAE
 COURSE CODE : DAE 21603

 


Figure Q5(a)

 


Figure Q6(b)

FINAL EXAMINATION

SEMESTER / SESSION : SEMESTER I/ 2012/2013
 COURSE : LOGIC SYSTEMS

PROGRAMME : 2 DAE
 COURSE CODE : DAE 21603

 


Figure Q6(c)