

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2012/2013**

COURSE NAME : DIGITAL ELECTRONICS
COURSE CODE : DAE 21203
PROGRAMME : 2 DAE
EXAMINATION DATE : MARCH 2013
DURATION : 2 ½ HOURS
INSTRUCTIONS : ANSWER **FOUR (4)**
QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF EIGHT (8) PAGES

- Q1** (a) Perform the following arithmetic operation. Show all your steps:
- (i) $18_{10} - 25_{10}$ using 2's complement.
 - (ii) $93_{\text{BCD}} + 15_{\text{BCD}}$.
 - (iii) Signed binary numbers: $11101101 + 00001100$. Give answer in decimal number.
- (9 marks)
- (b) Convert $3B9_{\text{HEX}}$ to base 2, 8 and 10 number systems.
- (5 marks)
- (c) Encode "A = 38/x" in ASCII code (excluding the quotes) using odd parity. The ASCII table is given in Table Q1(c).
- (8 marks)
- (d) A computer has a word length of 8 bits (including sign bit). If TWO's complement is used to represent negative numbers, what range of integers can be stored in the computer?
- (3 marks)
- Q2** (a) (i) Write the equations for DeMorgan's theorem.
- (ii) Use basic gates to illustrate the two DeMorgan's theorems
- (iii) Write the output expression for each gate.
- (6 marks)
- (b) A technician needs an AND gate to complete a design, but only NOR gates are available. Show how NOR gates can be used to implement an AND gate.
- (2 marks)
- (c) Simplify F using Boolean algebra laws for the following function:
- $$F = \overline{A}BC + ABC + (C + D)(\overline{D} + E)$$
- (4 marks)
- (d) Waveforms A, B and C of Figure Q2(d) are applied to a logic circuit. The output waveform, D, from the circuit is also shown in Figure Q2(d). Obtain the truth table and Boolean expression of the logic circuit. Simplify the expression for D and implement with NAND gates only.
- (13 marks)

Q3 (a) For the following function:

- (i) Simplify using a Karnaugh map and obtain a minimum SOP expression for f .
- (ii) Implement the simplified logic diagram using logic gates.

$$f(A, B, C, D) = \sum m(2, 3, 6, 9) + d(10, 11, 12, 13, 14, 15)$$

(9 marks)

(b) A combinational circuit has 4 inputs (A, B, C, D) and 3 outputs (X, Y, Z). X, Y, Z represent a binary number whose value equals the number of 1's at the input. For example, if ABCD = 1011, XYZ = 011. Find the

- (i) Obtain the truth table of the circuit.
- (ii) Write the minterm expression for outputs X, Y, and Z.
- (iii) Write the maxterm expression for outputs X, Y, and Z.
- (iv) Simplify the output function for X, Y, and Z.

(16 marks)

Q4 (a) From the truth table in Table Q4(a),

- (i) Write the standard sum of product (SOP) expression for output P.
- (ii) Write the standard product of sum (POS) expression for P.
- (iii) Use the K map to get the minimum sum of product (SOP) expression for P.
- (iv) Implement the simplified expression of P with logic gates.

(11 marks)

(b) For the logic circuit shown in Figure Q4(b)

- (i) Construct the truth table
- (ii) Write the output expression.

(5 marks)

(c) Represent each function below as a sum of minterms:

(i) $F = \overline{A}B + \overline{A}C + A\overline{B} + \overline{B}C$

(ii) $F = \overline{X}\overline{Z} + W\overline{X}\overline{Y} + \overline{W}XZ$

(9 marks)

Q5. (a) A full adder can be implemented in many different ways. Figure Q5(a) shows how one may be constructed from 2 Half Adders. Construct a truth table for this arrangement and verify that it operates as a Full Adder. (10 marks)

(b) Figure Q5(b) show a BCD adder circuit.

- (i) What are the THREE basic parts of this adder?
- (ii) Describe how the BCD adder circuit detects the need for a correction and executes it.
- (iii) Write the expression for X.
- (iv) Two numbers, A and B having values 9 and 5 respectively are feed into this BCD adder. Show the contents of $A_3A_2A_1A_0$, $B_3B_2B_1B_0$, $S_3S_2S_1S_0$, $\sum_3 \sum_2 \sum_1 \sum_0$ and the value of X. Verify that the contents of the BCD sum and value of X is correct. (15 marks)

Q6. (a) With the aid of diagrams, explain the function of the following devices:

- (i) A decoder
- (ii) An encoder
- (iii) A multiplexer

(9 marks)

(b) For the circuit in Figure Q6(b),

- (i) Construct the truth table
- (ii) Write the expression for outputs \sum and Co in sum of minterms.
- (iii) Use a 3 x 8 decoder with active Low output and appropriate logic gates to implement \sum and Co .

(11 marks)

(c) Implement this circuit using a 8 x 1 multiplexer to produce the Boolean expression:

$$Z = \overline{A}BC + A\overline{B}C + BC$$

(5 marks)

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2012/2013
 COURSE : DIGITAL ELECTRONICS

PROGRAMME : 2 DAE
 COURSE CODE : DAE21203

Table Q1(c)

CONTROL CHARACTERS				GRAPHIC SYMBOLS			
NAME	DEC	BINARY	HEX	SYMBOL	DEC	BINARY	HEX
NUL	0	0000000	00		64	1000000	40
SOH	1	0000001	01	@	65	1000001	41
STX	2	0000010	02	A	66	1000010	42
ETX	3	0000011	03	B	67	1000011	43
EOT	4	0000100	04	C	68	1000100	44
ENQ	5	0000101	05	D	69	1000101	45
ACK	6	0000110	06	E	70	1000110	46
BEL	7	0000111	07	F	71	1000111	47
BS	8	0001000	08	G	72	1001000	48
HT	9	0001001	09	H	73	1001001	49
LF	10	0001010	0A	I	74	1001010	4A
VT	11	0001011	0B	J	75	1001011	4B
FF	12	0001100	0C	K	76	1001100	4C
CR	13	0001101	0D	L	77	1001101	4D
SO	14	0001110	0E	M	78	1001110	4E
SI	15	0001111	0F	N	79	1001111	4F
DLE	16	0010000	10	O	80	1010000	50
DC1	17	0010001	11	P	81	1010001	51
DC2	18	0010010	12	Q	82	1010010	52
DC3	19	0010011	13	R	83	1010011	53
DC4	20	0010100	14	S	84	1010100	54
NAK	21	0010101	15	T	85	1010101	55
SYN	22	0010110	16	U	86	1010110	56
ETB	23	0010111	17	V	87	1010111	57
CAN	24	0011000	18	W	88	1011000	58
EM	25	0011001	19	X	89	1011001	59
SUB	26	0011010	1A	Y	90	1011010	5A
ESC	27	0011011	1B	Z	91	1011011	5B
FS	28	0011100	1C	[92	1011100	5C
GS	29	0011101	1D	\	93	1011101	5D
RS	30	0011110	1E	^	94	1011110	5E
US	31	0011111	1F	_	95	1011111	5F
				space	32	0100000	20
				!	33	0100001	21
				"	34	0100010	22
				#	35	0100011	23
				\$	36	0100100	24
				%	37	0100101	25
				&	38	0100110	26
				'	39	0100111	27
				(40	0101000	28
)	41	0101001	29
				*	42	0101010	2A
				+	43	0101011	2B
				,	44	0101100	2C
				-	45	0101101	2D
				.	46	0101110	2E
				/	47	0101111	2F
				0	48	0110000	30
				1	49	0110001	31
				2	50	0110010	32
				3	51	0110011	33
				4	52	0110100	34
				5	53	0110101	35
				6	54	0110110	36
				7	55	0110111	37
				8	56	0111000	38
				9	57	0111001	39
				:	58	0111010	3A
				;	59	0111011	3B
				<	60	0111100	3C
				=	61	0111101	3D
				>	62	0111110	3E
				?	63	0111111	3F
				.	96	1100000	60
				a	97	1100001	61
				b	98	1100010	62
				c	99	1100011	63
				d	100	1100100	64
				e	101	1100101	65
				f	102	1100110	66
				g	103	1100111	67
				h	104	1101000	68
				i	105	1101001	69
				j	106	1101010	6A
				k	107	1101011	6B
				l	108	1101100	6C
				m	109	1101101	6D
				n	110	1101110	6E
				o	111	1101111	6F
				p	112	1110000	70
				q	113	1110001	71
				r	114	1110010	72
				s	115	1110011	73
				t	116	1110100	74
				u	117	1110101	75
				v	118	1110110	76
				w	119	1110111	77
				x	120	1111000	78
				y	121	1111001	79
				z	122	1111010	7A
				[123	1111011	7B
				\	124	1111100	7C
]	125	1111101	7D
				^	126	1111110	7E
				_	127	1111111	7F

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2012/2013
 COURSE : DIGITAL ELECTRONICS

PROGRAMME : 2 DAE
 COURSE CODE : DAE21203

 


FIGURE Q2(d)

TABLE Q4(a)

INPUT			OUTPUT
A	B	C	P
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2012/2013
 COURSE : DIGITAL ELECTRONICS

PROGRAMME : 2 DAE
 COURSE CODE : DAE21203

 


FIGURE Q4(b)

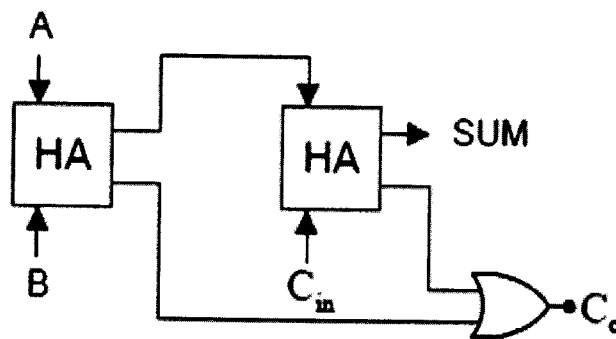


FIGURE Q5(a)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2012/2013
 COURSE : DIGITAL ELECTRONICS

PROGRAMME : 2 DAE
 COURSE CODE : DAE21203

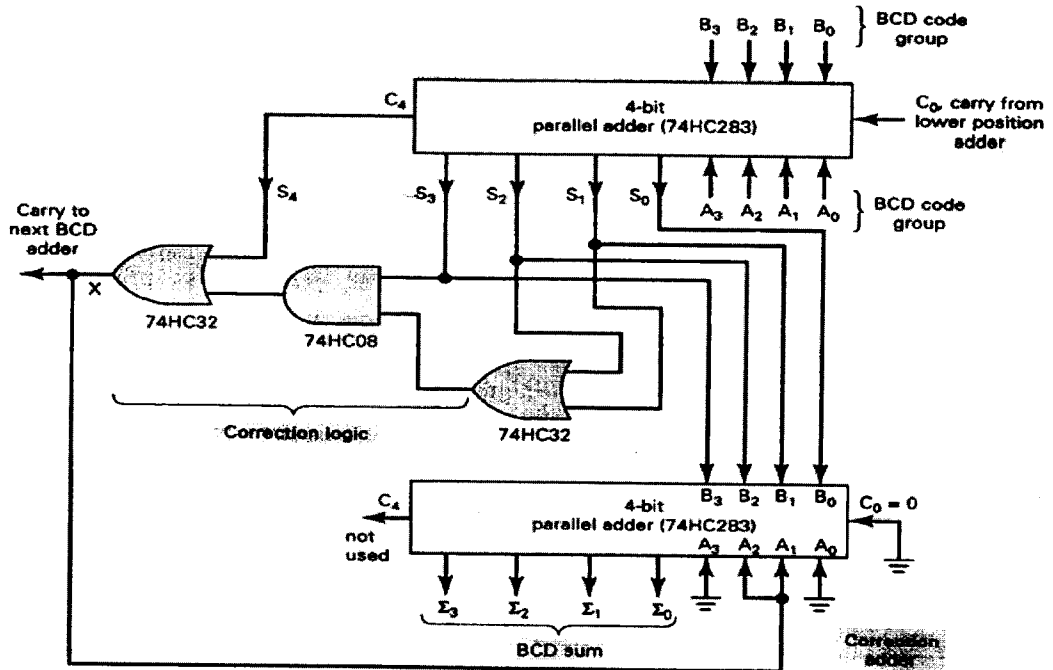


FIGURE O5(b)

 


FIGURE O6(b)