

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2012/2013**

COURSE NAME : ELECTRICAL PRINCIPLES II
COURSE CODE : DAR 11103
PROGRAMME : 1 DAR
EXAMINATION DATE : MARCH 2013
DURATION : 3 HOURS
INSTRUCTION : ANSWER FIVE(5) QUESTIONS ONLY

THIS PAPER CONSISTS OF NINE (9) PAGES

- Q1** (a) For the network of Figure Q1(a):
- (i) Find the total impedance Z_T . (4 marks)
 - (ii) Calculate the voltage V_2 and the current I_L . (4 marks)
 - (iii) Find the power factor of the network. (2 marks)
- (b) For the network of Figure Q1(b):
- (i) Find the currents I . (4 marks)
 - (ii) Find the voltage V_C . (4 marks)
 - (iii) Find the average power delivered to the network. (2 marks)
- Q2** (a) For the circuits of Figure Q2(a), write the mesh equations for the network and determine the current through the $1\text{k}\Omega$ and $2\text{k}\Omega$ resistors. (10 marks)
- (b) Determine the nodal voltages V_1 and V_2 for the networks of Figure Q2(b) (10 marks)
- Q3** (a) Find the Thévenin equivalent circuit for the portions of the networks of Figure Q3(a) external to the elements between points a and b . (10 marks)
- (b) Find the load impedance Z_L for the networks of Figure Q3(b) for maximum power to the load, and find the maximum power to the load. (10 marks)

Q4 For the network of Figure Q4:

- (a) Find the average power delivered to each element. (2 marks)
- (b) Find the reactive power for each element. (5 marks)
- (c) Find the apparent power for each element. (3 marks)
- (d) Find P_T , Q_T , S_T , and F_p for the system. (8 marks)
- (e) Find I_S . (2 marks)

Q5 For the series circuit of Figure Q5:

- (a) Find the value of X_L for resonance. (2 marks)
- (b) Determine the magnitude of the current I at resonance. (2 marks)
- (c) Find the voltages V_R , V_L , and V_C at resonance, and compare their magnitudes. (6 marks)
- (d) Determine the quality factor of the circuit. Is it a high or low-Q circuit? (2 marks)
- (e) If the resonant frequency is 5 kHz, determine the value of L and C . (4 marks)
- (f) Find the bandwidth of the response if the resonant frequency is 5 kHz. (2 marks)
- (g) What are the low and high cutoff frequencies? (2 marks)

- Q6** For the transformer of Figure Q6, determine:
- (a) the equivalent resistance R_e . (2 marks)
 - (b) the equivalent reactance X_e . (2 marks)
 - (c) the equivalent circuit reflected to the primary. (6 marks)
 - (d) the primary current for I_p . (2 marks)
 - (e) the load voltage V_L . (2 marks)
 - (f) the phasor diagram of the reflected primary circuit. (2 marks)
 - (g) the new load voltage if we assume the transformer to be ideal with a 4 : 1 turns ratio. Compare the result with that of part (e). (4 marks)
- Q7** The phase sequence for the Y- Δ system of Figure Q7 is ABC .
- (a) Find the angles θ_2 and θ_3 for the specified phase sequence. (2 marks)
 - (b) Find the voltage across each phase impedance in phasor form. (6 marks)
 - (c) Draw the phasor diagram of the voltages found in part (b), and show that their sum is zero around the closed loop of the Δ load. (2 marks)
 - (d) Find the current through each phase impedance in phasor form. (6 marks)
 - (e) Find the magnitude of the line currents. (2 marks)
 - (f) Find the magnitude of the generator phase voltages. (2 marks)

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2012/2013
 COURSE : ELECTRICAL PRINCIPLE II

PROGRAMME : 1 DAR
 COURSE CODE : DAR 11103

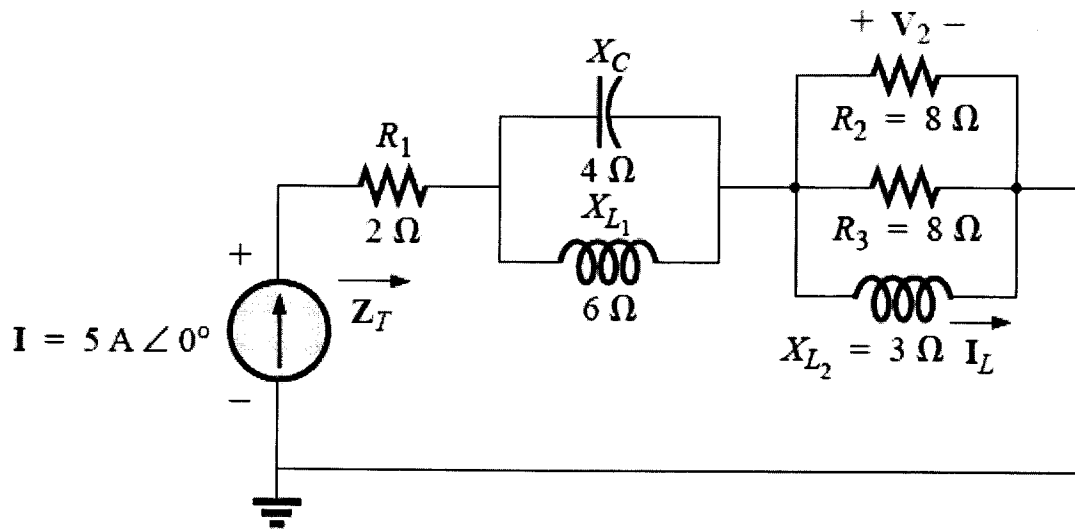


FIGURE Q1(a)

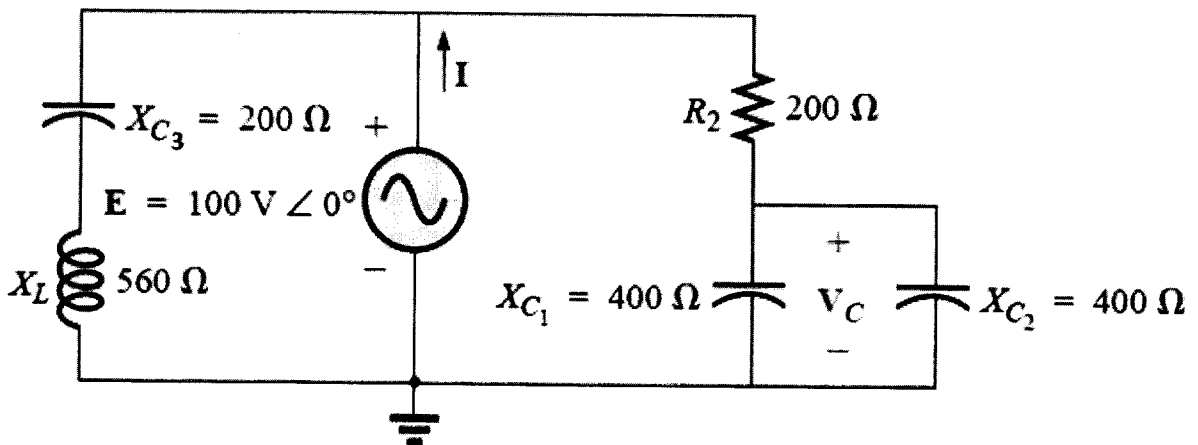


FIGURE Q1(b)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2012/2013
 COURSE : ELECTRICAL PRINCIPLE II

PROGRAMME : 1 DAR
 COURSE CODE : DAR 11103

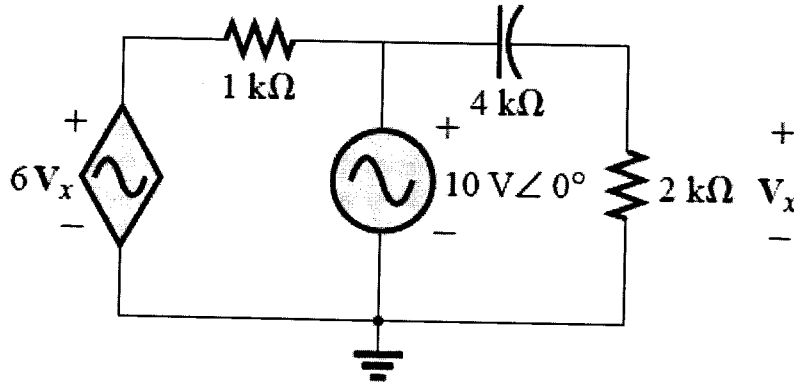


FIGURE Q2(a)

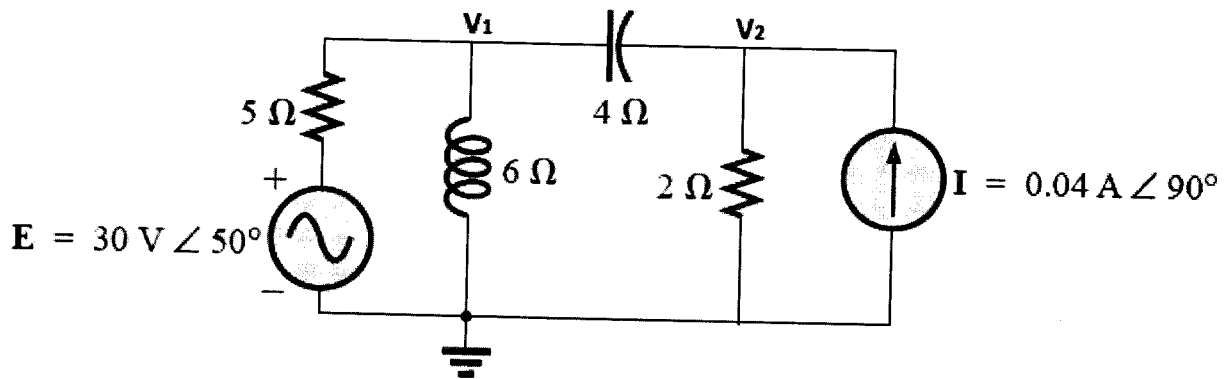


FIGURE Q2(b)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2012/2013
 COURSE : ELECTRICAL PRINCIPLE II

PROGRAMME : 1 DAR
 COURSE CODE : DAR 11103

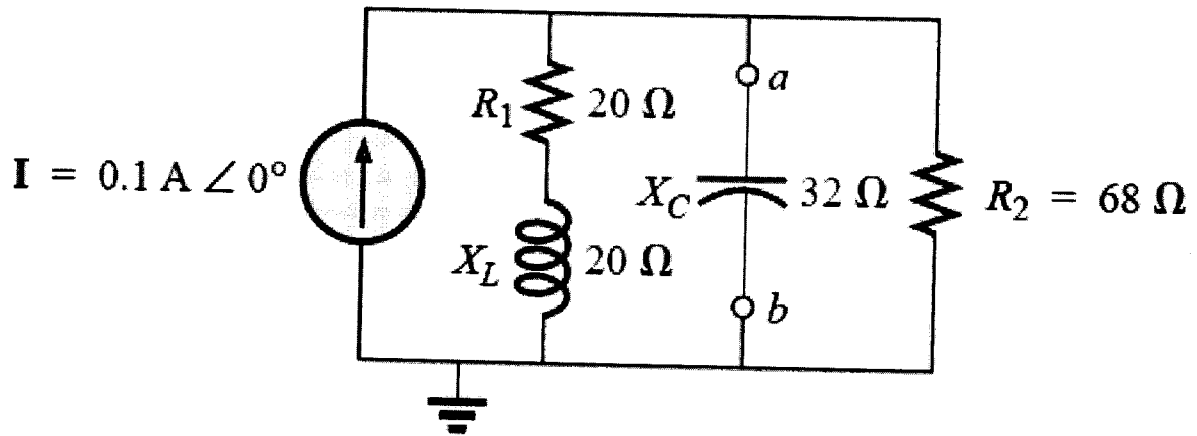


FIGURE Q3(a)

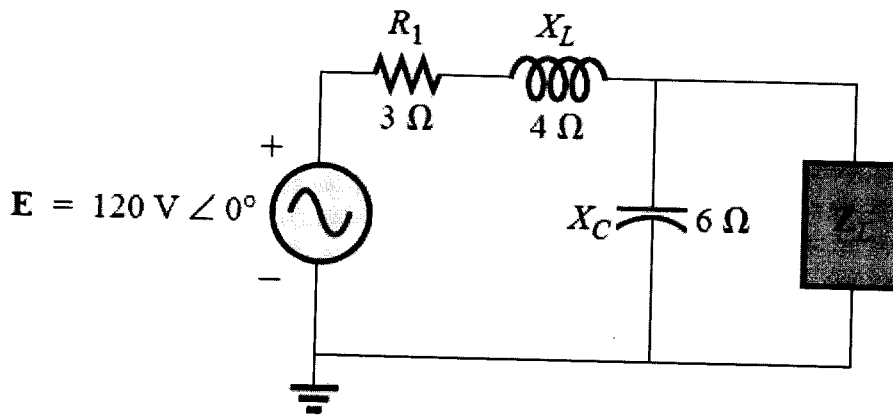


FIGURE Q3(b)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2012/2013
 COURSE : ELECTRICAL PRINCIPLE II

PROGRAMME : 1 DAR
 COURSE CODE : DAR 11103

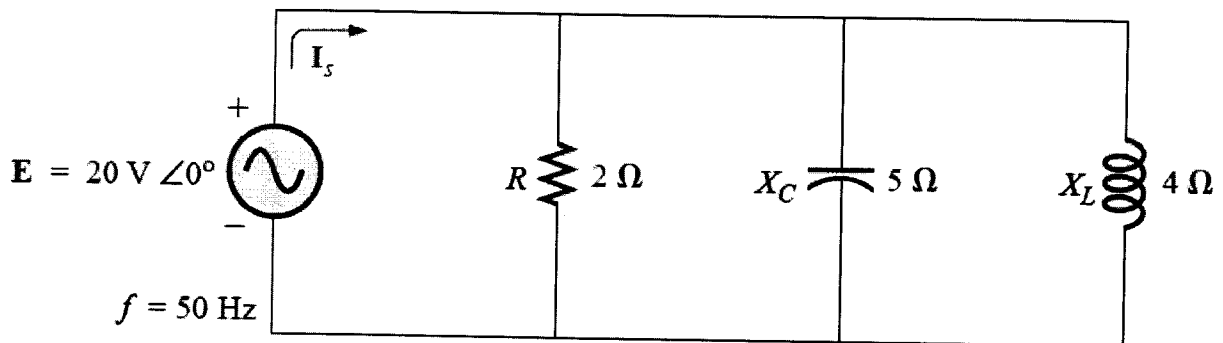


FIGURE Q4

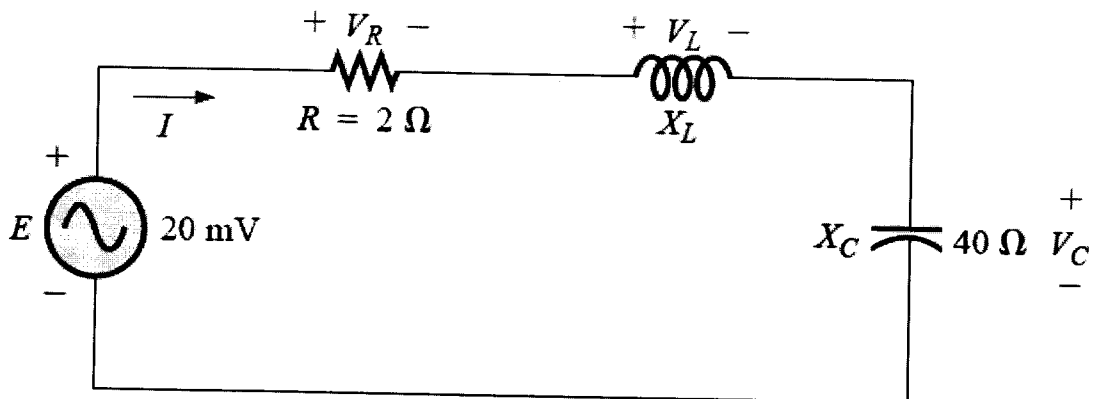


FIGURE Q5

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2012/2013
 COURSE : ELECTRICAL PRINCIPLE II

PROGRAMME : 1 DAR
 COURSE CODE : DAR 11103

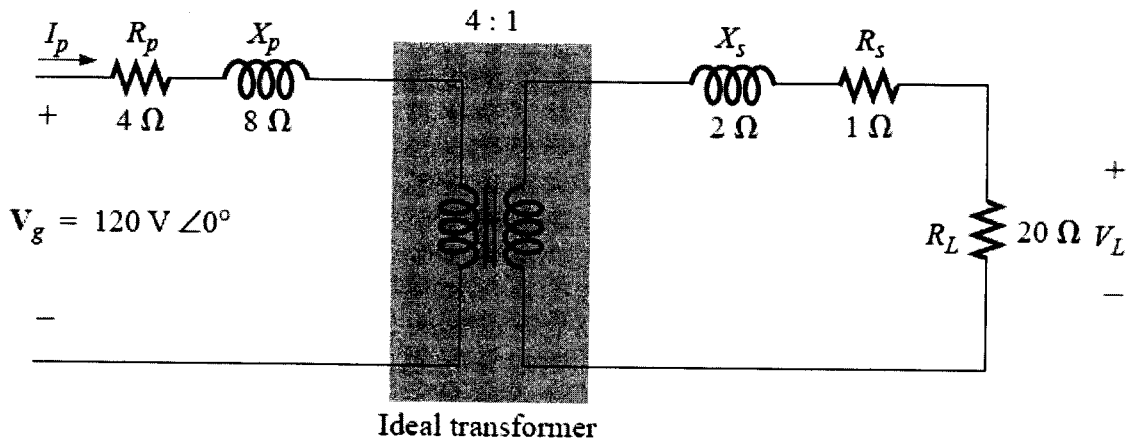


FIGURE Q6

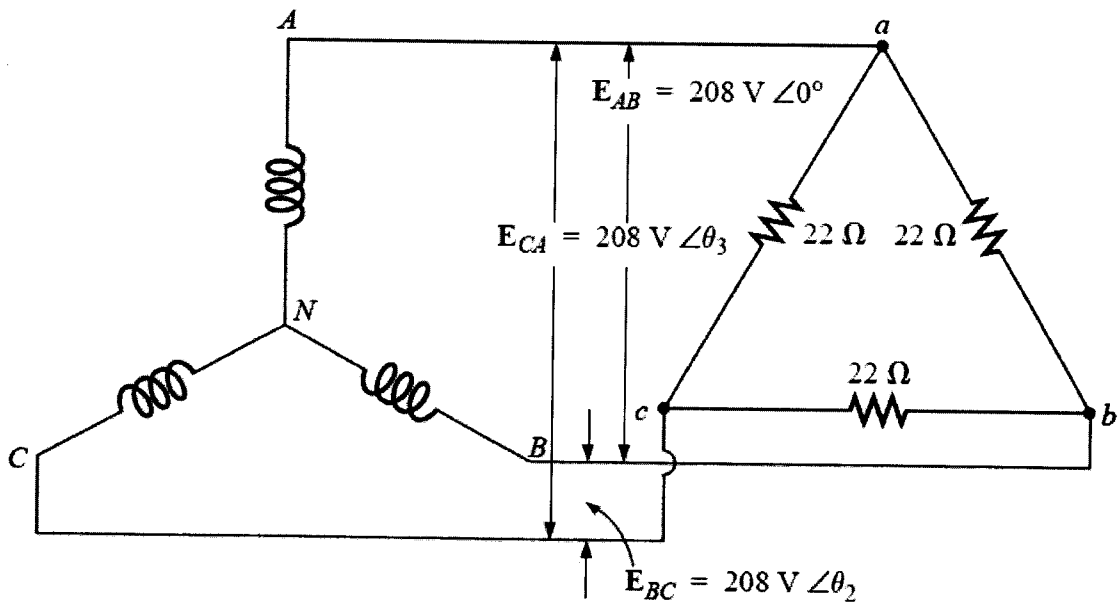


FIGURE Q7