



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESSION 2012/2013**

**COURSE NAME** : ELECTRONICS  
**COURSE CODE** : DAE 21303 / DEE 2133  
**PROGRAMME** : 1 DAE / 2 DEE  
**EXAMINATION DATE** : MARCH 2013  
**DURATION** : 2½ HOURS  
**INSTRUCTION** : ANSWER **FOUR (4)** QUESTIONS ONLY.

THIS QUESTION PAPER CONSISTS OF ELEVEN (11) PAGES

- Q1** (a) Figure Q1(a) shows a DC power supply circuit using a capacitor filter.
- (i) Sketch the output waveform with complete labeling for the given circuit configuration. (3 marks)
  - (ii) Assuming that  $C = 1000 \mu\text{F}$ , determine the output voltage,  $V_{r(p-p)}$  and average value of  $V_o$  for the full wave bridge circuit given in Figure Q1(a). The load current is 0.5 A. Use 2<sup>nd</sup> approximation model for diode with a forward voltage drop of 0.7 V. (6 marks)
- (b) Given the circuit shown in Figure Q1(b).
- (i) Identify the circuit given in Figure Q1(b) (1 mark)
  - (ii) Briefly explain the circuit analysis for the given circuit in Figure Q1(b) (5 marks)
  - (iii) Draw the output voltage waveform if the voltage supply is 120 V. (3 marks)
- (c) Based on Figure Q1(c)(i) and Figure Q1(c)(ii), assuming ideal diode :
- (i) Briefly explain the circuit analysis for each of the given figure. (4 marks)
  - (ii) Sketch the output voltage,  $V_o(t)$  for each of the circuits stated above, if the input voltage,  $V_i$ , is as given. (3 marks)
- Q2** (a) Based on the circuit configuration in Figure Q2(a), determine the following value
- (i) Base current,  $I_B$  (3 marks)
  - (ii) Collector current,  $I_C$  (1 mark)
  - (iii) Base voltage,  $V_B$  (2 marks)
  - (iv) Collector Voltage,  $V_C$  (2 marks)
  - (v) Collector – Emitter Q point voltage,  $V_{CEQ}$  (2 marks)
  - (vi) Base- Collector voltage,  $V_{BC}$  (2 marks)
  - (vii) Saturation Current,  $I_c$  (sat) (2 marks)
  - (viii) Cut-off value of Collector-Emitter voltage,  $V_{CE(\text{cut-off})}$  (2 marks)
  - (ix) Draw the load line. (2 marks)
  - (x) Plot the Q point on the resulted load line. (1 mark)

(b) By using all the data given in Figure Q2(b), determine the following values;

- (i) Beta
- (ii)  $V_{CC}$
- (iii)  $R_B$

(6 marks)

**Q3** The common-emitter amplifier circuit configuration is shown in Figure Q3. By referring to the figure;

(a) Draw the AC equivalent circuit by using the PIE ( II ) model with complete labeling. (2 marks)

(b) Calculate the following values by using the same model

- (i) AC emitter resistance ,  $r'_e$  (4 marks)
- (ii) The input impedance of the base ,  $z_{in}(\text{base})$  (2 marks)
- (iii) The input impedance of the stage ,  $z_{in}(\text{stage})$  (2 marks)
- (iv) The AC collector resistance,  $r_c$  (2 marks)
- (v) The input voltage,  $V_{in}$  (2 marks)
- (vi) The voltage gain,  $A_V$  (2 marks)
- (vii) The output voltage across  $R_L$ ,  $V_{out}$  (2 marks)

(c) Based on the circuit configuration in Figure Q3(c) ,

- (i) Draw the AC equivalent circuit with complete labeling. (2 marks)
- (ii) Calculate the value of  $r'_e$  (3 marks)
- (iii) Determine the value of  $Z_{in}$  (2 marks)

**Q4** For the self-bias common-source amplifier of Figure Q4.

(a) Solve for each of the following DC quantities:

- (i) Gate voltage,  $V_G$  (2 marks)
- (ii) Drain current,  $I_D$  (3 marks)
- (iii) Gate-source voltage,  $V_{GS}$  (2 marks)
- (iv) Drain voltage,  $V_D$  (3 marks)

(b) Solve for each of the following AC quantities:

- (i) Input impedance,  $Z_{in}$  (3 marks)
- (ii) Load resistance,  $r_L$  (2 marks)
- (iii) Transconductance when  $V_{GS} = 0$ ,  $g_{mo}$  (3 marks)
- (iv) Transconductance,  $g_m$  (2 marks)
- (v) Voltage gain,  $A_v$  (3 marks)
- (vi) Output voltage,  $v_{out}$  (2 marks)

**Q5** (a) List two characteristics for each of the following classes of amplifiers.

- (i) Class A (2 marks)
- (ii) Class B (2 marks)
- (iii) Class C (2 marks)

(b) In Figure Q5(b), solve for the following:

- (i) Transistor Power Dissipation ( $P_{DQ}$ ) (6 marks)
- (ii) Voltage gain ( $A_v$ ) (3 marks)
- (iii) Peak-peak output voltage ( $v_{out}$ ) (2 marks)
- (iv) AC load power ( $P_{out}$ ) (3 marks)
- (v) DC input power ( $P_{dc}$ ) (3 marks)
- (vi) Stage Efficiency ( $\eta$ ) (2 marks)

**Q6** (a) Explain the purpose of an oscillator and what are the conditions required for a circuit to oscillate.

(9 marks)

(b) Referring to Figure Q6(b), calculate :

- (i) Frequency of oscillation. (4 marks)
- (ii) Value of feedback fraction (B). (3 marks)
- (iii) Minimum value of voltage gain ( $A_v$ ) for the oscillator to start. (3 marks)

(c) The 555 timer of Figure Q6(c) has  $R_1 = 20 \text{ k}\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ , and  $C = 0.047 \text{ }\mu\text{F}$ .


- (i) Calculate frequency of the output signal. (3 marks)
- (ii) Compute the duty cycle. (3 marks)

- END OF QUESTION -


**FINAL EXAMINATION**

SEMESTER / SESSION : SEMESTER II/ 2012/2013  
 COURSE : ELECTRONICS


PROGRAMME : 1 DAE  
 COURSE CODE : DAE 21303

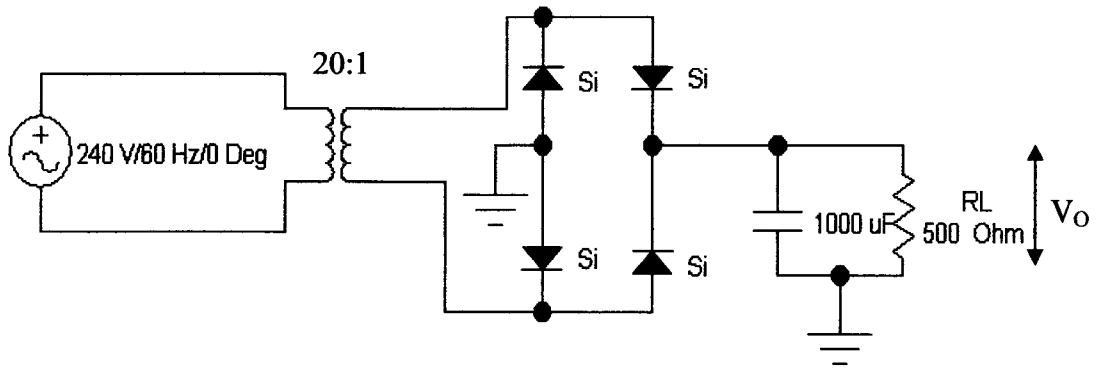

**FIGURE Q1(a)**

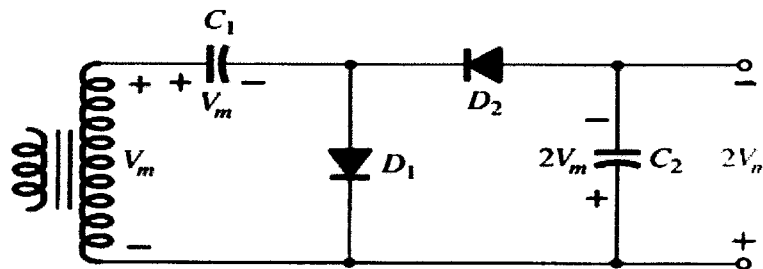

**FIGURE Q1(b)**

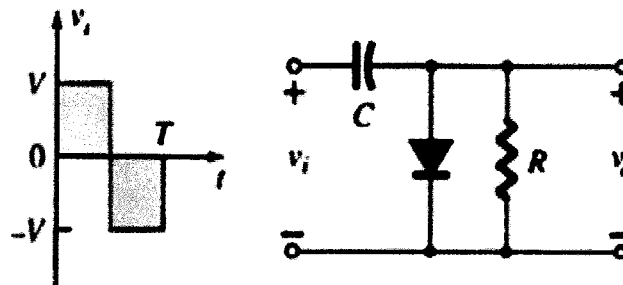


**FIGURE Q1(c)(i)**


**FINAL EXAMINATION**

SEMESTER / SESSION : SEMESTER II / 2012/2013  
 COURSE : ELECTRONICS

PROGRAMME : 1 DAE  
 COURSE CODE : DAE 21303

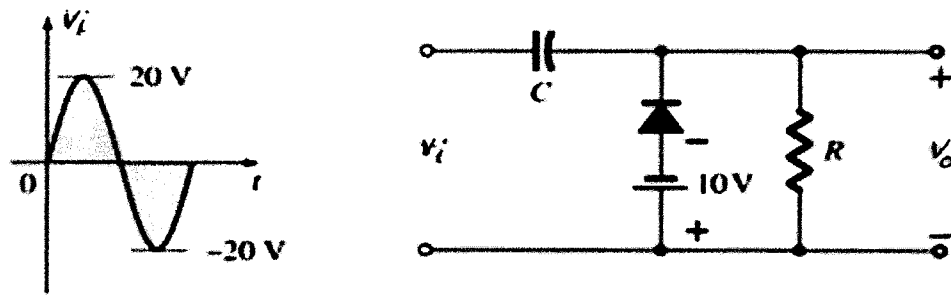

**FIGURE Q1(c)(ii)**

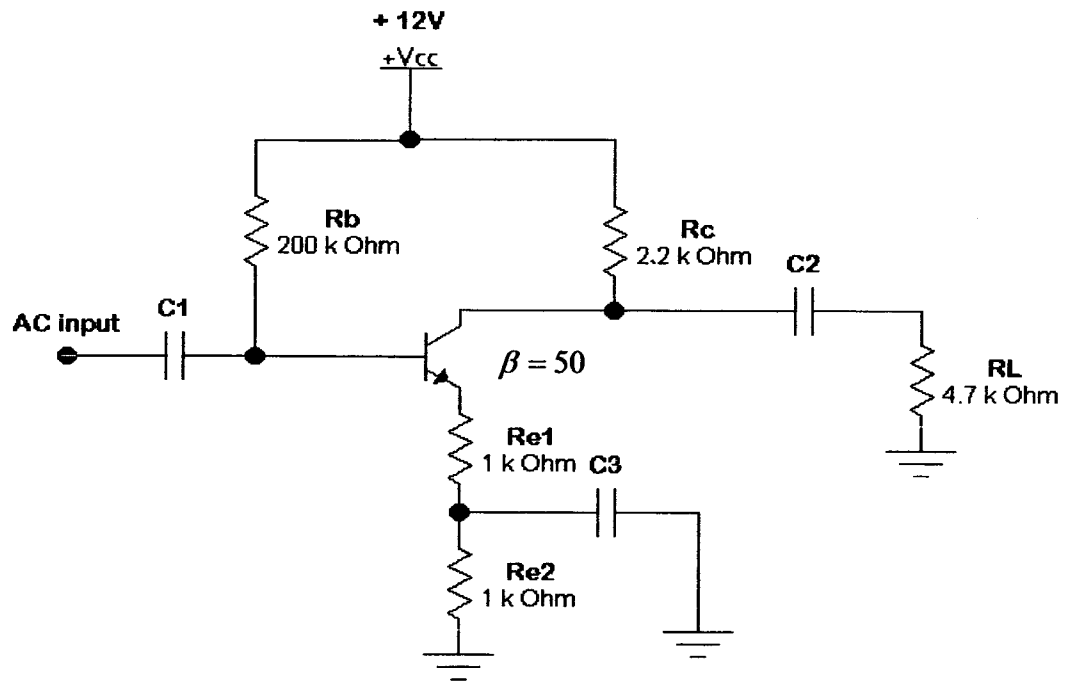


**FIGURE Q2(a)**


**FINAL EXAMINATION**

SEMESTER / SESSION : SEMESTER II / 2012/2013  
 COURSE : ELECTRONICS

PROGRAMME : 1 DAE  
 COURSE CODE : DAE 21303

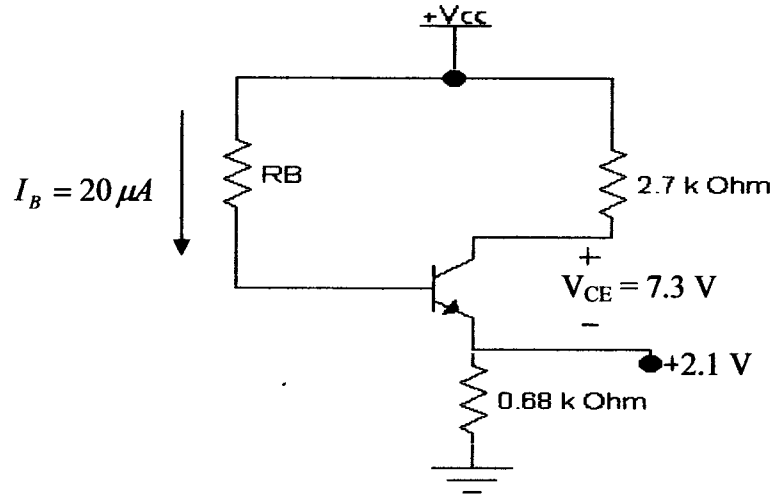

**FIGURE Q2(b)**

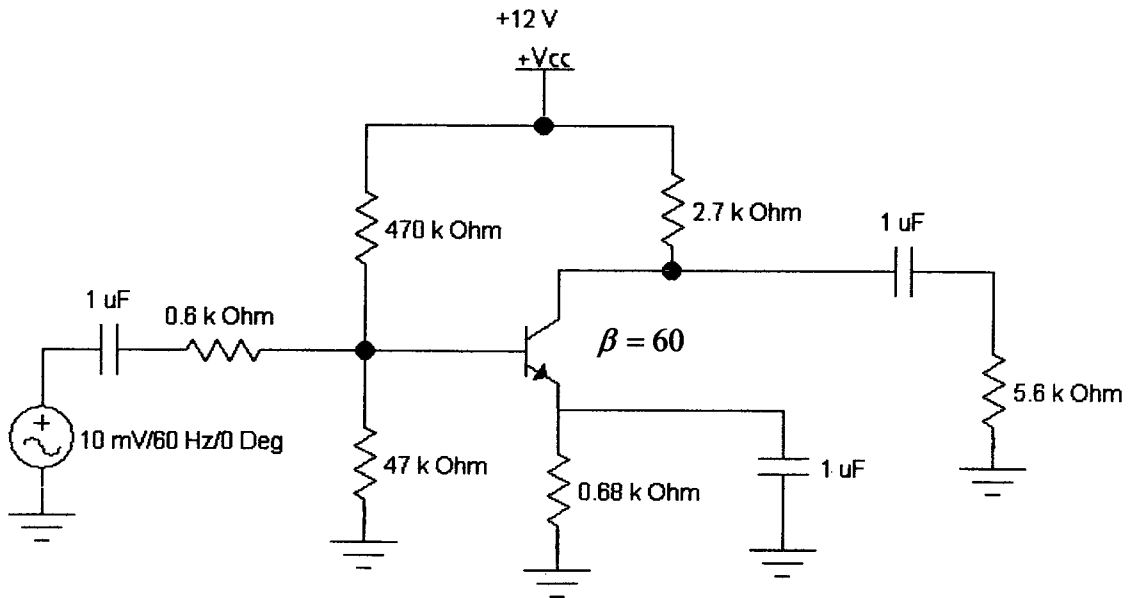


**FIGURE Q3**

**FINAL EXAMINATION**

SEMESTER / SESSION : SEMESTER II/ 2012/2013  
COURSE : ELECTRONICS

PROGRAMME : 1 DAE  
COURSE CODE : DAE 21303

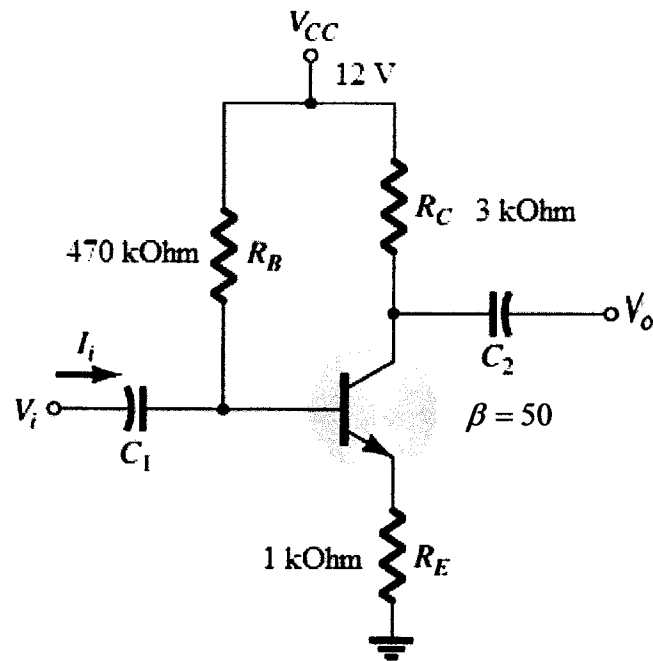


**FIGURE Q3(c)**



**FINAL EXAMINATION**

SEMESTER / SESSION : SEMESTER II / 2012/2013  
 COURSE : ELECTRONICS

PROGRAMME : 1 DAE  
 COURSE CODE : DAE 21303

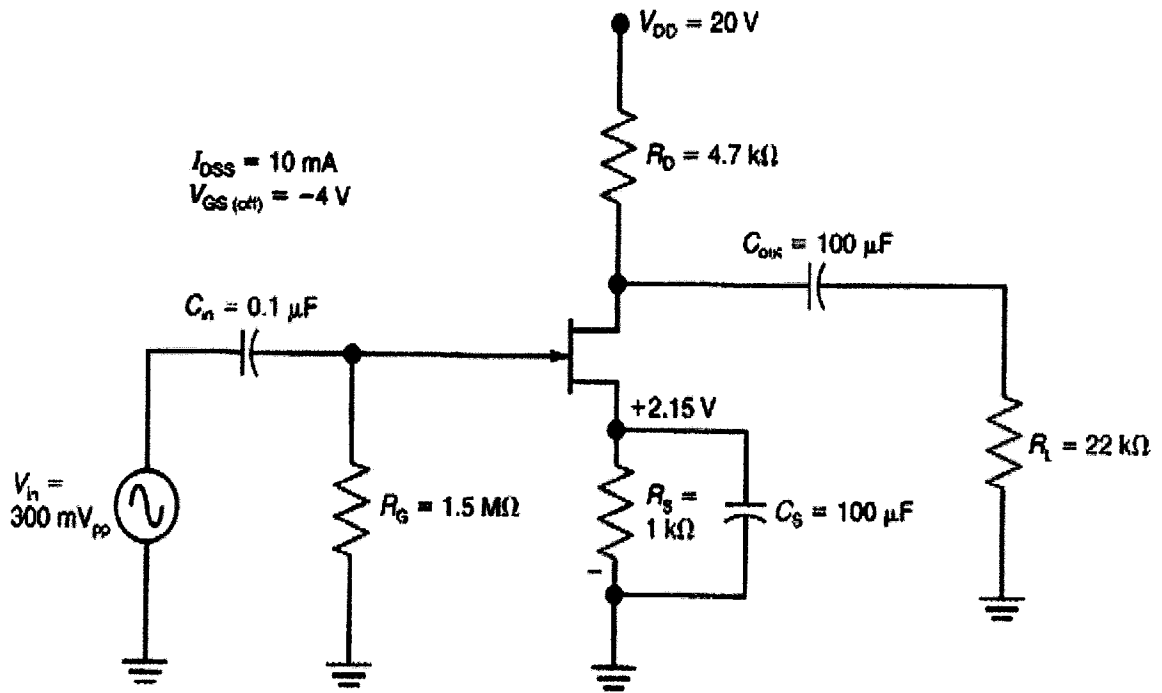


**FIGURE Q4**

## FINAL EXAMINATION

SEMESTER / SESSION : SEMESTER II/ 2012/2013  
COURSE : ELECTRONICS

PROGRAMME : 1 DAE  
COURSE CODE : DAE 21303

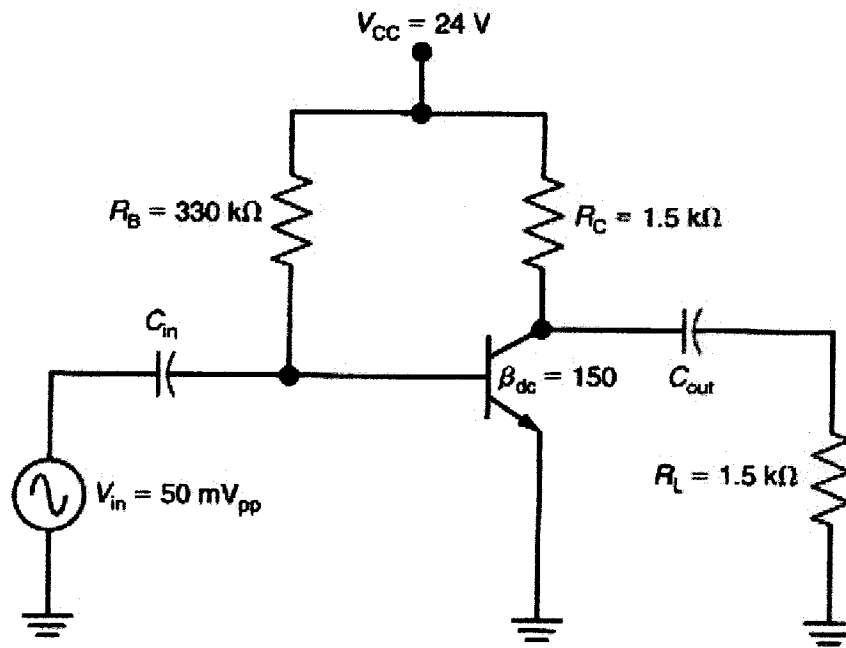


**FIGURE Q5(b)**


**FINAL EXAMINATION**

SEMESTER / SESSION : SEMESTER II / 2012/2013  
 COURSE : ELECTRONICS

PROGRAMME : 1 DAE  
 COURSE CODE : DAE 21303

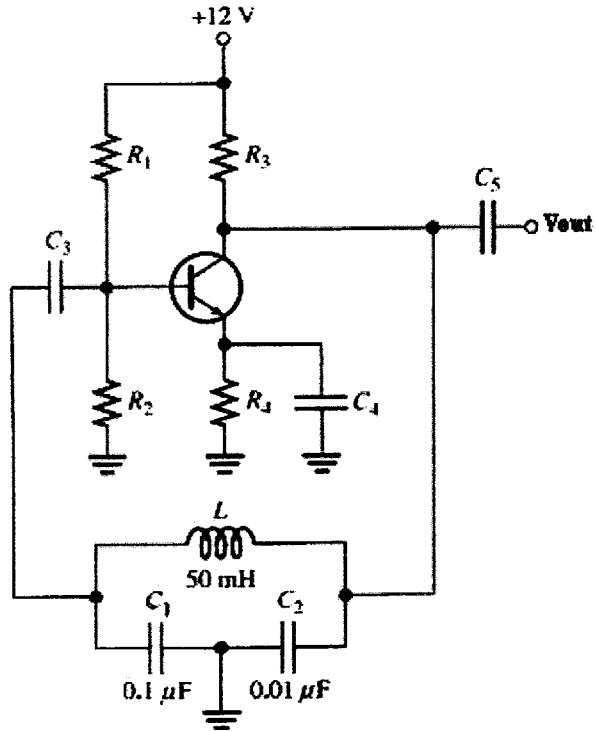

**FIGURE Q6(b)**

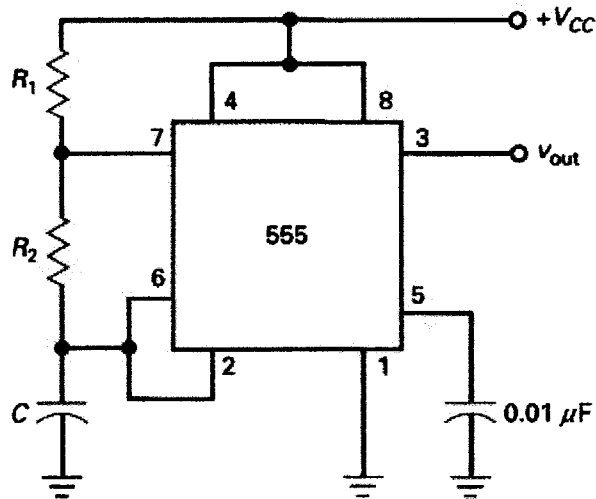

**FIGURE Q6(c)**